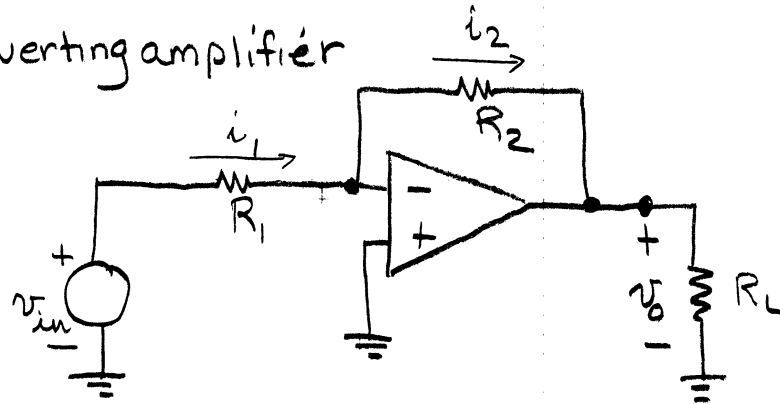


## Chapter 2 Operational Amplifiers

### Basic inverting amplifier



Negative feedback  
output  
returned in  
opposition to  
input.

Assumptions:  $I_{in} = 0$

$$V_+ = V_-$$

(virtual short)

summing point constraint

$$i_1 = \frac{v_{in}}{R_1}$$

since  $I_{in} = 0$

$$i_2 = i_1$$

$$v_o = V_- - i_2 R_2$$


voltage at inverting input

$$v_o = -i_2 R_2 = -i_1 R_2 = -\left(\frac{v_{in}}{R_1}\right) R_2$$


$$\frac{v_o}{v_{in}} = -\frac{R_2}{R_1}$$

Input impedance =  $R_1$

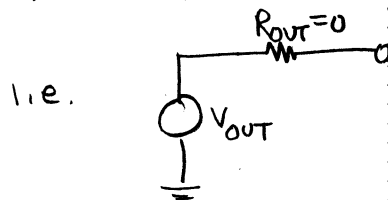Since output independent of  $R_L$  we conclude  
output is a perfect voltage source with  $R_{out} = 0$




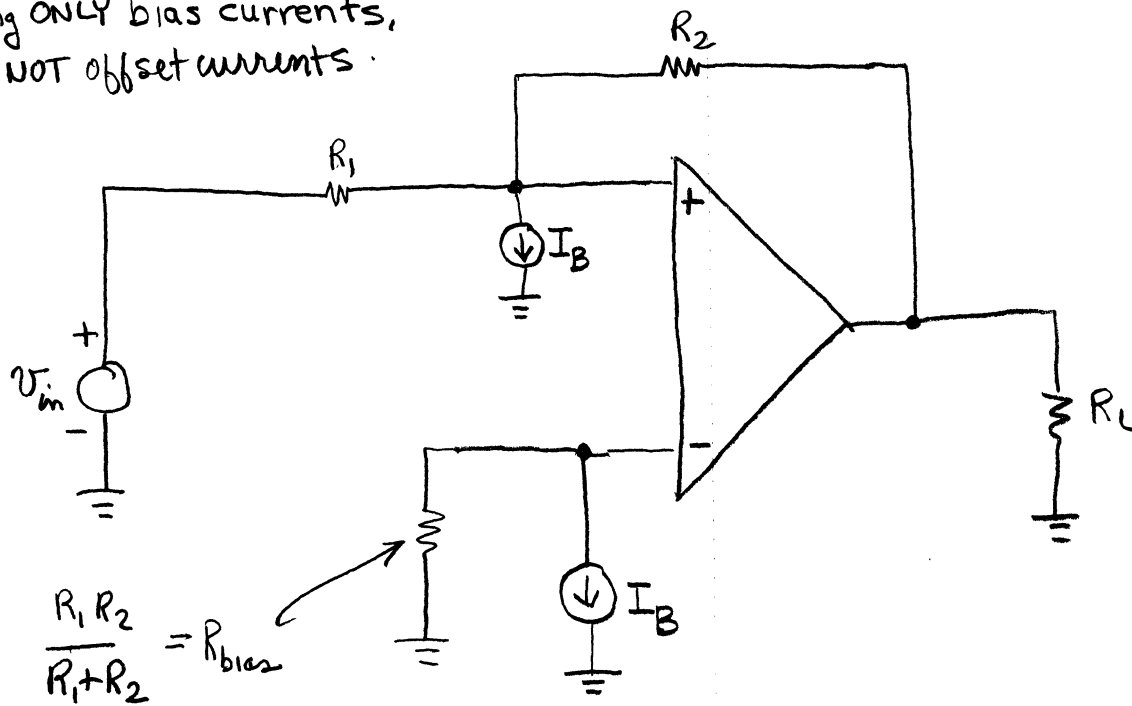Modeling ONLY bias currents,  
and NOT offset currents.



Assumes we neglect  $v_{offset}$  and  $\frac{1}{2} I_{off}$
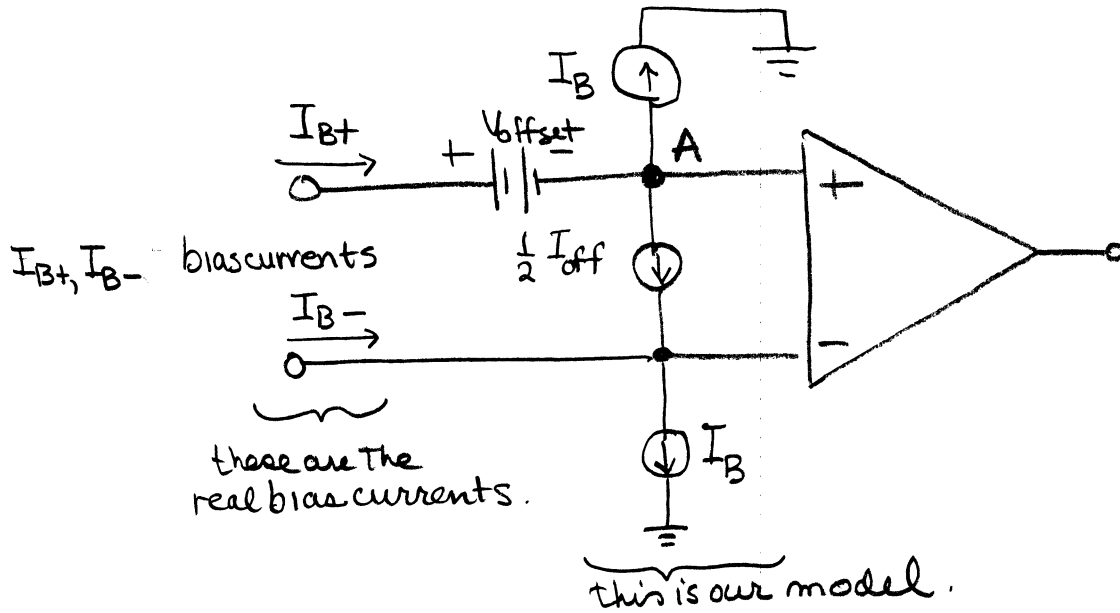
## 2.8 DC Imperfections - Bias current cancellation



difference between bias currents is called offset current

$$I_{off} = I_{B+} - I_{B-}$$

$$I_B = \frac{I_{B+} + I_{B-}}{2}$$


Sum currents @ A

to check this out. 
$$I_{B+} = I_B + \frac{1}{2} I_{off} = \frac{1}{2} I_{B+} + \frac{1}{2} I_{B-} + \frac{1}{2} I_{B+} - \frac{1}{2} I_{B-}$$

$$= \frac{1}{2} I_{B+} + \frac{1}{2} I_{B+} = I_{B+}$$

We can cause bias currents to cancel out with other currents.

Consider this circuit.

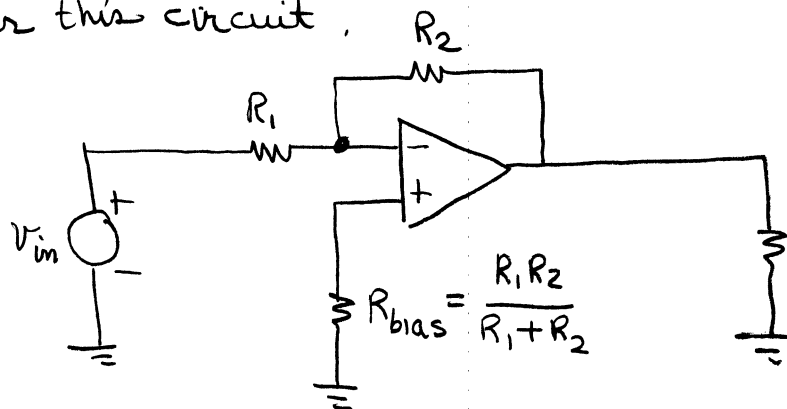

What does this look like in frequency domain?

$$A_{OL}(f) = \frac{A_{\phi OL}}{1 + j \frac{f}{f_{BOL}}}$$

$$A_{CL}(f) = \frac{A_{OL}(f)}{1 + \beta A_{OL}(f)} = \frac{\frac{A_{\phi OL}}{1 + j \frac{f}{f_{BOL}}}}{1 + \frac{\beta A_{\phi OL}}{1 + j \frac{f}{f_{BOL}}}}$$

$$= \frac{\frac{A_{\phi OL}}{1 + j \frac{f}{f_{BOL}}}}{\frac{1 + j \frac{f}{f_{BOL}} + \beta A_{\phi OL}}{1 + j \frac{f}{f_{BOL}}}} = \frac{A_{\phi OL}}{1 + \beta A_{\phi OL} + j \frac{f}{f_{BOL}}}$$

$$\frac{v_o}{v_s} = A_{CL}(f) = \frac{\frac{A_{\phi OL}}{1 + \beta A_{\phi OL}}}{1 + j \frac{f}{f_{BOL}(1 + \beta A_{\phi OL})}}$$

open loop dc gain.

define  $A_{\phi CL} = \frac{A_{\phi OL}}{1 + \beta A_{\phi OL}}$

closed loop dc gain less than open loop dc gain,


and  $f_{BCL} = f_{BOL}(1 + \beta A_{\phi OL})$  closed loop breakpoint frequency higher

then  $\frac{v_o}{v_s} = A_{CL}(f) = \frac{A_{\phi CL}}{1 + j \frac{f}{f_{BCL}}}$

$\beta$  is function of external resistors.

This is what equation means.

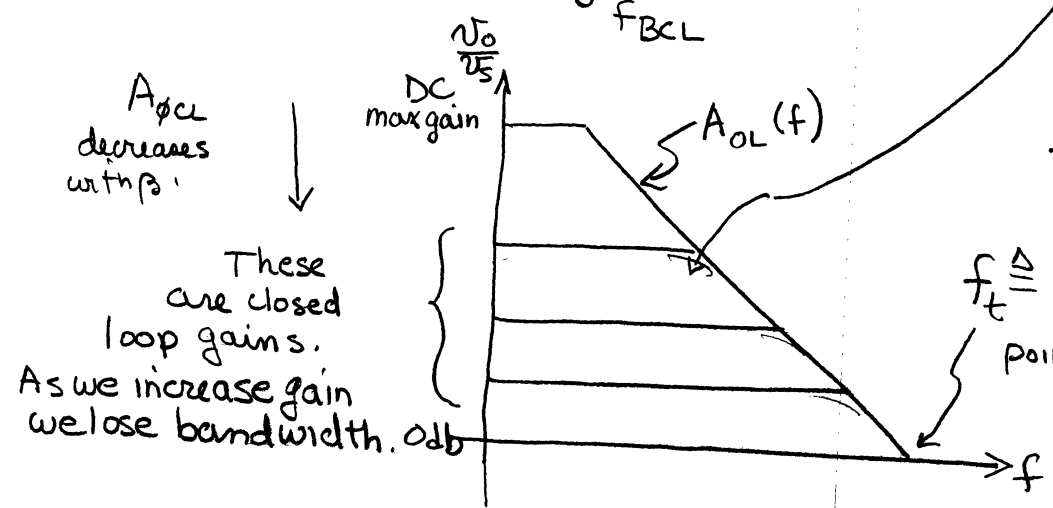$f_t \triangleq A_{\phi CL} f_{BCL}$   
point at which  $\frac{v_o}{v_s} = 1$  (0dB)



$A_{\phi CL}$  decreases with  $\beta$ .

Why do we see this frequency response.

This is getting slightly ahead of ourselves but


$$A_{OL}(f) = \frac{A_{\phi OL}}{1 + j\left(\frac{f}{f_{BOL}}\right)}$$

← dc, i.e. zero frequency  
 open loop gain  
 big but finite  
 typically  $10^4 \leq A_{\phi OL} \leq 10^6$

looks like  
single-pole, i.e. a low-pass filter

down to 0.707 (-3dB) at  $f_{BOL}$   
 called dominant pole assumption  
 ↑ break frequency

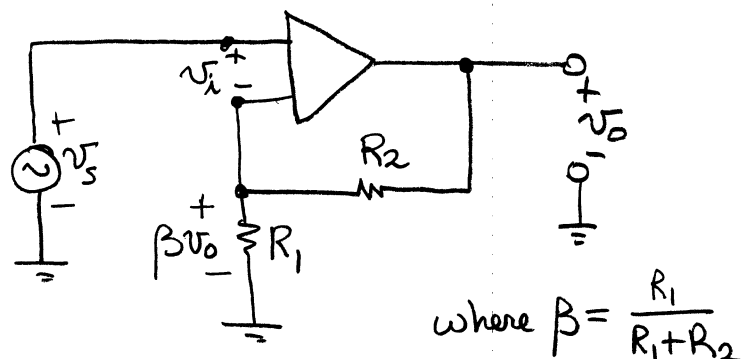Analyze non-inverting amplifier using above op-amp model



input loop  $-v_s + v_i + \beta v_o = 0$   
 $v_o = A_{OL} v_i$

eliminating  $v_i$  we get  $-v_s + \frac{v_o}{A_{OL}} + \beta v_o = 0$

$$v_s = \left(\frac{1}{A_{OL}} + \beta\right) v_o$$

define closed loop gain  $A_{CL} = \frac{v_o}{v_s} = \frac{1}{\frac{1}{A_{OL}} + \beta} = \frac{A_{OL}}{1 + A_{OL}\beta}$

Note that as  $A_{OL} \rightarrow \infty$   $A_{CL} \rightarrow \frac{1}{\beta} = 1 + \frac{R_2}{R_1}$

## 2.9 Computer analysis of op-amp circuits

often do bandwidth calculations


choose AC Sweep for this

use Decade sweep

specify points/decade

like a transient analysis plot (PROBE) would come up with frequency on the horizontal axis

Consider analysis of

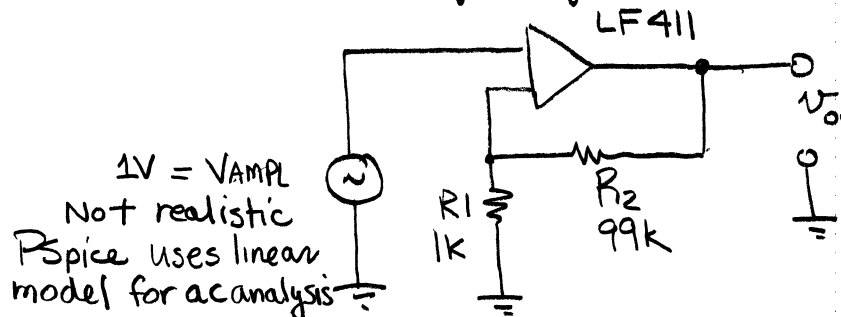


Not sure if LF411 in current PSpice library,  
Other popular op amps.  
UA741  
LM324 (single voltage)

ideal gain would be

$$A_v = \frac{v_o}{v_{in}} = 1 + \frac{R_2}{R_1} = 1 + \frac{99k}{1k} = 100.$$

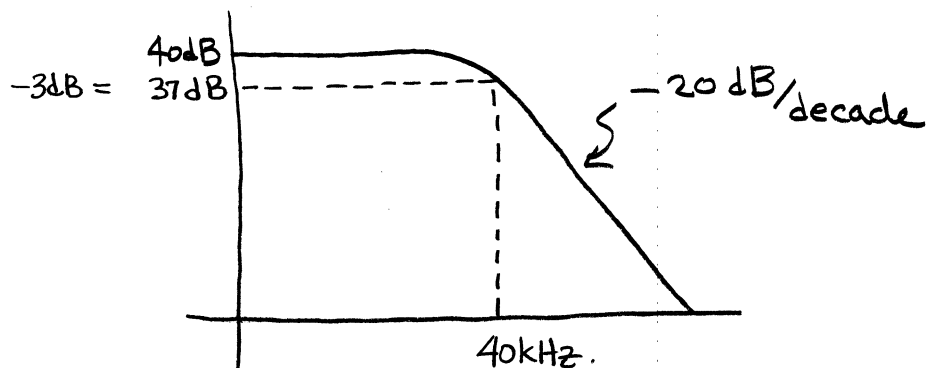If we plot vertical axis in dB  $20 \log(100) = +40 \text{ dB}$   
we get



## Op Amp non-ideal characteristics


1. Non-ideal  $R_{in}$ ,  $R_{out}$
2. finite, frequency dependent gain
3. output voltage limits, typically close to  $\pm V_{cc}$   
 $\pm 12$  volts for 741
4. output current limits  
up to  $\pm 25$  mA for 741

5. slew rate limitation  $\left| \frac{dv_o}{dt} \right| \leq SR$


6. power bandwidth

frequency range over which op amp can produce undistorted sine wave with  $V_{peak}$  equal to guaranteed maximum voltage

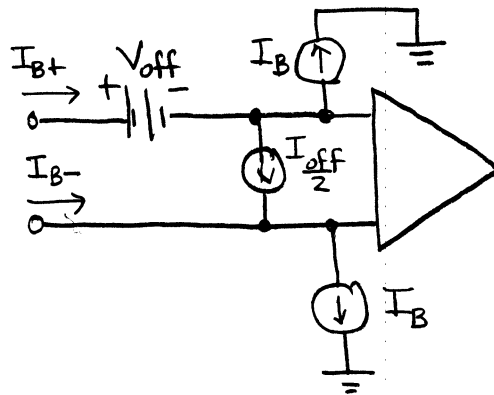7. input offset current and voltage model



## Basic noninverting amplifier

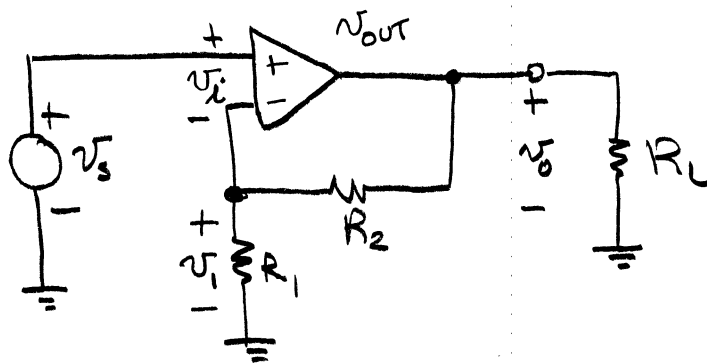

positive output to inverting input  $\rightarrow$  NEGATIVE feedback

$$\Rightarrow v_i = 0$$

$\Rightarrow v_i = v_s$  by virtual short.

$$\text{but } v_i = \frac{R_1}{R_1 + R_2} v_o$$

$$\therefore v_i = \frac{R_1}{R_1 + R_2} v_o \quad \text{or} \quad \frac{v_o}{v_i} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$


$$R_{in} \rightarrow \infty$$

As we argued for inverting amplifier  $R_{out} \rightarrow 0$  since  $v_{out}$  independent of  $R_L$




# Schmitt trigger

POSITIVE feedback.

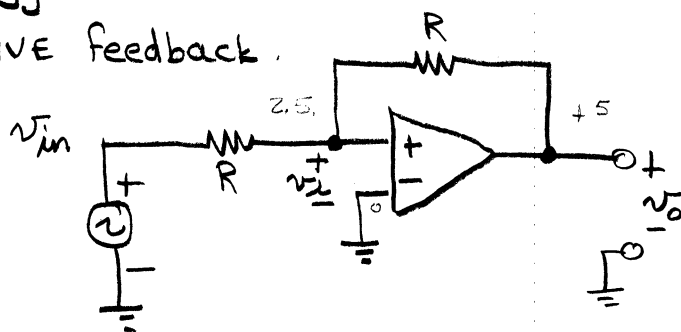


system transfer function

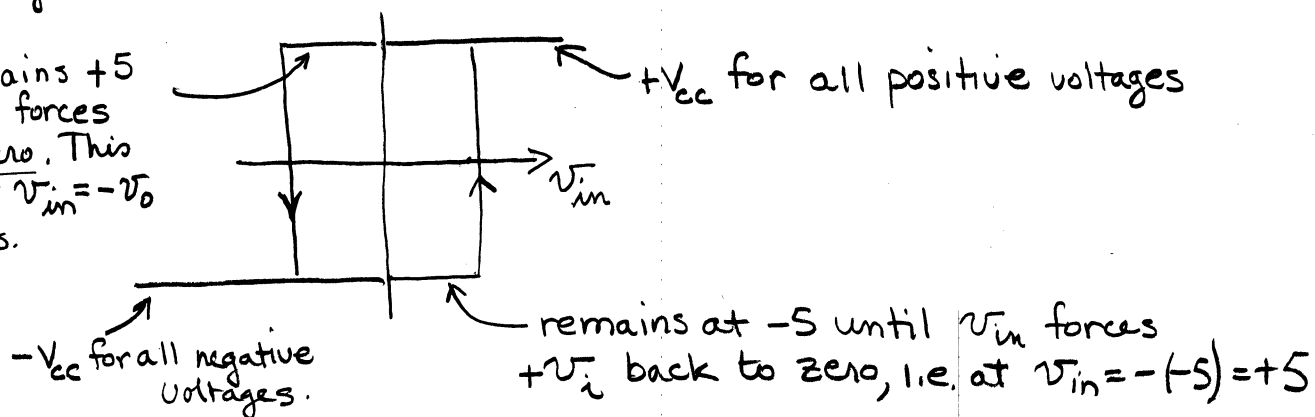remains  $+5$   
until input forces  
 $+V_i$  to zero. This  
occurs at  $V_{in} = -V_o$   
or  $-5$  volts.



Good circuit to square up waveforms.

## Summing amplifier

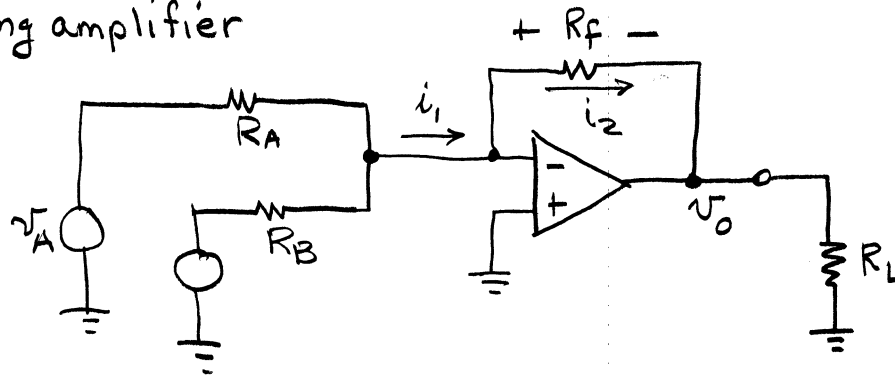

Same as before  $V_- = V_+ = 0$ .

$$i_1 = \frac{v_A}{R_A} + \frac{v_B}{R_B}$$

$$i_2 = i_1$$

$$v_o = V_- - i_2 R_f = 0 - i_2 R_f = -\left(\frac{v_A}{R_A} + \frac{v_B}{R_B}\right) R_f$$

$$v_o = -\frac{R_f}{R_A} v_A - \frac{R_f}{R_B} v_B$$