

<File: Exam #2 S'02>
EECS 245 - SPRING 2002

EXAM#2 – 4/8/02

NAME: _____ CWRUnet e-mail address: _____

Solutions – 51 people took exam, 1 makeup

IMPORTANT INFORMATION:

1. All questions are not worth the same.
2. Exam is closed book, closed notes. Calculators are allowed.

		Possible	
1.	<input type="text"/>	16	Large signal BJT models
2.	<input type="text"/>	16	BJT small signal model (CE)
3.	<input type="text"/>	20	DC biasing of BJTs
4.	<input type="text"/>	20	DC characteristics of MOSFETs
5.	<input type="text"/>	18	Biasing MOSFETs
6.	<input type="text"/>	24	Small signal MOSFET amplifier
SCORE	<input type="text"/>	114	

NOTE: Some formulas of potential interest

MOSFETs

$$I_D = K(V_{GS} - V_T)^2$$

$$g_m = 2K(V_{GS} - V_T)$$

BJTs

$$V_T = 26\text{mV @ } 300^\circ\text{C}$$


$$r_\pi = \frac{\beta V_T}{I_{C,Q}}$$

$$g_m = \frac{\beta}{r_\pi} = \frac{I_{C,Q}}{V_T}$$

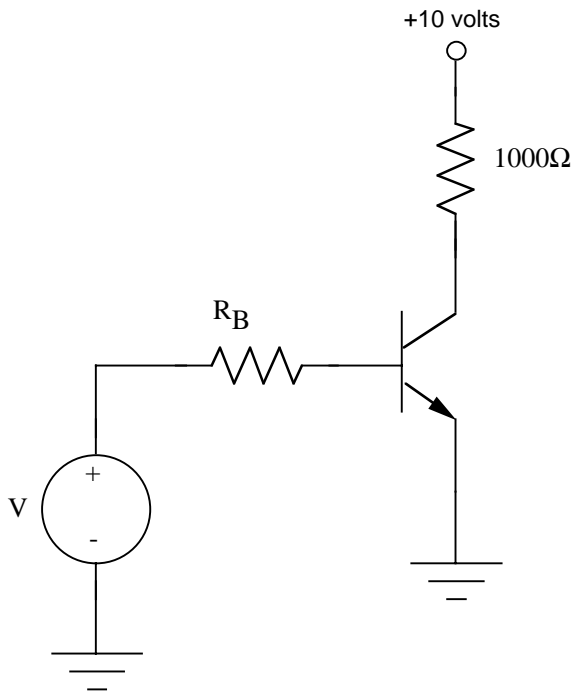1. Large Signal BJT Models

The following BJT transistor amplifier uses a transistor with $\beta=100$ and $V_{BE}=0.7$ volts; R_B is $100k\Omega$. State any assumptions you use to answer the following questions.

- Assume the transistor is in cutoff. What are the collector current and collector-emitter voltage for the transistor in cutoff. For what range of input voltages is the transistor in the cutoff region?
- For what range of input voltage V will the transistor be in the active region?



ANSWER:

(a) If the transistor is cutoff, the collector-emitter junction is open giving $V_{CE}=10$ volts, $I_C=0$. The transistor will be cutoff as long as $V \leq 0.7$ volts.

(b) For the transistor in the active region the base current will be $I_B = \frac{V - V_{BE}}{R_B} = \frac{V - 0.7}{100k}$

The collector current is then $I_C = \beta I_B = \beta \frac{V - 0.7}{100k}$.

The saturation current is $I_{C(SAT)} = \frac{V_{CC} - V_{CE,SAT}}{R_C} = \frac{10\text{volts} - 0.2\text{volts}}{1k\Omega} = 9.8\text{mA}$

Name: _____

EECS 245: Exam #2

e-mail: _____

April 8, 2002

For active region operation $I_C = \beta \frac{V - 0.7}{100k} \leq I_{C(SAT)} = 9.8mA$ which can be solved for V to give $(V - 0.7) \leq \frac{I_{C(SAT)}}{\beta} R_C = \frac{9.8mA}{100} 100k\Omega = 9.8volts$, or $V \leq 10.5volts$ for active mode operation. Together with (a), this defines the active region for $0.7volts \leq V \leq 10.5volts$

GRADING:

(a) 8 points

I_C -3 points

V_{CE} -2 points

no input voltage, -3 points


-1 if you identified the wrong voltage as less than 0.7 volts

(b) 8 points

-6 points if you got I_B but not V_{in}


-4 points if no upper limit for V_{in}

2. Small Signal BJT Equivalent Circuits

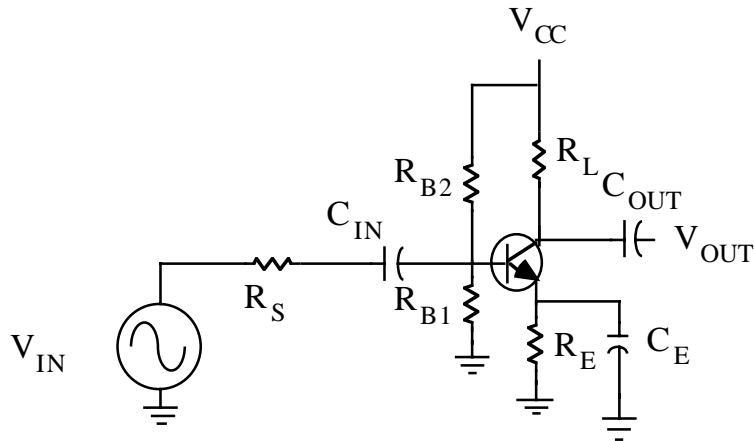

Consider the above BJT amplifier where $R_S=500\Omega$, $R_{B1}=2.7k\Omega$, $R_{B2}=7.5k\Omega$, $R_E=200\Omega$, $R_L=100\Omega$. The transistor is characterized by $\beta=80$. The amplifier is biased such that $V_{CE,Q}=10$ volts, $I_{C,Q}=15mA$. You may assume that C_E , C_{IN} and C_{OUT} have a low impedance at mid-frequency. Draw the small-signal equivalent circuit for the BJT small signal amplifier at mid-frequency. Indicate the values of all small signal parameters in your circuit. DO NOT CALCULATE A_v , R_{in} , etc..

ANSWER:

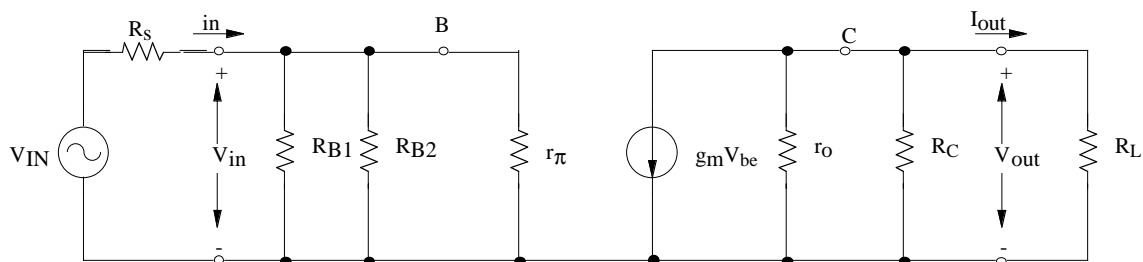

The only values which need to be computed are g_m and r_π . Using the formulas we get

$$r_\pi = \frac{\beta V_T}{I_{C,Q}} = \frac{(80)(26mV)}{15mA} = 138.7\Omega \quad \text{and} \quad g_m = \frac{\beta}{r_\pi} = \frac{I_{C,Q}}{V_T} = \frac{15mA}{26mV} = 0.576S$$

GRADING:

10 points for small signal circuit diagram;

-3 points each for g_m and r_π if you did not include them. NOTE you could use βi_b as well.


-1 for wrong resistor values

-2 for wrong values of small signal parameters

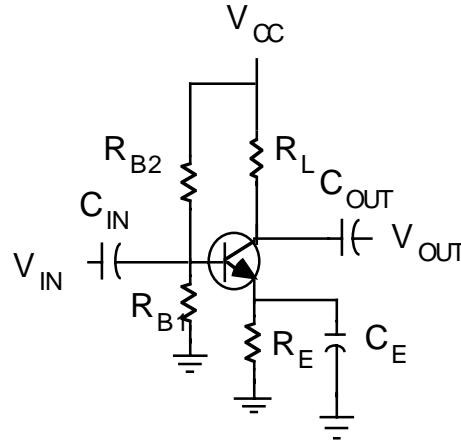3. DC Biasing of BJTs

Draw the DC circuit for the following AC amplifier. Determine $I_{C,Q}$ and $V_{CE,Q}$.

The circuit parameters are $R_L=1k\Omega$, $R_E=1k\Omega$, $R_{B1}=4.7k\Omega$, $R_{B2}=10k\Omega$ and $V_{CC}=18$ volts. The transistor has a DC current gain $\beta=130$.



ANSWER:


The problem is most easily solved by Thevenizing the input circuit. We can compute these as

$$R_T = \frac{R_{B1}R_{B2}}{R_{B1} + R_{B2}} = \frac{(10k\Omega)(4.7k\Omega)}{10k\Omega + 4.7k\Omega} = 3197\Omega$$

and

$$V_T = \frac{R_{B1}}{R_{B1} + R_{B2}} V_{CC} = \frac{4.7k\Omega}{10k\Omega + 4.7k\Omega} (18\text{Volts}) = 5.755\text{Volts}$$

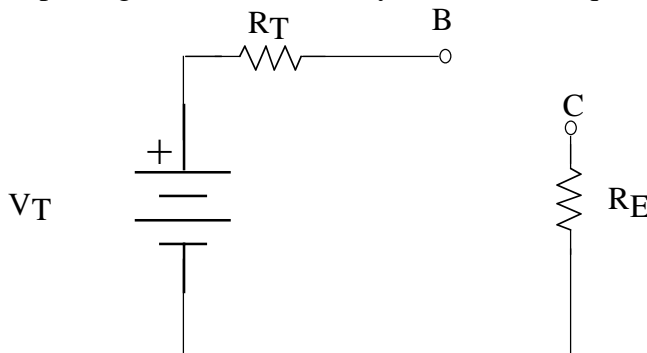Replacing the bias network by its Thevenin equivalent we get the circuit:



Doing KVL around this circuit we get $-V_T + I_B R_T + V_{BE} + (\beta + 1)I_B R_E = 0$ which becomes

$$-5.755 + I_B (3197\Omega) + 0.7 + (130 + 1)I_B (1000\Omega) = 0 \text{ or } I_B = \frac{5.055\text{volts}}{134197\Omega} = 37.67\mu A. \text{ Then}$$

$$I_{C,Q} = \beta I_B = (130)(37.67\mu A) = 4.897\text{mA}. \text{ Using this value we can compute } V_{CE,Q} \text{ as}$$

Name: _____

EECS 245: Exam #2

e-mail: _____

April 8, 2002

$V_{CC} = I_C R_L + V_{CE,Q} + (I_C + I_B) R_E$. Substituting gives

$18\text{volts} = (11.18\text{mA})(1\text{k}\Omega) + V_{CE,Q} + (11.18\text{mA} + 86.067\mu\text{A})(1\text{k}\Omega)$. Solving this equation gives

$$V_{CE,Q} = 18\text{volts} - 4.897\text{volts} - 4.935\text{volts} = 8.168\text{volts}$$

GRADING:

Getting the correct numerical value of the base current was worth 10 points.


V_T and R_T were worth 2 points each

You got 6 points if you got to a correct equation for the base current.


Getting the correct value for $I_{C,Q}$ and $V_{CE,Q}$ were worth 5 points each.

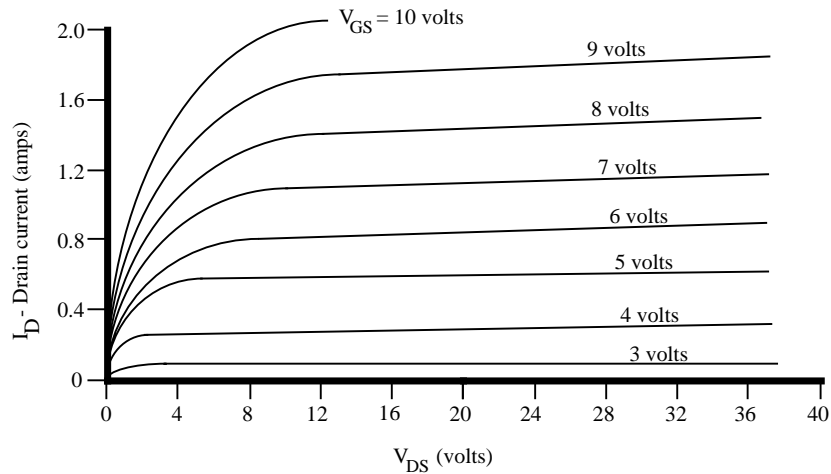4. DC characteristics of MOSFETs

The following questions refer to the measured characteristics (shown below) of a 2N5447 MOSFET. The data was taken with a Tektronix 575 curve tracer.





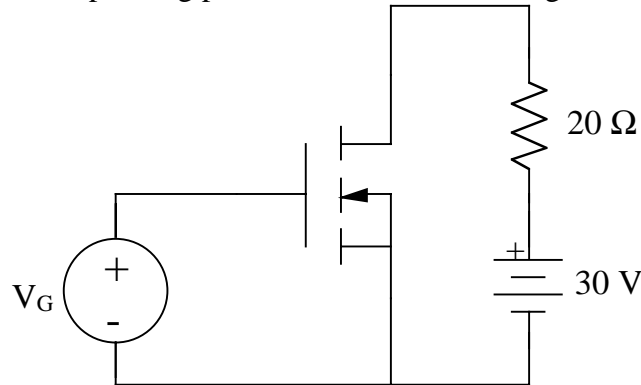- (a) Graphically estimate the threshold voltage (V_{TO}) of the MOSFET from the data.
- (b) The MOSFET described above is connected in the circuit shown below. For $V_G = 6$ volts, determine the DC operating point of the MOSFET using a load line analysis.



- (a) ANSWER: By inspection the threshold voltage must be smaller than 3 volts. A good answers would be 2-3 volts although anything above zero would be probably OK,
- (b) ANSWER: The x-intercept of the load line is 30 volts. The y-intercept of the load line is given by $i_D = \frac{30 \text{ volts}}{20 \Omega} = 1.5 \text{ amps}$. Drawing this line and estimating its intersection with the curve for $V_{GS} = 6$ volts gives (12 volts, 0.8 amps) for the operating point.

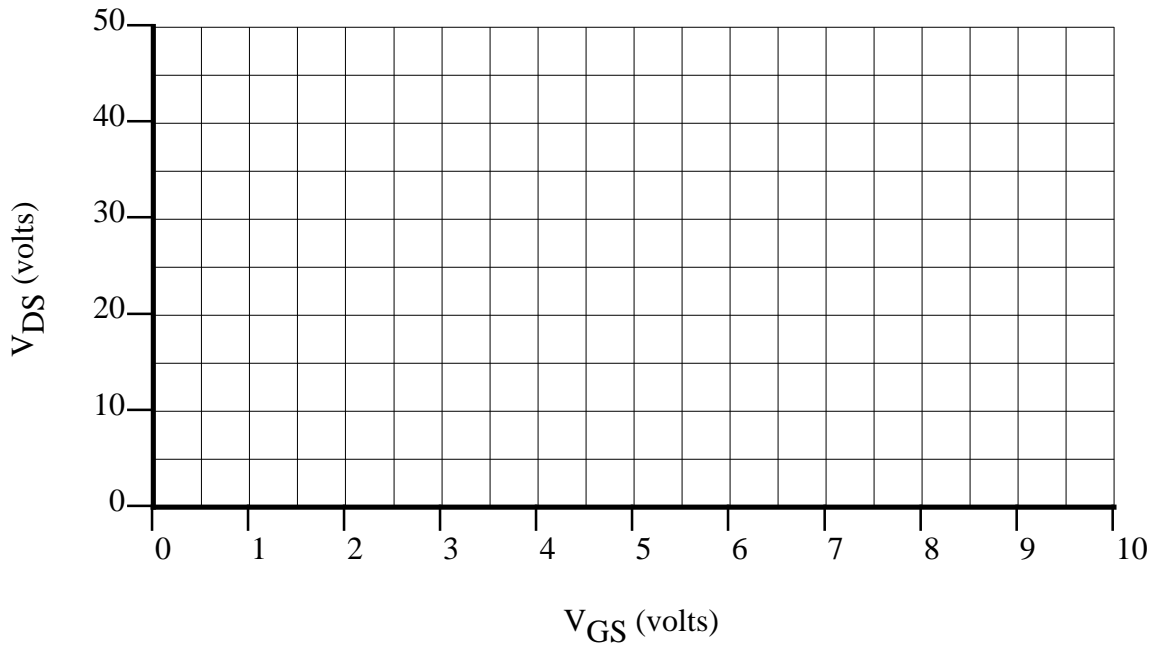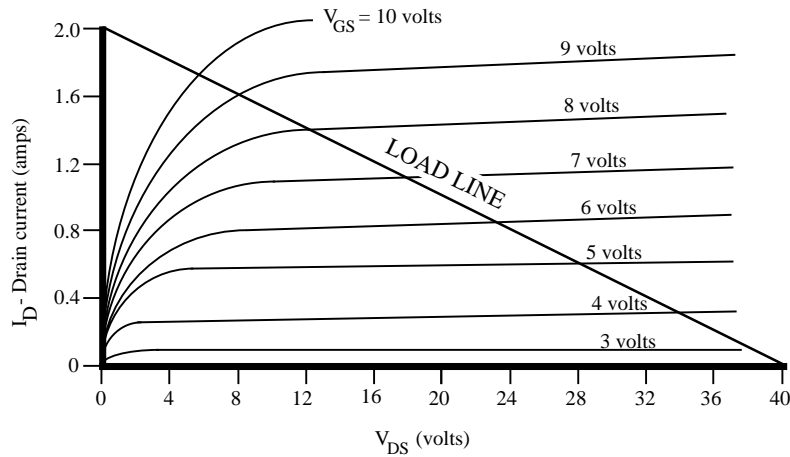- (c) Assuming the operation of the MOSFET circuit is described by the characteristic data/load line shown below, determine V_{DS} as a function of V_{GS} for V_{GS} ranging from 0 to 10 volts. Using this plot sketch the change in V_{DS} as a function of V_{GS} if $V_{GS} = 6 \text{ volts} + 2\cos\omega t$. Do you think this MOSFET circuit would make a good amplifier? Explain why or why not.




Name: _____

EECS 245: Exam #2

e-mail: _____

April 8, 2002

ANSWER:

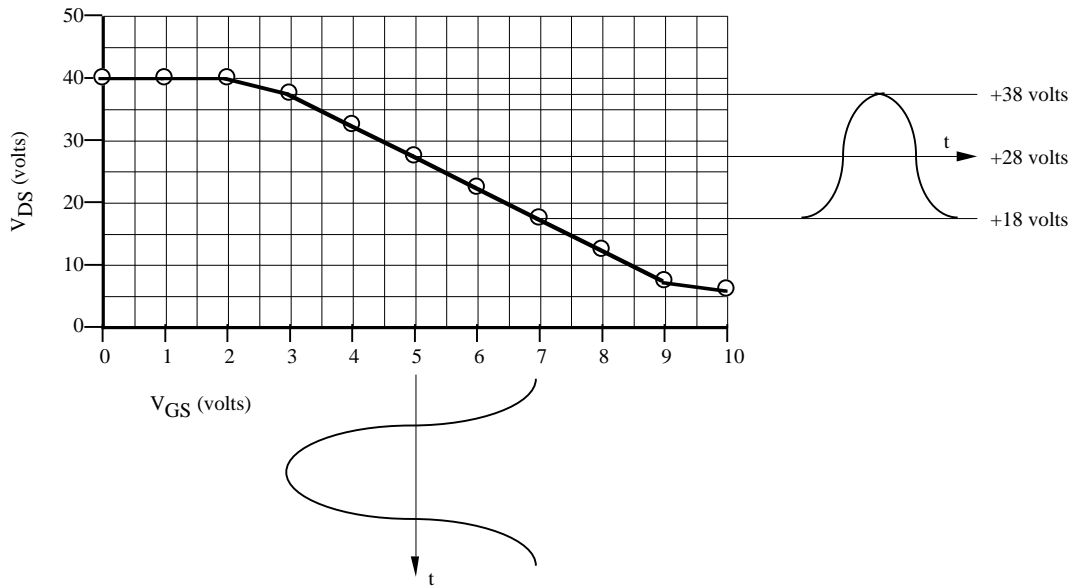


This circuit would make an excellent amplifier. It has a nice, long transfer curve and the input signal is approximately in the middle of the region resulting in undistorted output with a gain of approximately 5.

GRADING:

- (a) V_{TO} was worth 3 points
- (b) 3 points for each end of the load line, 2 points for the actual Q point
- (c) The sketch was worth 6 points; sketching and/or describing the amplifier output was worth 4 points. A number of people had the wrong output voltage for V_{GS} less than 2-3 volts — you lost 1 point for the wrong value of V_{DS} in this region. You lost 2 points for not discussing the amplifier output

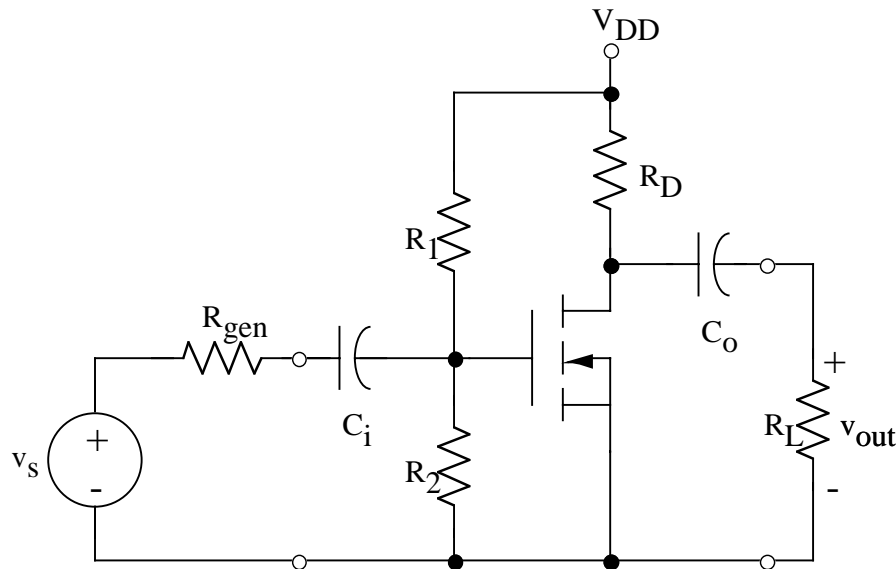5. Biasing MOSFETs

For the MOSFET amplifier circuit shown below determine the DC operating point of the transistor, i.e. determine I_D , V_{DS} , and V_{GS} .



The circuit uses the values $R_{gen}=10\text{k}\Omega$, $V_{DD}=18\text{V}$, $R_1=3.3\text{M}\Omega$, $R_2=1.2\text{M}\Omega$, $R_D=2\text{k}\Omega$, and $R_L=5\text{k}\Omega$. The MOSFET is characterized by $K=0.96\text{mA/V}^2$ and $V_T=2.5\text{V}$.

ANSWER:

There is no voltage at the source as it is connected directly to ground. V_{GS} is determined only by V_G which is set by the R_1 - R_2 voltage divider.

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{1.2\text{M}\Omega}{1.2\text{M}\Omega + 3.3\text{M}\Omega} (18\text{V}) = (0.27)(18\text{V}) = 4.8\text{Volts}$$

With the transistor parameter K AND V_{GS} we can calculate the drain current as:

$$I_D = K(V_G - V_T)^2 = 0.96 \frac{\text{mA}}{\text{V}^2} (4.8\text{V} - 2.5\text{V})^2 = 5.08\text{mA}$$


Once the drain current is known we can apply KVL to the loop from ground through the transistor, through R_D , and through the power supply to ground to get:

$$V_{DS} = V_{DD} - I_D R_D = 18 - (5.08\text{mA})(2\text{k}\Omega) = 7.84\text{Volts}$$

GRADING:

V_{GS} , I_D and V_{DS} were worth 6 points apiece each.

6. Small Signal Amplifier Analysis

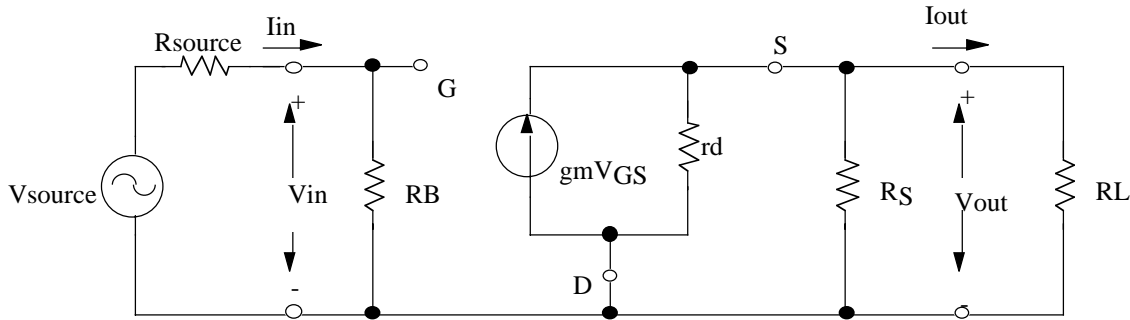

A student in EECS 245 has obtained the above small signal equivalent circuit for a MOSFET amplifier. The circuit parameters are $R_{\text{SOURCE}}=100\Omega$, $R_B=1.5\text{M}\Omega$, $R_S=330\Omega$, and $R_L=100\Omega$.

The transistors small signal parameters are $g_m=0.05\text{S}$ and $r_d=100\text{k}\Omega$.

- Determine the small signal voltage gain of this amplifier.
- What is the input impedance R_{in} of this amplifier? The output impedance R_{out} ?
- What is the current gain of this amplifier ASSUMING THAT $R_{\text{in}}=200\text{kohms}$,

$$R_{\text{out}}=1000\text{ohms}, \text{ and } \frac{V_{\text{out}}}{V_{\text{in}}} = 1?$$

Answer:

- R_d is so large compared to $R_S \parallel R_L$ that it can be neglected. Then

$$R_L' = R_S \parallel R_L = \frac{R_S R_L}{R_S + R_L} = \frac{(330\Omega)(100\Omega)}{330\Omega + 100\Omega} = 76.75\Omega$$

$$\text{In the output circuit } V_{\text{out}} = +(g_m V_{GS}) R_L' = +(0.05 V_{GS})(76.75\Omega) = 3.84 V_{GS} \quad [1]$$

$$\text{Using KVL around the circuit also gives } -V_{\text{in}} + V_{GS} + V_{\text{out}} = 0. \quad [2]$$

Substituting [1] into [2] gives $-V_{\text{in}} + \frac{V_{\text{out}}}{3.84} + V_{\text{out}} = 0$ which can be solved to give the voltage

$$\text{gain } -V_{\text{in}} + 1.26 V_{\text{out}} = 0, \text{ or } \frac{V_{\text{out}}}{V_{\text{in}}} = +0.79$$

-

By inspection. $R_{\text{in}}=R_B=1.5\text{M}\Omega$

Using the definition for the output resistance and applying a test voltage source we get

$$R_{\text{out}} = \frac{V_T}{I_T} = \frac{V_T}{\frac{V_T}{r_d} + \frac{V_T}{R_S} + g_m V_T} = r_d \parallel R_S \parallel \frac{1}{g_m}$$

Name: _____

EECS 245: Exam #2

e-mail: _____

April 8, 2002

After substituting values we have $R_{out} = r_d \parallel R_s \parallel \frac{1}{g_m} = 100k\Omega \parallel 330\Omega \parallel 20\Omega \cong 18.85\Omega$

(c)

$$A_i = \frac{i_{out}}{i_{in}} = \frac{V_{out} / R_{out}}{V_{in} / R_{in}} = \frac{V_{out}}{V_{in}} \frac{R_{in}}{R_{out}} = (1) \frac{200k\Omega}{1k\Omega} = 200$$

GRADING:

(a)

A_v was worth 10 points

-4 points for using wrong R_L

-5 points for calculating V_{GS} wrong. Typically, you forgot that $V_{GS} \neq V_{in}$ in this circuit.

(b) R_{in} and R_{out} were worth 4 points each

Failing to include g_m lost you 2 points. Math errors cost you 1 point.

(c)

This was worth 6 points.