

EEAP 245 Electronics

Homework Assignment #9

Due Wednesday April 24th no later than 5PM.

Read Thomas & Rosa

p.448-449, cover-up algorithm

Sect. 9.5 Special cases: improper functions, multiple poles

Sect. 10.3 p.495-500, zero-input response, zero-state response

Sect. 11.1 Definition of network functions

Sect. 11.3 p. 554-555, definition of impulse response

Sect. 11.4 p. 555-557, definition of step response

Do the following problems

10-15 L network, forced & natural poles

10-21 LC network, forced & natural poles

11.1 Network function, do not determine $Z(s)$ in (a) & (b)

11.4 Network function, do not determine $Z(s)$ in (a) & (b)

11.27 Step response, do not determine the impulse response waveform

11.28 Do not find the step response, just determine the transfer function $T(s)$