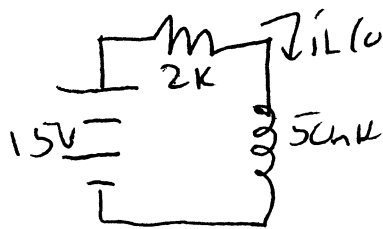


EECS 245 HWK #9 Solution



10.15

With the switch closed, the circuit reduces to that



shown. $i_L(t) = \frac{15V}{2000} = \underline{7.5mA}$

s-domain circuit:

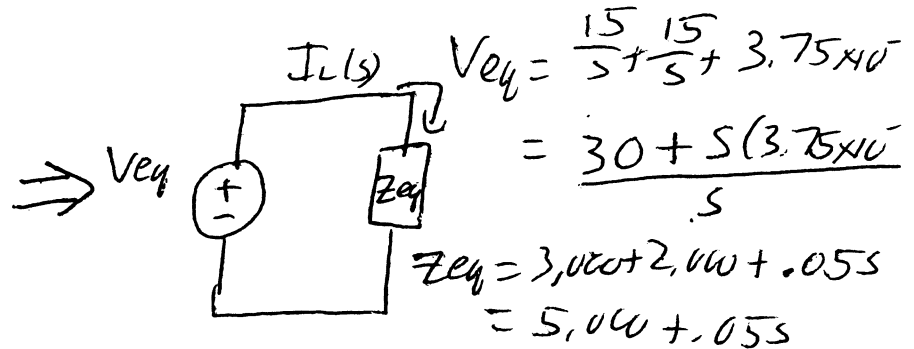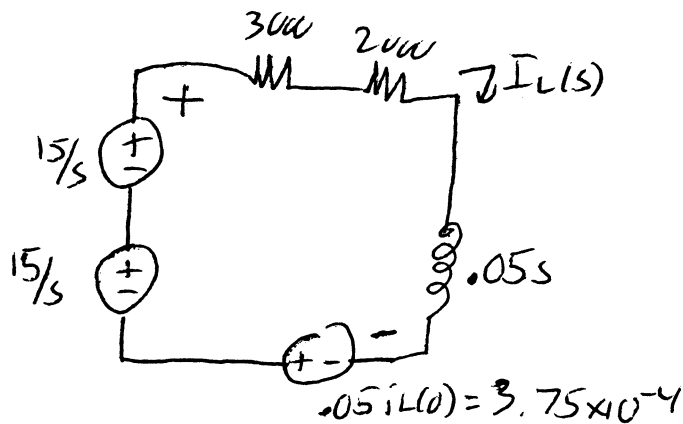

$$I_L(s) = \frac{V_{eq}}{Z_{eq}} = \frac{30 + s(3.75 \times 10^{-4})}{s(0.05s + 5,000)} = \frac{600 + 0.0075s}{s(s + 100,000)} = \frac{K_1}{s} + \frac{K_2}{s + 100,000}$$



$$K_1 s + 100,000 K_1 + K_2 s = 600 + 0.0075s \quad K_1 = \frac{3}{500} \quad K_2 = \frac{3}{2,000}$$

$$I_L(s) = s\left(\frac{3}{500}\right) + \left(\frac{3}{2,000}\right)\left(\frac{1}{s + 100,000}\right)$$

$$\hat{i}_L(t) = \frac{3}{500} \left(1 + \frac{1}{4} e^{-100,000t}\right) A$$

standard inverse Laplace using table 9-2.

10.21 (a)

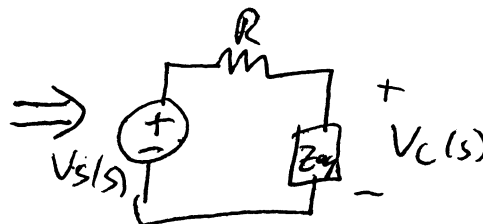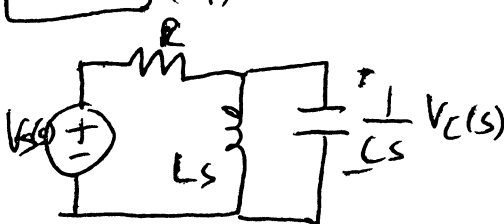

$$Z_{eq} = Ls \parallel \frac{1}{cs} = \frac{Ls(\frac{1}{cs})}{Ls + 1/cs} = \frac{Ls}{Lcs^2 + 1}$$

⇒

0.21 cont

By voltage division, $V_C(s) = \frac{V_S(s) Z_{eq}}{R + Z_{eq}}$

$$V_C(s) = V_S(s) \frac{\frac{Ls}{Ls^2 + 1}}{R + \frac{Ls}{Ls^2 + 1}}$$

$$V_C(s) = V_S(s) \left[\frac{Ls}{Ls^2 + R + Ls} \right]$$

3) $\mathcal{L}[100u(t)] = \frac{100}{s}$ $V_C(s) = \left(\frac{s \cdot 0.05}{1.25 \times 10^{-5} s^2 + 0.05s + 5,000} \right) \left(\frac{100}{s} \right)$

$$V_C(s) = \frac{4 \times 10^5}{s^2 + 4,000s + 4 \times 10^8}$$

Solving $s^2 + 4,000s + 4 \times 10^8$

$$s = -2,000 \pm j20,000$$


Natural poles: $-2,000 \pm j20,000$

Forced-poles: none

* The $s=0$ pole caused by the step function is cancelled by a natural zero

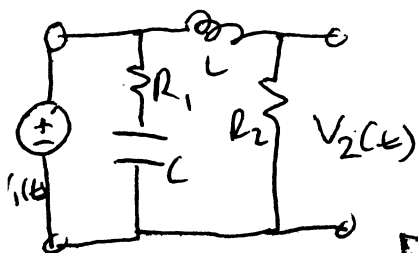1.1 (a)

$T_V(s) = \frac{V_2(s)}{V_1(s)}$ By simple voltage division, $V_2(s) = \frac{R_2}{Ls + R_2} V_1(s)$




$$T_V(s) = \frac{R_2}{Ls + R_2}$$

(b) $T_V(s) = \frac{2000}{s + 2000} = \frac{20,000}{s + 20,000}$

$T_V(s)$ has a pole at $s = -20,000$

1.4

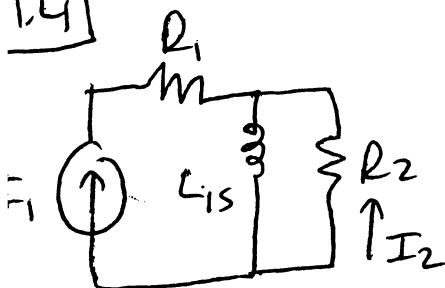

(a) By current division, $I_2 = \frac{-L_1 s}{L_1 s + R_2} \cdot I_1(s)$

$$T_I(s) = \frac{I_2(s)}{I_1(s)} = \frac{-L_1 s}{L_1 s + R_2}$$

$L_2 s$ is shorted out by the short over $V_2(t)$

(b) $T_I(s) = \frac{-0.4s}{0.4s + 2,000} = \frac{-s}{s + 5,000}$

$T_I(s)$ has a zero at $s=0$ and a pole at $s=-5,000$

11.27 Just find the transfer functions $T(s) = SG(s)$ by eqn 11-15

(a) $g(t) = u(t)e^{-2,000t}$ $T(s) = SG(s) = s \mathcal{L}\{g(t)\}$ $T(s) = \frac{-s}{s+2,000}$

(b) $T(s) = SG(s) = s \mathcal{L}\{u(t) - u(t)e^{-2,000t}\} = s \left(\frac{1}{s} - \frac{1}{s+2,000} \right)$

$$T(s) = \frac{2,000}{s+2,000}$$

11.28 $T(s) = H(s)$ by eqn. 11-14

(a) $H(s) = \frac{-1,000}{s+2,000} = T(s)$

(b) $H(s) = 1 - \frac{2,000}{s+2,000}$ $T(s) = \frac{s}{s+2,000}$

11.37 $G(s) = \mathcal{L}[e^{-1,000t}]u(t) = \frac{1}{s+1,000}$ $T(s) = SG(s) = \frac{s}{s+1,000}$

$x(t) = 5 \cos 2,000t$ by eqn 11-24:

Amplitude = $5 |T(j \cdot 2,000)| = 5 \left| \frac{j \cdot 2,000}{j \cdot 2,000 + 1,000} \right|$ Amplitude = 4.472

phase angle = $\phi + \theta = 0 + \text{angle} \left(\frac{j \cdot 2,000}{j \cdot 2,000 + 1,000} \right)$ $\phi = 26.565^\circ$

11.40 $h(t) = [400e^{-100t} - 400e^{-5,000t}]u(t)$ $H(s) = T(s) = 400 \left(\frac{1}{s+100} - \frac{1}{s+5,000} \right)$

$T(s) = \frac{1.96 \times 10^6}{(s+100)(s+5,000)}$ Amplitude = $5 \left| \frac{1.96 \times 10^6}{(700j+100)(700j+5,000)} \right| = 2.745$

$\phi = \text{angle} \left| \frac{1.96 \times 10^6}{(700j+100)(700j+5,000)} \right|$ $\phi = -89.84^\circ$