

# Field-Effect Transistors

## 9-1 INTRODUCTION

A field-effect transistor (FET) may be specified by a device statement. PSpice generates complex models for FETs. These models are quite complex and incorporate an extensive range of device characteristics (e.g., dc and small-signal behavior, temperature dependency, and noise generation). If such complex models are not necessary, users can ignore many model parameters, and PSpice assigns default values to the parameters. The FETs are of three types:


- Junction field-effect transistors (JFETs)
- Metal-oxide silicon field-effect transistors (MOSFETs)
- Gallium arsenide MESFETs

## 9-2 JUNCTION FIELD-EFFECT TRANSISTORS


The PSpice JFET model is based on the FET model of Schichman and Hodges [1]. The model of an  $n$ -channel JFET is shown in Fig. 9-1. The small-signal model and the static (or dc) model, which are generated by PSpice, are shown in Figs. 9-2 and 9-3, respectively. The model parameters for a JFET device and the default values assigned by PSpice are given in Table 9-1. The model equations of JFETs that are used by PSpice are described in Schichman and Hodges [1], Vladimirescu and Liu [3], and the *PSpice Manual* [7].

The model statement of an  $n$ -channel JFET has the general form


```
.MODEL JNAME NJF (P1=A1 P2=A2 P3=A3 ... PN=AN)
```

 

**Figure 9-1** PSpice *n*-channel JFET.

 

**Figure 9-2** Small-signal *n*-channel JFET model.

 

**Figure 9-3** Static *n*-channel JFET model.

**TABLE 9-1** MODEL PARAMETERS OF JFETS

Name	Area	Model parameters	Units	Default	Typical
VTO		Threshold voltage	Volts	-2	-2
BETA	*	Transconductance coefficient	Amps/Volts <sup>2</sup>	1E-4	1E-3
LAMBDA		Channel-length modulation	Volts <sup>-1</sup>	0	1E-4
RD	*	Drain ohmic resistance	Ohms	0	100
RS	*	Source ohmic resistance	Ohms	0	100
IS	*	Gate <i>p-n</i> saturation current	Amps	1E-14	1E-14
PB		Gate <i>p-n</i> potential	Volts	1	0.6
CGD	*	Gate-drain zero-bias <i>p-n</i> capacitance	Farads	0	5PF
CGS	*	Gate-source zero-bias <i>p-n</i> capacitance	Farads	0	1PF
FC		Forward-bias depletion capacitance coefficient		0.5	
VTOTC		VTO temperature coefficient	Volts/°C	0	
BETATCE		BETA exponential temperature coefficient	percent/°C	0	
KF		Flicker noise coefficient		0	
AF		Flicker noise exponent		1	

and for a *p*-channel JFET, the statement has the form

```
.MODEL JNAME PJF (P1=A1 P2=A2 P3=A3 . . . PN=AN)
```

where JNAME is the model name; it can begin with any character and its word size is normally limited to eight characters. NJF and PJF are the type symbols of *n*-channel and *p*-channel JFETs, respectively. P1, P2, . . . and A1, A2, . . . are the parameters and their values, respectively.

As with diodes and BJTs, an *area factor* is used to determine the number of equivalent parallel JFETs. The model parameters that are affected by the area factor are marked by an asterisk (\*) in Table 9-1. The [(area value)] scales BETA, RD, RS, CGD, CGS, and IS; it defaults to 1.

RD and RS represent the contact and bulk resistances per unit area of the drain and source, respectively. The JFET is modeled as an intrinsic device. The area value, which is the relative device area, is specified in the .MODEL statement and changes the actual resistance values. The default value of the area is 1.

The dc characteristics that are represented by the nonlinear current source  $I_D$  are defined (1) by parameters VTO and BETA, which determine the variation of the drain current with the gate voltage, (2) by LAMBDA, which determines the output conductance, and (3) by IS, which determines the reserve saturation current of the two gate junctions. VTO is negative for depletion-mode JFETs, both for *n*-channel and *p*-channel types, and it is positive for enhancement-mode JFETs. VTO does not identify whether the JFET is *n*-channel or *p*-channel.

The symbol for a JFET is *J*. The name of a JFET must start with *J* and it takes the general form of

```
J(name) ND NG JNAME [(area) value]
```

where ND, NG and NS are the drain, gate, and source nodes, respectively.

### Some JFET Statements

```
JIM 5 6 8 JNAME
.MODEL JNAME NJF
J15 3 9 12 SWITCH 1.5
.MODEL SWITCH NJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 VTO=-5)
JQ 1 5 9 JMOD
.MODEL JMOD PJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 CGD=5PF CGS=1PF
+VTO=5)
```

## 9-3 JFET PARAMETERS

The library file EVAL.LIB of the student version of PSpice supports models for  $n$ -channel JFETs: J2N3819 and J2N4393. As an example, we shall generate approximate values of some parameters [8, 9] from the data sheet of the  $n$ -channel JFET of type 2N5459, shown in Fig. 9-4.

$I_{DSS} = 4$  to  $16$  mA at  $V_{GS} = 0$  V, and  $V_{DS} = 15$  V. Taking the geometric mean,

$$I_{DSS} = \sqrt{(4 \times 16)} = 8 \text{ mA}$$

The threshold voltage,  $V_{Th} = V_{GS(off)} = -2$  to  $-8$  V. Taking the geometric mean,

$$V_{Th} = -\sqrt{(2 \times 8)} = -4 \text{ V}$$

That is,  $VTO = -4$  V (for depletion-mode).

The transconductance coefficient is given by

$$\begin{aligned} \text{BETA} &= \frac{I_{DSS}}{V_{Th}^2} \\ &= \frac{8 \text{ mA}}{(-4)^2} = 0.5 \text{ mA/V}^2 \end{aligned} \quad (9-1)$$

The gate reverse current  $I_{GSS} = -IS = -1$  nA at  $V_{GS} = -15$  V, and  $V_{DS} = 0$ .

The common-source reverse transfer capacitance,  $C_{rss} = C_{gd} = 1.5$  to  $3$  pF at  $V_{DS} = 15$  V, and  $V_{GS} = 0$  V. Taking the geometric mean,

$$C_{rss} = C_{gd} = \sqrt{(1.5 \times 3)} \text{ pF} = 2.12 \text{ pF}$$


At  $V_{DG} = V_{DS} - V_{GS} = 15 - 0 = 15$  V,  $C_{gdo}$  can be found from

$$C_{gd} = \frac{C_{gdo}}{(1 + V_{DG}/V_{off})^{1/3}} \quad (9-2)$$

where  $V_{off} = 0.75$  V. Equation (9-2) gives,  $C_{gdo} = 5.85$  pF.

# 2N5460 thru 2N5465

CASE 29-04, STYLE 7  
TO-92 (TO-226AA)

 

JFET  
AMPLIFIER

P-CHANNEL — DEPLETION

## MAXIMUM RATINGS

Rating	Symbol	2N5460 2N5461 2N5462	2N5463 2N5464 2N5465	Unit
Drain-Gate Voltage	V <sub>DG</sub>	40	60	Vdc
Reverse Gate-Source Voltage	V <sub>GSR</sub>	40	60	Vdc
Forward Gate Current	I <sub>G(f)</sub>	10		mA <sub>dc</sub>
Total Device Dissipation (at T <sub>A</sub> = 25°C Derate above 25°C)	P <sub>D</sub>	310	2.82	mW mW/°C
Junction Temperature Range	T <sub>J</sub>	-65 to +135		°C
Storage Channel Temperature Range	T <sub>stg</sub>	-65 to +150		°C

## ELECTRICAL CHARACTERISTICS (T<sub>A</sub> = 25°C unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
<b>OFF CHARACTERISTICS</b>					
Gate-Source Breakdown Voltage (I <sub>G</sub> = 10 μA <sub>dc</sub> , V <sub>DS</sub> = 0)	V(BR)GSS	40 60	—	—	Vdc
Gate Reverse Current (V <sub>GS</sub> = 20 Vdc, V <sub>DS</sub> = 0) (V <sub>GS</sub> = 30 Vdc, V <sub>DS</sub> = 0) (V <sub>GS</sub> = 20 Vdc, V <sub>DS</sub> = 0, T <sub>A</sub> = 100°C) (V <sub>GS</sub> = 30 Vdc, V <sub>DS</sub> = 0, T <sub>A</sub> = 100°C)	I <sub>GSS</sub>	—	—	5.0 5.0 1.0 1.0	nA <sub>dc</sub> μA <sub>dc</sub>
Gate Source Cutoff Voltage (V <sub>DS</sub> = 15 Vdc, I <sub>D</sub> = 1.0 μA <sub>dc</sub> )	V <sub>GS(off)</sub>	0.75 1.0 1.8	—	6.0 7.5 9.0	Vdc
Gate Source Voltage (V <sub>DS</sub> = 15 Vdc, I <sub>D</sub> = 0.1 mA <sub>dc</sub> ) (V <sub>DS</sub> = 15 Vdc, I <sub>D</sub> = 0.2 mA <sub>dc</sub> ) (V <sub>DS</sub> = 15 Vdc, I <sub>D</sub> = 0.4 mA <sub>dc</sub> )	V <sub>GS</sub>	0.5 0.8 1.5	—	4.0 4.5 6.0	Vdc

## ON CHARACTERISTICS

Zero-Gate-Voltage Drain Current (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 1.0 kHz)	I <sub>DSS</sub>	1.0 2.0 4.0	—	5.0 9.0 16	mA <sub>dc</sub>
--	------------------	-------------------	---	------------------	------------------

## SMALL-SIGNAL CHARACTERISTICS

Forward Transfer Admittance (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 1.0 kHz)	y <sub>fs</sub>	1000 1500 2000	—	4000 5000 6000	μmhos
Output Admittance (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 1.0 kHz)	y <sub>os</sub>	—	—	75	μmhos
Input Capacitance (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 1.0 MHz)	C <sub>iss</sub>	—	5.0	7.0	pF
Reverse Transfer Capacitance (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 1.0 MHz)	C <sub>rss</sub>	—	1.0	2.0	pF

## FUNCTIONAL CHARACTERISTICS

Noise Figure (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, R <sub>G</sub> = 1.0 Megohm, f = 100 Hz, BW = 1.0 Hz)	NF	—	1.0	2.5	dB
Equivalent Short-Circuit Input Noise Voltage (V <sub>DS</sub> = 15 Vdc, V <sub>GS</sub> = 0, f = 100 Hz, BW = 1.0 Hz)	e <sub>n</sub>	—	60	115	nV/√Hz

Figure 9-4 Data sheet for the n-channel JFET of type 2N5459 (Courtesy of Motorola, Inc.).

The common-source input capacitance,  $C_{iss} = 4.5$  to  $7$  pF at  $V_{DS} = 15$  V, and  $V_{GS} = 0$  V. Taking the geometric mean,

$$C_{iss} = \sqrt{(4.5 \times 7)} \text{ pF} = 5.61 \text{ pF}$$

Since  $C_{iss}$  is measured at  $V_{GS} = 0$  V,  $C_{gs} = C_{gso}$ . That is,

$$C_{iss} = C_{gso} + C_{gd}$$

which gives  $C_{gso} = C_{iss} - C_{gd} = 5.61 - 2.12 = 3.49$  pF.

The output admittance  $|Y_{os}| = 10$  to  $50$   $\mu\text{mhos}$  at  $V_{DS} = 15$  V, and  $V_{GS} = 0$ . Taking the geometric mean,

$$|Y_{os}| = \sqrt{(10 \times 50)} \mu\text{mhos} = 22.36 \mu\text{mhos}$$

Since  $|Y_{os}|$  is given at  $V_{GS} = 0$ , the channel-modulation length  $\lambda$  (LAMBDA) can be found approximately from

$$\text{LAMBDA} = \frac{|Y_{os}|}{I_{DSS}} \approx \frac{22.36 \mu\text{mhos}}{8 \text{ mA}} = 2.395\text{E}-3$$

The PSpice model statement for the JFET of type J2N5459 is


```
.MODEL J2N5459 NJF (IS=1N VTO=-4 BETA=0.5M CGDO=5.85PF
+ CGSO=3.49PF LAMBDA=2.395E-3)
```

## 9-4 EXAMPLES OF JFET AMPLIFIERS

The approximate values of JFET model parameters can be determined from the data sheet. If a model parameter is not specified, PSpice assumes its default value, as indicated in Table 9-1. The following examples illustrate the PSpice simulation of JFET circuits.

### Example 9-1

For the  $n$ -channel JFET in Fig. 9-5, plot the output characteristics if  $V_{DD}$  is varied from 0 to 12 V in steps of 0.2 V and  $V_{GS}$  is varied from 0 to  $-4$  V in steps of 1 V. The model parameters are  $IS=100\text{E}-14$ ,  $RD=10$ ,  $RS=10$ ,  $BETA=1\text{E}-3$ , and  $VTO=-5$ .

 

**Figure 9-5** A circuit with an  $n$ -channel JFET.

The common-source input capacitance,  $C_{iss} = 4.5$  to  $7$  pF at  $V_{DS} = 15$  V, and  $V_{GS} = 0$  V. Taking the geometric mean,

$$C_{iss} = \sqrt{(4.5 \times 7)} \text{ pF} = 5.61 \text{ pF}$$

Since  $C_{iss}$  is measured at  $V_{GS} = 0$  V,  $C_{gs} = C_{gso}$ . That is,

$$C_{iss} = C_{gso} + C_{gd}$$

which gives  $C_{gso} = C_{iss} - C_{gd} = 5.61 - 2.12 = 3.49$  pF.

The output admittance  $|Y_{os}| = 10$  to  $50$   $\mu\text{mhos}$  at  $V_{DS} = 15$  V, and  $V_{GS} = 0$ . Taking the geometric mean,

$$|Y_{os}| = \sqrt{(10 \times 50)} \mu\text{mhos} = 22.36 \mu\text{mhos}$$

Since  $|Y_{os}|$  is given at  $V_{GS} = 0$ , the channel-modulation length  $\lambda$  (LAMBDA) can be found approximately from

$$\text{LAMBDA} = \frac{|Y_{os}|}{I_{DSS}} \approx \frac{22.36 \mu\text{mhos}}{8 \text{ mA}} = 2.395\text{E-}3$$

The PSpice model statement for the JFET of type J2N5459 is


```
.MODEL J2N5459 NJF (IS=1N VTO=-4 BETA=0.5M CGDO=5.85PF
+ CGSO=3.49PF LAMBDA=2.395E-3)
```

## 9-4 EXAMPLES OF JFET AMPLIFIERS

The approximate values of JFET model parameters can be determined from the data sheet. If a model parameter is not specified, PSpice assumes its default value, as indicated in Table 9-1. The following examples illustrate the PSpice simulation of JFET circuits.

### Example 9-1

For the  $n$ -channel JFET in Fig. 9-5, plot the output characteristics if  $V_{DD}$  is varied from 0 to 12 V in steps of 0.2 V and  $V_{GS}$  is varied from 0 to  $-4$  V in steps of 1 V. The model parameters are  $IS=100\text{E-}14$ ,  $RD=10$ ,  $RS=10$ ,  $BETA=1\text{E-}3$ , and  $VTO=-5$ .

 


**Figure 9-5** A circuit with an  $n$ -channel JFET.

**Solution** The listing of the circuit file follows.

**Example 9-1 Output characteristics of an n-channel JFET**

```
▲ * Gate to source voltage of 0 V
  VGS 1 0 DC 0V
  * A dummy voltage source of 0 V
  VX 3 2 DC 0V
  * Dc supply voltage of 12 V
  VDD 3 0 DC 12V
▲▲ * J1 with model JMOD
  J1 2 1 0 JMOD
  .MODEL JMOD NJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 VTO=-5)
▲▲▲ * VDD is swept from 0 to 12 V and VGS from 0 to -4 V.
  .DC VDD 0 12 0.2 VGS 0 -4 1
  .PLOT DC I(VX)
  .PROBE
.END
```

The output characteristics, which are plots of  $I_D$  versus  $V_{DD}$ , are shown in Fig. 9-6.

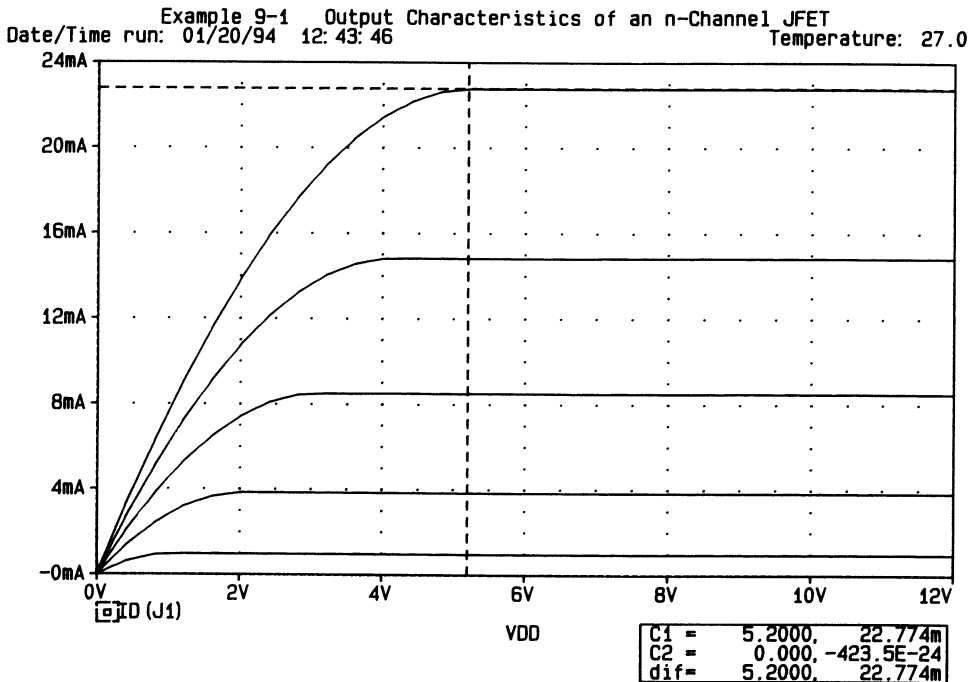

**Figure 9-6** Output characteristics of the JFET in Example 9-1.

**Example 9-2**

For the JFET in Example 9-1, plot the input characteristic if  $V_{GS}$  is varied from 0 to  $-5$  V in steps of  $0.1$  V, and  $V_{DD} = 10$  V.

**Solution** The listing of the circuit file follows.



### Example 9-2 Input characteristics of an $n$ -channel JFET

```
▲ VGS 1 0 DC 0V
  VX 3 2 DC 0V
  * Dc supply voltage of 10 V
  VDD 3 0 DC 10V
▲▲ * J1 with model JMOD
  J1 2 1 0 JMOD
  .MODEL JMOD NJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 VTO=-5)
▲▲▲ * VGS is swept from 0 to -5 V.
  .DC VGS 0 -5V 0.1V
  .PLOT DC I(VX)
  .PROBE
.END
```

The input characteristic, which is a plot of  $I_D$  versus  $V_{GS}$ , is shown in Fig. 9-7.

 


Figure 9-7 Input characteristic for Example 9-2.

### Example 9-3

A JFET transistor amplifier circuit is shown in Fig. 9-8. The output is taken from node 6. If the input voltage is  $v_{in} = 0.5 \sin(2000\pi t)$ , use ac analysis to calculate and print the magnitudes and phase angles of the output voltage, the input current, and the load current. Plot the transient responses of the voltages at nodes 1, 4, and 6 from 0 to 1 ms in steps of  $10 \mu\text{s}$ . The model parameters of the JFET are  $IS = 100E-$

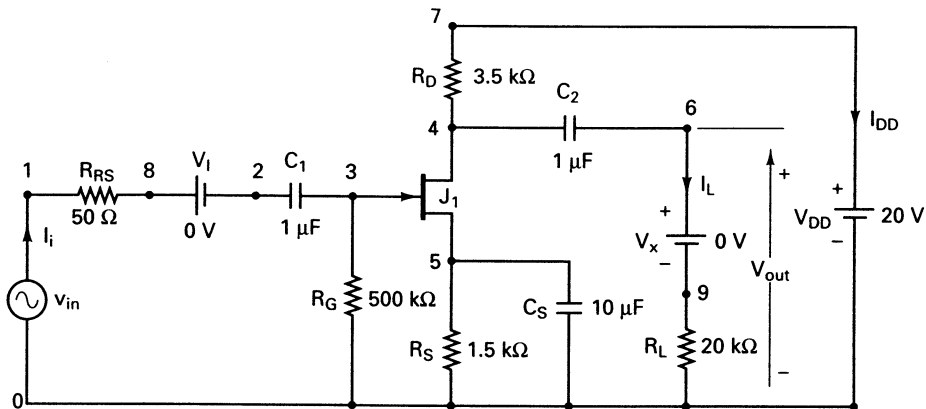


Figure 9-8 An  $n$ -channel JFET amplifier circuit.

14,  $R_D=10$ ,  $R_S=10$ ,  $BETA=1E-3$ ,  $CGD=5PF$ ,  $CGS=1PF$ , and  $VTO=-5$ . The details of the dc analysis and transient analysis operating points should be printed.

**Solution** The listing of the circuit file follows.

### Example 9-3 An $n$ -channel JFET amplifier

```

▲ .OPTIONS NOPAGE NOECHO
* Input voltage has 0.5 V peak at 1 kHz with zero offset value for
* transient response and 0.5 V peak for frequency response.
VIN 1 0 AC 0.5V SIN (0 0.5V 1KHZ)
VDD 7 0 DC 20V
* Dummy voltage source of 0 V
VI 8 2 DC 0V
VX 6 9 DC 0V
▲▲ RRS 1 8 50
   RG 3 0 0.5MEG
   RD 7 4 3.5K
   RS 5 0 1.5K
   RL 9 0 20K
   C1 2 3 1UF
   C2 4 6 1UF
   CS 5 0 10UF
* n-channel JFET with model JMOD
J1 4 3 5 JMOD
.MODEL JMOD NJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 CGD=5PF CGS=1PF VTO=-5)
▲▲▲ * Ac analysis at 1 kHz with a linear increment and only 1 point
.AC LIN 1 1KHZ 1KHZ
* Transient analysis with details of transient analysis operating point
.TRAN/OP 10US 1MS
* Print the details of the ac analysis operating point.
.OP
* Print the results of the ac analysis for the magnitudes of voltages at
* node 6 and 1 and for the magnitude of current through resistance RRS
* and the current through VX.


```

```

.PRINT AC VM(6) VP(6) IM(RRS) IP(RRS)
.PRINT AC IM(VI) IP(VI) IM(VX) IP(VX)
* Plot transient response.
.PLOT TRAN V(6) V(1)
.PROBE
.END

```

The equivalent circuit for determining the dc bias point is shown in Fig. 9-9. The details of the dc bias are given next.

 

**Figure 9-9** Equivalent circuit for dc bias calculation.

```

****      SMALL-SIGNAL BIAS SOLUTION
NODE      VOLTAGE   NODE      VOLTAGE   NODE      VOLTAGE
(  1)     0.0000   (  2)     0.0000   (  3)     8.694E-06
(  5)     3.4585   (  6)     0.0000   (  7)     20.0000
(  9)     0.0000

```

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
VIN	0.000E+00
VDD	-2.306E-03
VI	0.000E+00
VX	0.000E+00

TOTAL POWER DISSIPATION 4.61E-02 WATTS

Once the dc bias points are determined, the small-signal parameters of the JFET in Fig. 9-8 are calculated. The details of the operating points are given next.

```


****      OPERATING POINT INFORMATION
****      JFETS
NAME      J1
MODEL     JMOD
ID        2.31E-03
VGS       -3.46E+00
VDS       8.47E+00
GM        3.04E-03
GDS       0.00E+00
CGS       4.72E-13
CGD       1.39E-12

```

The outputs at a frequency of 1 kHz are as follows.

FREQ	VM (6)	VP (6)	IM (RRS)	IP (RRS)
1.000E+03	4.382E+00	-1.769E+02	9.990E-07	2.555E+00
FREQ	IM (VI)	IP (VI)	IM (VX)	IP (VX)
1.000E+03	9.990E-07	2.555E+00	2.191E-04	-1.769E+02


The equivalent circuit for determining the transient analysis bias point is shown in Fig. 9-10. The transient analysis bias point and the operating point are the same as those of the dc analysis because the capacitors do not have any initial voltages. The transient responses are shown in Fig. 9-11.

 

**Figure 9-10** Equivalent circuit for transient analysis bias calculation.

Example 9-3    N-Channel JFET Amplifier    Temperature: 27.0

Date/Time run: 01/20/94 12:53:20

 

**Figure 9-11** Transient responses for Example 9-3.

### Example 9-4

If the JFET in Fig. 9-8 is replaced by the subcircuit model of Figure 9-12, plot the frequency response of the output voltage. The frequency is varied from 10 Hz to 100 MHz with a decade increment and 10 points per decade.

 


Figure 9-12 Subcircuit model for JFET of Example 9-4.

**Solution** The listing of the circuit file follows.

#### Example 9-4 An *n*-channel JFET amplifier


```
▲ .OPTIONS NOPAGE NOECHO
* Input voltage has 0.5 V peak for frequency response.
VIN 1 0 AC 0.5V
VDD 7 0 DC 20V
* Dummy voltage source of 0V
VI 8 2 DC 0V
VX 6 9 DC 0V
▲▲ RRS 1 8 50
RG 3 0 0.5MEG
RD 7 4 3.5K
RS 5 0 1.5K
RL 9 0 20K
C1 2 3 1UF
C2 4 6 1UF
CS 5 0 10UF
* Calling subcircuit for TRANS
XQ1 4 3 5 TRANS
* Subcircuit definition for TRANS
.SUBCKT TRANS 6 2 5
RD 4 6 100
RS 3 5 100
RGS 2 3 1MEG
CGS 2 3 5PF
RGD 2 4 1MEG
CGS 2 4 1PF
```

```

RDS 4 3 500K
* Voltage-controlled current source with a gain of 5E-3
G1 4 3 2 3 5E-3
.ENDS TRANS
▲▲▲ * Ac analysis for 100 Hz to 100 MHz with a decade increment and
* 10 points per decade
.AC DEC 10 10HZ 100MEGHZ
* Plot the results of the ac analysis for the magnitudes and phases of
* output voltage and the magnitudes of input and load currents.
.PLOT AC VM(6) VP(6)
.PLOT AC IM(VI) IM(VX)
.PROBE
.END

```


The frequency response for Example 9-4 is shown in Fig. 9-13. The .PLOT statement generates graphical plots in the output file. If the .PROBE command is included, there is no need for the .PLOT command.

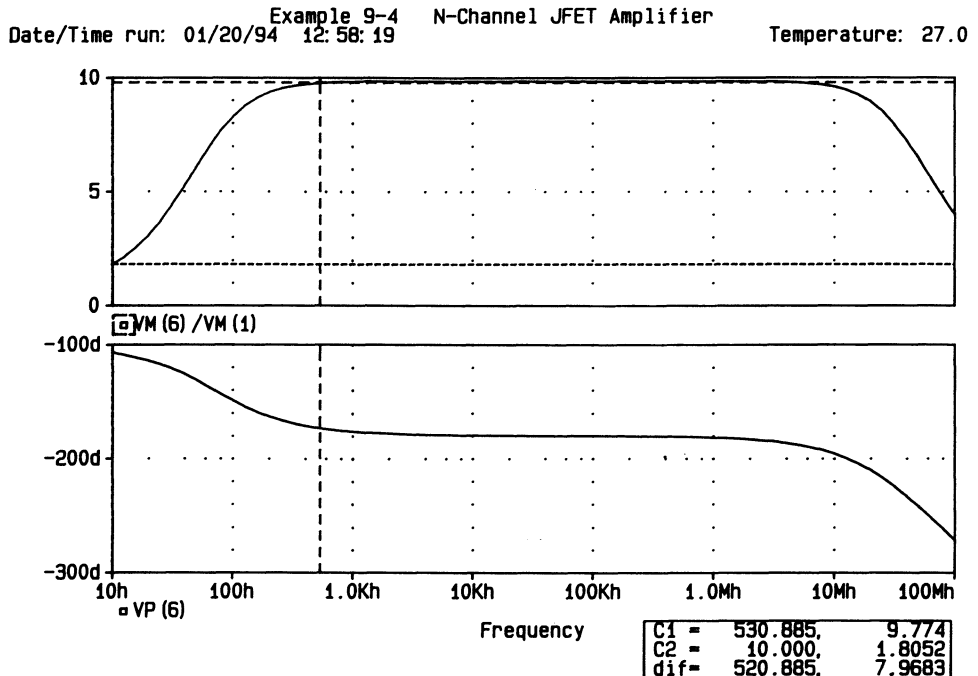

**Figure 9-13** Frequency response for Example 9-4.

### Example 9-5

A *p*-channel JFET bootstrapped amplifier is shown in Fig. 9-14. The output is taken from node 5. Calculate and print the voltage gain, the input resistance, and the output resistance. The model parameters of the JFET are IS=100E-14, RD=10, RS=10, BETA=1E-3, and VTO=5.

 

**Figure 9-14** A *p*-channel JFET bootstrapped amplifier.

**Solution** The listing of the circuit follows.

**Example 9-5 Bootstrapped JFET amplifier**

```

▲ VDD 0 6 15V
* Input voltage of 5 V dc
VIN 1 0 DC 5V
* A dummy voltage source of 0 V
VX 1 2 DC 0V
▲▲ RS 2 3 500
RG 3 4 10MEG
RS1 5 4 1.5K
RS2 4 0 7.5K
RL 5 0 10K
* p-channel JFET of model JMOD
JX 6 3 5 JMOD
* Model statement for p-channel JFET
.MODEL JMOD PJF (IS=100E-14 RD=10 RS=10 BETA=1E-3 VTO=5)
▲▲▲ * Transfer function analysis between the output and input voltages
.TF V(5) VIN
.END

```

The results of the transfer function analysis are


```

**** SMALL-SIGNAL CHARACTERISTICS
V(5)/VIN = -9.257E-01
INPUT RESISTANCE AT VIN = 4.375E+07
OUTPUT RESISTANCE AT V(5) = 3.521E+02
JOB CONCLUDED
TOTAL JOB TIME 9.50

```


## 9-5 METAL OXIDE SILICON FIELD-EFFECT TRANSISTORS

The PSpice model of an *n*-channel MOSFET [1–3] is shown in Fig. 9-15. The small-signal model and the static (or dc) model generated by PSpice are shown in

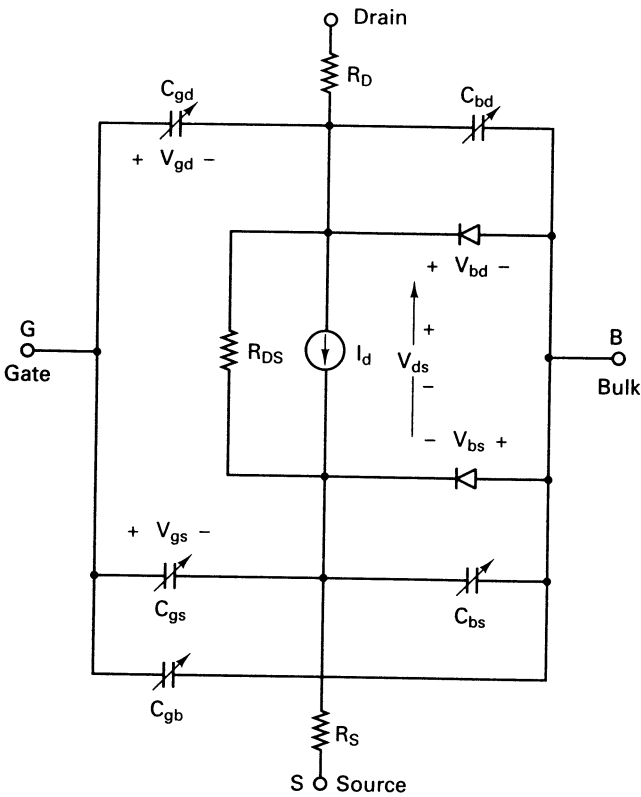


**Figure 9-15** PSpice  $n$ -channel MOSFET model.

Figs. 9-16 and 9-17, respectively. The model parameters for a MOSFET device and the default values assigned by PSpice are given in Table 9-2. The model equations of MOSFETs that are used by PSpice are described in Schichman and Hodges [1], Vladimirescu and Liu [3], and the *PSpice Manual* [7].

 

**Figure 9-16** Small-signal  $n$ -channel MOSFET model.



 

**Figure 9-17** Static *n*-channel MOSFET model.

**TABLE 9-2** MODEL PARAMETERS OF MOSFETS

Name	Model parameters	Units	Default	Typical
LEVEL	Model type (1, 2, or 3)		1	
L	Channel length	meters	DEFL	
W	Channel width	meters	DEFW	
LD	Lateral diffusion length	meters	0	
WD	Lateral diffusion width	meters	0	
VTO	Zero-bias threshold voltage	Volts	0	0.1
KP	Transconductance	Amps/Volts <sup>2</sup>	2E-5	2.5E-5
GAMMA	Bulk threshold parameter	Volts <sup>1/2</sup>	0	0.35
PHI	Surface potential	Volts	0.6	0.65
LAMBDA	Channel-length modulation (LEVEL = 1 or 2)	Volts <sup>-1</sup>	0	0.02
RD	Drain ohmic resistance	Ohms	0	10
RS	Source ohmic resistance	Ohms	0	10
RG	Gate ohmic resistance	Ohms	0	1
RB	Bulk ohmic resistance	Ohms	0	1
RDS	Drain-source shunt resistance	Ohms	∞	
RSH	Drain-source diffusion sheet resistance	Ohms/square	0	20
IS	Bulk <i>p-n</i> saturation current	Amps	1E-14	1E-15
JS	Bulk <i>p-n</i> saturation current/ area	Amps/meters <sup>2</sup>	0	1E-8
PB	Bulk <i>p-n</i> potential	Volts	0.8	0.75
CBD	Bulk-drain zero-bias <i>p-n</i> capac- itance	Farads	0	5PF
CBS	Bulk-source zero-bias <i>p-n</i> capacitance	Farads	0	2PF
CJ	Bulk <i>p-n</i> zero-bias bottom capacitance/length	Farads/meters <sup>2</sup>	0	
CJSW	Bulk <i>p-n</i> zero-bias perimeter capacitance/length	Farads/meters	0	
MJ	Bulk <i>p-n</i> bottom grading coeffi- cient		0.5	

(continued)

**TABLE 9-2** *Continued*

Name	Model parameters	Units	Default	Typical
MJSW	Bulk <i>p-n</i> sidewall grading coefficient		0.33	
FC	Bulk <i>p-n</i> forward-bias capacitance coefficient		0.5	
CGSO	Gate-source overlap capacitance/channel width	Farads/meters	0	
CGDO	Gate-drain overlap capacitance/channel width	Farads/meters	0	
CGBO	Gate-bulk overlap capacitance/channel length	Farads/meters	0	
NSUB	Substrate doping density	1/centimeter <sup>3</sup>	0	
NSS	Surface-state density	1/centimeter <sup>2</sup>	0	
NFS	Fast surface-state density	1/centimeter <sup>2</sup>	0	
TOX	Oxide thickness	meters	∞	
TPG	Gate material type: +1 = opposite of substrate, -1 = same as substrate, 0 = aluminum		+1	
XJ	Metallurgical junction depth	meters	0	
UO	Surface mobility	centimeters <sup>2</sup> /Volts · seconds	600	
UCRIT	Mobility degradation critical field (LEVEL = 2)	Volts/centimeter	1E4	
UEXP	Mobility degradation exponent (LEVEL = 2)		0	
UTRA	(Not used) mobility degradation transverse field coefficient			
VMAX	Maximum drift velocity	meters/second	0	
NEFF	Channel charge coefficient (LEVEL = 2)		1	
XQC	Fraction of channel charge attributed to drain		1	
DELTA	Width effect on threshold		0	
THETA	Mobility modulation (LEVEL = 3)	Volts <sup>-1</sup>	0	
ETA	Static feedback (LEVEL = 3)		0	
KAPPA	Saturation field factor (LEVEL = 3)		0.2	
KF	Flicker noise coefficient		0	1E-26
AF	Flicker noise exponent		1	1.2

The model statement for *n*-channel MOSFETs has the general form

```
.MODEL MNAME NMOS (P1=A1 P2=A2 P3=A3 ... PN=AN)
```

and the statement for *p*-channel MOSFETs has the form

```
.MODEL MNAME PMOS (P1=A1 P2=A2 P3=A3 ... PN=AN)
```

where MNAME is the model name; it can begin with any character, and its word size is normally limited to eight characters. NMOS and PMOS are the type symbols of  $n$ -channel and  $p$ -channel MOSFETs, respectively. P1, P2, . . . and A1, A2, . . . are the parameters and their values, respectively.

In Table 9-2 L and W are the channel length and width, respectively. AD and AS are the drain and source diffusion areas. L is decreased by twice LD to get the effective channel length. Similarly, W is decreased by twice WD to get the effective channel width. L and W can be specified for the device, the model, or in the .OPTION statement. PSpice sets priority in selecting their values. The value specified for the device supersedes that for the model, which supersedes that in the .OPTION statement.

AD and AS are the drain and source diffusion areas. PD and PS are the drain and source diffusion perimeters. The drain  $p$ - $n$ -saturation current can be specified either by IS in an absolute value, or by JS, which is multiplied by AD and AS. The zero-bias depletion capacitances can be specified (1) by CBD and CBS in absolute values, (2) by CJ, which is multiplied by AD and AS, or (3) by CJSW, which is multiplied by PD and PS.

Contact and bulk resistances are included in series with the drain, source, gate, and bulk (substrate). The MOSFET is modeled as an intrinsic device. RDS is a shunt resistance in parallel with the drain-source channel. These ohmic resistances can be specified in absolute values of RD, RS, RG, and RB. Alternatively, one could specify these resistances by RSH, which is multiplied by NRD, NRS, NRG, and NRB, respectively. NRD, NRS, NRG, and NRB are the relative resistivities of the drain, source, gate, and substrate in squares.

PD, PS, NRG, and NRB default to 0. NRD and NRS default to 1. Defaults for L, W, AD, and AS may be set in the .OPTIONS statement. The default value of AD or AS is 0. The default value of L or W is 100  $\mu\text{m}$ .

The dc characteristics are defined by parameters VTO, KP, LAMBDA, PHI, and GAMMA, which are computed by PSpice by using the fabrication-process parameters NSUB, TOX, NSS, NFS, TPG, and so on. The values of VTO, KP, LAMDA, PHI, and GAMMA, which are specified in the model statement, supersede the values calculated by PSpice based on fabrication-process parameters. *VTO is positive for enhancement type  $n$ -channel MOSFETs and for depletion type  $p$ -channel MOSFETs. VTO is negative for enhancement type  $p$ -channel MOSFETs and for depletion type  $n$ -channel MOSFETs.*

PSpice incorporates three MOSFET device models. The LEVEL parameter selects among different models for the intrinsic MOSFET. If LEVEL = 1, the Schichman-Hodges model [1] is used. If LEVEL = 2, an advanced version of the Schichman-Hodges model, which is a geometry-based analytical model and incorporates extensive second-order effects [3], is used. If LEVEL = 3, a modified version of the Schichman-Hodges model, which is a semiempirical short-channel model [3], is used.

The LEVEL 1 model, which employs fewer fitting parameters, gives approximate results. However, it is useful for a quick and rough estimate of the circuit performances and it is normally adequate for the analysis of basic electronic circuits. The LEVEL 2 model, which can take into consideration various

parameters, requires a great amount of CPU time for the calculations and could cause convergence problems. The LEVEL 3 model introduces a smaller error as compared to the LEVEL 2 model, and the CPU time is also approximately 25% less. The LEVEL 3 model is designed for MOSFETs with short channels.

The symbol for a metal-oxide silicon field-effect transistor (MOSFET) is *M*. The name of a MOSFET must start with *M* and takes the general form

```
M(name) ND NG NS NB MNAME
+ [L=(value)] [W=(value)]
+ [AD=(value)] [AS=(value)]
+ [PD=(value)] [PS=(value)]
+ [NRD=(value)] [NRS=(value)]
+ [NRG=(value)] [NRB=(value)]
```

where ND, NG, NS, and NB are the drain, gate, source, and bulk (or substrate) nodes, respectively. MNAME is the model name, and it can begin with any character; its word size is normally limited to eight characters. Positive current is the current that flows into a terminal. That is, the current flows from the drain node through the device to the source node for an *n*-channel MOSFET.

### Some MOSFET Statements


```
M1 4 2 7 0 MMOD L=10U W=20U
.MODEL MMOD NMOS
M13 15 3 0 0 IRF150
.MODEL IRF150 NMOS (LEVEL=3 TOX=.10U L=3.0U LD=.5U W=2.0 WD=0
+XJ=1.2U
+ NSUB=4E14 IS=2.1E-14 RB=0 RD=.01 RS=.03 RDS=1E6 VTO=3.25
+ U0=550 THETA=.1 ETA=0 VMAX=1E6 CBS=1P CBD=4000P PB=.7 MJ=.5
+ RG=4.9 CGSO=1690P CGDO=365P CGBO=1P)
M2A 0 2 20 20 IRF9130
.MODEL IRF9130 PMOS (LEVEL=3 TOX=.1U L=3.0U LD=.5U W=1.3 WD=0
+XJ=1.2U
+ NSUB=4E14 IS=2.1E-14 RB=0 RD=.03 RS=.2 RDS=5E5 VTO=-3.7
+ U0=600 THETA=.1 ETA=0 VMAX=1E6 CBS=1P CBD=2000P PB=.7 MJ=.5
+ RG=5 CGSO=520P CGDO=180P CGBO=1P)
MA 0 2 15 15 PMOD L=20U W=20U AD=100U AS=200U PD=50U
+ PS=50U NRD=10 NRS=20 NRG=10
.MODEL PMOD PMOS
```

## 9-6 MOSFET PARAMETERS

The data sheet for the *n*-channel MOSFET of type IRF150 is shown in Fig. 9-18. The library file EVAL.LIB of the student version of PSpice supports models for the *n*-type MOSFET of type IRF150 and the *p*-type MOSFET of type IRF9140. As an example, we shall generate approximate values of some parameters [8, 9] from the data sheet of IRF150.

INTERNATIONAL RECTIFIER 

## HEXFET® TRANSISTORS IRF150

 

N-Channel

IRF151

IRF152

IRF153

## 100 Volt, 0.055 Ohm HEXFET

The HEXFET® technology is the key to International Rectifier's advanced line of power MOSFET transistors. The efficient geometry and unique processing of the HEXFET design achieve very low on-state resistance combined with high transconductance and great device ruggedness.

The HEXFET transistors also feature all of the well established advantages of MOSFETs such as voltage control, freedom from second breakdown, very fast switching, ease of paralleling, and temperature stability of the electrical parameters.

They are well suited for applications such as switching power supplies, motor controls, inverters, choppers, audio amplifiers, and high energy pulse circuits.



## Features:

- Fast Switching
- Low Drive Current
- Ease of Paralleling
- No Second Breakdown
- Excellent Temperature Stability

## Product Summary

Part Number	V <sub>DS</sub>	R <sub>DS(on)</sub>	I <sub>D</sub>
IRF150	100V	0.055Ω	40A
IRF151	60V	0.055Ω	40A
IRF152	100V	0.08Ω	33A
IRF153	60V	0.08Ω	33A

## CASE STYLE AND DIMENSIONS

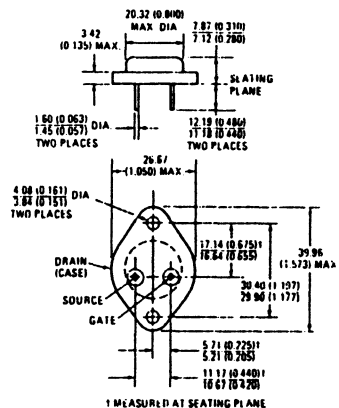 

Conforms to JEDEC Outline TO-204AE (Modified TO-3)  
Dimensions in Millimeters and (Inches)


Figure 9-18 Data sheet for MOSFET type IRF150 (Courtesy of International Rectifier).

# IRF150, IRF151, IRF152, IRF153 Devices

## Absolute Maximum Ratings

Parameter	IRF150	IRF151	IRF152	IRF153	Units
V <sub>DS</sub> Drain - Source Voltage ①	100	60	100	60	V
V <sub>DGR</sub> Drain - Gate Voltage (R <sub>GS</sub> = 20 k $\Omega$ ) ①	100	60	100	60	V
I <sub>D</sub> @ T <sub>C</sub> = 25°C Continuous Drain Current	40	40	33	33	A
I <sub>D</sub> @ T <sub>C</sub> = 100°C Continuous Drain Current	25	25	20	20	A
I <sub>DM</sub> Pulsed Drain Current ③	160	160	132	132	A
V <sub>GS</sub> Gate - Source Voltage	± 20				V
P <sub>D</sub> @ T <sub>C</sub> = 25°C Max. Power Dissipation	150 (See Fig. 14)				W
Linear Derating Factor	1.2 (See Fig. 14)				W/K
I <sub>LM</sub> Inductive Current, Clamped	(See Fig. 15 and 16) L = 100 $\mu$ H				A
T <sub>J</sub> Operating Junction and Storage Temperature Range	-55 to 150				°C
T <sub>stg</sub> Lead Temperature	300 (0.063 in. (1.6mm) from case for 10s)				°C

## Electrical Characteristics @ T<sub>C</sub> = 25°C (Unless Otherwise Specified)


Parameter	Type	Min.	Typ.	Max.	Units	Test Conditions	
BV <sub>DSS</sub> Drain - Source Breakdown Voltage	IRF150 IRF152	100	-	-	V	V <sub>GS</sub> = 0V I <sub>D</sub> = 250 $\mu$ A	
	IRF151 IRF153	60	-	-	V		
	ALL	2.0	-	4.0	V		
V <sub>GS(th)</sub> Gate Threshold Voltage	ALL	2.0	-	4.0	V	V <sub>DS</sub> = V <sub>GS</sub> , I <sub>D</sub> = 250 $\mu$ A	
I <sub>GSS</sub> Gate-Source Leakage Forward	ALL	-	-	100	nA	V <sub>GS</sub> = 20V	
I <sub>GSS</sub> Gate-Source Leakage Reverse	ALL	-	-	-100	nA	V <sub>GS</sub> = -20V	
I <sub>DSS</sub> Zero Gate Voltage Drain Current	ALL	-	-	250	$\mu$ A	V <sub>DS</sub> = Max. Rating, V <sub>GS</sub> = 0V	
		-	-	1000	$\mu$ A	V <sub>DS</sub> = Max. Rating x 0.8, V <sub>GS</sub> = 0V, T <sub>C</sub> = 125°C	
I <sub>D(on)</sub> On-State Drain Current ②	IRF150 IRF151	40	-	-	A	V <sub>DS</sub> > I <sub>D(on)</sub> x R <sub>DS(on) max.</sub> , V <sub>GS</sub> = 10V	
	IRF152 IRF153	33	-	-	A		
R <sub>DS(on)</sub> Static Drain-Source On-State Resistance ②	IRF150 IRF151	-	0.045	0.055	$\Omega$	V <sub>GS</sub> = 10V, I <sub>D</sub> = 20A	
	IRF152 IRF153	-	0.06	0.08	$\Omega$		
	ALL	9.0	11	-	S (ft)		
g <sub>fs</sub> Forward Transconductance ②	ALL	9.0	11	-	S (ft)	V <sub>DS</sub> > I <sub>D(on)</sub> x R <sub>DS(on) max.</sub> , I <sub>D</sub> = 20A	
C <sub>iss</sub> Input Capacitance	ALL	-	2000	3000	pF	V <sub>GS</sub> = 0V, V <sub>DS</sub> = 25V, f = 1.0 MHz See Fig. 10	
C <sub>oss</sub> Output Capacitance	ALL	-	1000	1500	pF		
C <sub>rss</sub> Reverse Transfer Capacitance	ALL	-	350	500	pF	V <sub>DD</sub> = 24V, I <sub>D</sub> = 20A, Z <sub>o</sub> = 4.7 $\Omega$ See Figure 17. (MOSFET switching times are essentially independent of operating temperature.)	
t <sub>d(on)</sub> Turn-On Delay Time	ALL	-	-	35	ns		
t <sub>r</sub> Rise Time	ALL	-	-	100	ns		
t <sub>d(off)</sub> Turn-Off Delay Time	ALL	-	-	125	ns		
t <sub>f</sub> Fall Time	ALL	-	-	100	ns		
Q <sub>g</sub> Total Gate Charge (Gate-Source Plus Gate-Drain)	ALL	-	63	120	nC	V <sub>GS</sub> = 10V, I <sub>D</sub> = 50A, V <sub>DS</sub> = 0.8 Max. Rating. See Fig. 18 for test circuit. (Gate charge is essentially independent of operating temperature.)	
Q <sub>gs</sub> Gate-Source Charge	ALL	-	27	-	nC		
Q <sub>gd</sub> Gate-Drain ("Miller") Charge	ALL	-	36	-	nC		
L <sub>D</sub> Internal Drain Inductance	ALL	-	5.0	-	nH	Measured between the contact screw on header that is closer to source and gate pins and center of die.	Modified MOSFET symbol showing the internal device inductances. 
L <sub>S</sub> Internal Source Inductance	ALL	-	12.5	-	nH	Measured from the source pin, 6 mm (0.25 in.) from header and source bonding pad.	

## Thermal Resistance

R <sub>thJC</sub> Junction-to-Case	ALL	-	-	0.83	K/W	
R <sub>thCS</sub> Case-to-Sink	ALL	-	0.1	-	K/W	Mounting surface flat, smooth, and greased.
R <sub>thJA</sub> Junction-to-Ambient	ALL	-	-	30	K/W	Free Air Operation

Figure 9-18 Continued

## Source-Drain Diode Ratings and Characteristics

$I_S$	Continuous Source Current (Body Diode)	IRF150	-	-	40	A	Modified MOSFET symbol showing the integral reverse P-N junction rectifier. <div style="text-align: right; margin-top: 10px;">  </div>
		IRF151	-	-	33	A	
$I_{SM}$	Pulse Source Current (Body Diode) ③	IRF150	-	-	160	A	
		IRF151	-	-	132	A	
$V_{SD}$	Diode Forward Voltage ②	IRF150	-	-	2.5	V	$T_C = 25^\circ\text{C}, I_S = 40\text{A}, V_{GS} = 0\text{V}$
		IRF151	-	-	2.3	V	$T_C = 25^\circ\text{C}, I_S = 33\text{A}, V_{GS} = 0\text{V}$
$t_{rr}$	Reverse Recovery Time	ALL	-	600	-	ns	$T_J = 150^\circ\text{C}, I_F = 40\text{A}, dI_F/dt = 100\text{A}/\mu\text{s}$
$Q_{RR}$	Reverse Recovered Charge	ALL	-	3.3	-	$\mu\text{C}$	$T_J = 150^\circ\text{C}, I_F = 40\text{A}, dI_F/dt = 100\text{A}/\mu\text{s}$
$t_{on}$	Forward Turn-on Time	ALL	Intrinsic turn-on time is negligible. Turn-on speed is substantially controlled by $L_S + L_D$ .				

①  $T_J = 25^\circ\text{C}$  to  $150^\circ\text{C}$ .

② Pulse Test: Pulse width  $\leq 300\mu\text{s}$ , Duty Cycle  $\leq 2\%$ .

③ Repetitive Rating: Pulse width limited

by max. junction temperature.

See Transient Thermal Impedance Curve (Fig. 5).

 


Fig. 1 — Typical Output Characteristics

 


Fig. 2 — Typical Transfer Characteristics

 


Fig. 3 — Typical Saturation Characteristics

 


Fig. 4 — Maximum Safe Operating Area

# IRF150, IRF151, IRF152, IRF153 Devices

 


Fig. 5 – Maximum Effective Transient Thermal Impedance, Junction-to-Case Vs. Pulse Duration

 


Fig. 6 – Typical Transconductance Vs. Drain Current

 


Fig. 7 – Typical Source-Drain Diode Forward Voltage

 


Fig. 8 – Breakdown Voltage Vs. Temperature

 


Fig. 9 – Normalized On-Resistance Vs. Temperature



# IRF150, IRF151, IRF152, IRF153 Devices

 


Fig. 10 – Typical Capacitance Vs. Drain-to-Source Voltage

 


Fig. 11 – Typical Gate Charge Vs. Gate-to-Source Voltage

 


Fig. 12 – Typical On-Resistance Vs. Drain Current

 


Fig. 13 – Maximum Drain Current Vs. Case Temperature

 


Fig. 14 – Power Vs. Temperature Derating Curve

From the data sheet we get  $I_{DSS} = 250 \mu\text{A}$  at  $V_{GS} = 0 \text{ V}$ ,  $V_{DS} = 100 \text{ V}$ .  $V_{Th} = 2$  to  $4 \text{ V}$ . Geometric mean,  $V_{Th} = V_{TO} = \sqrt{2 \times 4} = 2.83 \text{ V}$ . The constant  $K_p$  can be found from

$$I_D = K_p(V_{GS} - V_{Th})^2 \quad (9-3)$$

For  $I_D = I_{DSS} = 250 \mu\text{A}$ , and  $V_{Th} = 2.83 \text{ V}$ , Eq. (9-3) gives  $K_p = 250 \mu\text{A}/2.83^2 = 31.2 \mu\text{A}/\text{V}^2$ .  $K_p$  is related to channel length  $L$  and channel width  $W$  by

$$K_p = \frac{\mu_a C_o}{2} \left( \frac{W}{L} \right) \quad (9-4)$$

where  $C_o$  is the capacitance per unit area of the oxide layer, a typical value for a power MOSFET being  $3.5 \times 10^{-11} \text{ F}/\text{cm}^2$  at a thickness of  $0.1 \text{ nm}$  (assumed), and  $\mu_a$  is the surface mobility of electrons,  $600 \text{ cm}^2/(\text{V} \cdot \text{s})$ .

The ratio  $W/L$  can be found from Eq. (9-4),

$$\frac{W}{L} = \frac{2K_p}{\mu_a C_o} = \frac{2 \times 31.2 \times 10^{-6}}{600 \times 3.5 \times 10^{-11}} = 3000$$

Let  $L = 1 \text{ nm}$  and  $W = 3 \mu\text{m}$ .  $C_{rss} = 350 - 500 \text{ pF}$  at  $V_{GS} = 0$ ,  $V_{DS} = 25 \text{ V}$ . Geometric mean,  $C_{rss} = C_{gd} = \sqrt{350 \times 500} = 418.3 \text{ pF}$  at  $V_{DG} = 25 \text{ V}$ .

For a MOSFET, the values of  $C_{gs}$  and  $C_{gd}$  remain relatively constant with changing  $V_{GS}$  or  $V_{DS}$ . They are determined mainly by the thickness and type of the insulating oxide. Although, the curves of the capacitances versus drain-source voltage show some variations, we will assume constant capacitances. Thus,  $C_{gdo} = 418.3 \text{ pF}$ .  $C_{iss} = 2000$  to  $3000 \text{ pF}$ . Geometric mean  $C_{iss} = \sqrt{2000 \times 3000} = 2450 \text{ pF}$ . Since  $C_{iss}$  is measured at  $V_{GS} = 0 \text{ V}$ ,  $C_{gs} = C_{gso}$ . That is,

$$C_{iss} = C_{gso} + C_{gd}$$

which gives  $C_{gso} = C_{iss} - C_{sd} = 2450 - 418.3 = 2032 \text{ pF} = 2.032 \text{ nF}$ . Thus the PSpice model statement for MOSFET IRF150 is

```
.MODEL IRF150 NMOS (VTO=2.83 KP=31.2U L=1N W=3U CGDO=0.418N CGSO=2.032N)
```

The model can be used to plot the characteristics of the MOSFET. It may be necessary to modify the parameter values to conform with the actual characteristics. It should be noted that the parameters would differ from those given in the PSpice library, because their values are dependent on the constants used in derivations. Students are encouraged to run a circuit file with the PSpice library model and compare the results obtained with the above model statement.

## 9-7 EXAMPLES OF MOSFET AMPLIFIERS

The large number of parameters involved is an indication of the complexity of modeling a MOSFET. An accurate modeling requires a SPICE library file of a MOSFET. The parameters that are determined from the data sheet in Section 9-6

are the approximate values only. If a model parameter is not available, its typical value as indicated in Table 9-2 should be used. The following examples illustrate the PSpice simulation of MOSFET circuits.

### Example 9-6

An  $n$ -channel enhancement-type MOSFET amplifier with series-shunt feedback is shown in Fig. 9-19. Plot the magnitude of output voltage. The frequency is varied from 10 Hz to 100 MHz in decade steps with 10 points per decade. The peak input voltage is 100 mV. The model parameters of the MOSFET are  $V_{TO}=1$ ,  $K_P=6.5E-3$ ,  $C_{BD}=5PF$ ,  $C_{BS}=2PF$ ,  $R_D=5$ ,  $R_S=2$ ,  $R_B=0$ ,  $R_G=0$ ,  $R_{DS}=1MEG$ ,  $C_{GSO}=1PF$ ,  $C_{GDO}=1PF$ , and  $C_{GBO}=1PF$ . Print the details of the bias and operating points.

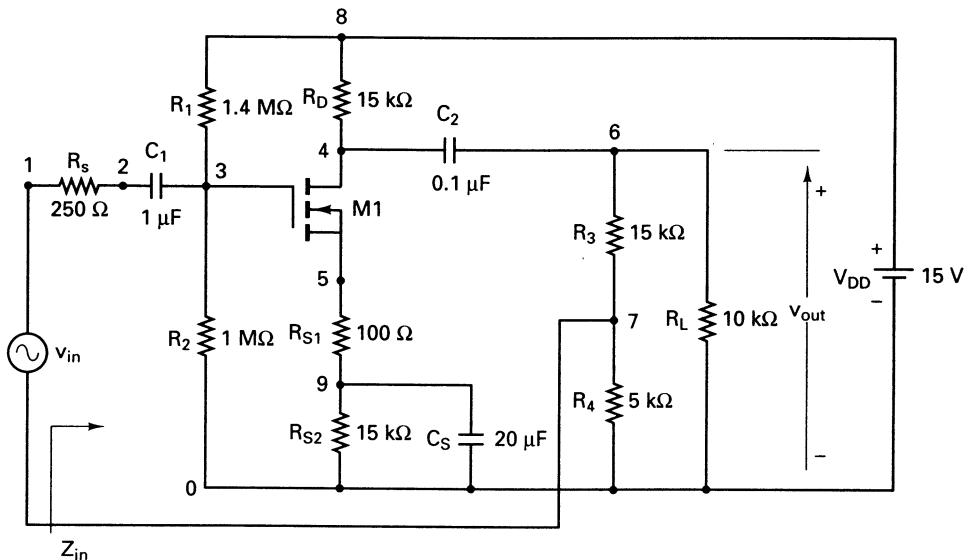


Figure 9-19 A MOSFET feedback amplifier.

**Solution** The listing of the circuit file follows.

#### Example 9-6 A MOSFET feedback amplifier

▲ \* Input voltage of 100 mV peak for frequency response

VIN 1 7 AC 100mV

VDD 8 0 15V

▲▲ RS 1 2 250

C1 2 3 1UF

R1 8 3 1.4MEG

R2 3 0 1MEG

RD 8 4 15K

RS1 5 9 100

RS2 9 0 15K

CS 9 0 20UF

C2 4 6 0.1UF

R3 6 7 15K

```

R4 7 0 5K
RL 6 0 10K
* MOSFET M1 with model MQ is connected to 4 (drain), 3 (gate), 5
* (source) and 5 (substrate).
M1 4 3 5 5 MQ
* Model for MQ
.MODEL MQ NMOS (VTO=1 KP=6.5E-3 CBD=5PF CBS=2PF RD=5 RS=2 RB=0
+ RG=0 RDS=1MEG CGS0=1PF CGD0=1PF CGB0=1PF)
▲▲▲ * Ac analysis for 10 Hz to 100 MHz with a decade increment and 10
* points per decade
.AC DEC 10 10HZ 100MEGHZ
* Plot the results of ac analysis: voltage at node 6.
.PLOT AC VM(6)
* Print the details of the dc operating point.
.OP
.PROBE
.END

```

The details of the bias and operating points are given next.

```

**** SMALL-SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C
NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE
( 1) 0.0000 ( 2) 0.0000 ( 3) 6.2500 ( 4) 10.1000
( 5) 4.9323 ( 6) 0.0000 ( 7) 0.0000 ( 8) 15.0000
( 9) 4.8997
VOLTAGE SOURCE CURRENTS
NAME CURRENT
VIN 0.000E+00
VDD -3.329E-04
TOTAL POWER DISSIPATION 4.99E-03 WATTS


```

```

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C
**** MOSFETS
NAME M1
MODEL MQ
ID 3.32E-04
VGS 1.32E+00
VDS 5.17E+00
VBS 0.00E+00
VTH 1.00E+00
VDSAT 3.17E-01
GM 2.06E-03
GDS 1.00E-06
GMB 0.00E+00
CBD 1.83E-12
CBS 2.00E-12
CGSOV 1.00E-16
CGDOV 1.00E-16
CGBOV 1.00E-16

```



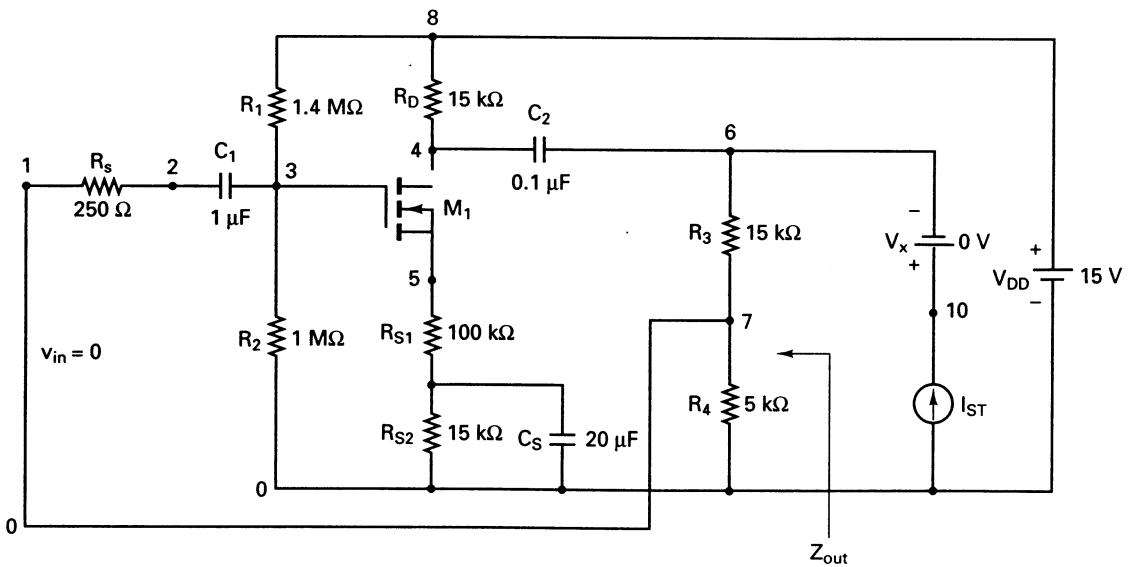

**Figure 9-21** Equivalent circuit for output impedance calculation (Example 9-7).

```

IST 0 10 AC 1MA
* A dummy source of 0 V dc
VX 10 6 DC 0V
VDD 8 0 15V
▲▲ RS 1 2 250
C1 2 3 1UF
R1 8 3 1.4MEG
R2 3 0 1MEG
RD 8 4 15K
RS1 5 9 100
RS2 9 0 15K
CS 9 0 20UF
C2 4 6 0.1UF
R3 6 7 15K
R4 7 0 5K
RL 6 0 10K
* M1 with model MQ, whose substrate is connected to node 5
M1 4 3 5 5 MQ
* Model for n-channel MOSFET with model name MQ
.MODEL MQ NMOS (VTO=1 KP=6.5E-3 CBD=5PF CBS=2PF RD=5 RS=2 RB=0
+ RG=0 RDS=1MEG CGSO=1PF CGDO=1PF CGBO=1PF)
▲▲▲ * Ac analysis for 10 Hz to 100 MHz with a decade increment and 10
* points per decade
.AC DEC 10 10HZ 10MEGHZ
* Plot the results of the ac analysis: voltage at node 6.
.PLOT AC VM(6)
.PROBE
.END

```

The frequency response of the output impedance for Example 9-7 is shown in Fig. 9-22. If the .PROBE command is included, there is no need for the .PLOT command.

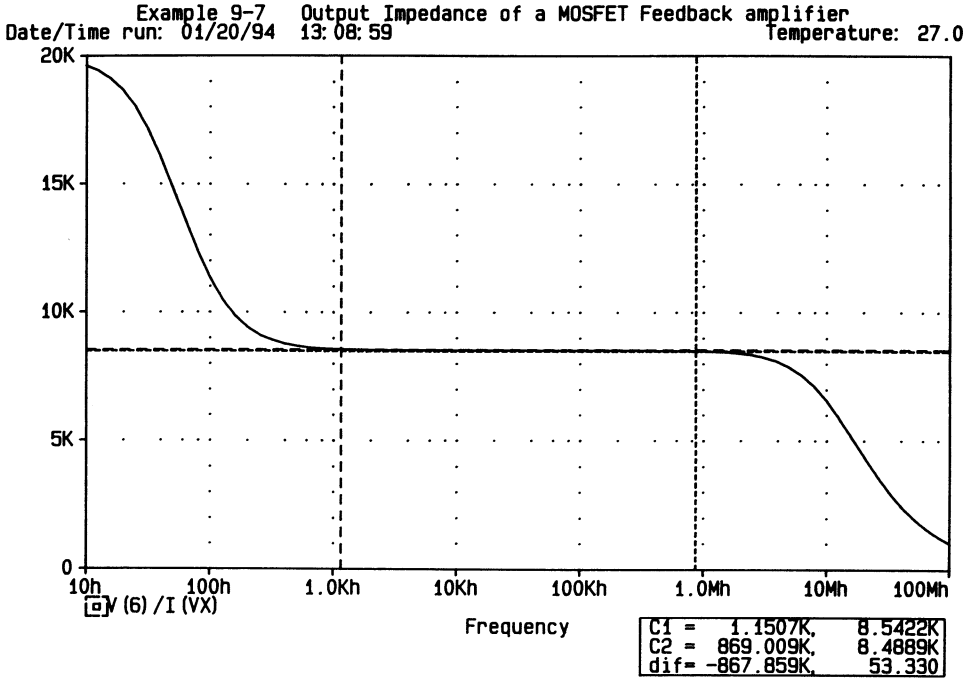


Figure 9-22 Output impedance for Example 9-7.

**Example 9-8**

A CMOS inverter circuit is shown in Fig. 9-23(a). The output is taken from node 3. The input voltage is shown in Fig. 9-23(b). Plot the transient response of the output voltage from 0 to 80  $\mu$ s in steps of 2  $\mu$ s. If the input voltage is 5 V, calculate

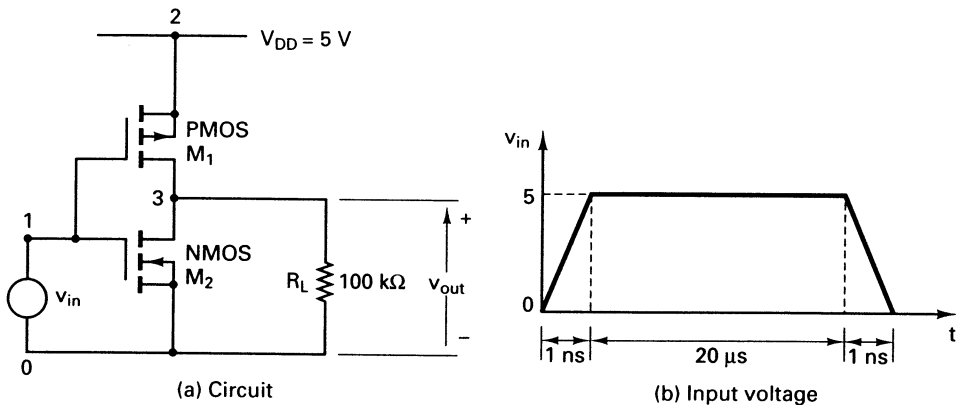


Figure 9-23 A CMOS inverter (Example 9-8).

the voltage gain, the input resistance, and the output resistance. Print the small-signal parameters of the MOS and NMOS. The model parameters of the PMOS are  $L=1U$ ,  $W=20U$ ,  $VTO=-2$ ,  $KP=4.5E-4$ ,  $CBD=5PF$ ,  $CBS=2PF$ ,  $RD=5$ ,  $RS=2$ ,  $RB=0$ ,  $RG=0$ ,  $RDS=1MEG$ ,  $CGSO=1PF$ ,  $CGDO=1PF$ , and  $CGBO=1PF$ . The model parameters of the NMOS are  $L=1U$ ,  $W=5U$ ,  $VTO=2$ ,  $KP=4.5E-5$ ,  $CBD=5PF$ ,  $CBS=2PF$ ,  $RD=5$ ,  $RS=2$ ,  $RB=0$ ,  $RG=0$ ,  $RDS=1MEG$ ,  $CGSO=1PF$ ,  $CGDO=1PF$ , and  $CGBO=1PF$ .

**Solution** The listing of the circuit file follows.

### Example 9-8 A CMOS inverter

```


▲ VDD 2 0 5V
  * The input voltage is 5 V for dc analysis and pulse waveform for
  * transient analysis.
  VIN 1 0 DC 5V PULSE (0 5V 0 1NS 1NS 20US 40US)
▲▲ RL 3 0 100K
  * PMOS with model PMOD
  M1 3 1 2 2 PMOD L=1U W=20U
  .MODEL PMOD PMOS (VTO=-2 KP=4.5E-4 CBD=5PF CBS=2PF RD=5 RS=2 RB=0
  + RG=0 RDS=1MEG CGSO=1PF CGDO=1PF CGBO=1PF)
  M2 3 1 0 0 NMOS L=1U W=5U
  * NMOS with model NMOS
  .MODEL NMOS NMOS (VTO=2 KP=4.5E-5 CBD=5PF CBS=2PF RD=5 RS=2 RB=0
  + RG=0 RDS=1MEG CGSO=1PF CGDO=1PF CGBO=1PF)
  * Transient analysis from 0 to 80μs in steps of 1 μs
▲▲▲ .TRAN 1US 80US
  * Transfer-function analysis
  .TF V(3) VIN
  * Print details of operating points.
  .OP
  .PLOT TRAN V(3) V(1)
  .PROBE
.END

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C
**** MOSFETS
NAME M1 M2
MODEL MQ NMOS
ID -5.00E-06 1.53E-11
VGS 0.00E+00 5.00E+00
VDS -5.00E+00 2.27E-08
VBS 0.00E+00 0.00E+00
VTH -2.00E+00 2.00E+00
VDSAT 0.00E-00 3.00E+00
GM 0.00E-00 5.09E-12
GDS 1.00E-06 6.76E-04
GMB 0.00E+00 0.00E+00
CBD 1.86E-12 5.00E-12
CBS 2.00E-12 2.00E-12
CGSOV 2.00E-17 5.00E-18
CGDOV 2.00E-17 5.00E-18


```





 

**Figure 9-25** PSpice *n*-channel GaAsFET model.

 

**Figure 9-26** Small-signal *n*-channel GaAsFET model.

assigned by PSpice are listed in Table 9-3. The model equations of GaAsFETs that are used by PSpice are described in Curtice [5], Sussman-Fort et al. [6], and the *PSpice Manual* [7].

The model statement of *n*-channel GaAsFETs has the general form

```
.MODEL BNAME GASFET (P1=A1 P2=A2 P3=A3 ... PN=AN)
```

where GASFET is the type symbol of *n*-channel GaAsFETs. BNAME is the model name. It can begin with any character and its word size is normally limited

**TABLE 9-3** MODEL PARAMETERS OF GaAs MESFETs

Name	Area	Model parameters	Units	Default	Typical
VTO		Threshold voltage	Volts	-2.5	-2.0
ALPHA		Tan $h$ constant	Volts <sup>-1</sup>	2.0	1.5
BETA		Transconductance coefficient	Amps/Volts <sup>2</sup>	0.1	25U
LAMBDA		Channel-length modulation	Volts	0	1E-10
RG	*	Gate ohmic resistance	Ohms	0	1
RD	*	Drain ohmic resistance	Ohms	0	1
RS	*	Source ohmic resistance	Ohms	0	1
IS		Gate $p$ - $n$ saturation current	Amps	1E-14	
M		Gate $p$ - $n$ grading coefficient		0.5	
N		Gate $p$ - $n$ emission coefficient		1	
VBI		Threshold voltage	Volts	1	0.5
CGD		Gate-drain zero-bias $p$ - $n$ capacitance	Farads	0	1FF
CGS		Gate-source zero-bias $p$ - $n$ capacitance	Farads	0	6FF
CDS		Drain-source capacitance	Farads	0	0.3FF
TAU		Transit time	seconds	0	10PS
FC		Forward-bias depletion capacitance coefficient		0.5	
VTOTC		VTO temperature coefficient	Volts/°C	0	
BETATCE		BETA exponent temperature coefficient	%/°C	0	
KF		Flicker noise coefficient		0	
AF		Flicker noise exponent		1	

to eight characters. P1, P2, . . . and A1, A2, . . . are the parameters and their values, respectively.

RD, RS, and RG represent the contact and bulk resistances per unit area of the drain, source, and gate, respectively. The GaAsFET is modeled as an intrinsic device. The area value, which is the relative device area, is specified in the .MODEL statement and changes the actual resistance values. The default value of the area is 1.

The symbol for a gallium arsenide MESFET (GaAs MESFET or GaAsFET) is  $B$ . The name of a GaAs MESFET must start with  $B$ , and it takes the general form

```
B(name) ND NG NS BNAME [(area) value]
```

where ND, NG, ND are the drain, gate, and source nodes, respectively. BNAME, which is the model name, can begin with any character, and its word size is normally limited to eight characters. Positive current flows into a terminal.

### **Some GaAs MESFET Statements**

```
BIX 2 5 7 NMOD
.MODEL NMOD GASFET
BIM 15 1 0 GMOD
.MODEL GMOD GASFET (VTO=-2.5 BETA=60U VBI=0.5 ALPHA=1.5 TAU=10PS)
B5 7 9 3 NMOM 1.5
.MODEL MNOM GASFET (VTO=-2.5 BETA=32U VBI=0.5 ALPHA=1.5)
```

### Example 9-9

A GaAsFET inverter with active load is shown in Fig. 9-27(a). The input voltage is a pulse waveform, as shown in Fig. 9-27(b). Plot the transient response of the output voltage for a time duration of 240 ps in steps of 2 ps. Plot the dc transfer characteristic if the input voltage is varied from  $-2.5$  V to  $1$  V in steps of  $0.1$  V. The model parameters of the GaAsFET are  $V_{TO}=-2$ ,  $BETA=60U$ ,  $V_{BI}=0.5$ ,  $ALPHA=1.5$ , and  $TAU=10PS$ , and those of B2 are  $V_{TO}=-2$ ,  $BETA=3U$ ,  $V_{BI}=0.5$ , and  $ALPHA=1.5$ . Calculate the dc voltage gain, the input resistance, and the output resistance. Print the small-signal parameters for the dc analysis.

 


Figure 9-27 GaAsFET inverter with active load.

**Solution** The listing of the circuit file follows.

#### Example 9-9 A GaAsFET inverter with active load

```

▲ VDD 1 0 5V
* Pulsed input voltage
VIN 3 0 DC -2V PWL (0 0 100PS -2V 1NS -2V)
▲▲ * GaAsFET, which is connected to 1 (drain), 2 (gate) and
* 2 (source), has a model of GF1.
B1 1 2 2 GF1
B2 2 4 0 GF2
C1 2 0 6F IC=0V
RS 3 4 50
* Model for GF1
.MODEL GF1 GASFET (VTO=-2.5 BETA=65U VBI=0.5 ALPHA=1.5 TAU=10PS)
.MODEL GF2 GASFET (VTO=-2.5 BETA=32.5U VBI=0.5 ALPHA=1.5)
▲▲▲ * Transient analysis for 0 to 240 ps with 2-ps increment
.TRAN 2PS 240PS UIC
.DC VIN -2.5 1 0.1
* Plot the results of transient analysis.
.PLOT TRAN V(3) V(2)
.PLOT DC V(2)
* Dc transfer characteristics
.TF V(2) VIN

```

```

* Small-signal parameters for dc analysis
.OP
.PROBE
.END

```

```

**** SMALL-SIGNAL BIAS SOLUTION          TEMPERATURE = 27.000 DEG C
NODE      VOLTAGE      NODE      VOLTAGE      NODE      VOLTAGE      NODE      VOLTAGE
( 1)      5.0000      ( 2)      4.8787      ( 3)      -1.0000      ( 4)      -1.0000
VOLTAGE SOURCE CURRENTS
NAME      CURRENT
VDD        -7.313E-05
VIN         6.899E-12
TOTAL POWER DISSIPATION 3.66E-04 WATTS

```

```

**** OPERATING POINT INFORMATION          TEMPERATURE = 27.000 DEG C
**** GASFETS
NAME      B1          B2
MODEL     GF1         GF2
ID         7.31E-05    7.31E-05
VGS        0.00E+00   -1.00E+00
VDS         1.21E-01   4.88E+00
GM          5.85E-05   9.75E-05

```

Example 9-9 A GaAsFET inverter with active load  
Date/Time run: 01/20/94 13:56:18 Temperature: 27.0

 


Figure 9-28 Transient response for Example 9-9.

GDS	5.90E-04	1.93E-10
CGS	0.00E+00	0.00E+00
CGD	0.00E+00	0.00E+00
CDS	0.00E+00	0.00E+00

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

V(2)/VIN = -1.654E-01  
 INPUT RESISTANCE AT VIN = 4.618E+11  
 OUTPUT RESISTANCE AT V(2) = 1.696E+03

The transient response and the dc transfer characteristics for Example 9-9 are shown in Fig. 9-28. If the .PROBE command is included, there is no need for the .PLOT command.

## SUMMARY

The model statements for FETs can be summarized as follows:

```

B(name) ND NG NS BNAME [(area) value]
.MODEL BNAME GASFET (P1=V1 P2=V2 P3=V3 ...PN=VN)
J(name) ND NG NS JNAME [(area) value]
.MODEL JNAME NJF (P1=V1 P2=V2 P3=V3 ...PN=VN)
.MODEL JNAME PJF (P1=V1 P2=V2 P3=V3 ...PN=VN)
N(name) ND NG NS NB MNAME
+ [L=(value)] [W=(value)]
+ [AD=(value)] [AS=(value)]
+ [PD=(value)] [PS=(value)]
+ [NRD=(value)] [NRS=(value)]
+ [NRG=(value)] [NRB=(value)]
.MODEL MNAME NMOS (P1=V1 P2=V2 P3=V3 ...PN=VN)
.MODEL MNAME PMOS (P1=V1 P2=V2 P3=V3 ...PN=VN)

```


## REFERENCES

1. H. Schichman and D. A. Hodges, "Modeling and simulation of insulated gate field effect transistor switching circuits," *IEEE Journal of Solid-State Circuits*, Vol. SC-3, September 1968, pp. 285-289.
2. J. F. Meyer, "MOS models and circuit simulation," *RCA Review*, Vol. 32, March 1971, pp. 42-63.
3. A. Vladimirescu and Sally Liu, *The simulation of MOS integrated circuits using SPICE2*, Memorandum no. M80/7, February 1980, University of California, Berkeley.
4. L. M. Dang, "A simple current model for short channel IGFET and its application to circuit simulation," *IEEE Journal of Solid-State Circuits*, Vol. SC-14, No. 2, 1979, pp. 358-367.

5. W. R. Curtice, "A MESFET model for use in the design of GaAs integrated circuits," *IEEE Transactions on Microwave Theory and Techniques*, Vol. MTT-23, May 1980, pp. 448–456.
6. S. E. Sussman-Fort, S. Narasimhan, and K. Mayaram, "A complete GaAs MESFET computer model for SPICE," *IEEE Transactions on Microwave Theory and Techniques*, Vol. MTT-32, April 1984, pp. 471–473.
7. *PSpice Manual*. Irvine, Calif.: MicroSim Corporation, 1992.
8. S. Natarajan, "An effective approach to obtain model parameters for BJTs and FETs from data books," *IEEE Transactions on Education*, Vol. 35, No. 2, 1992, pp. 164–169.
9. M. H. Rashid, *SPICE for Power Electronics and Electric Power*. Englewood Cliffs, N.J.: Prentice Hall, 1993.

## PROBLEMS

- 9-1. For the amplifier circuit in Fig. 6-8, calculate and plot the frequency responses of the output voltage and the input current. The frequency is varied from 10 Hz to 10 MHz in decade steps with 10 points per decade.
- 9-2. A shunt-shunt feedback is applied to the amplifier circuit in Fig. 9-8. This is shown in Fig. P9-2. Calculate and print the frequency responses of the output voltage and the input current. The frequency is varied from 10 Hz to 10 MHz in decade steps with 10 points per decade. The model parameters are  $I_S=1N$ ,  $V_{TO}=-4$ ,  $BETA=0.5M$ ,  $CGDO=5.85P$ ,  $CGSO=3.49P$ , and  $LAMBDA=2.395E-3$ .

 

**Figure P9-2**

- 9-3. Repeat Example 9-5 if the transistor is an  $n$ -channel JFET. The model parameters are  $I_S=100E-14$ ,  $R_D=10$ ,  $R_S=10$ ,  $BETA=1E-3$ , and  $V_{TO}=-2$ . Assume  $R_{S2} = 0$ .
- 9-4. For the  $n$ -channel enhancement-type MOSFET in Fig. P9-4, plot the output characteristics if  $V_{DS}$  is varied from 0 to 15 V in steps of 0.1 V and  $V_{GS}$  is varied from 0 to 6 V in steps of 1 V. The model parameters are  $L=10U$ ,  $W=20U$ ,  $V_{TO}=2.5$ ,  $KP=6.5E-3$ ,  $R_D=5$ ,  $R_S=2$ ,  $R_B=0$ ,  $R_G=0$ , and  $R_{DS}=1MEG$ .
- 9-5. For Problem 9-4, plot the input characteristics if  $V_{GS}$  is varied from 0 to 6 V in steps of 0.1 V and  $V_{DS} = 15$  V.

 


Figure P9-4

9-6. An inverter circuit is shown in Fig. P9-6. For the input voltage as shown in Fig. 9-23(b), plot the transient response of the output voltage from 0 to  $80 \mu\text{s}$  in steps of  $2 \mu\text{s}$ . If the input voltage is 5 V dc, calculate the voltage gain, the input resistance, and the output resistance. Print the small-signal parameters of the PMOS. The model parameters of the PMOS are  $V_{TO} = -2.5$ ,  $K_P = 4.5E-3$ ,  $C_{BD} = 5\text{PF}$ ,  $C_{BS} = 2\text{PF}$ ,  $C_{GSO} = 1\text{PF}$ ,  $C_{GDO} = 1\text{PF}$ , and  $C_{GBO} = 1\text{PF}$ .

 


Figure P9-6

9-7. For the NMOS AND-logic circuit in Fig. P9-7, plot the transient response of the output voltage from 0 to  $100 \mu\text{s}$  in steps of  $1 \mu\text{s}$ . The model parameters of the  $p$ -channel depletion-type MOSFETs are  $V_{TO} = 2$ ,  $K_P = 4.5E-3$ ,  $C_{BD} = 5\text{PF}$ ,  $C_{BS} = 2\text{PF}$ ,  $R_D = 5$ ,  $R_S = 2$ ,  $R_B = 0$ ,  $R_G = 0$ ,  $R_{DS} = 1\text{MEG}$ ,  $C_{GSO} = 1\text{PF}$ ,  $C_{GDO} = 1\text{PF}$ , and  $C_{GBO} = 1\text{PF}$ .


 


Figure P9-7

 


**9-8.** For the NMOS NAND-logic gate circuit in Fig. P9-8, plot the transient response of the output voltage from 0 to 100  $\mu\text{s}$  in steps of 1  $\mu\text{s}$ . The model parameters of the PMOS are  $V_{TO} = -2.5$ ,  $K_P = 4.5E-3$ ,  $CBD = 5\text{PF}$ ,  $CBS = 2\text{PF}$ ,  $R_D = 5$ ,  $R_S = 2$ ,  $R_B = 0$ ,  $R_G = 0$ ,  $R_{DS} = 1\text{MEG}$ ,  $CGSO = 1\text{PF}$ ,  $CGDO = 1\text{PF}$ , and  $CGBO = 1\text{PF}$ . The model parameters of the NMOS are  $V_{TO} = 2.5$ ,  $K_P = 4.5E-3$ ,  $CBD = 5\text{PF}$ ,  $CBS = 2\text{PF}$ ,  $R_D = 5$ ,  $R_S = 2$ ,  $R_B = 0$ ,  $R_G = 0$ ,  $R_{DS} = 1\text{MEG}$ ,  $CGSO = 1\text{PF}$ ,  $CGDO = 1\text{PF}$ , and  $CGBO = 1\text{PF}$ .



**Figure P9-8**

**9-9.** A MOSFET amplifier with active load is shown in Fig. P9-9. Plot the magnitudes of the output voltage and the input current. The frequency is varied from 10 Hz to 100 MHz with a decade increment and 10 points per decade. The peak input voltage is 200 mV. The model parameters of the NMOS are  $V_{TO} = 2.5$ ,  $K_P = 4.5E-2$ ,  $CBD = 5\text{PF}$ ,  $CBS = 2\text{PF}$ ,  $R_D = 5$ ,  $R_S = 2$ ,  $R_B = 0$ ,  $R_G = 0$ ,  $R_{DS} = 1\text{MEG}$ ,  $CGSO = 1\text{PF}$ ,  $CGDO = 1\text{PF}$ , and  $CGBO = 1\text{PF}$ . Print the details of the bias point and the small-signal parameters of the NMOS.

 

**Figure P9-9**

- 9-10.** Use PSpice to perform a Monte Carlo analysis for six runs and for the frequency of Problem 9-2. The model parameter is  $R=1$  for resistors. The lot deviation for all resistances is  $\pm 15\%$ . The transistor parameter having uniform deviations is

$$V_{TO} = -4 \pm 1.5$$

- (a) The greatest difference from the nominal run is to be printed.
- (b) The maximum value of the output voltage is to be printed.
- (c) The minimum value of the output voltage is to be printed.

- 9-11.** Use PSpice to perform the worst-case analysis for Problem 9-10.

- 9-12.** Use PSpice to perform a Monte Carlo analysis for six runs and for the transient response of Problem 9-6. The transistor parameter having uniform deviations is

$$V_{TO} = -2.5V \pm 1.2V$$

- (a) The greatest difference from the nominal run is to be printed.
- (b) The maximum value of the output voltage is to be printed.
- (c) The minimum value of the output voltage is to be printed.

- 9-13.** Use PSpice to perform the worst-case analysis for Problem 9-12.

- 9-14.** Use PSpice to perform a Monte Carlo analysis for five runs and for the transient response of Problem 9-7. The transistor parameter having uniform deviations is

$$V_{TO} = 2V \pm 1.5V$$

- (a) The greatest difference from the nominal run is to be printed.
- (b) The maximum value of the output voltage is to be printed.
- (c) The minimum value of the output voltage is to be printed.

- 9-15.** Use PSpice to perform the worst-case analysis for Problem 9-14.

- 9-16.** Use PSpice to perform a Monte Carlo analysis for five runs and for the transient response of Problem 9-8. The transistor parameter having uniform deviations is

$$V_{TO} = -2.5V \pm 1.5V$$

- (a) The greatest difference from the nominal run is to be printed.
- (b) The maximum value of the output voltage is to be printed.
- (c) The minimum value of the output voltage is to be printed.

- 9-17.** Use PSpice to perform the worst-case analysis for Problem 9-16.

- 9-18.** Use PSpice to perform a Monte Carlo analysis for five runs and for the frequency response of Problem 9-9. The transistor parameter having uniform deviations is

$$V_{TO} = 2.5V \pm 1.5V$$

- (a) The greatest difference from the nominal run is to be printed.
- (b) The maximum value of the output voltage is to be printed.
- (c) The minimum value of the output voltage is to be printed.

- 9-19.** Use PSpice to perform the worst-case analysis for Problem 9-18.