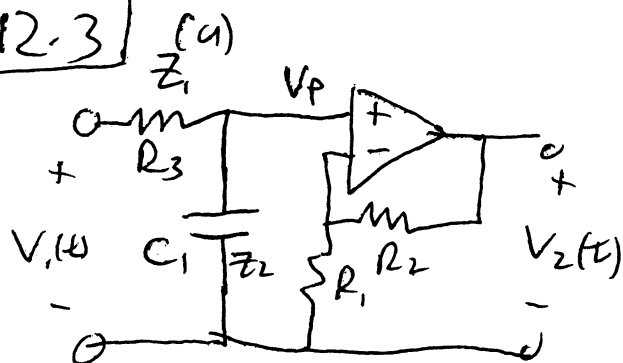


EECS 245 Homework 10 solution

Problems 11-37 & 11-40 are in the Homework 9 solution

12.3



From OP-Amps, $V_2(s) = V_p \left(\frac{R_1 + R_2}{R_1} \right)$
(standard non-inverting OP-Amp amplifier)

$$V_p = V_1(s) \left[\frac{Z_2}{Z_1 + Z_2} \right] \therefore$$

$$V_2(s) = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{\frac{1}{C_1 s}}{R_3 + \frac{1}{C_1 s}} \right) V_1(s)$$

$$V_2(s) = \left(\frac{10 + 30}{10} \right) \left(\frac{1}{.005s + 1} \right) V_1(s)$$

$$\frac{V_2(s)}{V_1(s)} = T_V(s) = \frac{800}{s + 200}$$



(b) • DC gain = $T_V(0) = \frac{800}{200} = \boxed{4}$

• ∞ frequency gain = $T_V(\infty) = \frac{800}{\infty} = \boxed{0}$


Cutoff frequency: Circuit is of type shown in eqn 12-4;
type of filter

low-pass filter w/ $\omega_c = 200$

(c) $G(\omega)$

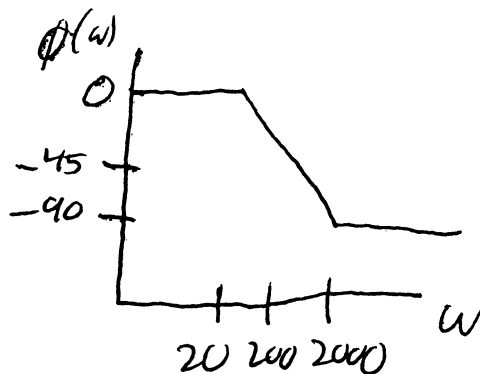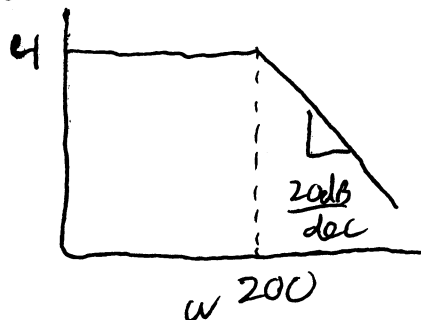

12.7

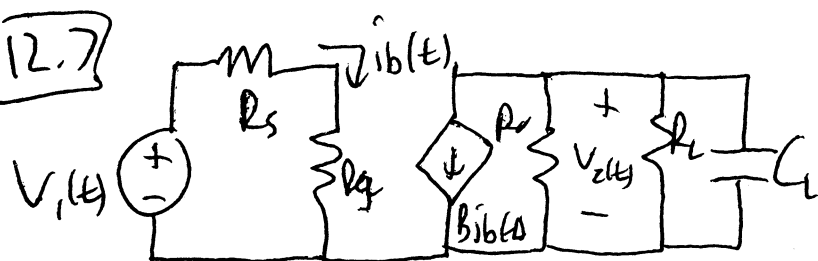

$$I_B(s) = \frac{V_1(s)}{R_s + R_g}$$

$$V_2(s) = (-B I_B(s)) (R_o \parallel R_L \parallel C)$$

$$V_2(s) = \left(\frac{R_o R_L}{R_L + R_o + C s R_o R_L} \right) \left(-B \frac{V_1(s)}{R_s + R_g} \right)$$

$$T_V(s) = \left(\frac{-B R_o R_L}{R_s + R_g} \right) \left(\frac{1}{s(R_o \cdot R_L \cdot C) + R_o + R_L} \right)$$

$$|T_V(0)| = \frac{B}{R_s + R_g} \left(\frac{R_o R_L}{R_o + R_L} \right) = 0.665$$

$$T_V(s) = \frac{-9980}{s(2.5 \times 10^{-4}) + 15,000}$$


$$|T_V(j\omega = \infty)| = 0$$

Pass-band gain: $K = T_V(0) = 0.665$

$$\omega_c = \frac{R_o + R_L}{R_o \cdot R_L \cdot C} \quad \omega_c = 6 \times 10^7$$

Circuit is low-pass

12.8

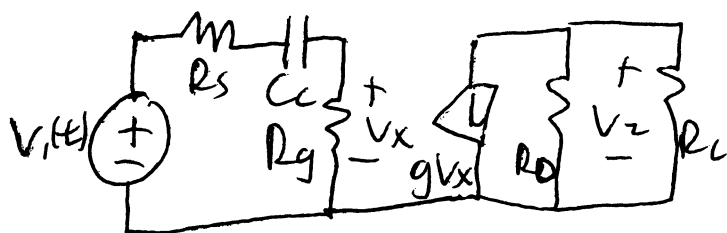

$$V_X(s) = \frac{V_1(s) R_g}{R_g + R_s + \frac{1}{C_c s}} = \frac{V_1(s) R_g C_c s}{C_c s (R_g + R_s) + 1}$$

$$V_2(s) = \left(\frac{R_o R_L}{R_o + R_L} \right) (-g \cdot V_X(s)) \therefore$$

$$T_V(s) = \frac{-g R_o R_L}{R_o + R_L} \left[\frac{R_g C_c s}{(R_g + R_s) C_c s + 1} \right] = \frac{-0.83 s}{0.025 s + 1}$$

$$|T_V(0)| = 0$$

$$|T_V(\infty)| = \left[\frac{g R_o R_L}{R_o + R_L} \right] \left[\frac{R_g C_c}{(R_g + R_s) C_c} \right] = 33.2$$

$$K = T_V(\infty) = 33.2$$

$$\omega_c = \frac{1}{(R_g + R_s) C_c}$$

$$\omega_c = 39,492$$

Circuit is high pass

Take all terms in $\frac{R_g C_c s}{(R_g + R_s) C_c s + 1}$ & divide by $s \rightarrow \frac{R_g C_c}{(R_g + R_s) C_c + 1/s} \quad 1/s = 0$