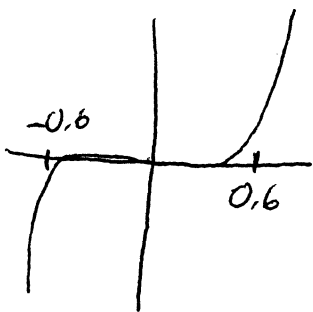


EELS 245


Hmwk #1 solution

3.5 Note, these are not ideal, but typical diodes. Thus, they have $\sim 0.6V$ drop when conducting, and slight curve

(a)




(b)

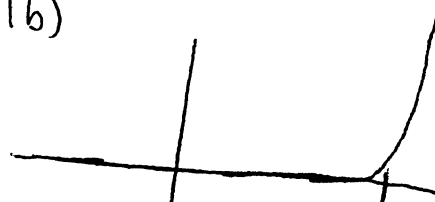

Note: The Zener will conduct at $-0.6V$ and lower, but the other diode won't until it breaks



Needed for diode to conduct
Needed for Zener to conduct

(c)

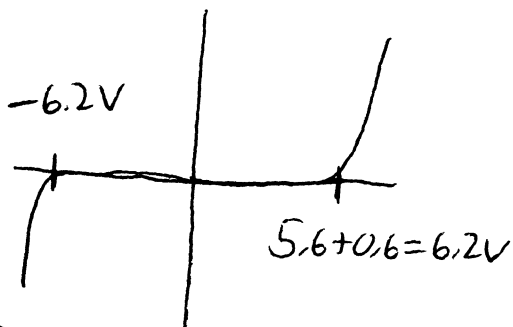


In both directions, we need 0.6 volts to turn on the forward diode, and 5.6 move to push the reverse diode into breakdown

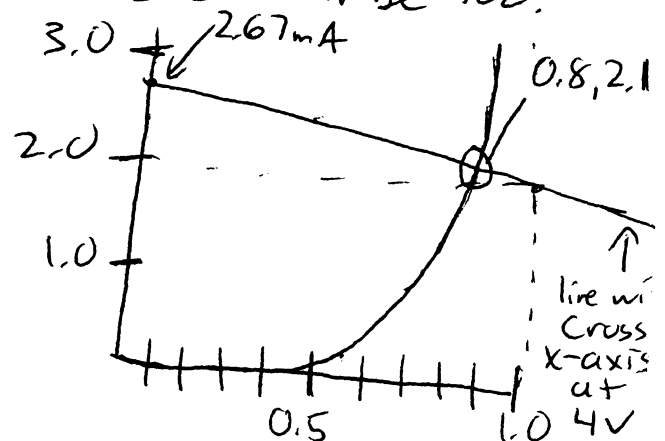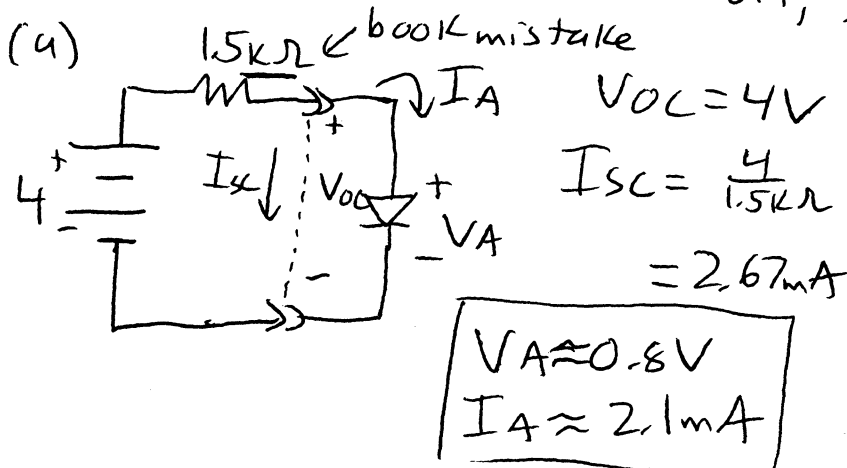3.9 The Key to load-line is to find the open-circuit voltage and short-circuit current, plot them, draw a line, and then find the operating point. BE CAREFUL in drawing your graphs; if the scale is off, your answer will be too.



(b)

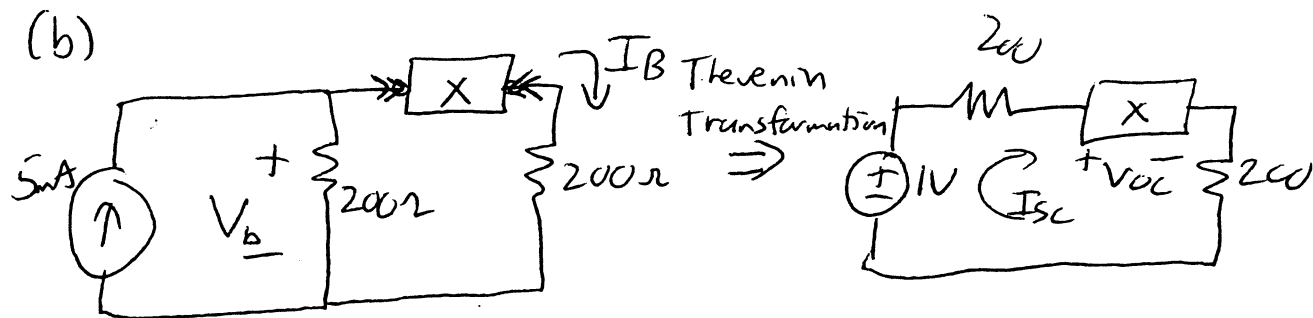


$$V_{OC} = 1V$$

$$I_{SC} = \frac{1V}{400\Omega} = 2.5mA$$


$$I_b = i_x = \boxed{1.7mA}$$

$$V_b = V_x + 200i_x$$

$$\boxed{V_b \approx 0.69V}$$

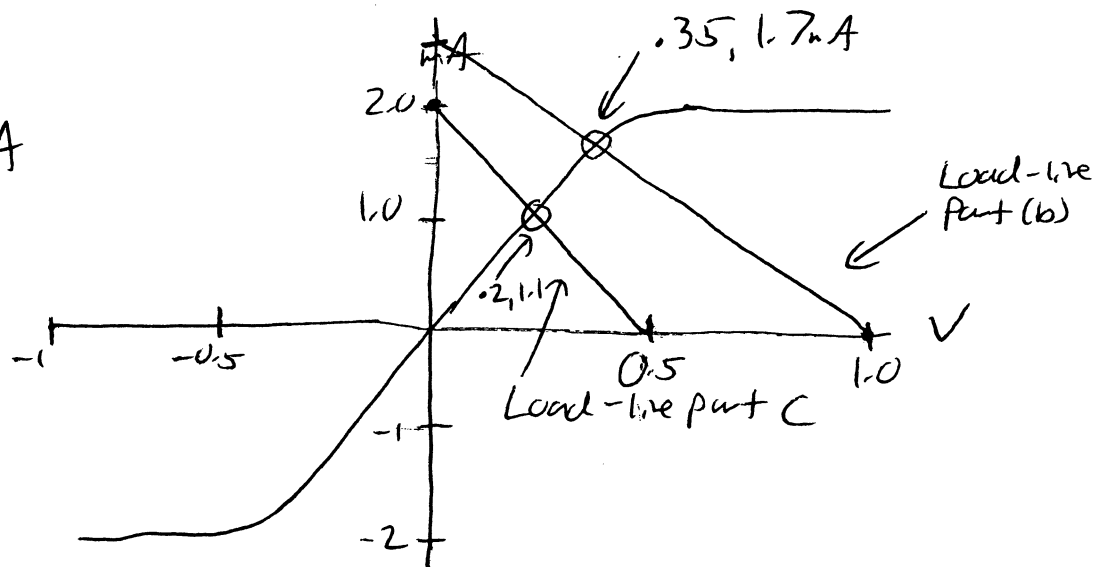

(c)

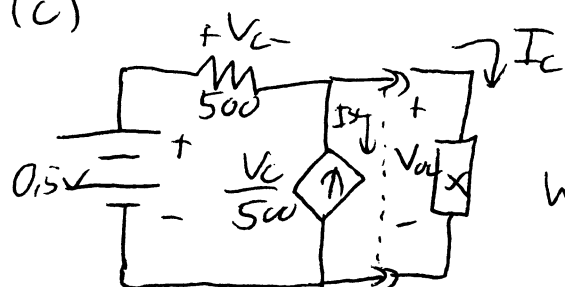

$$V_{OC} = 0.5V$$

$$I_{SC} = \frac{V_C}{500} + \frac{V_C}{500} = \frac{V_C}{250}$$

$$\text{When shorted, } V_C = 0.5V \therefore \underline{I_{SC} = 2mA}$$

$$\boxed{I_C = i_x \approx 1.1mA \quad V_C = 0.5 - V_x \approx 0.3V}$$

(3.15) Note that these are ideal diodes; they have the following transfer:

Thus, when on, $V_d = 0$, not 0.6


A good way to analyze is to assume the diodes are off, then turn them on when forward biased and re-analyze circuit until everything fits.

(a) $+10V$ at the anode, 0 at the cathode $\rightarrow$ diode will turn on. Thus, $V=0$ and $I = \frac{10V}{2.7k\Omega} = 3.7mA$

(b) 0 at the anode, $10V$ at the cathode $\rightarrow$ diode remains off. $V=10, I=0$ (diode acts like open circuit)

(c) $5V$ at anode, 0 at cathode $\rightarrow$ diode turns on. Since $R_{on} = 0$ ~~for~~ ^{for} diode, all current will flow through it. Thus, $I=0, V=0$ (diode acts like a wire)

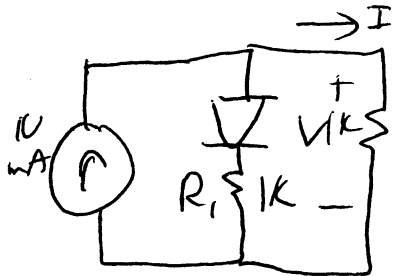(d) Initially, diode is off. All current flows through R_2 , causing



V to rise to $(10mA)(1k) = 10V$. Diode

turns on, and we have a current divider.

$$I = 5mA, V = 5V$$