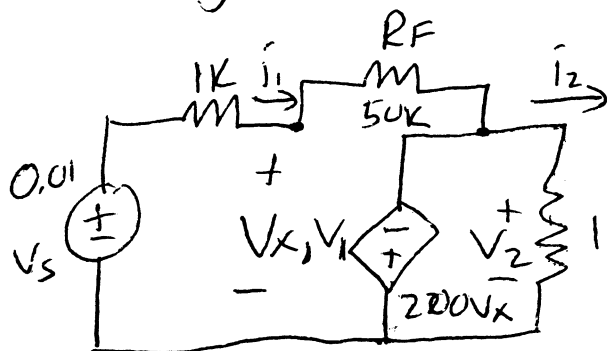


EECS 245 HMWK Solution #2

4.4 The key to solving linear-dependent source circuits is writing down all of the device equations.



$$(1) V_2 = -200V_x \quad (2) V_x = V_1$$

$$(3) V_S = V_x + i_1(1K)$$

$$(4) i_1 = \frac{V_x - V_2}{R_F} \quad (5) i_2 = \frac{V_2}{1K}$$


Substituting (1) into (4) gives $\frac{V_x + 200V_x}{R_F} = i_1$. By (3), $i_1 = \frac{V_S - V_x}{1K} \therefore$

$$\frac{V_x + 200V_x}{R_F} = \frac{V_S - V_x}{1K}, \quad V_S = 0.01, \text{ so } V_x = 2mV \quad \text{By (2), } V_2 = -0.4V$$

$$\text{By (5), } i_2 = -0.4mA, \quad \text{By (4), } i_1 = 8.04\mu A \quad \frac{i_2}{i_1} = -49.8$$

$$\frac{V_1}{i_1} = 249\Omega$$

4.5

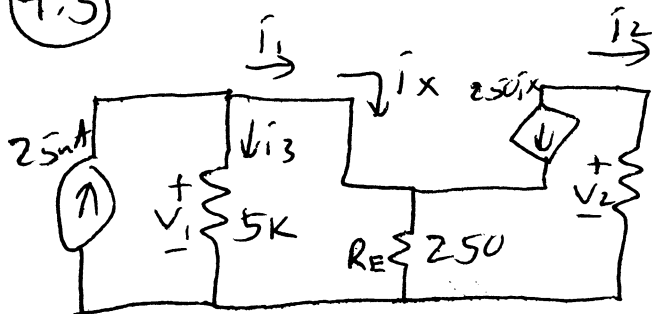

$$(1) i_1 = i_x \quad (2) i_2 = -250i_x$$

$$(3) V_1 = 250i_x R_E \quad (4) i_1 + i_3 = 25\mu A$$

$$(5) V_1 = i_3 \cdot 5K$$

$$(6) V_2 = i_2 \cdot 1K$$

Substituting (5) + (1) into (4) gives $i_x + \frac{V_1}{5K} = 25\mu A$. Placing (3) into


this yields $i_x + 250i_x \frac{R_E}{5K} = 25\mu A \quad R_E = 250 \therefore i_x = 1.845\mu A$

$$\text{By (2), } i_2 = -0.461mA \quad \text{By (6), } V_2 = -0.461 \quad \text{By (3), } V_1 = 0.11577$$

$$\frac{V_2}{V_1} = -3.98$$

$$\frac{V_1}{i_1} = 62.75K\Omega$$

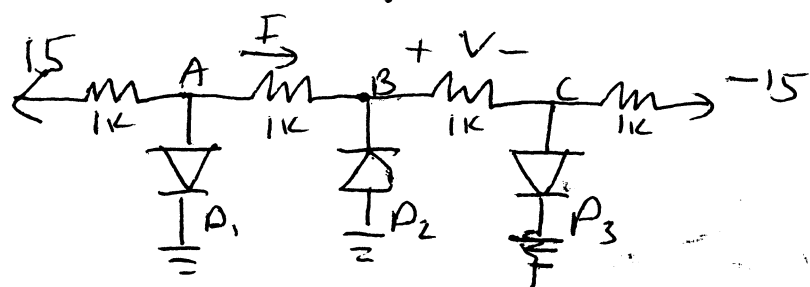(3.17) Start analysis by assuming all diodes off, then turn on and re adjust




D_1 sees +15 forward bias, it turns on. $V_A = 0$

D_3 sees -15 reverse bias, stays off.

D_2 sees +15 ($0 - (-15)$) fwd bias turns on. $V_B = 0$.

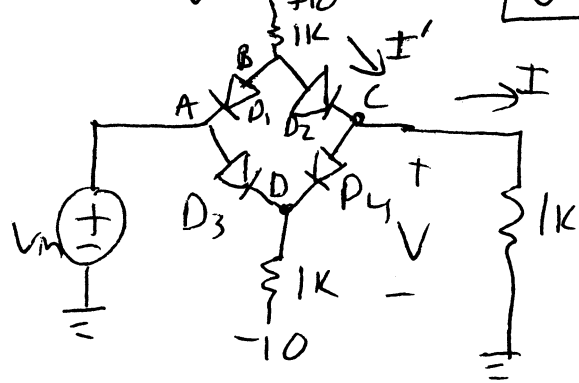$V_A = V_B = 0 \therefore \boxed{I = 0}$ $V_C = -7.5V$ (voltage divider) D_3 is still off. $V = 0 - (-7.5) \boxed{V = 7.5V}$



$V_{in} = 0 \rightarrow$ All diodes on. $V_A = V_B = V_C = V_D = 0$, $\boxed{V = 0, I = 0}$ $I' = 10mA$, but all goes through D_4 to -10.

$V_{in} = 2 \rightarrow$ All diodes on. $V_A = V_B = V_C = V_D = 2$. $V = 2, I = 2mA$ $I' = 8mA$,

excess goes through D_4 . Circuit still works. $\boxed{V = 2, I = 2mA}$

$V_{in} = 6 \rightarrow$ All diodes on. $V_A = V_B = V_C = V_D = 6$. $V = 6, I = 6mA$.

However, $I' = 4mA$. Extra current must come through D_1 or D_3 , but can't travel backwards through diode. Therefore, $I \leq I'$







$I = I'$ at $5mA$. $V_B = V_C = 5$. However, this turns D_1 & D_4 off.

So, for V_{input} voltages greater than 5, output remains at $\boxed{V = 5, I = 5mA}$

and the excess current from the input is shunted to -10.

$V_{in} = 10$ See above $\boxed{V = 5, I = 5mA}$

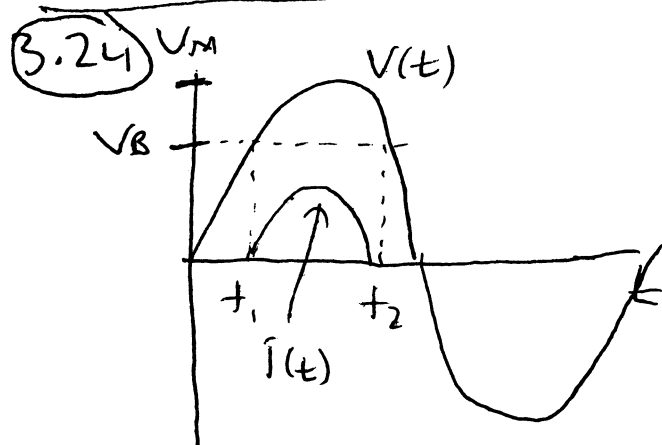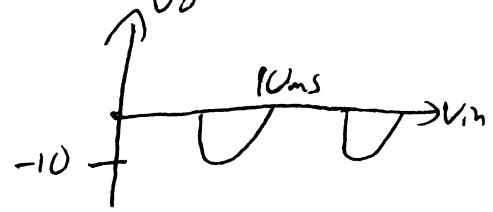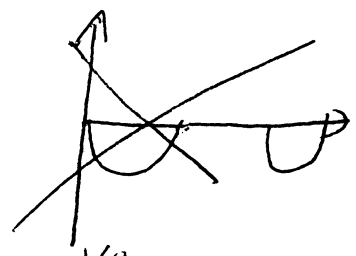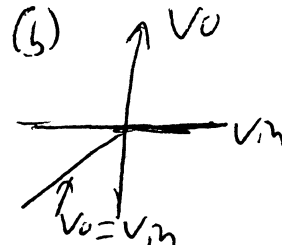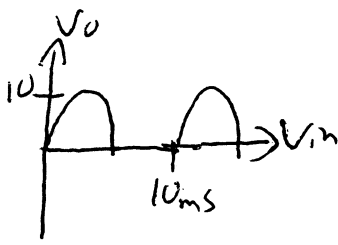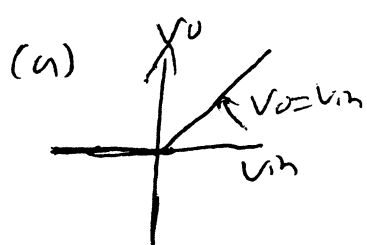(3.2p) ideal diode $\rightarrow$ short when on. In both circuits, diodes conduct for $V_{in} > 0$. In (A) this causes V_{in} to pass to R . In (B) it shorts V_o . For $V_{in} < 0$, in (a) Voltage cannot get to V_o . In (b), all V_{in} will be across V_o since it is an open circuit.



$i(t)$ is non-zero only when $V(t) > V_B$. $i(t)$ will peak when $V_s(t)$ peaks at V_m . Thus, $i_{max} = \frac{V_m - V_B}{R}$. $i_{max} = 0.6 A$

As a function of time, $i(t) = \frac{V_m \sin(\omega t) - V_B}{R}$ setting $i(t) = 0$,

$\sin(\omega t) = \frac{V_B}{V_m}$. We have two solutions: $t_1 = \frac{0.775}{\omega}$, $t_2 = \frac{2.37}{\omega}$.


These are marked on the graph. Sine wave period is $T = 2\pi/\omega$.

diode on = $\frac{2.37/\omega - 0.775/\omega}{2\pi/\omega} = \boxed{25.3\%}$

(3.22) The current through the meter is a half-wave rectified sinusoid. Since voltage is $10 V_{RMS}$, $V_{p-p} = 10\sqrt{2}$. Thus, current will be $\frac{10\sqrt{2}}{R}$. As given in the problem, the Avg = $\frac{V_{PP}}{\pi}$.

Avg current = $\frac{10\sqrt{2}}{\pi R} = 5mA$ $R = 900\Omega$

3.35

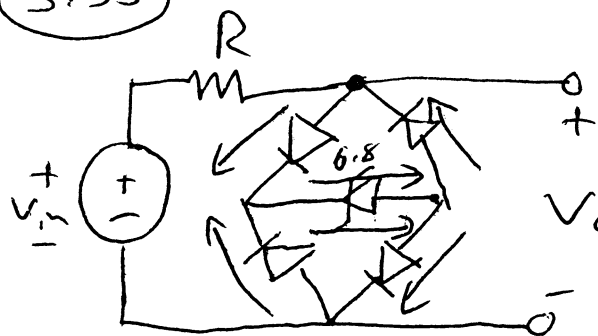


If the bridge is off, $V_o = V_{in}$. Once the bridge turns on, V_o will be held at that voltage. Higher voltages will cause more current over R & the output will be held at the initial "on" voltage.


In either direction, to turn the bridge on, we must fwd bias 2 diodes, and reverse-bias the zener into break down.

Thus, On voltage = $0.6 + 6.8 + 0.6 = \pm 8V$

Current paths are labeled above.

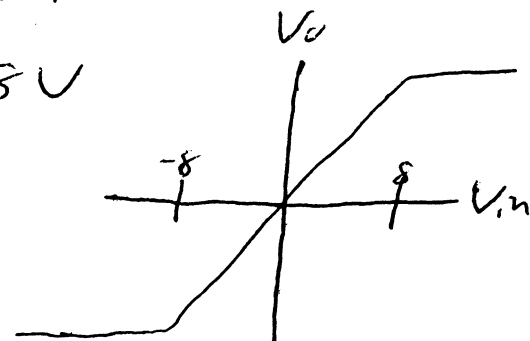

3.38

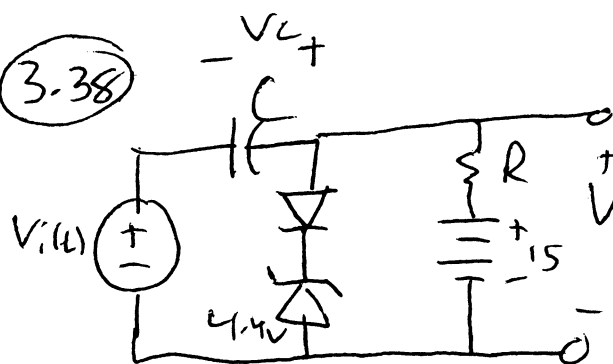

Circuit operation: With no input,

($V_i(t) = 0$), Diodes will activate,

Charging capacitor until $V_C = V_o = 5V$. Then, diodes shut off. If

$R_C \gg T$, where T is the period of $V_i(t)$, when $V_i(t)$ is turned

on, V_C will remain almost constant. If $V_i(t) < 5V$, this

will be passed directly to V_o . If $V_i(t) > 5V$, diodes will

conduct, increasing V_C & keeping maximum at $5V$, the buffer

is here to initially charge the capacitor to the $5V$ bias.