

EECS 245 HMWK 5 Sol'n

20

4.42 From pg 250, $r_{\pi} = \frac{BV_T}{I_{CQ}}$ & $g_m = \frac{\beta}{r_{\pi}} = \frac{I_{CQ}}{V_T}$

$V_T \approx 26mV$, $\beta = 100$, we get the following:



I_{CQ}	r_{π}	g_m
$1\mu A$	$2.6M\Omega$	$38.5\mu S$
$0.1mA$	$26k\Omega$	$3.85mS$
$1mA$	$2.6k\Omega$	$38.5mS$

Note: unit for g_m , mS , is milliSiemens, not milliseconds.

Siemen: $S = \frac{Amp}{Volt}$

(2)

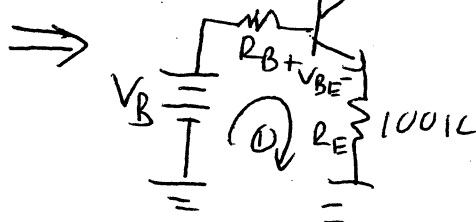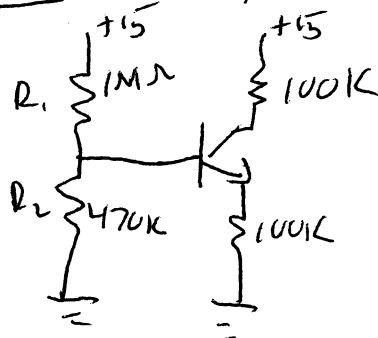4.46 First, find I_{BQ} w/ DC equivalent circuit: Section 4.7



$$V_B = \frac{15(470K)}{470K + 1M} = 4.8V = V_B$$

$$R_B = R_1 || R_2 = \frac{470K(1M)}{470K + 1M}$$


$$R_B = 320K\Omega$$

(2)

CL around ①: $V_B = I_B R_B + V_{BE} + I_E R_E$ $I_E = (\beta + 1)I_B$ $V_{BE} = 0.7$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E} \quad I_{BQ} = 0.393\mu A \quad I_{CQ} = \beta I_{BQ} \quad \boxed{I_{CQ} = 39.3\mu A}$$

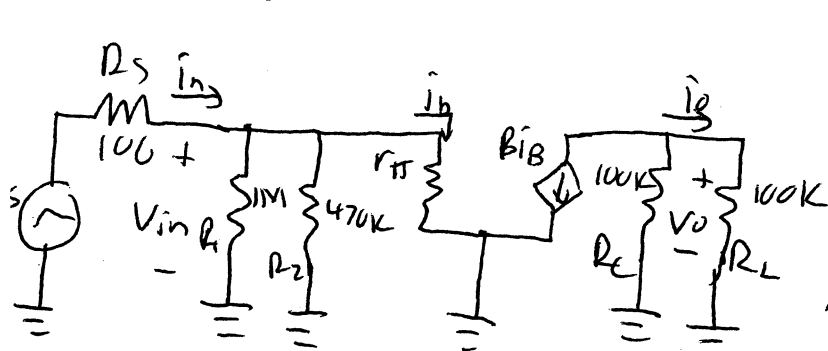Small signal model: (see next problem for how to draw SSm's)



$$r_{\pi} = \frac{BV_T}{I_{CQ}} = \frac{100(26mV)}{39.3\mu A} = \boxed{66.2K\Omega}$$

$$R_L' = R_L || R_C = 50K\Omega$$

$$A_v = \frac{-\beta R_L'}{r_{\pi} + (\beta + 1)R_E} \quad R_E = 0 \therefore A_v = \frac{-\beta R_L'}{r_{\pi}}$$

$$\boxed{A_v = -75.5}$$

$$A_{v0} = \frac{-\beta R_C}{r_{\pi}} = \boxed{-151 = A_{v0}}$$

$$Z_{in} = \frac{1}{\frac{1}{R_B} + \frac{1}{r_{\pi} + (\beta + 1)R_E}} =$$

$$\frac{1}{\frac{1}{20K} + \frac{1}{66.2K}} \quad \boxed{Z_{in} = 54.8K\Omega}$$

$$A_i = \frac{A_v Z_{in}}{R_C} = \frac{(-75.5)(54.8K)}{100K} = \boxed{-41.4 = A_i}$$




(2)

$$G = A_i A_v \quad \boxed{G = 3,126} \quad Z_o = R_C \quad \boxed{Z_o = 100K\Omega}$$

4.49 In writing small signal models, remember the following rules:

1) All DC voltage sources become short circuits & current sources become open circuits

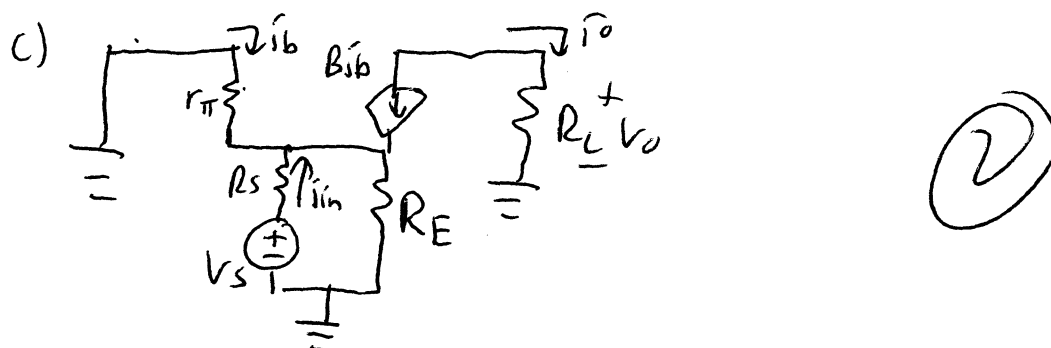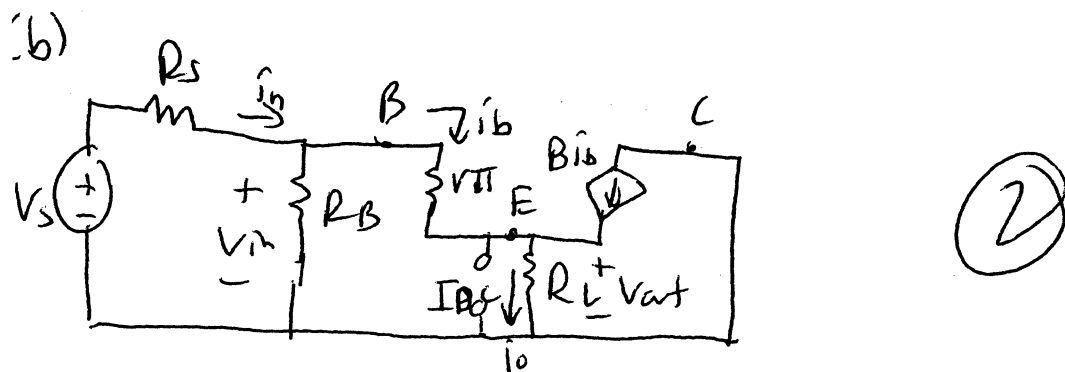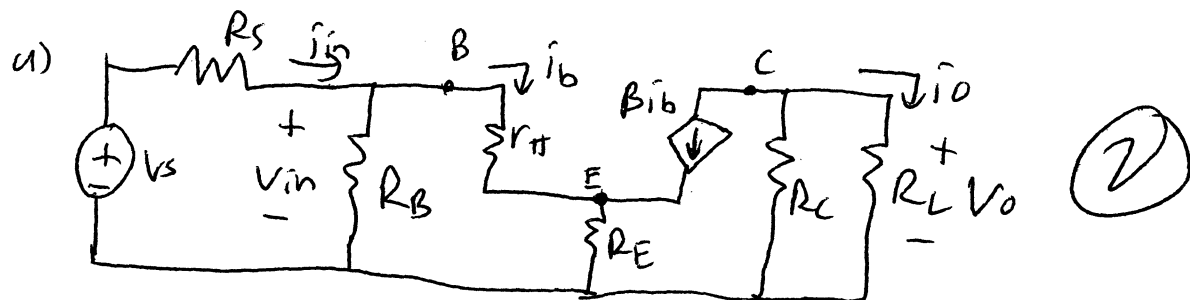2) All capacitors become short circuits 3) BJT's are replaced w/ model on pg 251



1.52 All equations come from section 4.8 directly $\rightarrow$ see circuit!

DC: $V_B = \frac{15(1M)}{1M+1M} = 7.5$ $R_B = 1M // 1M = 500k$ $I_{CQ} = \beta I_{BQ} = 100 \left(\frac{7.5 - 0.7}{500k + (100+1)100k} \right)$ $I_{CQ} = 64.1 \mu A$


$r_{\pi} = \frac{\beta V_T}{I_{CQ}}$ $r_{\pi} = 40.56 k\Omega$ $R_L' = 100k // 150k$ $R_L' = 33.3 k\Omega$

$A_v = \frac{R_L'(B+1)}{r_{\pi} + R_L'(B+1)} = A_v = 0.988$ $A_{v0} = \frac{R_E(B+1)}{r_{\pi} + R_E(B+1)} = A_{v0} = 0.996$ $R_s' = R_B // R_s$ $R_s' = 83.3 k\Omega$

$Z_{in} = R_B // (r_{\pi} + R_L'(B+1))$ $Z_{in} = 436 k\Omega$ $A_i = \frac{A_v Z_{in}}{R_L}$ $A_i = 8.61$

$G = A_v A_i$ $G = 8.51$ $Z_o = R_E // \left(\frac{R_s' + r_{\pi}}{B+1} \right)$ $Z_o = 1.21 k\Omega$

1.56 Small signal equivalent:

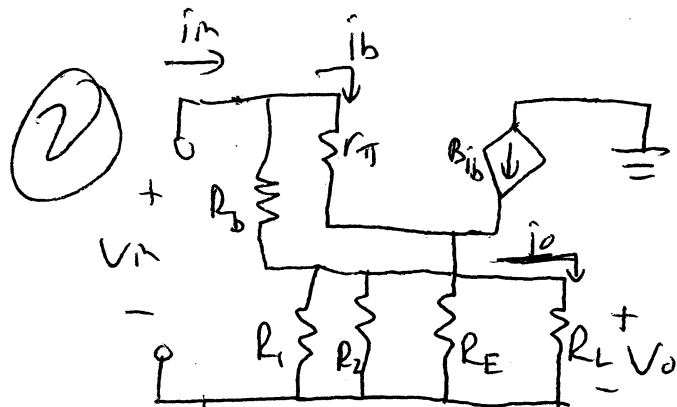

First, combine bottom 4 resistors:

$$R_L' = R_1 \parallel R_2 \parallel R_E \parallel R_L$$

$$V_o = i_L'(R_L')$$

$$i_L' = i_b + \beta i_b + i_x$$

$$i_x = \frac{i_b r_{\pi}}{R_B}$$

$$V_o = R_L' (i_b + \beta i_b + \frac{r_{\pi} i_b}{R_B})$$

$$V_{in} = V_o + r_{\pi} i_b$$

$$A_v = \frac{V_o}{V_{in}} =$$

$$\frac{R_L' (1 + \beta + \frac{r_{\pi}}{R_B})}{r_{\pi} + R_L' (1 + \beta + \frac{r_{\pi}}{R_B})} = A_v$$


$$i_{in} = \frac{V_{in} - V_o}{R_B \parallel R_{\pi}} = \frac{V_{in} - A_v V_{in}}{R_B \parallel R_{\pi}}$$

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{\frac{V_{in} - A_v V_{in}}{R_B \parallel R_{\pi}}}$$

②

$$Z_{in} = \frac{R_B \parallel R_{\pi}}{1 - A_v}$$

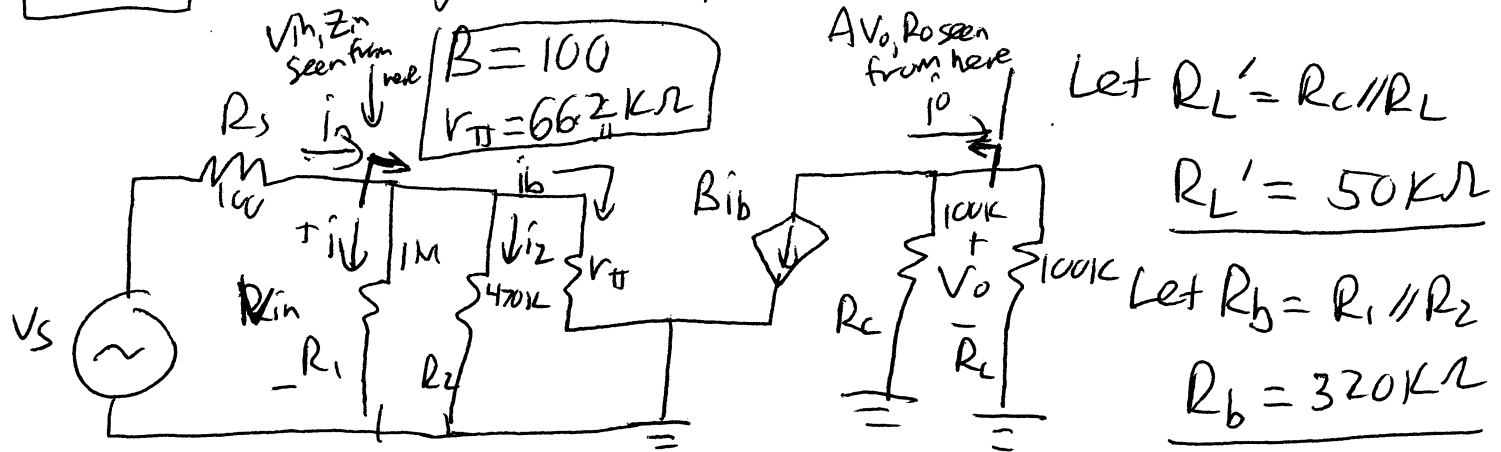4.46 Small signal analysis in depth $\rightarrow$ much like section 4.7



$$A_v = \frac{V_o}{V_{in}} \quad V_o = i_o R_L' = -B i_b R_L' \quad V_{in} = i_b r_{\pi} \therefore \frac{V_o}{V_{in}} = \frac{-B i_b R_L'}{i_b r_{\pi}} = \boxed{-755}$$

$$A_{v_o}, V_o = i_o R_C \therefore \frac{V_o}{V_{in}} = \frac{-B R_C i_b}{i_b r_{\pi}} = \boxed{-151}$$

$$Z_{in} = \frac{V_{in}}{i_{in}} \quad i_{in} = i_1 + i_2 + i_b = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_2} + \frac{V_{in}}{R_b} \therefore \frac{V_{in}}{i_{in}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_b}} = \boxed{54.8 \text{ K}\Omega}$$

$$A_i = \frac{i_o}{i_{in}} \quad A_v \cdot Z_{in} = \left(\frac{V_o}{V_{in}}\right) \left(\frac{V_{in}}{i_{in}}\right) = \frac{V_o}{i_{in}} \quad V_o = i_o R_C \therefore A_i = \frac{A_v \cdot Z_{in}}{R_C}$$

$A_i = -41.4$ Note A_i does not depend on R_L . In reality, it does, but this quantity measures current gain independent of R_L

$$G = A_i \cdot A_v = \boxed{3,126} \quad Z_o = \frac{V_o}{i_o} = R_C = \boxed{100 \text{ K}\Omega}$$