

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

FORMULA SHEET

TRIG IDENTITIES:

$$\cos(x + y) = \cos x \cos y - \sin x \sin y \qquad \sin(x + y) = \sin x \cos y + \cos x \sin y$$

$$\sin(2x) = 2 \sin x \cos x \qquad \cos(2x) = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$$



FOURIER COEFFICIENTS: $v(t) = V_A \cos(\omega t + \phi) = a \cos(\omega t) + b \sin(\omega t)$ where

$$V_A = \sqrt{a^2 + b^2} \text{ and } \phi = \text{Tan}^{-1}\left(\frac{-b}{a}\right). \text{ Conversely, } a = V_A \cos \phi \text{ and } b = -V_A \sin \phi$$

	INDUCTORS	CAPACITORS
Terminal relationship	$v_L = L \frac{di_L}{dt}$	$i_C = C \frac{dv_C}{dt}$
Impedance	$Z_L = j\omega L$	$Z_C = \frac{1}{j\omega C}$
Time constant	$T_C = \frac{L}{R_T}$	$T_C = R_T C$

INITIAL/FINAL VALUE THEOREM: $f(t) = [IV - FV]e^{-\frac{t}{T_C}} + FV$
 where IV=initial value and FV=final value.

OP AMP CIRCUITS:

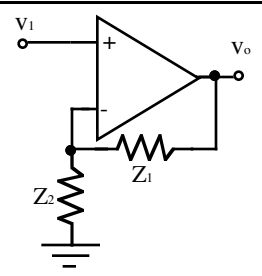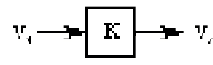CIRCUIT	BLOCK DIAGRAM	GAINS
	 Non-inverting amplifier	$K = \frac{Z_1 + Z_2}{Z_2}$

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

	<p style="text-align: center;">Inverting amplifier</p>	$K = -\frac{Z_2}{Z_1}$
	<p style="text-align: center;">Summer</p>	$K_1 = -\frac{Z_F}{Z_1}, K_2 = -\frac{Z_F}{Z_2}$
	<p style="text-align: center;">Subtractor</p>	$K_1 = -\frac{Z_2}{Z_1}, K_2 = \left(\frac{Z_1 + Z_2}{Z_1}\right) \left(\frac{Z_4}{Z_3 + Z_4}\right)$
	<p style="text-align: center;">Integrator</p>	$K = -\frac{1}{RC}$
	<p style="text-align: center;">Differentiator</p>	$K = -RC$