

**CASE WESTERN RESERVE UNIVERSITY**  
Case School of Engineering  
Department of Electrical Engineering and Computer Science

**ENGR 210. Introduction to Circuits and Instruments (4)**

**Homework Set No. 4**

References: [T&R4] sections 3-1, 3-2, 3-3

Issued 2/4/04

Due 2/11/04

**NODE VOLTAGE ANALYSIS**

1) (5 pts) Problem 3-2, p. 129.

2) (5 pts) Problem 3-4, p. 129.

3) (5 pts) Problem 3-8, p. 130.

This circuit is called a Wheatstone Bridge and is often used for making precise measurements of small changes in resistance.

For information about early Wheatstone bridges check out:

[http://physics.kenyon.edu/EarlyApparatus/Electrical\\_Measurements/Wheatstone\\_Bridge/Wheatstone\\_Bridge.html](http://physics.kenyon.edu/EarlyApparatus/Electrical_Measurements/Wheatstone_Bridge/Wheatstone_Bridge.html)

For a mathematical analysis of the Wheatstone Bridge see:

[http://www.efunda.com/designstandards/sensors/methods/wheatstone\\_bridge.cfm](http://www.efunda.com/designstandards/sensors/methods/wheatstone_bridge.cfm)

4) (5 pts) Problem 3-19, p. 132.

**MESH CURRENT ANALYSIS**

5) (5 pts) Problem 3-10, p. 130.

6) (5 pts) Problem 3-12, p. 131.

**HINT:** Don't forget to consider using source transformations and supernodes/supermeshes if nothing else works.

**NOTE:** Please put section code AND your CWRU e-mail next to name at top of page.

Section codes are

MA (Monday Afternoon)

ME (Monday Evening)

TA (Tuesday Afternoon)

TE (Tuesday Evening)

WA (Wednesday Afternoon)

WE (Wednesday Evening)