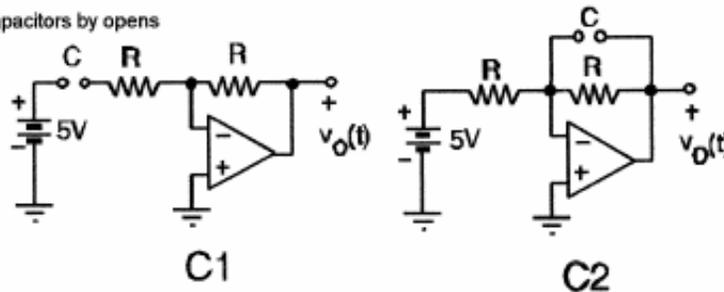


Homework Solutions 11

(6-45)

6-45 Replace capacitors by opens



For C1 when C is open the source and OP AMP are disconnected hence $v_O := 0$ V

For C2 when C is open the OP AMP circuit is an inverter hence $v_O := -5$ V

(7-15)

7-16

$$\frac{d}{dt}v(t) + 200v(t) = 25\sin(100t) \quad v_N(t) = K \exp(-200t) \quad v_F(t) = A \cos(100t) + B \sin(100t)$$

$$\frac{d}{dt}v_F(t) + 200v_F(t) = -100A \sin(100t) + 100B \cos(100t) + 200(A \cos(100t) + B \sin(100t)) = 25 \sin(100t)$$

$$\text{hence} \quad -100A + 200B = 25 \quad 100B + 200A = 0 \quad B = -2A \quad -500A = 25 \quad A := -\frac{1}{20} \quad B := \frac{1}{10}$$

$$v(t) = \frac{-1}{20} \cos(100t) + \frac{1}{10} \sin(100t) + K \exp(-200t) \quad v(0) = \frac{-1}{20} + K = 0 \quad K := \frac{1}{20}$$

$$v(t) = \frac{-1}{20} \cos(100t) + \frac{1}{10} \sin(100t) + \frac{1}{20} \exp(-200t) \quad \text{checking in Mathcad}$$

$$\frac{d}{dt} \left(\frac{-1}{20} \cos(100t) + \frac{1}{10} \sin(100t) + \frac{1}{20} \exp(-200t) \right) + 200 \left(\frac{-1}{20} \cos(100t) + \frac{1}{10} \sin(100t) + \frac{1}{20} \exp(-200t) \right)$$


(8-2)

8-2, 15-2 $I_1 := 6 \exp(j \cdot 0) \quad I_1 = 6$

$$I_2 := 3 \exp\left(j \cdot \frac{-\pi}{2}\right) \quad I_2 = -3j$$

$$|I_1 + I_2| = 6.708 \quad \frac{180}{\pi} \cdot \arg(I_1 + I_2) = -26.565$$
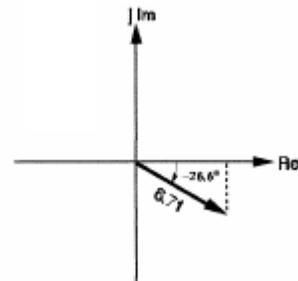
$$i_1(t) + i_2(t) = 6.708 \cos(\omega t - 26.565)$$




(8-12)

$$\mathbf{8-12, 15-12} \quad Z := 25 - j \cdot 25 + \frac{1}{\left(\frac{1}{-j \cdot 100} + \frac{1}{20 + j \cdot 50} \right)}$$

$$Z = 93.966 + 47.414j$$

$$|Z| = 105.25 \quad \frac{180}{\pi} \cdot \arg(Z) = 26.775$$

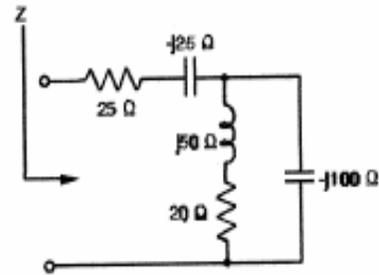

(8-15)

$$\mathbf{8-15, 15-15} \quad V := 200 \cdot \exp\left(-j \cdot \frac{\pi}{3}\right) \quad I := 20 \cdot 10^{-3} + j \cdot 0$$

$$\mathbf{(a)} \quad Z := \frac{V}{I} \quad Z = 5000 - 8660j \quad \Omega$$

$$\mathbf{(b)} \quad V := 150 \cdot \exp\left(-j \cdot 3 \cdot \frac{\pi}{2}\right) \quad I := \frac{V}{Z} \quad I = -1.299 \times 10^{-2} + 7.5j \times 10^{-3}$$

$$|I| = 1.5 \times 10^{-2} \quad \frac{180}{\pi} \cdot \arg(I) = 150$$

$$i(t) = 1.5 \cdot 10^{-2} \cdot \cos(1000t + 150^\circ) \text{ A}$$

(8-26)

$$\mathbf{8-26, 15-26} \quad Z := \frac{1}{j \cdot 2000 \cdot 2 \cdot 10^{-6} + \frac{1}{250 + j \cdot 2000 \cdot 0.25}}$$

$$Z_{IN} := 500 + Z \quad Z_{IN} = 625 - 375j \quad \leftarrow \text{Input Imp.}$$

By double voltage division

$$V_x := \left(\frac{Z}{Z_{IN}} \cdot 15 \right) \cdot \frac{250}{250 + j \cdot 2000 \cdot 0.25}$$

$$V_x = -0.882 - 3.529j \quad |V_x| = 3.638$$

$$\frac{180}{\pi} \cdot \arg(V_x) = -104 \quad v_x(t) = 3.638 \cdot \cos(2000t - 104^\circ)$$

