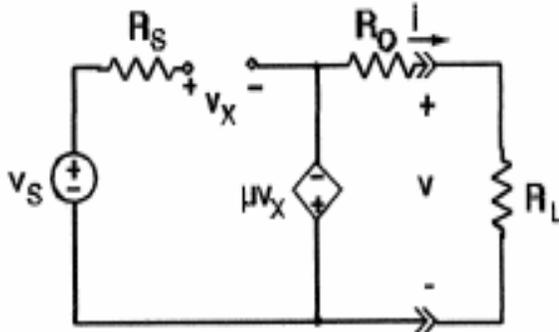


## Homework Solutions 7

4-12 The input loop contains an open circuit, hence  $i_S = 0$ . A KVL equation around the input loop is  $-v_S + v_X - \mu \cdot v_X = 0$



Solving for  $v_X$  yields  $v_X = \frac{v_S}{1 - \mu}$


The open-ckt voltage is

$$v_T = -\mu \cdot v_X = \frac{-\mu}{1 - \mu} v_S$$

The short-ckt current is  $i_N = \frac{-\mu \cdot v_X}{R_O}$

The Thevenin resistance is  $R_T = \frac{v_T}{i_N} = R_O$


4-22 Ckt is in summing amp

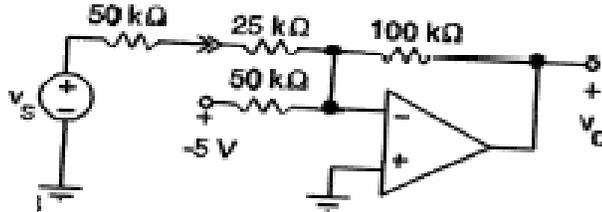

$$v_O = \frac{-100 \cdot 10^3}{50 \cdot 10^3 + 25 \cdot 10^3} v_S + \frac{-100 \cdot 10^3}{50 \cdot 10^3} (-5) \quad (-5)$$

$$v_O = 10 - \frac{4}{3} v_S$$

4-24

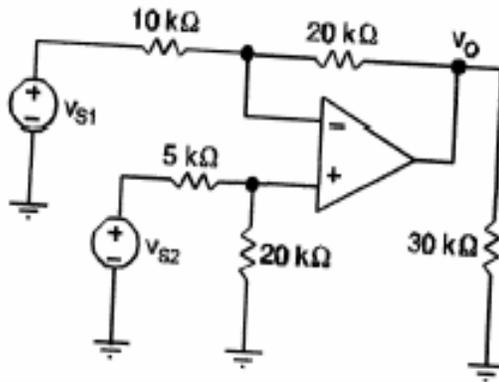

(a)  $v_O = K_1 \cdot v_{S1} + K_2 \cdot v_{S2}$

$$K_1 = \frac{R_2}{R_1} = -2$$

$$K_2 = \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} = \frac{12}{5}$$

$$v_O = -2 \cdot v_{S1} + 2.4 \cdot v_{S2}$$


(b)  $V_{CC} := 15 \quad v_{S2} := 10$

$$-V_{CC} < -2 \cdot v_{S1} + 2.4 \cdot v_{S2} < V_{CC}$$

$$\frac{-V_{CC} + 2.4 \cdot v_{S2}}{2} < v_{S1} < \frac{V_{CC} + 2.4 \cdot v_{S1}}{2}$$

$$4.5 < v_{S1} < 19.5$$

4-26

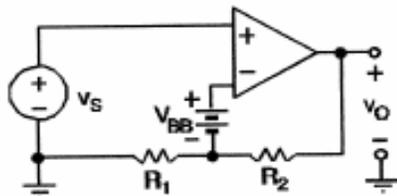

(a)  $v_P = v_S \quad v_N = \left( \frac{R_1}{R_1 + R_2} \right) \cdot v_O + V_{BB}$


$$v_P = v_N \rightarrow v_S = \left( \frac{R_1}{R_1 + R_2} \right) \cdot v_O + V_{BB}$$

$$v_O = \frac{R_1 + R_2}{R_1} \cdot (v_S - V_{BB}) = K \cdot (v_S - V_{BB})$$

$$K = \frac{R_1 + R_2}{R_1}$$

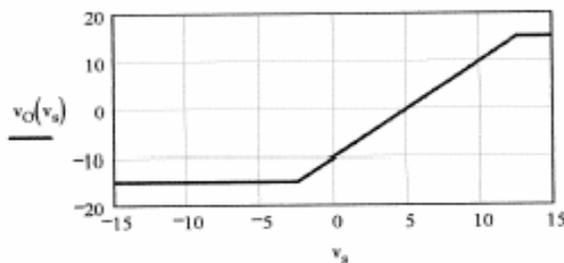(b)  $V_{BB} := 5 \quad V_{CC} := 15 \quad R_1 = R_2 \quad K := 2 \quad v_S := -15, -14.9, \dots, 15$

$$v_O(v_S) := \begin{cases} -V_{CC} & \text{if } v_S < \frac{-V_{CC}}{K} + V_{BB} \\ K(v_S - V_{BB}) & \text{if } \frac{-V_{CC}}{K} + V_{BB} \leq v_S \leq \frac{V_{CC}}{K} + V_{BB} \\ V_{CC} & \text{if } \frac{V_{CC}}{K} + V_{BB} < v_S \end{cases}$$



$$v_O(12.5) = 15$$

$$v_O(5) = 0$$

$$v_O(0) = -10$$

$$v_O(-2.5) = -15$$