

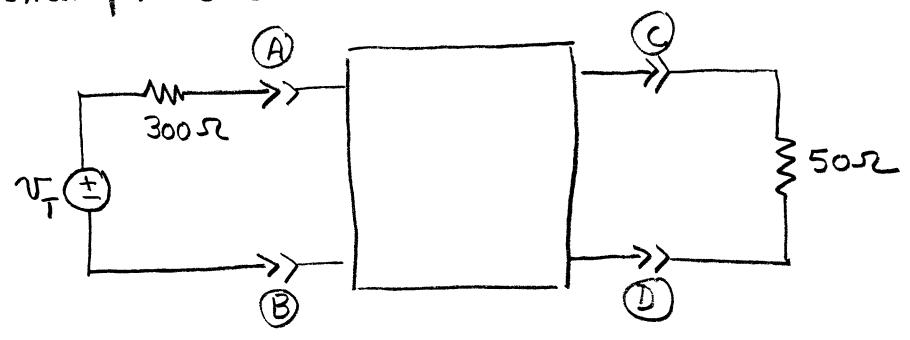
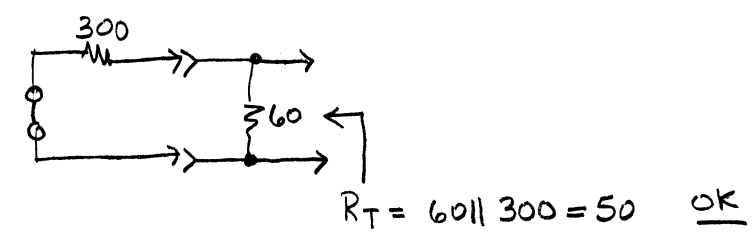
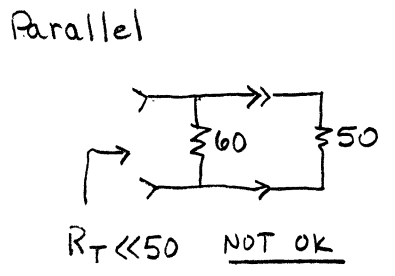


Design Example 3-23

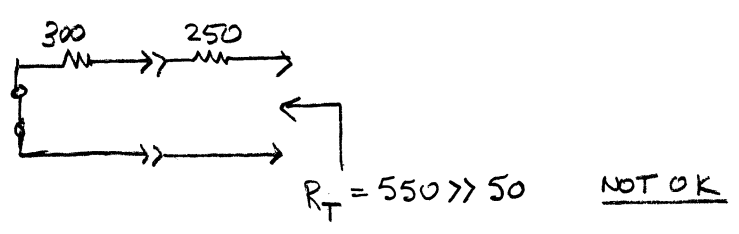


Design the two-port interface circuit so the load "sees" a Thevenin resistance of  $50\Omega$  between terminals C and D, while simultaneously the source "sees" a load resistance of  $300\Omega$  between A and B

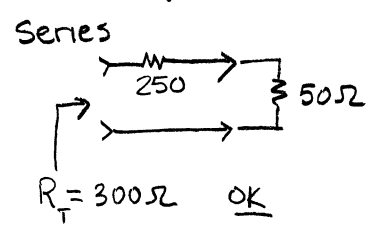
Design We can try different interface circuits



Try two resistor circuits

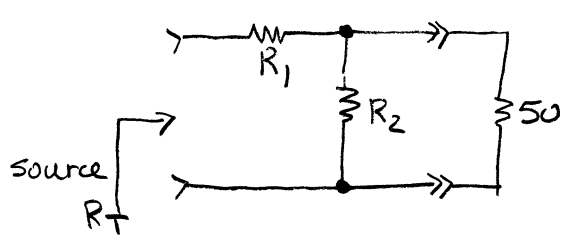

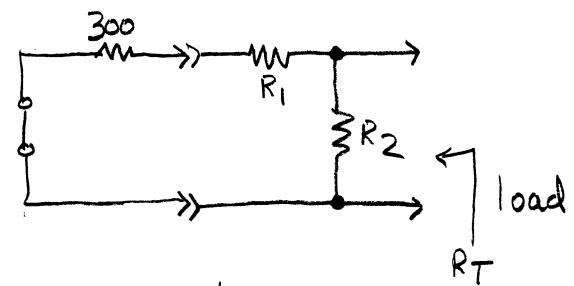Want source to see larger resistance than 50 so this requires a series R.



Want load to see a  $R_T$  smaller than source so there has to be a parallel resistance.

Design  $R_1 + \frac{50 R_2}{R_2 + 50} = 300$


$\frac{(R_1 + 300) R_2}{R_1 + 300 + R_2} = 50$

Non-linear equations with solutions  $R_1 = 273.9$  and  $R_2 = 54.8 \Omega$ .

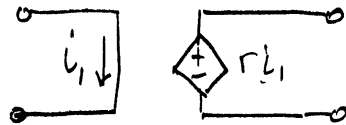
#### 4.1 Linear Dependent Sources

- basis of the operational amplifier
- basis of feedback control


There are four basic types — these are all linear



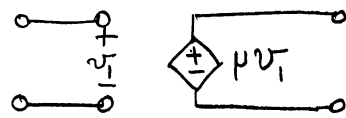
current controlled voltage source  
 $r$  has units of ohms  
 transresistance



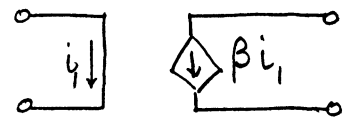voltage controlled voltage source  
 $\mu$  is voltage gain



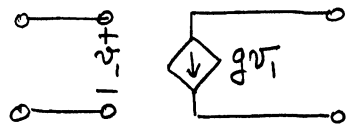current controlled current source  
 $\beta$  is current gain



voltage controlled current source  
 $g$  has units of siemens  
 transconductance

1. dependent sources are not in catalogs
2. can not be turned on/off individually — always a source and a controlling voltage/current