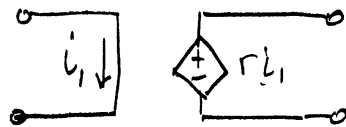



#### 4.1 Linear Dependent Sources

- basis of the operational amplifier
- basis of feedback control


There are four basic types — these are all linear



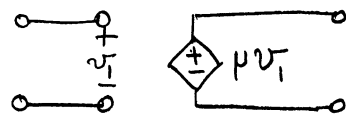
current controlled voltage source  
 $r$  has units of ohms  
 transresistance



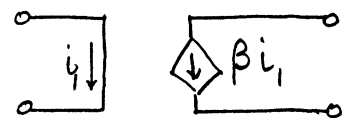voltage controlled voltage source  
 $\mu$  is voltage gain



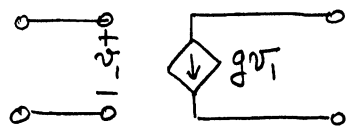
current controlled current source  
 $\beta$  is current gain



voltage controlled current source  
 $g$  has units of siemens  
 transconductance

1. dependent sources are not in catalogs
2. can not be turned on/off individually — always a source and a controlling voltage/current

Figure 4-4

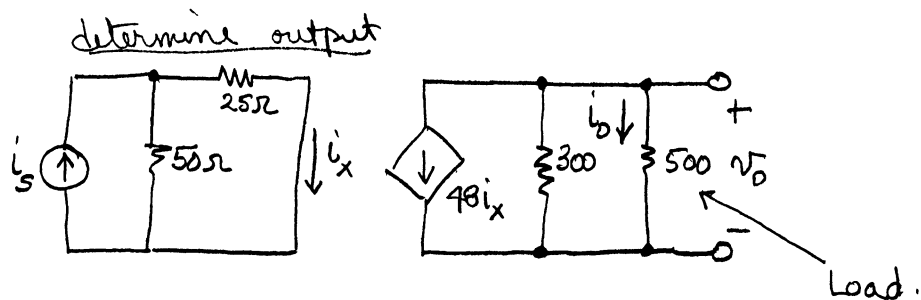

$$i_x = \frac{50}{50+25} i_s = \frac{2}{3} i_s$$


$$v_o = -48 i_x \frac{(300)(500)}{(300+500)} = -48 \left( \frac{2}{3} i_s \right) (1875) = -6000 i_s$$

- ① can amplify very small currents
- ② signal is inverted. This is common in many amplifiers.

$$i_o = \frac{v_o}{R_L} = \frac{-6000 i_s}{500} = -12 i_s$$

$$P_o = v_o i_o = (-6000 i_s)(-12 i_s) = 72,000 i_s^2$$


Exercise 4-1 determine output

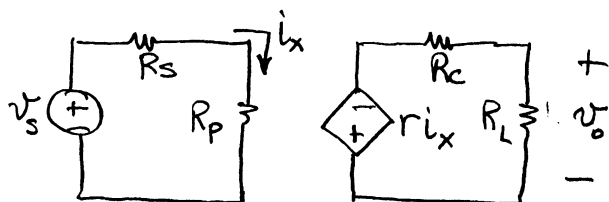

$$i_x = \frac{v_s}{R_s + R_p}$$

$$v_o = \left( \frac{R_L}{R_L + R_c} \right) (-r i_x) = \left( \frac{R_L}{R_L + R_c} \right) \left( -\frac{r v_s}{R_s + R_p} \right)$$

Fig. 4-6

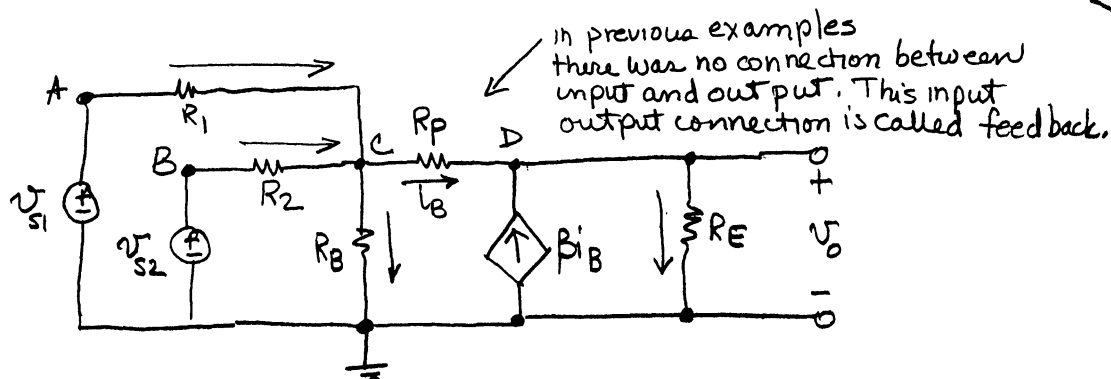

$v_A, v_B$  are known  
find  $v_C, v_D$  using KCL

Procedure: solve without dependent source being explicit, then add control relationship

@ C  $\sum i = 0$  + in

$$\frac{v_{S1} - v_C}{R_1} + \frac{v_{S2} - v_C}{R_2} - \frac{v_C}{R_B} - \frac{v_C - v_D}{R_P} = 0$$

@ D

$$\frac{v_C - v_D}{R_P} + \beta i_B - \frac{v_D}{R_E} = 0$$

Don't use  $i_B$  here

$$\left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_B} - \frac{1}{R_P}\right) v_C + \left(\frac{1}{R_P}\right) v_D = \frac{v_{S1}}{R_1} + \frac{v_{S2}}{R_2} \quad (1)$$

$$\left(\frac{1}{R_P}\right) v_C + \left(-\frac{1}{R_P} - \frac{1}{R_E}\right) v_D = -\beta i_B$$

Now use controlling connection  $\frac{v_C - v_D}{R_P} = \beta i_B$

$$\left(\frac{1}{R_P}\right) (v_C) + \left(-\frac{1}{R_P} - \frac{1}{R_E}\right) v_D = -\frac{\beta}{R_P} v_C + \frac{\beta v_D}{R_P}$$


$$\left(\frac{1}{R_P} + \frac{\beta}{R_P}\right) v_C + \left(-\frac{1}{R_P} - \frac{\beta}{R_P} - \frac{1}{R_E}\right) v_D = 0$$

$$\frac{(\beta+1)}{R_P} v_C - \left(\frac{\beta+1}{R_P} + \frac{1}{R_E}\right) v_D = 0 \quad (2)$$

Solve 1 & 2 simultaneously.


MAY WANT TO MENTION CAN'T SUPERIMPOSE.

Figure 4-7

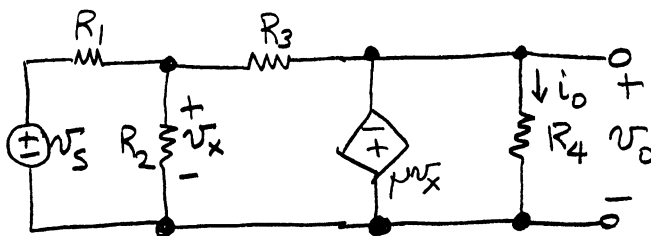

simplified  
OP-AMP

do source transformation

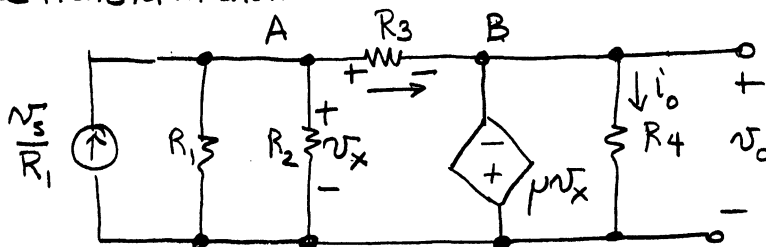

ONLY ONE INDEPENDENT NODE  $\Rightarrow$  ONE EQUATION

$$\sum_{+m} i @ \quad +\frac{v_s}{R_1} - \frac{v_A}{R_1} - \frac{v_A}{R_2} - \frac{v_A - v_B}{R_3} = 0$$

control constraint  $v_A = v_x ; v_B = v_o$

$$-v_o = \mu v_x = \mu v_A \quad v_A = v_x = -\frac{v_o}{\mu}$$

$$\frac{v_s}{R_1} - \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)v_A + \frac{v_B}{R_3} = 0$$

$$\frac{v_s}{R_1} - \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)\left(-\frac{v_o}{\mu}\right) + \frac{v_o}{R_3} = 0$$

$$\frac{v_s}{R_1} = -\left[\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)\frac{1}{\mu} + \frac{1}{R_3}\right]v_o$$

$$\frac{v_s}{v_o} = -\frac{\mu \frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1+\mu}{R_3}}$$

↑ signal inversion

output independent of  $R_4$

consider situation where  $\mu \gg 1$

$$\frac{v_s}{v_o} \approx -\frac{\frac{1}{R_1}}{\frac{1}{R_3}} = -\frac{R_3}{R_1}$$