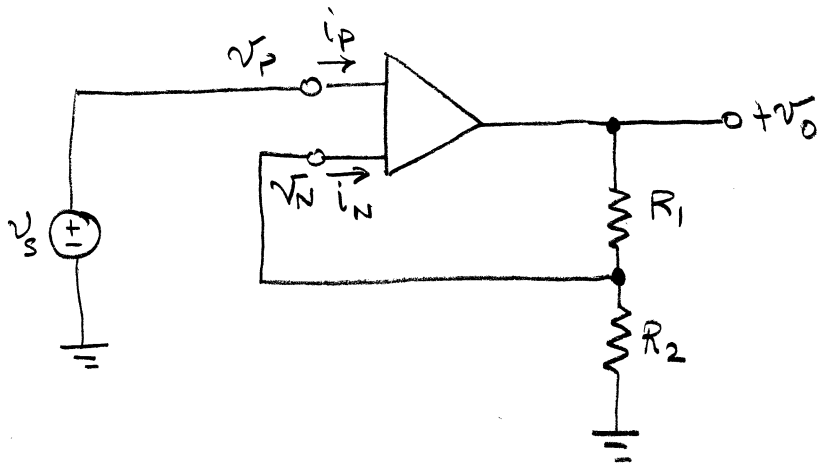


Non-inverting OP-AMP (assume ideal OP AMP)



Since $i_p = i_n = 0$ we can find v_N by voltage division

$$v_N = \frac{R_2}{R_1 + R_2} v_o$$

Since the OP AMP is ideal ($A \rightarrow \infty$) $v_p = v_N$

By inspection $v_p = v_s$


$$\therefore v_s = \frac{R_2}{R_1 + R_2} v_o$$

$$\text{or } v_o = \underbrace{\frac{R_1 + R_2}{R_2}}_{\text{constant of proportionality } K} v_s$$

constant of proportionality K - sometimes called the closed-loop gain

Since v_o is of the same sign as v_s this is called a non-inverting amplifier.

Effects of finite OP AMP gain.

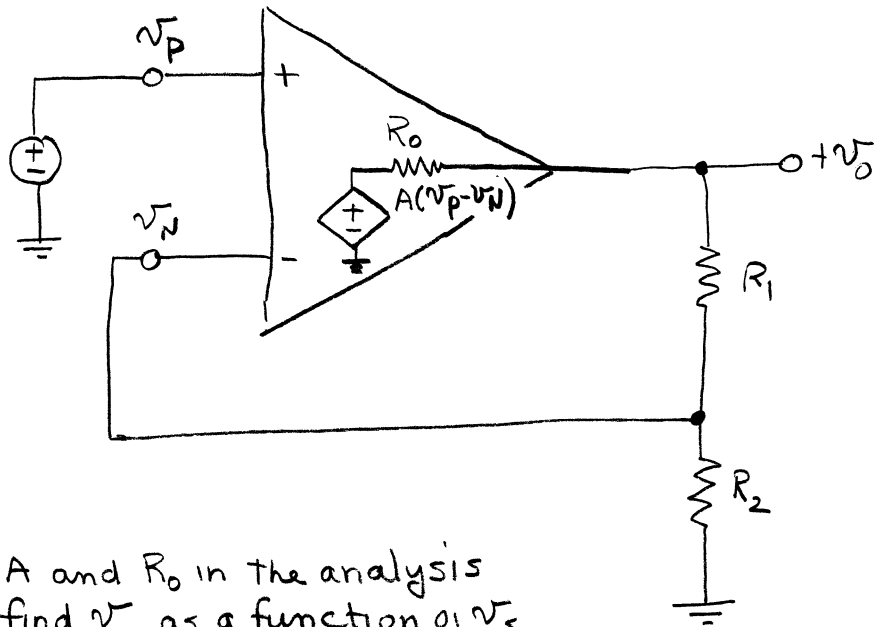

Keep A and R_0 in the analysis and find v_o as a function of v_s

v_o is given by the voltage divider as

$$v_o = \frac{R_1 + R_2}{R_0 + R_1 + R_2} A(v_p - v_N)$$

but $v_p = v_s$

and also using a voltage divider

$$v_N = \frac{R_2}{R_1 + R_2} v_o$$

Substituting

$$v_o = \frac{R_1 + R_2}{R_0 + R_1 + R_2} A \left[v_s - \frac{R_2}{R_1 + R_2} v_o \right]$$

$$v_o + \frac{R_2 A}{R_0 + R_1 + R_2} v_o = \frac{R_1 + R_2}{R_0 + R_1 + R_2} A v_s$$

$$v_o [R_0 + R_1 + R_2 + R_2 A] = (R_1 + R_2) A v_s$$

$$v_o = \frac{A(R_1 + R_2)}{R_0 + R_1 + R_2(1 + A)} v_s$$

As $A \rightarrow \infty$ this reduces to

$$v_o = \frac{R_1 + R_2}{R_2} v_s = K v_s$$


To see the effects of A ignore R_o since $R_o \ll R_1 + R_2$

$$\underline{v_o} \approx \frac{A(R_1 + R_2)}{R_1 + R_2(1+A)} v_s = \frac{R_1 + R_2}{\frac{R_1 + R_2}{A} + R_2} v_s = \frac{\frac{R_1 + R_2}{R_2}}{\frac{R_1 + R_2}{R_2 A} + 1} v_s$$

$$\underline{v_o} = \frac{K}{\frac{K}{A} + 1} v_s$$

Clearly as the open loop gain $A \rightarrow \infty$ the closed loop gain reduces to K , the closed loop gain. This is the effect of feedback.

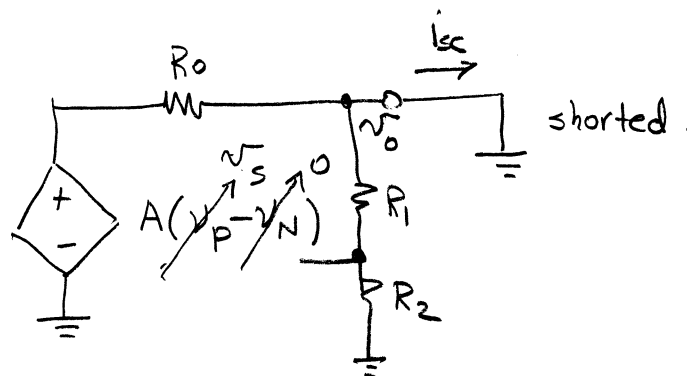Another effect of feedback occurs at the output. Short circuit the output to zero. This forces v_o and v_N to zero, but $v_P = v_s$.



By inspection


$$i_{sc} = \frac{A v_s}{R_o}$$

The Thevenin output resistance is given by

$$R_T = \frac{v_{oc}}{i_{sc}} = \frac{\frac{K}{1 + K/A} v_s}{\frac{A v_s}{R_o}} = \frac{K/A}{1 + K/A} R_o$$

As $A \rightarrow \infty$ $R_T \rightarrow 0 \Omega$

The inverting amplifier

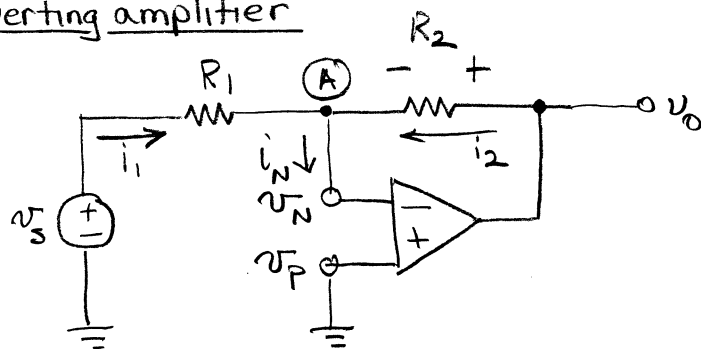

This is probably the most common OP AMP circuit.

For an ideal OP AMP $i_N = 0$ and $v_N = v_P = 0$

Applying KCL at node A.

$$\sum_{\text{in}} i = 0 \quad + \frac{v_s - v_A}{R_1} + \frac{v_o - v_A}{R_2} = 0$$

but $v_A = v_N = 0$.

$$\frac{v_s}{R_1} + \frac{v_o}{R_2} = 0$$

$$v_o = - \frac{R_2}{R_1} v_s$$

For this ideal OP AMP

$$R_{in} = \frac{v_s}{i_1} = \frac{v_s}{\frac{v_s - 0}{R_1}} = R_1$$