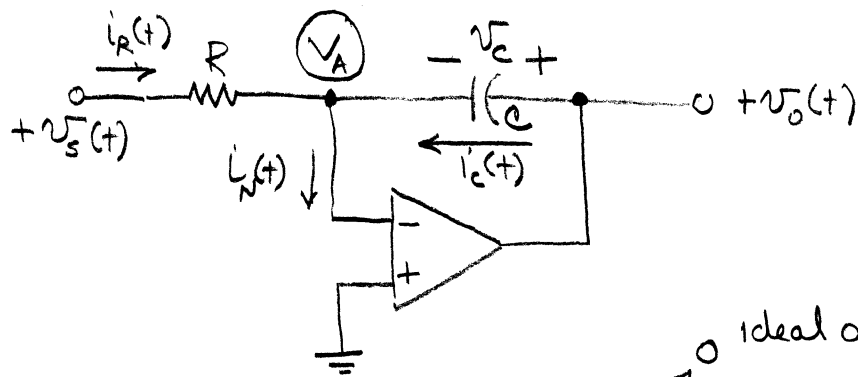


6-3 Dynamic Op-Amp Circuits



KCL @ node A $\sum_{+m} i = 0 \quad i_R(t) - i_N(t) + i_c(t) = 0$

$$i_R(t) = \frac{v_s(t) - v_A(t)}{R}$$

$$i_c(t) = C \frac{dv_c}{dt} = C \frac{d}{dt} [v_o(t) - v_A(t)]$$

since $v_N = v_P = 0$

$$\frac{1}{R} v_s(t) + C \frac{dv_o(t)}{dt} = 0$$

$$dv_o = -\frac{1}{RC} v_s(t) dt$$


$$\int_{v_o(0)}^{v_o(t)} dv_o = -\frac{1}{RC} \int_0^t v_s(x) dx$$

If $v_c(t=0) = 0$ then $v_c(t) = v_o(t)$ so $v_o(t=0) = 0$

$$\therefore v_o(t) = -\frac{1}{RC} \int_0^t v_s(x) dx$$

This is an integrator!

(technically an inverting integrator).

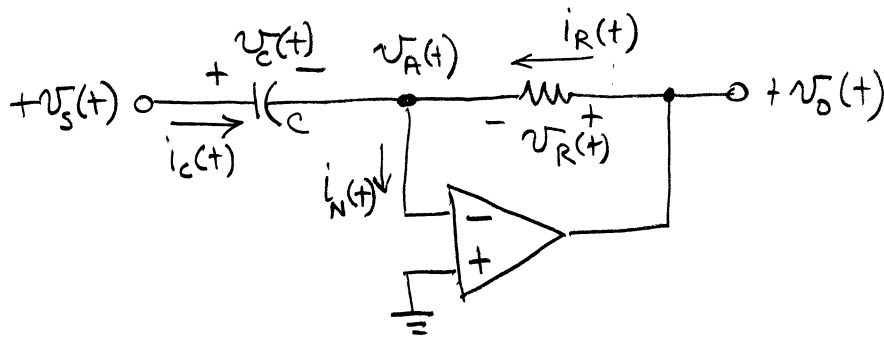

doing KCL @ node A $\sum i = 0$ $i_c(t) - i_N(t) + i_R(t) = 0$

$$i_R(t) = \frac{v_o(t) - v_A(t)}{R}$$


$$i_c(t) = C \frac{dv_c}{dt} = C \frac{d}{dt} [v_s(t) - v_A(t)] = C \frac{dv_s(t)}{dt}$$

$$C \frac{dv_s(t)}{dt} + \frac{1}{R} v_o(t) = 0$$

$$v_o(t) = -\frac{1}{RC} \frac{dv_s(t)}{dt}$$

This is an inverting differentiator.

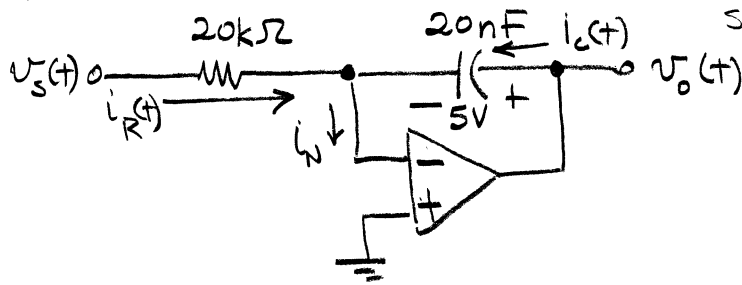Example 6-9 For $v_s(t) = 10u(t)$ find $v_o(t)$. The OPAMP saturates at $v_o = \pm 15$.



$$\sum i = 0 \quad i_R(t) - i_N(t) + i_C(t) = 0$$

$$\frac{v_s(t) - 0}{R} - i_N(t) + C \frac{d}{dt} [v_o(t) - 0]$$

$$\frac{1}{RC} v_s(t) = - \frac{dv_o(t)}{dt}$$

$$dv_o = - \frac{1}{RC} v_s(t) dt$$

$$\int_{v_o(0)}^{v_o(t)} dv_o = - \frac{1}{RC} \int_0^t v_s(t) dt$$

$$v_o(t) - v_o(0) = - \frac{1}{(20 \times 10^3)(20 \times 10^{-9})} \int_0^t 10 dt$$

$$v_o(0) = +5 \text{ volts}$$

$$v_o(t) = 5 - \frac{1}{4 \times 10^{-3}} 10(t-0) = 5 - 25000t$$

This is a negative going ramp. This will reach saturation

when $v_o(t) = -15$,



$$5 - 25000t = -15$$

$$25000t = 15 + 5 = 20$$

$$t = \frac{20}{25000} = 0.8 \times 10^{-3} = 0.8 \text{ msec.}$$

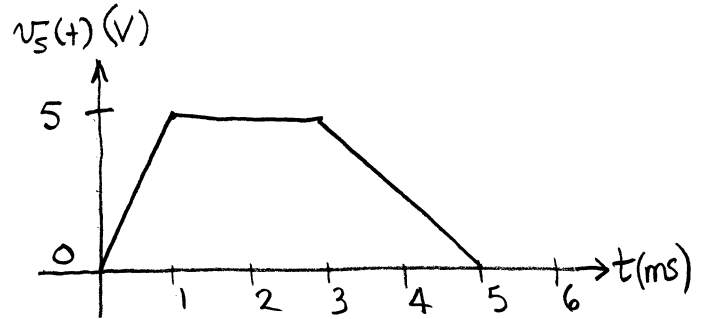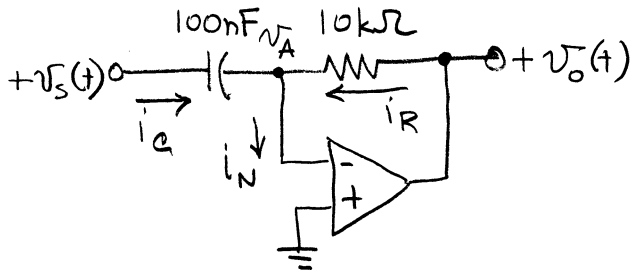Example 6-10

Find the circuit's output to the given trapezoidal waveform. The OP-AMP saturates for $v_o(t) = \pm 15V$.



$$\sum i = 0 \quad +i_c + i_R - i_N = 0$$

$$C \frac{d}{dt} [v_s - v_A] + \frac{1}{R} [v_o - v_A] = 0$$

$$RC \frac{dv_s}{dt} + v_o = 0$$

$$v_o(t) = -RC \frac{dv_s}{dt}$$

$$= -(10^4)(10^2 \times 10^{-9}) \frac{dv_s}{dt}$$

$$= -\frac{1}{1000} \frac{dv_s}{dt}$$

