

Example 8-2

(a) Construct the phasors representing the following signals

$$i_A(t) = 5 \cos(377t + 50^\circ)$$

$$i_B(t) = 5 \cos(377t + 170^\circ)$$

$$i_C(t) = 5 \cos(377t - 70^\circ)$$

$$\underline{I}_A = 5 e^{j50^\circ} = 5 (\cos 50^\circ + j \sin 50^\circ) = 3.214 + j 3.830$$

$$\underline{I}_B = 5 e^{j170^\circ} = 5 (\cos 170^\circ + j \sin 170^\circ) = -4.924 + j 0.868$$

$$\underline{I}_C = 5 e^{-j70^\circ} = 5 (\cos(-70^\circ) + j \sin(-70^\circ)) = 1.710 - j 4.698$$

(b) Use the additive property of phasors and the phasors found in (a) to find the sum of these waveforms.

$$\underline{I} = \underline{I}_A + \underline{I}_B + \underline{I}_C = (3.214 - 4.924 + 1.710) + j(3.830 + 0.868 - 4.698)$$

$$\underline{I} = 0 + j 0$$

Example 8-3

Use the derivative property of phasors to find the time derivative of $v(t) = 15 \cos(200t - 30^\circ)$

$$v(t) = 15 \cos(200t - 30^\circ)$$

$$\underline{V} = 15 e^{-j30^\circ}$$

$$\underline{V}' = (j200) 15 e^{-j30^\circ} = j300 e^{-j30^\circ} = 300 e^{-j30^\circ} e^{j90^\circ}$$

$$\underline{V}' = 300 e^{j60^\circ}$$

$$\frac{dv}{dt} = 300 \cos(200t + 60^\circ)$$

Example 8-4

(a) Convert the following phasors into sinusoidal waveforms.

$$\underline{V}_1 = 20 + j20 \quad \omega = 500$$

convert to polar $\underline{V}_1 = 28.28 \angle 45^\circ$

$$v_1(t) = 28.28 \cos(500t + 45^\circ)$$

$$\underline{V}_2 = 10\sqrt{2} e^{-j45^\circ} \quad \omega = 500$$

$$v_2(t) = 14.14 \cos(500t - 45^\circ)$$

(b) Use phasor addition to find the sinusoidal waveform

$$v_3(t) = v_1(t) + v_2(t)$$

$$\underline{V}_3 = (20 + j20) + (10.0 - j10.0)$$

$$\underline{V}_3 = 30 + j10 = 31.62 \angle 18.44^\circ$$

$$v_3(t) = 31.62 \cos(500t + 18.4^\circ)$$

8-2 Phasor circuit analysis

Connection constraints in phasor form

KVL: The algebraic sum of phasor voltages around a loop is zero.

KCL: The algebraic sum of phasor currents at a node is zero.

Device constraints in phasor form

Resistor: $v_R(t) = R i_R(t)$

$$\underline{V}_R = R \underline{I}_R$$

Inductor: $v_L(t) = L \frac{di_L(t)}{dt}$

$$\underline{V}_L = L j\omega \underline{I}_L$$

used derivative property

$$\underline{V}_L = j\omega L \underline{I}_L$$

Capacitor $i_C(t) = C \frac{dv_C(t)}{dt}$

$$\underline{I}_C = C j\omega \underline{V}_C$$

used derivative property

$$\underline{V}_C = \frac{1}{j\omega C} \underline{I}_C$$

The Impedance Concept

All of the above relationships are of the form $\underline{V} = Z \underline{I}$

This is analogous to Ohm's Law where Z is defined to be the impedance.


For resistors $Z_R = R$

For inductors: $Z_L = j\omega L$

For capacitors: $Z_C = \frac{1}{j\omega C}$

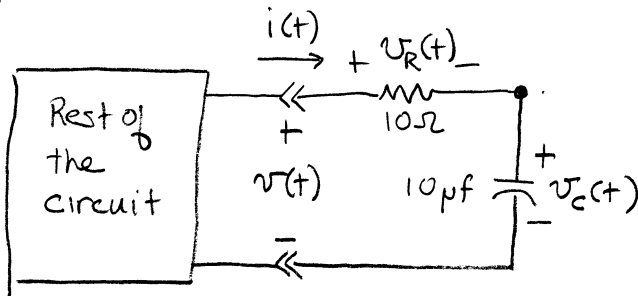Example 8-5

The circuit shown below is operating in the sinusoidal steady-state with $i(t) = 4\cos(5000t)$. Find the steady-state voltage.



You start the problem by finding the impedances of the individual components.

$$Z_R = R = 10\Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(5000)(10 \times 10^{-6})} = -j20$$

↑ this comes from $\cos(5000t)$

Since R and C are in series the same current flows through each.

$$\underline{I} = 4\angle 0^\circ = 4 + j0$$

$$\underline{V}_R = Z_R \underline{I} = (10)(4 + j0) = 40 + j0$$

$$\underline{V}_C = Z_C \underline{I} = (-j20)(4 + j0) = 0 - j80$$

Applying KVL gives

$$-\underline{V} + \underline{V}_R + \underline{V}_C = 0$$

$$\underline{V} = \underline{V}_R + \underline{V}_C = (40 + j0) + (0 - j80) = 40 - j80 = 89.44\angle -63.4^\circ$$

$$\therefore v(t) = 89.4\cos(5000t - 63.4^\circ)$$

8-3 Basic Circuit Analysis with Phasors

- STEP 1: Transform the circuit into the phasor domain by representing input and response sinusoids as phasors and the passive circuit elements by their impedances.
- STEP 2: Use standard algebraic circuit analysis techniques to the phasor domain circuit to solve for the desired phasor responses.
- STEP 3: Inverse transform the phasor responses back into the time domain.

For N elements connected in series

$$Z_{EQ} = Z_1 + Z_2 + \dots + Z_N$$

$$Z_{EQ} = R + jX$$

\uparrow resistance
 \uparrow reactance + for inductor
 $-$ for capacitor

Since the current is the same for each element connected in a series connection

$$V_k = Z_k \underline{I} = \frac{Z_k}{Z_{EQ}} \underline{I}$$

\uparrow
voltage divider