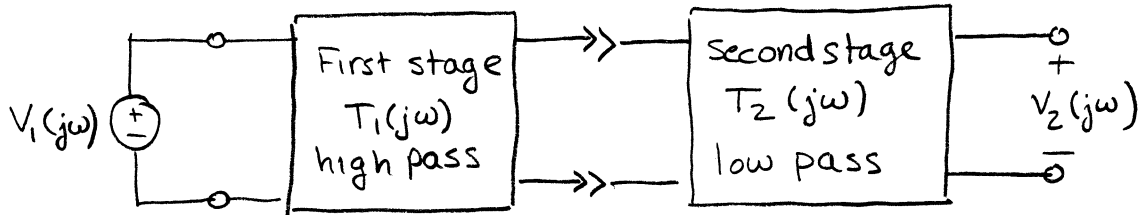


## Bandpass and bandstop responses using first-order circuits


We can construct more complicated frequency responses by cascading filters.



$$T(j\omega) = T_1(j\omega) \times T_2(j\omega)$$

$$= \left( \frac{j\omega K_1}{j\omega + \alpha_1} \right) \left( \frac{K_2}{j\omega + \alpha_2} \right)$$


high pass      low pass

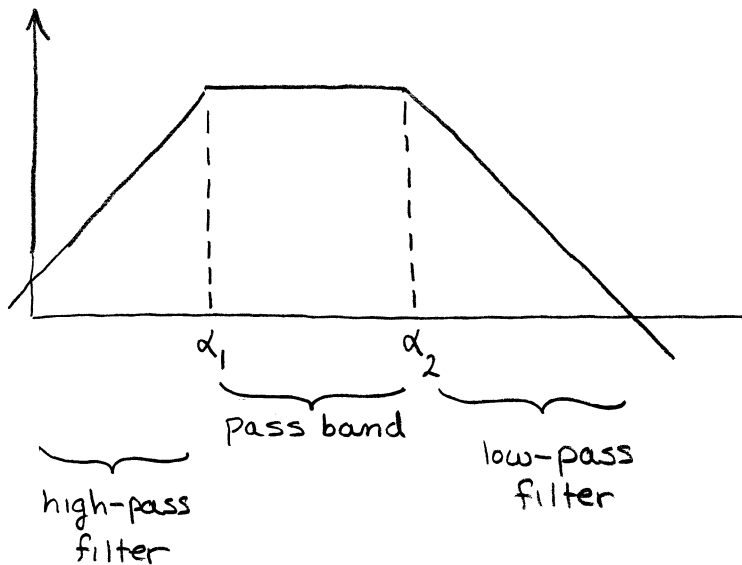

The secret is that the cutoff for the low pass filter must be larger than that for the high-pass filter


$$\alpha_2 > \alpha_1$$

We can also connect filters in parallel.

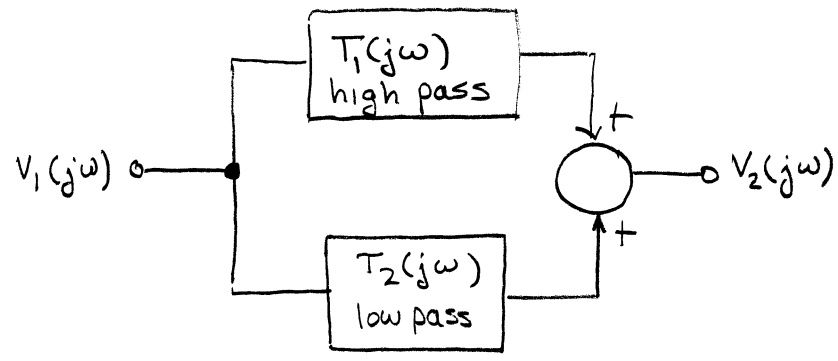

$$T(j\omega) = T_1(j\omega) + T_2(j\omega)$$


high-pass      low-pass

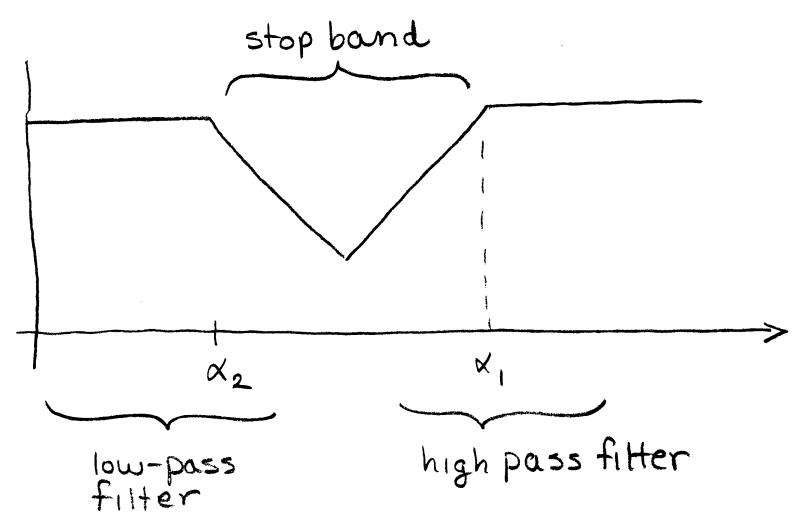

The secret here is that  $\alpha_1 > \alpha_2$  so that both filters reject a range of frequencies — the stop band.

Design Example 12-7

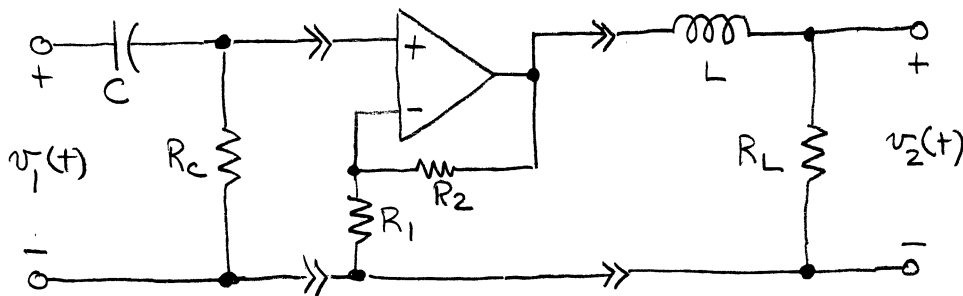Determine the transfer function  $T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$  of the circuit shown below.



This is a cascade collection of (a) a high-pass filter  
 (b) an amplifier (a gain section)  
 (c) a low-pass filter

This can be written as a product of the transfer functions

$$T(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)} = \underbrace{\left( \frac{R_L}{R_L + j\omega L} \right)}_{\text{low-pass}} \underbrace{\left( \frac{R_1 + R_2}{R_1} \right)}_{\text{gain}} \underbrace{\left( \frac{R_c}{R_c + \frac{1}{j\omega C}} \right)}_{\text{high-pass}}$$

$$T(j\omega) = \frac{1}{1 + j\omega \frac{L}{R_L}} \cdot \frac{R_1 + R_2}{R_1} \cdot \frac{j\omega R_c C}{1 + j\omega R_c C}$$

$$20 \log |T(j\omega)| = 20 \log \left| \frac{R_1 + R_2}{R_1} \right| + 20 \log |\omega R_c C| - 20 \log \left| 1 + j\omega \frac{L}{R_L} \right| - 20 \log |1 + \omega R_c C|$$

You really can't plot this without knowing circuit values.

Use

$$R_c C = \frac{1}{40\pi} \quad R_c = 100000$$

$$R_L / L = 40000\pi$$

$$R_1 = 200k \quad R_2 = 90k \quad \Rightarrow \quad \frac{R_1 + R_2}{R_1} = 10$$

$$T(j\omega) = 20 \log_{10} |10| + 20 \log_{10} \left| \frac{\omega}{40\pi} \right| - 20 \log_{10} \left| 1 + j \frac{\omega}{40000\pi} \right| - 20 \log_{10} \left| 1 + j \frac{\omega}{40\pi} \right|$$

$40\pi = 125.7$        $40000\pi = 125663$        $40\pi = 125.7$

