

Chapter 7 - First- and Second- Order Circuits

7-1 RC and RL Circuits

Linear Circuit

use device and connection equations to write differential equation describing the circuit

Differential Equation



solve differential equation

Classical Techniques

use classical techniques for solving D.E. (other techniques include phasors & Laplace transform)

Response Waveform

RC and RL Equations

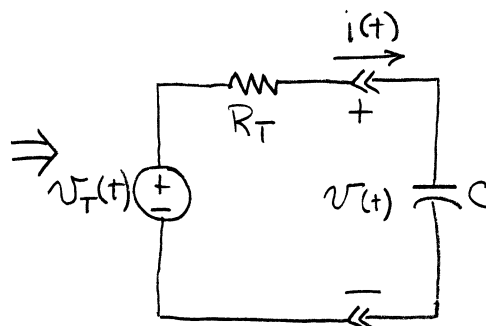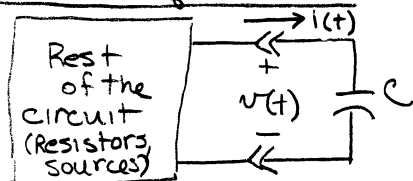

Doing KVL gives

$$-v_T(t) + i(t)R_T + v(t) = 0$$

From the previous chapter the capacitor is described by

$$i(t) = C \frac{dv(t)}{dt}$$

Substituting

$$-v_T(t) + C \frac{dv(t)}{dt} R_T + v(t) = 0$$

Re-arranging


first order linear differential equation with constant coefficients

$$R_T C \frac{dv(t)}{dt} + v(t) = v_T(t)$$

$v_T(t)$ is the input and $v(t)$ is the response

$v(t)$ is called the state variable and determines the amount of energy stored in the RC circuit.

We can do the same with an inductor.

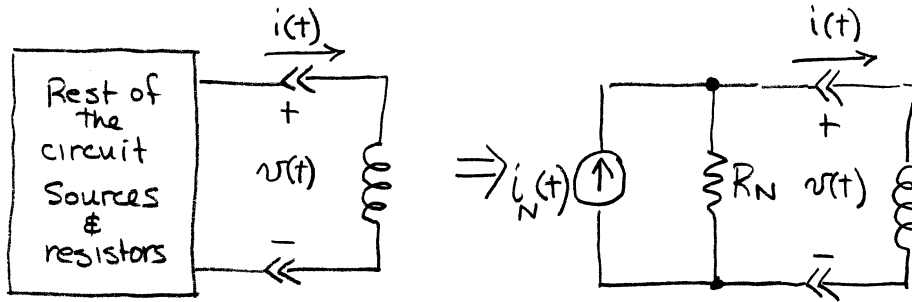

Using KCL at the node gives $\sum_{+in} i = 0$

$$+i_N(t) - \frac{v(t)}{R_N} - i(t) = 0$$

The element constraint is $v(t) = L \frac{di(t)}{dt}$

Substituting

$$i_N(t) - \frac{L}{R_N} \frac{di(t)}{dt} - i(t) = 0$$

Re-arranging

$$\frac{L}{R_N} \frac{di(t)}{dt} + i(t) = i_N(t)$$

- first-order linear differential equation with constant coefficients
- $i_N(t)$ is the forcing function
- $i(t)$ is the state variable as it defines the amount of energy stored in the RL circuit

Any circuit containing a single capacitor or inductor and resistors is a first-order circuit described by a first-order differential equation.

Zero-input response of First-order circuits

The response $v(t)$ for an RC circuit depends upon

1. The input $v_T(t)$
2. The circuit values R_T and C
3. The initial condition, i.e., $v(t=0)$

This can use a response even when $v_T(t) = 0$.

Consider the zero-input response when $v_T(t) = 0$ for $t \geq 0$

$$R_T C \frac{dv(t)}{dt} + v(t) = 0$$

This is a homogeneous differential equation with a solution of the form

$$v(t) = K e^{st}$$

Substituting gives

$$R_T C (K s e^{st}) + K e^{st} = 0$$

$$K e^{st} (R_T C s + 1) = 0$$

This can only be zero if

$$R_T C s + 1 = 0$$

This is called the characteristic equation of the differential equation.

$$\text{Solving gives } s = -\frac{1}{R_T C}$$

The solution $v(t)$ is then

$$v(t) = K e^{-\frac{t}{R_T C}} \quad t \geq 0$$

The constant K comes from the initial condition $v(t=0) = V_0$

$$v(t=0) = K e^0 = K = V_0$$

The final zero-input response is then

$$v(t) = V_0 e^{-\frac{t}{R_T C}} \quad t \geq 0$$

We can do the same for the RL circuit.

$$\frac{L}{R_N} \frac{di(t)}{dt} + i(t) = 0 \quad \text{where we set } i_N(t) = 0, t \geq 0$$

This is also a homogeneous linear differential equation with a solution of the form

$$i(t) = Ke^{st}$$

Substituting gives

$$\frac{L}{R_N} Kse^{st} + Ke^{st} = 0$$

$$Ke^{st} \left(\frac{L}{R_N} s + 1 \right) = 0$$

This requires the characteristic equation

$$\frac{L}{R_N} s + 1 = 0$$

Solving gives $s = -\frac{1}{\frac{L}{R_N}} = -\frac{R_N}{L}$

The solution is

$$i(t) = Ke^{-\frac{R_N}{L}t} \quad t \geq 0$$

The constant K comes from the initial condition $i(t=0) = I_0$


$$i(t=0) = Ke^0 = K = I_0$$

The final zero-input response is then

$$i(t) = I_0 e^{-\frac{R_N}{L}t} \quad t \geq 0$$

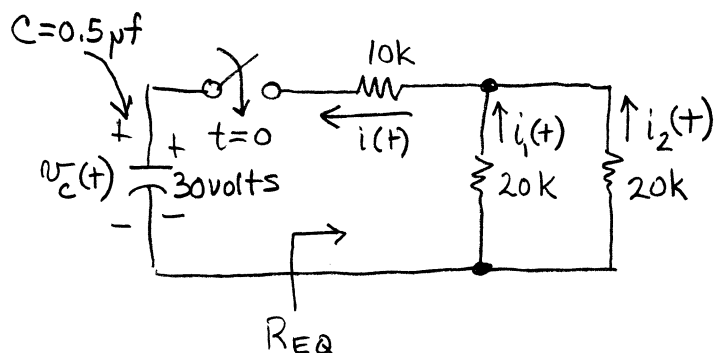
Example 7-1

The switch in the circuit shown below is closed at $t=0$, connecting a capacitor with an initial voltage of 30V to the resistances shown. Find the responses $v_c(t)$, $i(t)$, $i_1(t)$, and $i_2(t)$ for $t \geq 0$.



We first determine the equivalent resistance R_{EQ} as seen by the capacitor,
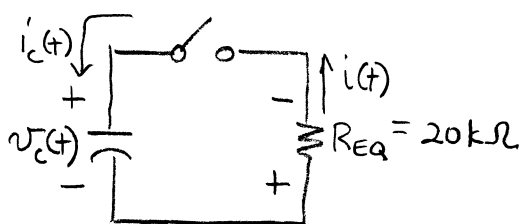
$$R_{EQ} = 10k + 20k \parallel 20k = 10k + 10k = 20k\Omega$$



Doing KVL gives

$$-v_c(t) - i(t)R_{EQ} = 0$$

The element constraint for C is $i_c = C \frac{dv_c}{dt}$

Since we chose $i_c(t)$ to be in the same direction as $i(t)$, $i_c(t) = i(t)$

Substituting,

$$-v_c(t) - C \frac{dv_c(t)}{dt} R_{EQ} = 0$$

$$R_{EQ} C \frac{dv_c(t)}{dt} + v_c(t) = 0$$

The solution is $v_c(t) = K e^{st}$. Substituting gives

$$R_{EQ} C K s e^{st} + K e^{st} = 0$$

$$R_{EQ} C s + 1 = 0$$

$$s = -\frac{1}{R_{EQ} C} = -\frac{1}{(20 \times 10^3)(0.5 \times 10^{-6})} = -100.$$

Using the initial condition $v_c(t=0) = 30$ volts

$$v_c(t=0) = K e^0 = 30 \text{ volts} \Rightarrow K = 30$$

The solution is $v_c(t) = 30 e^{-100t}$, $t \geq 0$

We can now calculate the other circuit values using $v_c(t)$

$$i(t) = i_c(t) = C \frac{dv_c}{dt} = (0.5 \times 10^{-6}) \frac{d}{dt} (30e^{-100t})$$

$$= (0.5 \times 10^{-6})(30)(-100) e^{-100t} = -1.5 \times 10^{-3} e^{-100t}, t \geq 0$$

i_1 and i_2 are given by a current divider.

$$i_1 = \frac{20k}{20k+20k} i(t) = \frac{1}{2} i(t) = -0.75 \times 10^{-3} e^{-100t}, t \geq 0$$

$$i_2 = \frac{20k}{20k+20k} i(t) = \frac{1}{2} i(t) = -0.75 \times 10^{-3} e^{-100t}, t \geq 0$$