
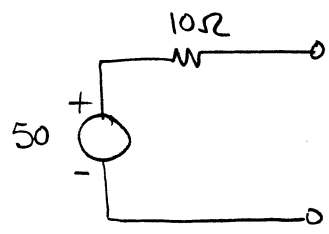


Example 2-12

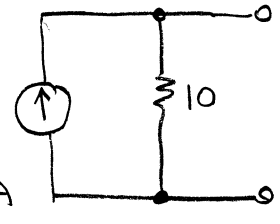


is equivalent to

$$i_s = \frac{V_s}{R}$$
$$i_s = \frac{50}{10} = 5A$$



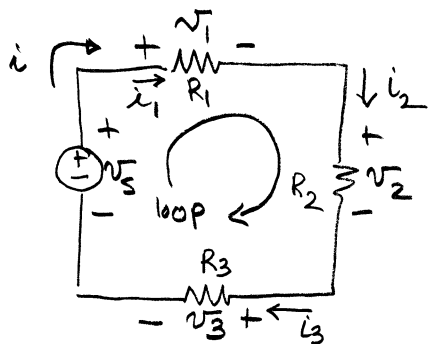2.5 VOLTAGE DIVISION

A voltage divider is a simple, quick way to calculate voltages in a series circuit.



Typical voltage divider circuit

The elements are in series so $i = i_1 = i_2 = i_3$

Apply KVL $\sum v = 0$

$$-v_s + v_1 + v_2 + v_3 = 0$$

$$-v_s + iR_1 + iR_2 + iR_3 = 0$$

$$i = \frac{v_s}{R_1 + R_2 + R_3} \quad (1)$$

Using (1) we can compute all the voltages as

$$v_1 = iR_1 = \frac{R_1}{R_1 + R_2 + R_3} v_s$$


$$v_2 = iR_2 = \frac{R_2}{R_1 + R_2 + R_3} v_s$$

$$v_3 = iR_3 = \frac{R_3}{R_1 + R_2 + R_3} v_s$$

In a voltage divider

$$v_k = \frac{R_k}{\sum R_{\text{series}}} v_s$$

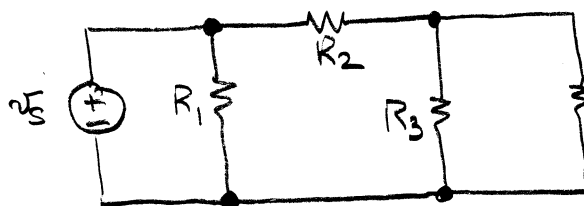
NOTE: There cannot be any nodes from which current is drawn out of the series circuit.



This is NOT a series circuit.


Example 2-15

Determine v_o .

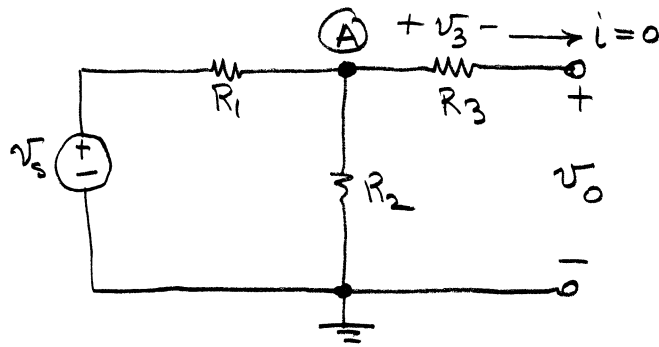

This is a tricky circuit. There is nothing connected to the output so there is no current thru R_3 . From ohm's Law
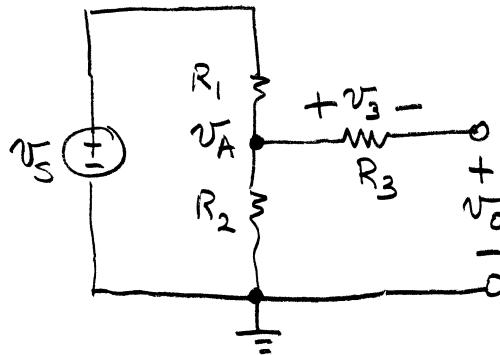
$$v_3 = iR_3 = 0 \quad \text{so} \quad v_A = v_o.$$




Redrawing the circuit we clearly see that this is a simple voltage divider as long as there is no current thru R_3 .

Using the voltage divider rule
$$v_A = \frac{R_2}{R_1 + R_2} v_s$$

The output is then
$$v_o = v_A$$

CURRENT DIVISION

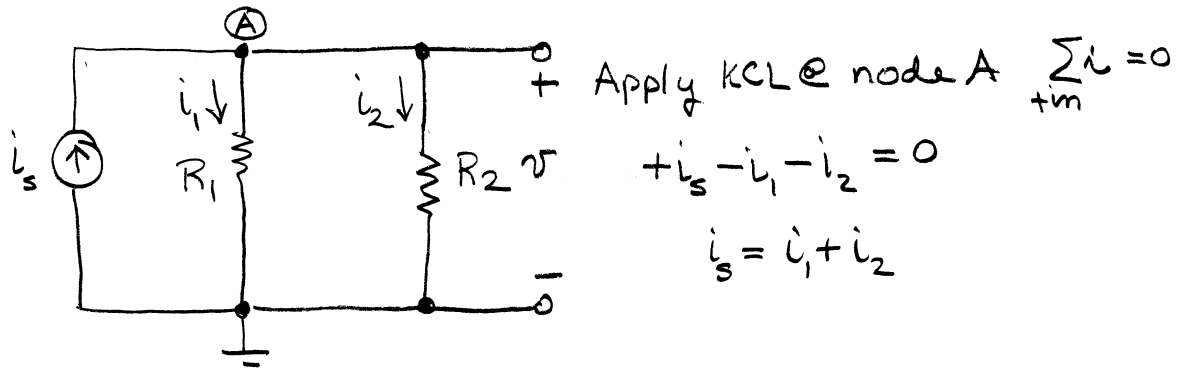Current division is a simple, quick way to calculate currents in a parallel circuit.



Since this is a parallel circuit we have the voltage v across R_1 , R_2 and the current source.

Using Ohm's Law $i_1 = \frac{v}{R_1}$ and $i_2 = \frac{v}{R_2}$

$$i_s = \frac{v}{R_1} + \frac{v}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) v = \frac{R_1 + R_2}{R_1 R_2} v$$

Solving for v

$$v = \frac{R_1 R_2}{R_1 + R_2} i_s$$

Solving for i_1 and i_2 gives

$$i_1 = \frac{v}{R_1} = \frac{R_1 R_2}{R_1 + R_2} i_s \frac{1}{R_1} = \frac{R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{v}{R_2} = \frac{R_1 R_2}{R_1 + R_2} i_s \frac{1}{R_2} = \frac{R_1}{R_1 + R_2} i_s$$