
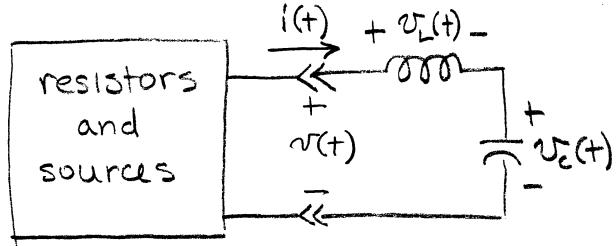

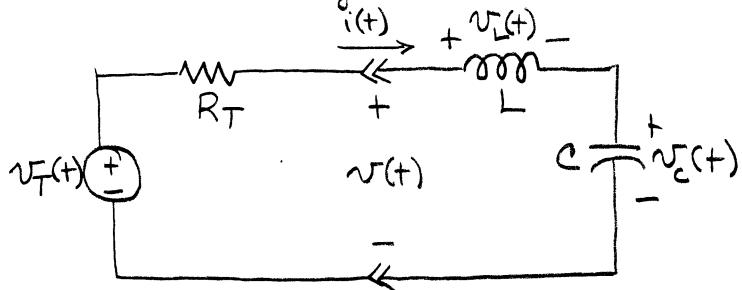
## 7-5 The Series RLC circuit

Second order circuits contain two energy storage elements that cannot be replaced by a single equivalent element.



Thevenize the circuit to get



This is known as a series RLC circuit.

On the left hand side use KVL to get  $-v_T(t) + i(t)R_T + v(t) = 0$

On the right hand side use KVL to get  $-v(t) + v_L(t) + v_C(t) = 0$

The i-v characteristics of the inductor and capacitor give

$$v_L = L \frac{di}{dt}$$

$$i = C \frac{dv_C}{dt}$$

These are four equations in four unknowns ( $i, v, v_C, v_L$ )

To get a single equation in  $v_C(t)$

$$v_L(t) + v_C(t) - v_T(t) + i(t)R_T = 0$$

$$v_L(t) + v_C(t) + R_T C \frac{dv_C}{dt} = v_T(t)$$

substituting  $L \frac{di}{dt} = L \frac{d}{dt} \left( C \frac{dv_C}{dt} \right) = LC \frac{d^2v_C}{dt^2}$

$$LC \frac{d^2v_C}{dt^2} + R_T C \frac{dv_C}{dt} + v_C = v_T(t)$$

This is a second-order linear differential equation with constant coefficients.

The initial conditions are

$$v_c(0) = V_0$$

$$\frac{dv_c(0)}{dt} = \frac{1}{C} i(0) = \frac{I_0}{C}$$

### Zero-input response

With  $v_T = 0$  the differential equation for  $v_c$  becomes

$$LC \frac{d^2 v_c}{dt^2} + R_T C \frac{dv_c}{dt} + v_c = 0 \quad (1)$$

We could also solve the circuit in terms of the inductor current  $i$ .

$$v_L(t) + v_c(t) - v_T(t) + i(t) R_T = 0$$

$$v_L = L \frac{di}{dt}$$

$$v_L = \frac{1}{C} \int_0^t i(x) dx + v_c(0)$$

$$L \frac{di}{dt} + \frac{1}{C} \int_0^t i(x) dx + v_c(0) + i R_T = 0$$

Differentiate once more to get

$$LC \frac{d^2 i(t)}{dt^2} + R_T C \frac{di(t)}{dt} + i(t) = 0 \quad (2)$$

Equations (1) and (2) are identical in form so we will analyze just (1)

## Example 7-14

A series RLC circuit has  $C = 0.25 \mu F$  and  $L = 1 H$ . Find the roots of the characteristic equation for  $R_T = 8.5k$ ,  $4k$  and  $1k\Omega$ .

The characteristic equation for a series RLC is

$$LCs^2 + R_T Cs + 1 = 0$$

For  $R_T = 8.5k$

$$LC = (1)(0.25 \times 10^{-6}) = 0.25 \times 10^{-6}$$

$$R_T C = (8.5 \times 10^3)(0.25 \times 10^{-6}) = 2.125 \times 10^{-3}$$

$$s_1, s_2 = \frac{-2.125 \times 10^{-3} \pm \sqrt{(2.125 \times 10^{-3})^2 - 4(0.25 \times 10^{-6})(1)}}{2(0.25 \times 10^{-6})}$$

$$s_1, s_2 = \frac{-2.125 \times 10^{-3} \pm 1.875 \times 10^{-3}}{0.5 \times 10^{-6}} = -4250 \pm 3750$$

$$s_1 = -500 \quad s_2 = -8000$$

For  $R_T = 4k$

$$R_T C = (4 \times 10^3)(0.25 \times 10^{-6}) = 10^{-3}$$

$$s_1, s_2 = \frac{-10^{-3} \pm \sqrt{(10^{-3})^2 - 4(0.25 \times 10^{-6})(1)}}{2(0.25 \times 10^{-6})} = \frac{-10^{-3} \pm \sqrt{10^{-6} - 10^{-6}}}{2(0.25 \times 10^{-6})}$$

$$s_1, s_2 = -2000$$

For  $R_T = 1k$

$$R_T C = (1 \times 10^3)(0.25 \times 10^{-6}) = 0.25 \times 10^{-3}$$

$$s_1, s_2 = \frac{-0.25 \times 10^{-3} \pm \sqrt{(0.25 \times 10^{-3})^2 - 4(0.25 \times 10^{-6})(1)}}{2(0.25 \times 10^{-6})}$$

$$s_1, s_2 = \frac{-0.25 \times 10^{-3} \pm \sqrt{6.25 \times 10^{-8} - 1 \times 10^{-6}}}{0.5 \times 10^{-6}}$$

$$s_1, s_2 = \frac{-0.25 \times 10^{-3} \pm \sqrt{-9.375 \times 10^{-7}}}{0.5 \times 10^{-6}} = \frac{-0.25 \times 10^{-3} \pm j9.682 \times 10^{-4}}{0.5 \times 10^{-6}}$$

$$s_1, s_2 = -500 \pm j1936.5$$

Based upon previous experience we try a solution of the form  $v_C = Ke^{st}$  to get the characteristic equation

$$LC \cdot Ks^2 e^{st} + R_T C \cdot Ks e^{st} + Ks e^{st} = 0$$

$$Ke^{st}(LCs^2 + R_T Cs + 1) = 0$$

This equation has two roots. Using the quadratic formula

$$s_1, s_2 = \frac{-R_T C \pm \sqrt{(R_T C)^2 - 4LC}}{2LC}$$

This has three cases depending upon the square root.

CASE A:  $(R_T C)^2 - 4LC > 0$  two real, unequal roots  
 $s_1 = -\alpha_1, s_2 = -\alpha_2$

CASE B:  $(R_T C)^2 - 4LC = 0$  two equal, real roots  
 $s_1 = s_2 = -\alpha$

CASE C:  $(R_T C)^2 - 4LC < 0$  two complex conjugate roots  
 $s_1 = -\alpha - j\beta$  and  $s_2 = -\alpha + j\beta$

CASE A:  $s_1 = -\alpha_1, s_2 = -\alpha_2$

$$v_c(t) = \frac{-\alpha_2 V_0 - I_0/c}{-\alpha_2 + \alpha_1} e^{-\alpha_1 t} + \frac{+\alpha_1 V_0 + I_0/c}{-\alpha_2 + \alpha_1} e^{-\alpha_2 t}$$

$$v_c(t) = \frac{\alpha_2 V_0 + I_0/c}{\alpha_2 - \alpha_1} e^{-\alpha_1 t} + \frac{-\alpha_1 V_0 - I_0/c}{\alpha_2 - \alpha_1} e^{-\alpha_2 t}$$

This is a sum of two exponential functions.  
See Example 5-14.

CASE B:  $s_1 = s_2 = -\alpha$

The solution becomes

$$v_c(t) = \frac{-\alpha V_0 - I_0/c}{-\alpha + \alpha} e^{-\alpha t} + \frac{-\alpha V_0 + I_0/c}{-\alpha + \alpha} e^{-\alpha t}$$

The denominators go to zero but the numerator also goes to zero.

Let  $s_1 = -\alpha$  and  $s_2 = -\alpha + x$  and take limit as  $x \rightarrow 0$

$$v_c(t) = \frac{(-\alpha + x)V_0 - I_0/c}{-\alpha + x + \alpha} e^{-\alpha t} + \frac{+\alpha V_0 + I_0/c}{-\alpha + x + \alpha} e^{(-\alpha+x)t}$$

$$v_c(t) = e^{-\alpha t} \left[ \frac{\checkmark \quad \checkmark \quad \checkmark}{-\alpha V_0 + x V_0 - \frac{I_0/c}{c} + \alpha V_0 e^{xt} + \frac{I_0/c}{c} e^{xt}} \right]$$

$$v_c(t) = e^{-\alpha t} \left[ V_0 - \frac{\alpha V_0}{x} - \frac{I_0/c}{x} + \frac{\alpha V_0}{x} e^{xt} + \frac{I_0/c}{x} e^{xt} \right]$$

$$v_c(t) = e^{-\alpha t} \left[ V_0 - (\alpha V_0 + \frac{I_0/c}{c}) \frac{1}{x} + (\alpha V_0 + \frac{I_0/c}{c}) \frac{e^{xt}}{x} \right]$$

$$v_c(t) = e^{-\alpha t} \left[ V_0 - \left( \alpha V_0 + \frac{I_0/c}{c} \right) \frac{1 - e^{xt}}{x} \right]$$

## Zero-input response

There are two roots to the characteristic equation which correspond to two solutions.

The general solution for zero-input is the sum of these solutions

$$v_c(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

The initial conditions are

$$v_c(0) = V_0$$

$$\frac{dv_c(0)}{dt} = \frac{1}{C} i(0) = \frac{I_0}{C}$$

$$\text{For } t=0 \quad v_c(0) = K_1 e^0 + K_2 e^0 = K_1 + K_2 = V_0$$

To use the second initial condition we need to differentiate our expression for  $v_c(t)$

$$\frac{dv_c(t)}{dt} = K_1 s_1 e^{s_1 t} + K_2 s_2 e^{s_2 t}$$

$$\frac{dv_c(0)}{dt} = K_1 s_1 + K_2 s_2 = \frac{I_0}{C}$$

$$\begin{aligned} s_1 K_1 + s_2 K_2 &= \frac{I_0}{C} \\ K_1 + K_2 &= V_0 \end{aligned}$$

$$s_1 K_1 + s_2 K_2 = \frac{I_0}{C}$$

$$s_1 K_1 + s_1 K_2 = s_1 V_0$$

$$(s_2 - s_1) K_2 = \frac{I_0}{C} - s_1 V_0$$

$$K_2 = \frac{-s_1 V_0 + I_0/C}{s_2 - s_1}$$

$$K_1 = V_0 - K_2 = V_0 - \frac{-s_1 V_0 + I_0/C}{s_2 - s_1}$$

$$K_1 = \frac{s_2 V_0 - s_1 V_0 + s_1 V_0 - I_0/C}{s_2 - s_1} = \frac{s_2 V_0 - I_0/C}{s_2 - s_1}$$

This response is different depending upon cases A, B, or C,

The indeterminacy in this equation comes from the second term. We can use L'Hopital's rule to evaluate it

$$\lim_{x \rightarrow 0} \frac{1-e^{xt}}{x} = \lim_{x \rightarrow 0} \underbrace{\left( -te^{xt} \right)}_{\text{take derivatives with respect to } x} = -t$$

take derivatives with respect to  $x$

Substituting this result gives

$$v_c(t) = e^{-\alpha t} \left[ V_0 - (\alpha V_0 + \frac{I_0}{C})(-t) \right]$$

$$v_c(t) = V_0 e^{-\alpha t} + (\alpha V_0 + \frac{I_0}{C}) t e^{-\alpha t} \quad t \geq 0$$

This solution is an exponential and a damped ramp.

CASE C is perhaps the most interesting.

$$s_1 = -\alpha - j\beta \quad s_2 = -\alpha + j\beta$$

Substituting gives

$$v_c(t) = \frac{(-\alpha + j\beta)V_0 - \frac{I_0}{C}}{(-\alpha + j\beta) - (-\alpha - j\beta)} e^{-\alpha t - j\beta t} + \frac{-(-\alpha - j\beta)V_0 + \frac{I_0}{C}}{(-\alpha + j\beta) - (-\alpha - j\beta)} e^{-\alpha t + j\beta t}$$

$$v_c(t) = \frac{-\alpha V_0 + j\beta V_0 - \frac{I_0}{C}}{j2\beta} e^{-\alpha t - j\beta t} + \frac{\alpha V_0 + j\beta V_0 + \frac{I_0}{C}}{j2\beta} e^{-\alpha t + j\beta t}$$

$$v_c(t) = \frac{j\beta V_0 e^{-\alpha t - j\beta t} + j\beta V_0 e^{-\alpha t + j\beta t}}{j2\beta} + \frac{-\alpha V_0 e^{-j\beta t} - \frac{I_0}{C} e^{-j\beta t} + \alpha V_0 e^{j\beta t} + \frac{I_0}{C} e^{j\beta t}}{j2\beta} e^{-\alpha t}$$

$$v_c(t) = V_0 e^{-\alpha t} \left[ \frac{e^{-j\beta t} + e^{+j\beta t}}{2} \right] + \frac{\alpha V_0 + \frac{I_0}{C}}{\beta} e^{-\alpha t} \left[ \frac{e^{j\beta t} - e^{-j\beta t}}{j2} \right]$$

We can use Euler's identity to re-write the expressions in the square brackets.

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$e^{-j\theta} = \cos\theta - j\sin\theta$$

$$\left. \begin{aligned} \cos\theta &= \frac{e^{j\theta} + e^{-j\theta}}{2} \\ \sin\theta &= \frac{e^{j\theta} - e^{-j\theta}}{2j} \end{aligned} \right\} \text{adding and subtracting the above equations gives these useful expressions for the sine and cosine.}$$

We can use these expressions to simplify our solution

$$v_c(t) = V_o e^{-\alpha t} \cos\beta t + \frac{\alpha V_o + I_o/c}{\beta} e^{-\alpha t} \sin\beta t$$

These are two damped sinusoids. The real part of the roots describes the exponential decay, and the imaginary part of the roots defines the frequency of the sinusoidal oscillations.


$s$  - has units of complex frequency

$\alpha$  - has units of neper frequency

$\beta$  - has units of radian frequency
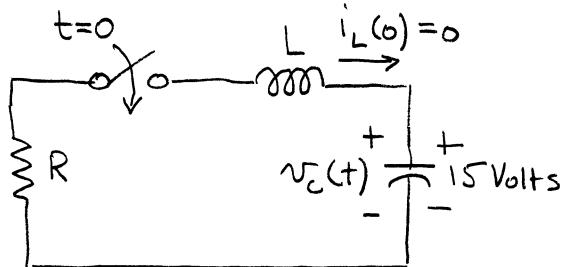
## Example 7-15

The circuit shown below has  $C = 0.25\mu F$  and  $L = 1H$ . The switch has been open for a long time and is closed at  $t=0$ . Find the capacitor voltage for  $t \geq 0$  for (a)  $R_T = 8.5k$ , (b)  $R = 4k$  and (c)  $R = 1k$ . The initial conditions are  $I_0 = 0$  and  $V_0 = 15$ .



SOLUTION:

The roots of the characteristic equation were found in Example 7-14.

$$(a) R_T = 8.5k \quad s_1 = -500 \quad s_2 = -8000$$

$$V_C(t) = K_1 e^{-500t} + K_2 e^{-8000t}$$

$$V_C(0) = K_1 + K_2 = V_0 = 15$$

$$\frac{dV_C(t)}{dt} = \frac{I_0}{C} = K_1(-500)e^{-500t} + K_2(-8000)e^{-8000t}$$

$$\frac{dV_C(0)}{dt} = 0 = -500K_1 - 8000K_2$$

$$K_1 + K_2 = 15$$

$$K_1 + 16K_2 = 0$$

---


$$K_2 - 16K_2 = 15$$

$$K_2 = \frac{15}{-15} = -1$$

$$K_1 + 16(-1) = 0$$

$$K_1 = 16$$

$$V_C(t) = 16e^{-500t} - e^{-8000t} \quad t \geq 0$$

$$(b) R_T = 4k\Omega \quad s_1 = s_2 = -2000.$$

The zero-input solution is an exponential plus an exponentially damped ramp.

$$v_c(t) = K_1 e^{-2000t} + K_2 t e^{-2000t}$$

We now solve for the initial conditions in the same manner as (a),

$$v_c(0) = K_1 = V_0 = 15$$

$$\frac{dv_c(t)}{dt} = K_1(-2000)e^{-2000t} + K_2(-2000)t e^{-2000t} + K_2 e^{-2000t} = \frac{I_0}{C}$$

$$\frac{dv_c(0)}{dt} = -2000 K_1 e^0 + 0 + K_2 e^0 = \frac{0}{C}$$

$$-2000 K_1 + K_2 = 0 \Rightarrow K_2 = 2000 K_1 = 30000$$

$$v_c(t) = 15 e^{-2000t} + 30000 t e^{-2000t}, \quad t \geq 0$$

$$(c) R_T = 1k\Omega \quad s_1 = -500 - j1936.5 \quad s_2 = -500 + j1936.5$$

$$v_c(t) = K_1 e^{-500t} \cos(1936.5t) + K_2 e^{-500t} \sin(1936.5t)$$

$$v_c(0) = K_1 e^0 + K_2 \cdot 0 = 15 \quad \therefore K_1 = 15$$

$$\frac{dv_c(t)}{dt} = K_1(-500)e^{-500t} \cos(1936.5t) + K_1 e^{-500t} (-1936.5) \sin(1936.5t)$$

$$+ K_2(-500) e^{-500t} \sin(1936.5t) + K_2 e^{-500t} (1936.5) \cos(1936.5t)$$


$$\frac{dv_c(0)}{dt} = K_1(-500)e^0 \cdot 1 + K_1 e^0 (-1936.5)(0) + K_2(-500)e^0(0) + K_2 e^0 (1936.5)(1) = 0$$

$$-500 K_1 + 1936.5 K_2 = 0$$

$$K_2 = \frac{500}{1936.5} K_1 = \frac{500}{1936.5} (15) = 3.873$$

$$v_c(t) = 15 e^{-500t} \cos(1936.5t) + 3.873 e^{-500t} \sin(1936.5t) \quad t \geq 0$$

The plots of these are very interesting.

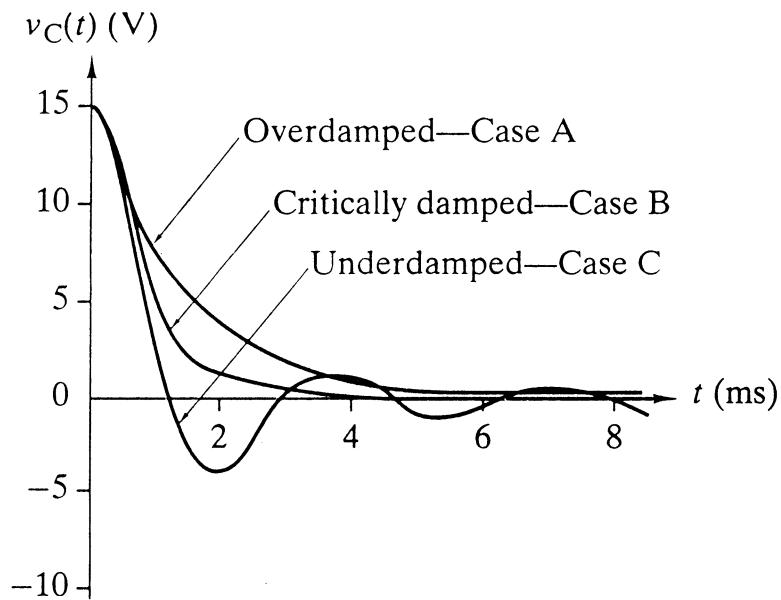

All three cases start at  $V_C(0) = 15$  and all damp out but in different ways.

Example 7-16

79

In a series RLC circuit the zero-input voltage across the  $1\mu F$  capacitor is

$$v_c(t) = 10e^{-1000t} \sin 2000t \quad V \geq 0$$

(a) Find the circuit characteristic equation.

The circuit is underdamped because it has a sine  
By inspection  $\alpha = 1000$ ,  $\beta = 2000$   
the solutions are then

$$\begin{aligned} (s + \alpha + j\beta)(s + \alpha - j\beta) &= (s + 1000 + j2000)(s + 1000 - j2000) \\ &= s^2 + (1000 + j2000 + 1000 - j2000)s + (1000^2 + 2000^2) \\ &= s^2 + 2000s + 5 \times 10^6 = 0 \end{aligned}$$

(b) Find the  $R$  and  $L$ .

The characteristic equation can also be written as

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Since  $C = 1\mu F$  we can solve for  $L$  and  $R$ .

$$\frac{1}{LC} = 5 \times 10^6 \Rightarrow L = \frac{1}{(5 \times 10^6)(1 \times 10^{-6})} = 0.2 H$$

$$\frac{R}{L} = 2000 \Rightarrow R = 2000L = 2000(0.2) = 400 \Omega$$

(c) Find  $i_L(t)$  for  $t \geq 0$

In a series RLC circuit  $i_L(t) = i_c(t)$  and we know  $i_c(t) = C \frac{d}{dt} v_c(t)$

$$i_L(t) = (1 \times 10^{-6}) \left[ (10)(-1000)e^{-1000t} \sin 2000t + 10e^{-1000t} (2000) \cos 2000t \right]$$

$$i_L(t) = 0.01e^{-1000t} \sin 2000t + 0.02e^{-1000t} \cos 2000t$$

(d) Find the initial values of the state variables.

By inspection  $v_c(0) = 0$

$i_L(0) = 0.02$  Amps.