

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 11


11/21/03

Name (Section): Solutions

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK

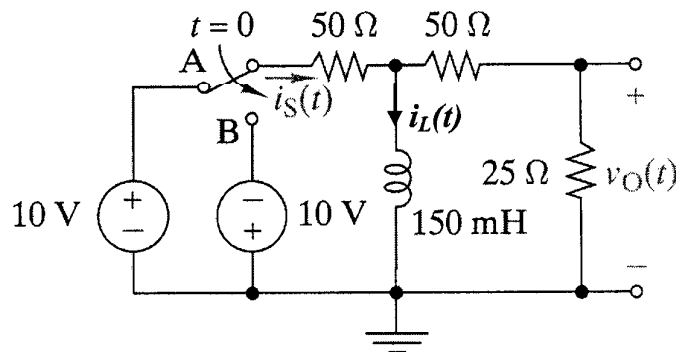Problem 1 (10 points)

In the circuit shown here, the switch has been in position A for a long time, and is set to position B at $t = 0$. Find the initial and final values of the state variable i_L , the time constant T_C , and write the expression for $i_L(t)$ for $t > 0$. Numerical values are required. Complete the table.



VARIABLE	VALUE / EXPRESSION
Initial value $i_L(t = 0)$	0.2 A
Final value $i_L(t \rightarrow \infty)$	-0.2 A
Time constant T_C , for $t > 0$	5 m
Inductor current $i_L(t)$, $t > 0$	$0.4 e^{-t/5\text{m}} - 0.2$

(over)

Problem 2 (10 points)

Write the following phasors as sinusoidal waveforms, i.e. in the form $A \cos(\omega t + \phi)$. Numerical values are required for A , ω , and ϕ . Complete the table.

PHASOR	COS()
$20 + j20, \omega = 500 \text{ rad/sec}$	$20\sqrt{2} \cos(500t + 45^\circ)$
$10\sqrt{2} \angle -45^\circ, \omega = 500 \text{ rad/sec}$	$10\sqrt{2} \cos(500t - 45^\circ)$

(over)