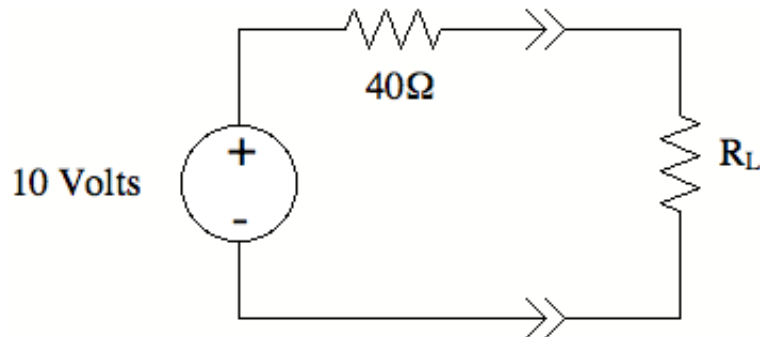


**CASE WESTERN RESERVE UNIVERSITY**  
Case School of Engineering  
Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

**Quiz No. 6**

**2/27/04**


**PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS**



**Problem 1** (10 points)

- (a) The power dissipated by  $R_L$  will be a maximum for  $R_L =$  \_\_\_\_\_  $\Omega$
- (b) The power dissipated by  $R_L$  for  $R_L = 10\Omega$  is \_\_\_\_\_ watts.
- (c) If  $R_L$  increases from  $10\Omega$  to  $25\Omega$ , the power dissipated by it will (circle one)
  - (i) increase
  - (ii) remain the same
  - (iii) decrease.

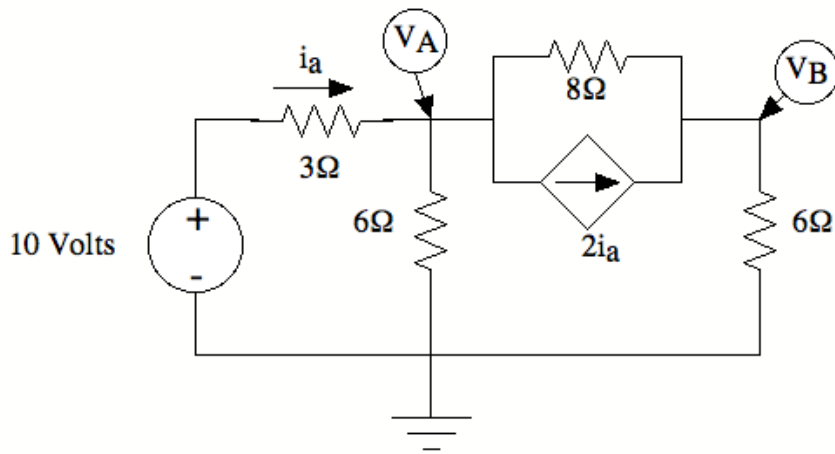**Problem 2** (10 points)  
 Consider this active circuit.



**a)** Write node analysis equations (KCL) for nodes A and B.

Node	Node-Voltage Equation		
<b>A</b>	$\cdot V_A$	$+$	$\cdot V_B =$
<b>B</b>	$\cdot V_A$	$+$	$\cdot V_B =$

**b)** Find the node voltages for the above circuit values.

$V_A$		$V_B$	
-------	--	-------	--