Name :	Section:	CWRU e-mail:
--------	----------	--------------

## CASE WESTERN RESERVE UNIVERSITY Case School of Engineering Department of Electrical Engineering and Computer Science ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 10

4/02/04

## PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE BE SURE TO STATE ALL ASSUMPTIONS

Problem 1 Power and Energy in Inductors/Capacitors (10 points)

The figure below shows the voltage across a 0.1  $\mu\text{F}$  capacitor.



(a) Sketch the current, power and energy as a function of time. Be sure to indicate the minimum/maximum values of these waveforms.

$$\begin{split} &i_c(t) = C \frac{dV_c(t)}{dt} = 0.1 \mu F \cdot \frac{dV_c(t)}{dt} \\ &\text{From 0 ms~1 ms, } i_c(t) = 0 \text{;} \\ &\text{From 1 ms~3 ms, } i_c(t) = C \frac{dV_c(t)}{dt} = 0.1 \mu F \cdot \frac{100V}{2ms} = 5mA \text{;} \\ &\text{From 3 ms~5 ms, } i_c(t) = C \frac{dV_c(t)}{dt} = 0.1 \mu F \cdot \frac{-200V}{2ms} = -10mA \text{;} \\ &\text{From 5 ms~6 ms, } i_c(t) = C \frac{dV_c(t)}{dt} = 0.1 \mu F \cdot \frac{100V}{2ms} = 10mA \text{;} \\ &\text{Base on these calculated values, we can get the plot of } i_c \text{ as follows.} \end{split}$$



## (3 points);

Using  $p_c(t) = i_c(t) \cdot V_c(t)$ , we can get the values of powers at different times. At t= 1 ms,  $p_c(t) = i_c(t) \cdot V_c(t) = 0W$ ; At t= 3- ms,  $p_c(t) = i_c(t) \cdot V_c(t) = 5mA*100V = 0.5W$ ; At t= 3+ ms,  $p_c(t) = i_c(t) \cdot V_c(t) = -10mA*100V = -1W$ ; At t= 4 ms,  $p_c(t) = i_c(t) \cdot V_c(t) = -10mA*0V = 0W$ ; At t= 5- ms,  $p_c(t) = i_c(t) \cdot V_c(t) = -10mA*(-100V) = 1W$ ; At t= 5- ms,  $p_c(t) = i_c(t) \cdot V_c(t) = -10mA*100V = -1W$ ; At t= 5- ms,  $p_c(t) = i_c(t) \cdot V_c(t) = -10mA*100V = -1W$ ;



Name : \_\_\_\_\_



- (b) Indicate on your sketch of power as a function of time when the capacitor is absorbing power, and when it is providing (delivering) power.
- If  $P_c>0$ , then capacitor is absorbing power;
- If  $P_c < 0$ , then capacitor is delivering power;



(1 points)

Name :	Section:	CWRU e-mail:
--------	----------	--------------

## Problem 2 OP AMP integrator/differentiator (10 points)

Consider the OP AMP circuit shown below. There is no energy initially stored in the capacitor. A voltage of 6 volts is applied at t=0. The OP AMP is powered from a  $\pm$  15V volt power supply.



(a) If R=10 k $\Omega$  and C=0.25  $\mu F,$  determine the output voltage as a function of time.

The circuit acts as an integrator as  $v_o(t) = v_o(t) - \frac{1}{RC} \int_0^t v_1(t)$ . For this problem,  $v_1(t) = 6u(t)V$  and

$$-\frac{1}{RC} = -\frac{1}{10k\Omega \cdot 0.25\mu F} = -400.$$
  
So  $v_o(t) = v_o(t) - \frac{1}{RC} \int_0^t v_1(t) = -400 \int_0^t 6dt = -2400t$  (5 points)

(b) When will the output voltage reach saturation? When voltage is equal to  $\pm 15V$ , the output voltage reaches saturation. So  $-2400t = -15V \Rightarrow t = 6.25ms$  (5 points)