CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering Department of Electrical Engineering and Computer Science ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 11

4/09/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE **BE SURE TO STATE ALL ASSUMPTIONS**

Problem 1 Elementary phasors (10 points)

(a) Evaluate the complex number expression $\frac{61.7 \angle -27^{\circ}}{19 + i33}$. Your answer should be in rectangular form.

 $\frac{61.7\angle -27^{\circ}}{19+j33} = \frac{61.7\angle -27^{\circ}}{38.08\angle 60.07^{\circ}} = 1.62\angle -87.07^{\circ} = 0.08-j1.62$ (4 points)

(b) Convert the sinusoid $v(t) = 36\cos(754t + 80^\circ)$ to a phasor.

The phasor representation of v(t) is:

$$V = 36e^{j80^{\circ}} = 36\cos(80^{\circ}) + j36\sin(80^{\circ}) = 6.25 + j35.45 \text{ (3 points)}$$

(c) Convert the phasor (-1+j) to a real time-dependent function. Assume the frequency ω is in your answer.

$$-1+j = \sqrt{2}\left(-\frac{\sqrt{2}}{2}+j\frac{\sqrt{2}}{2}\right) = \sqrt{2}\left[\cos(135^\circ)+j\sin(135^\circ)\right] = \sqrt{2}e^{135^\circ}$$

So $v(t) = \operatorname{Re}\{\sqrt{2}e^{j135^{\circ}}\} = \sqrt{2}\cos(\omega t + 135^{\circ})$ (3 points)

Name :

Problem 2 Simple circuit analysis using phasors (10 points)

There are 500 to 1000 deaths each year in the United States from electric shock. If a person makes a good contact whit his/her hands, the resulting electrical circuit can be represented by the figure below where $v(t) = 160 \cos(\omega t)$ volts and $\omega = 377$.



(a) Redraw the above circuit replacing all real quantities by their phasor equivalents. Use numerical values for all impedances.

Resistor: $Z_R = R = 300\Omega$; (1 point) Inductor: $Z_L = j\omega L = j377 \cdot 100 mH = j37.7\Omega$; (1 point) Capacitor: $Z_c = \frac{1}{i\omega C} = \frac{1}{i377 \cdot 2\mu F} = -\frac{j1326.3\Omega}{j1326.3\Omega}$; (1 point)

(b) What is the complex impedance of the human body as seen by the voltage source? Your answer should be a numerical value. a manala su imana a da ma a la

$$Z = -j1326.3/(300 + j37.7) = \frac{-j1326.3 \cdot (300 + j37.7)}{-j1326.3 + (300 + j37.7)} = 301.47 - j31.38;$$
(3 points)

(c) What is the steady-state current i(t) flowing through the human body for the give v(t)?

 $Z = 301.47 - i31.38 = 303.1 \angle -5.9^{\circ}$ And $V = 160 \angle 0^{\circ}$, so $I = \frac{V}{R} = \frac{160 \angle 0^{\circ}}{303.1 \angle -5.9^{\circ}} = 0.53 \angle 5.9^{\circ}$ We can get $i(t) = 0.53 \cos(377t + 5.9^\circ)$; (4 points)