CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering Department of Electrical Engineering and Computer Science ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 12

4/16/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE **BE SURE TO STATE ALL ASSUMPTIONS**

Problem 1 Op Amp with Phasors (10 points)

Determine the transfer function $T(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$ of the following OP AMP circuit.



Think it is a subtractor with Z4= ∞ , Z2=10k Ω //1µF and V1=0V. So we can use the formula to calculate the gain.

$$T(j\omega) = (\frac{Z_1 + Z_2}{Z_1})(\frac{Z_4}{Z_3 + Z_4}) = \frac{\frac{2.5k\Omega + (10k\Omega / / \frac{1}{j\omega \cdot 1\mu F})}{2.5k\Omega} \cdot \frac{\infty}{10k\Omega + \infty}}{2.5k\Omega} + \frac{\frac{10k\Omega \cdot \frac{1}{1\mu Fj\omega}}{10k\Omega + \frac{1}{1\mu Fj\omega}}}{2.5k\Omega} = \frac{2.5k\Omega + \frac{10^4}{1 + 10^{-2}j\omega}}{2.5k\Omega} = \frac{5 + j10^{-2}\omega}{1 + j10^{-2}\omega}$$
(10 points)

Name :

Name : ______ Section: _____ CWRU e-mail:_____

Problem 2 Frequency dependent transfer functions (10 points)

(a) Using the chart below plot the frequency dependence of $20 \log_{10} |j \frac{\omega}{2000}|$.



(3 points)

(b) Using the chart below plot the frequency dependence of $-20\log_{10}|1+j\frac{\omega}{2000}|$.



(3 points)

(c) If the expression of (a) and (b) are added together, what type of filter does this present? Sketch this frequency response on the plot below.



(3 points)

High pass filter (1 point)