



**CASE WESTERN RESERVE UNIVERSITY**  
 Case School of Engineering  
 Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

**Quiz No. 3**

2/6/04


**PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE**  
**STATE ALL ASSUMPTIONS**

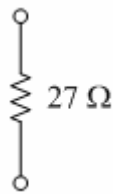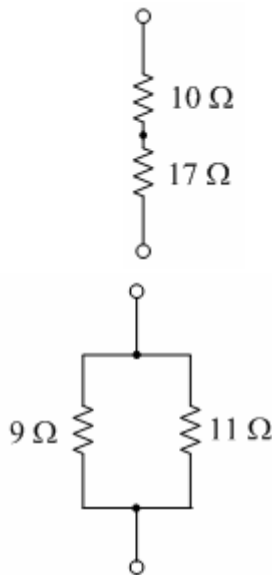**Problem 1** (10 points) In (a) and (b) show the equivalent circuit. In (c) and (d) transform the source. Be sure to indicate voltage and current directions.





$R_{eq} = R_1 + R_2$ ; that is two resistors in series;
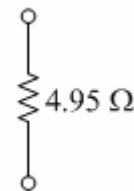
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}; \text{ that is two}$$





resistors in parallel;

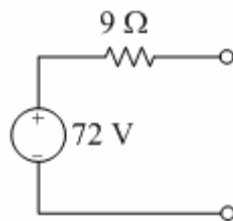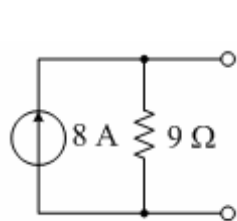

$V_{eq} = I_s R$ ;  $R_{eq} = R$ ; detailed analysis refers to p.36 in

textbook;

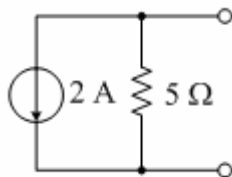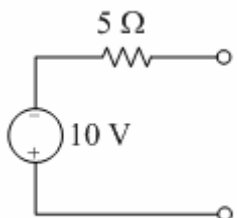

$I_{eq} = \frac{V_s}{R}$ ;  $R_{eq} = R$ ; detailed analysis refers to p.37 in


textbook;

Please note that the current directions of two circuits should be kept same after the transformation.

**Problem 2** (10 points)

Determine the numeric values of the indicated parameters for the circuits shown below.

$V_{DB}=V_D-V_B$ , the voltage of node D with respect to node B	40 V
$I_1$ , the current through the $12\ \Omega$ resistor (note the indicated direction)	$16/3=5.33\text{ A}$
$V_{AC}=V_A-V_C$ , the voltage of node A with respect to node C	24 V

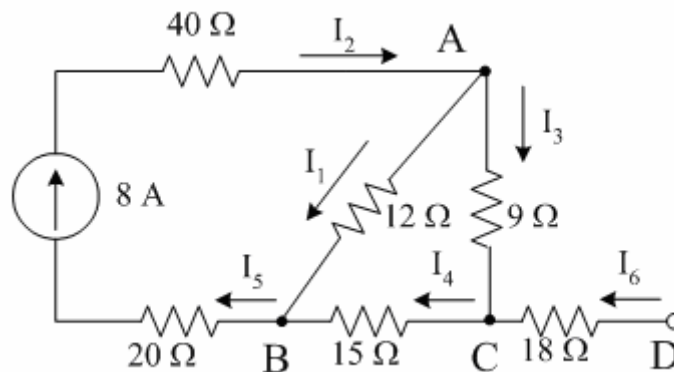

**SOLUTIONS:**

I. By inspection of the current sources

$$I_2 = I_s = 8 \text{ Ampere}$$

$$I_5 = I_s = 8 \text{ Ampere}$$

II. Connection equations come from KCL and KVL

Remember that I said that we always use KCL when we see current sources. I will always use +in notation for the currents at all nodes.

$$\text{At the node A: } +I_2 - I_1 - I_3 = 0 \text{ Therefore } I_2 = I_1 + I_3 = 8 \text{ Ampere}$$


$$\text{At the node B: } +I_1 + I_4 - I_5 = 0 \text{ Therefore } I_5 = I_1 + I_4 = 8 \text{ Ampere}$$

At the node D, which is floating, therefore there is no current from C to D, that is  $I_6 = 0$ . Since there is no current through the resistor between C and D, then  $V_{DC} = V_D - V_C = I_6 * 18\Omega = 0 * 18\Omega = 0$  Volt. That means,  $V_D = V_C$ , then  $V_{DB} = V_D - V_B = V_C - V_B = V_{CB}$

$$\text{At the node C, } +I_3 + I_6 - I_4 = 0. \text{ Therefore, } I_3 = I_4$$

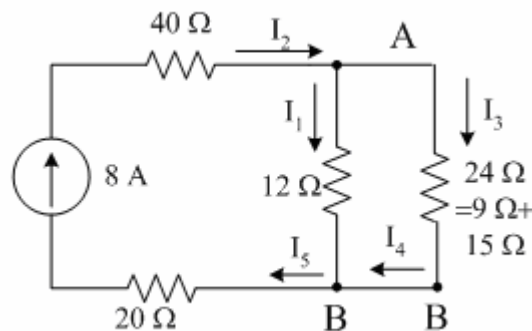III. Current division and circuit reduction

If we ignore the resistor between C and D, then we can get the equivalent circuit as follows:



Using current division equations,

Name : \_\_\_\_\_ Section: \_\_\_\_\_ CWRU e-mail: \_\_\_\_\_

$$I_1 = \frac{G_1}{G_1 + G_2} I_2 \text{ and } I_3 = \frac{G_2}{G_1 + G_2} I_2$$

$$\text{So } I_1 = \frac{G_1}{G_1 + G_2} I_2 = \frac{\frac{1}{12}}{\frac{1}{12} + \frac{1}{24}} \cdot 8 = \frac{16}{3} \text{ Amperes and } I_3 = \frac{G_2}{G_1 + G_2} I_2 = \frac{\frac{1}{24}}{\frac{1}{12} + \frac{1}{24}} \cdot 8 = \frac{8}{3} \text{ Amperes;}$$

Actually, we can simplify a little bit here by

$$I_1 = \frac{G_1}{G_1 + G_2} I_2 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot I_2 = \frac{R_2}{R_1 + R_2} \cdot I_2 = \frac{24}{12 + 24} \cdot 8 = \frac{16}{3} \text{ Amperes;}$$

$$\text{And } I_3 = I_2 - I_1 = 8 - \frac{16}{3} = \frac{8}{3} \text{ Amperes;}$$

We have known the value of  $I_3$ , then we can calculate  $V_{DB}$ .

$$\text{As stated above, } V_{DB} = V_{CB} = I_3 \cdot 15\Omega = \frac{8}{3} \cdot 15 = 40 \text{ Volts}$$

$$\text{Likewise, } V_{AC} = I_3 \cdot 9\Omega = \frac{8}{3} \cdot 9 = 24 \text{ Volts}$$