Section:

Case School of Engineering Department of Electrical Engineering and Computer Science ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 4

2/13/04

CWRU e-mail:

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE STATE ALL ASSUMPTIONS

Problem 1 (10 points) What is the current I supplied by the 10 volt source in the figure below? Be sure to used the polarity indicated in the drawing.



ANSWER:

Using mesh currents to formulate the circuit equations, quite similar to the analysis listed in p.85 in the textbook.

Mesh 1: $-V_{s1} + V_1 + V_3 = 0$ Mesh 2: $+V_{s2} - V_3 + V_2 = 0$

We can also write the element voltage in terms of mesh currents and input voltages:

 $V_{1}=i_{1} * 4\Omega,$ $V_{2}=i_{2} * 2\Omega,$ $V_{3}=(i_{1}-i_{2}) * 2\Omega,$ $V_{s1}=10V,$ $V_{s2}=20V$ So -10+4i_{1}+2(i_{1}-i_{2})=0 => -10+6i_{1}-2i_{2}=0 => -5+3i_{1}-i_{2}=0 $=>i_{2}=-5+3i_{1} (1)$ $20-2(i_{1}-i_{2})+2i_{2}=0 => 20-2i_{1}+4i_{2}=0$ $=> 10-i_{1}+2i_{2}=0 (2)$ Using (1) in (2), we can get $10-i_{1}+2(-5+3i_{1})=0 => 5i_{1}=0 => i_{1}=0$

Problem 2 (10 points)

Find the node-voltage equations for this circuit. Complete the table.



Answer:

Using KCL to write the equations: Σ in = Σ out At node A: $i_0=i_1+i_2$ At node B: $i_1+i_5=i_3$ At node C: $i_2=i_4+i_5$

Also we can write the element current based on the voltage drop across it and input current source: $i_0 = i_{s1}$

And using these equations in the KCL equations listed above, we can get $i_{s1}=(V_A-V_B)/R_1+(V_A-V_C)/R_2$ $(V_A-V_B)/R_1+is2=V_B/R_3$ $(V_A-V_C)/R_2=V_C/R_4+i_{s2}$

 $\begin{array}{l} \text{Simplifying these equations:} \\ (1/R_1+1/R_2)V_A+(-1/R_1)V_B+(-1/R_2)V_C=i_{s1}\\ (-1/R_1)V_A+(1/R_1+1/R_2)V_B+0V_C=i_{s2}\\ (-1/R_2)V_A+0V_B+(1/R_2+1/R_4)V_C=-i_{s2} \end{array}$