

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 5


2/20/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE
BE SURE TO STATE ALL ASSUMPTIONS

Problem 1 (10 points) Using superposition determine


(a) the current i_1 through the $5\ \Omega$ resistor (observe the direction for i given in the circuit below) from the 10 volts source. $i_1 = 0.588\text{ A}$

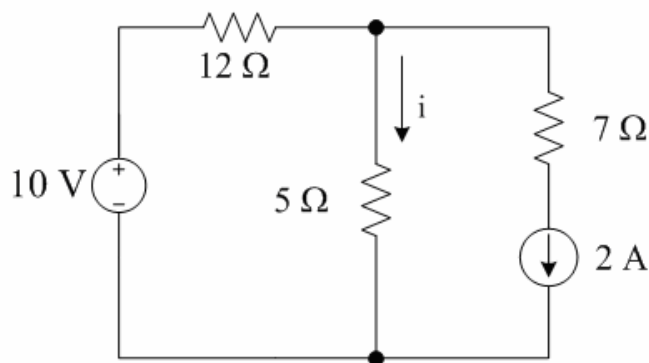(b) the current i_2 through the $5\ \Omega$ resistor (observe the direction for i given in the circuit below) from the 2 ampere source. $i_2 = -1.41\text{ A}$



ANSWER:

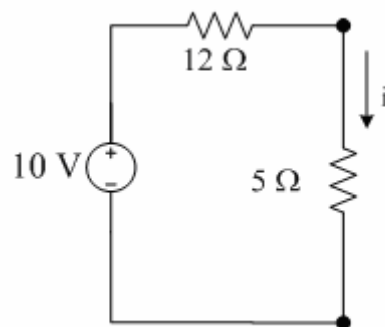(a) First turn off the current source and replace it with an open circuit. Then the equivalent circuit is as follows:




So we can easily calculate the current through the $5\ \Omega$ resistor:

Name : _____ Section: _____ CWRU e-mail: _____

$$i_1 = \frac{10V}{12\Omega + 5\Omega} = 0.588A$$

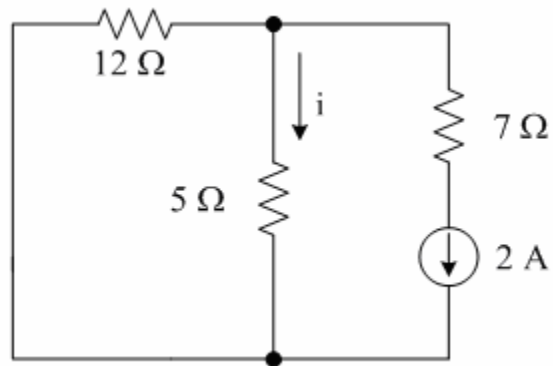(b) Turn off the voltage source and replace it with an short circuit. The equivalent circuit is as follows:




$$\text{Then } i_2 = -2A \cdot \frac{12\Omega}{12\Omega + 5\Omega} = -1.412A$$

Problem 2 (10 points)

What is the Thevenin equivalent of the circuit shown below

$$V_T = 7.5 \text{ V}$$


$$R_T = 5 \text{ k}\Omega$$

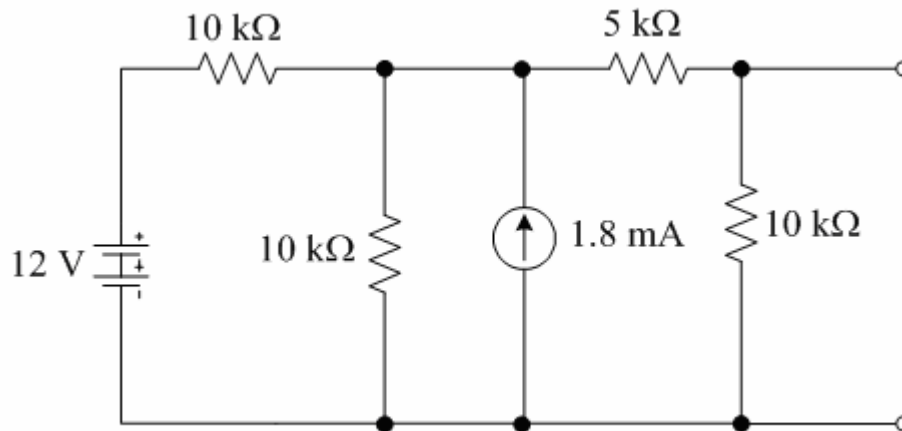

ANSWER:


The problem is similar to the example listed in p.106. And we could use the same method to solve it step by step.

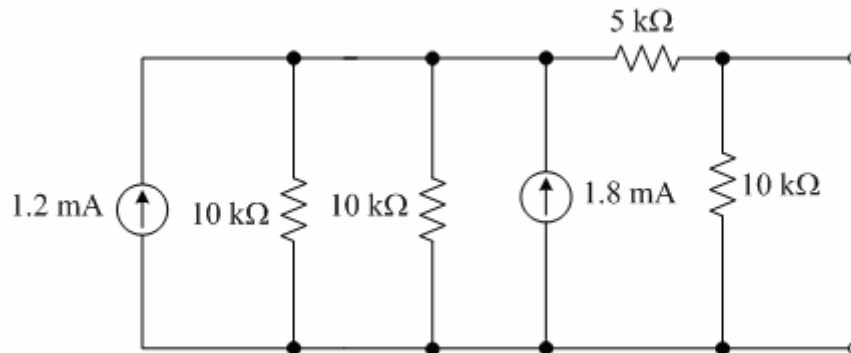(1) Convert 12 V in series with 10 kΩ to 1.2 mA in parallel with 10 kΩ;




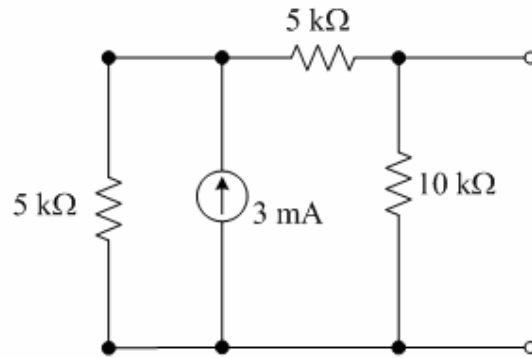(2) Combine two current sources and resistors;


$1.2 \text{ mA} + 1.8 \text{ mA} = 3.0 \text{ mA}$; $10 \text{ k}\Omega // 10 \text{ k}\Omega = 5 \text{ k}\Omega$;



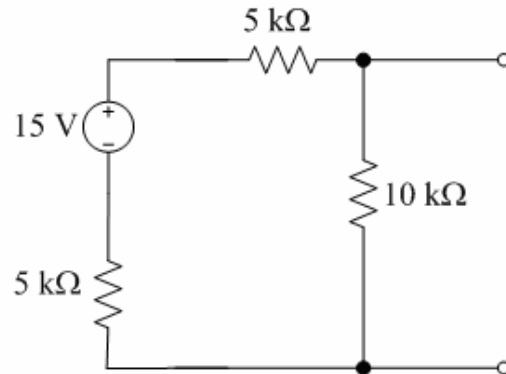(3) Convert 3 mA in parallel with $5\text{ k}\Omega$ to 15 V in series with $5\text{ k}\Omega$;




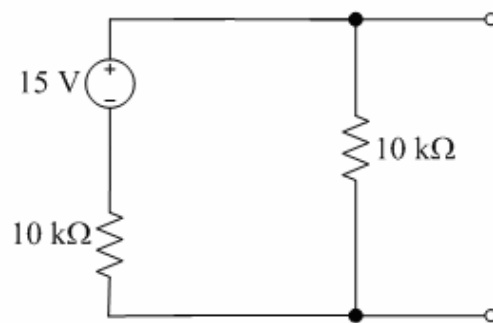(4) Combine two resistors together;
 $5\text{ k}\Omega + 5\text{ k}\Omega = 10\text{ k}\Omega$;




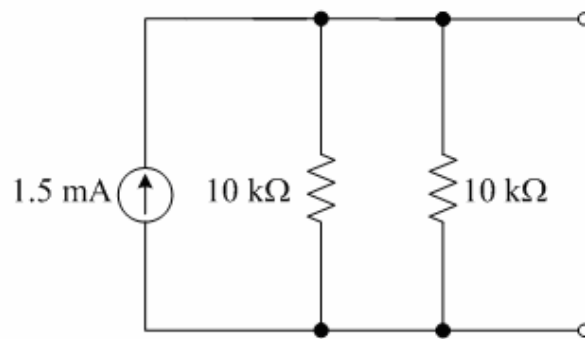(5) Convert 15 V in series with $10\text{ k}\Omega$ to 1.5 mA in parallel with $10\text{ k}\Omega$;

Name : _____ Section: _____ CWRU e-mail: _____



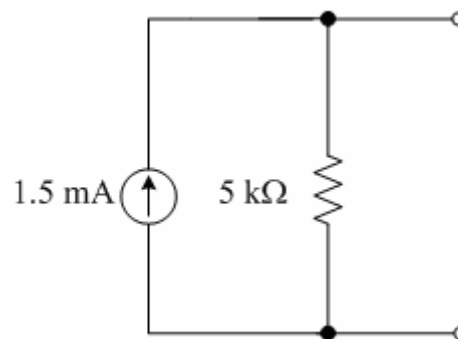(6) Combine two resistor together;
 $10\text{ k}\Omega // 10\text{ k}\Omega = 5\text{ k}\Omega$;



(7) Convert 1.5 mA in parallel with 5 kΩ to 7.5 V in series with 5 kΩ;

