CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering Department of Electrical Engineering and Computer Science ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 6

2/27/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE BE SURE TO STATE ALL ASSUMPTIONS

Problem 1 (10 points)



(a) The power dissipated by R_L will be a maximum for $R_L=40 \Omega$; (3 points)

A source with a fixed Thevenin resistance R_T delivers maximum power to an adjustable load R_L when $R_L=R_T$. Detailed analysis is listed in p.114.

(b) The power dissipated by R_{L} for $R_{L}=10 \Omega$ is 0.4 Watts;

$$I = \frac{10V}{40\Omega + 10\Omega} = 0.2A \quad \text{(2 points)}, \quad P = I^2 R = (0.2A)^2 \cdot 10\Omega = 0.4W \text{ (2 points)}$$

(c) If R_{L} increases from 10 Ω to 25 Ω , the power dissipated by it will **INCREASE**;

If R_L=25
$$\Omega$$
, then $I = \frac{10V}{40\Omega + 25\Omega} = 0.15A$ (2 points), $P = I^2 R = (0.15A)^2 \cdot 25\Omega = 0.59W$ (1 point)

Problem 2 (10 points)

Consider this active circuit.



(a) Write node analysis equations (KCL) for nodes A and B. $\Sigma I_{_{in}} = \Sigma I_{_{out}}$

At node A:
$$i_a = i_2 + i_3 + 2i_a$$
 (2 point)
 $i_a = \frac{10V - V_A}{3\Omega}$, $i_2 = \frac{V_A - V_B}{8\Omega}$ and $i_3 = \frac{V_A}{6\Omega}$ (2 points)
So $\frac{10 - V_A}{3} = \frac{V_A - V_B}{8} + \frac{V_A}{6} + 2 \cdot \frac{10 - V_A}{3}$
 $=> (-\frac{1}{3} - \frac{1}{8} - \frac{1}{6} + \frac{2}{3})V_A + (\frac{1}{8})V_B = -\frac{10}{3} + \frac{20}{3}$
 $=> \frac{1}{24}V_A + \frac{1}{8}V_B = \frac{10}{3}$ or $V_A + 3V_B = 80$ (1 point)

At node B: $i_2 + 2i_a = i_4$ (1 point) and $i_4 = \frac{V_B}{6\Omega}$ (1 points) $\frac{V_A - V_B}{8} + 2\frac{10 - V_A}{3} = \frac{V_B}{6}$ $=> (\frac{1}{8} - \frac{2}{3})V_A + (-\frac{1}{8} - \frac{1}{6})V_B = -\frac{20}{3}$ $=> -\frac{13}{24}V_A - \frac{7}{24}V_B = -\frac{20}{3} \text{ or } 13V_A + 7V_B = 160 \text{ (1 point)}$ (b) Find the node voltages for the above circuit values. So just solve for $V_{\rm A}$ and $V_{\rm B}$ from the above two equations:

$$\begin{cases} V_A + 3V_B = 80 \\ 13V_A + 7V_B = 160 \\ 13V_A + 39V_B = 1040 \\ 13V_A + 7V_B = 160 \\ => 32V_B = 880 \\ => V_B = 27.5V \quad (1 \text{ point) and} \quad V_A = -2.5V \quad (1 \text{ point)} \end{cases}$$