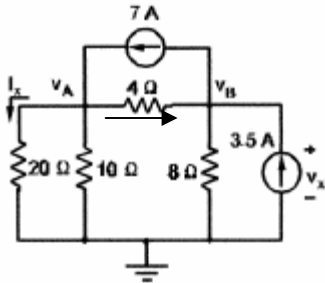


Homework Solutions 4

- (3-2) (a) Formulate node-voltage equations for the circuit in Figure P3-2
 (b) Use these equations to find V_x and I_x



Current through 4Ω resistor (choose direction of current). I chose $V_a \longrightarrow V_b$. Then, current through the resistor is:

$$I_{4\Omega} = \frac{V_a - V_b}{4\Omega}; \text{ and } I_x = \frac{V_a}{20\Omega}$$

Node voltage equations

A : $-V_a/20 + -V_a/10 + -(V_a-V_b)/4 = 7A$
 B: $(V_a-V_b)/4 + -V_b/8 = -7 + 3.5$

$$\mathbf{3-2 (a)} \quad \begin{pmatrix} \frac{1}{20} + \frac{1}{10} + \frac{1}{4} & \frac{-1}{4} \\ \frac{-1}{4} & \frac{1}{4} + \frac{1}{8} \end{pmatrix} \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 7 \\ -7 + 3.5 \end{pmatrix}$$

$$\mathbf{(b)} \quad \begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} \frac{1}{20} + \frac{1}{10} + \frac{1}{4} & \frac{-1}{4} \\ \frac{-1}{4} & \frac{1}{4} + \frac{1}{8} \end{pmatrix}^{-1} \begin{pmatrix} 7 \\ -7 + 3.5 \end{pmatrix}$$

$$\begin{pmatrix} v_A \\ v_B \end{pmatrix} = \begin{pmatrix} 20 \\ 4 \end{pmatrix} \quad v_x := v_B \quad i_x := \frac{v_A}{20} \quad v_x = 4$$

Therefore, V_x is simply the voltage across the 8Ω resistor since $V_b = 4$ the only voltage drop will occur across the 8Ω resistor, hence V_x must equal V_b .

- (3-4) (a) Formulate a set of node-voltages for the circuit in Figure P3-4
 (b) Use these equations to find V_x and I_x

First draw your current directions, then use your KCL equations to simplify the problem then, find the nodal voltages through each resistor.

KCL at nodes A, B

$$\text{KCL@A} : 2\text{mA} - i_{2\text{k}\Omega} + i_{4\text{k}\Omega} = 0$$

$$\text{KCL@B} : -2\text{mA} - i_{3\text{k}\Omega} (\text{left of node B}) + i_{3\text{k}\Omega} (\text{up arrow into node B}) = 0$$

$$\text{KCL@Center-Node} : i_{2\text{k}\Omega} + i_{3\text{k}\Omega} (\text{left of node B}) = I_x$$


$$3-4 \text{ (a)} \quad \left(\frac{1}{2000} + \frac{1}{4000} \right) v_A - \frac{10}{2000} = 2 \cdot 10^{-3}$$

$$\left(\frac{1}{3000} + \frac{1}{3000} \right) v_B - \frac{10}{3000} = -2 \cdot 10^{-3}$$

$$\text{(b) Solving the 1st equation for } v_A \quad v_A := \frac{28}{3}$$

$$\text{Solving the 2nd equation for } v_B \quad v_B := 2$$
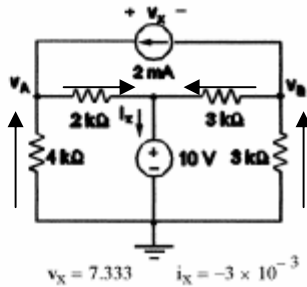
$$v_x := v_A - v_B \quad i_x := \left(\frac{v_A - 10}{2000} \right) + \frac{v_B - 10}{3000}$$



After all the simplifications, **$V_x = 7.333$ and $I_x = -3\text{mA}$**


- (3-8) (a) Formulate the node-voltage equations for the circuit in Figure P3-8
 (b) Solve for V_x and I_x using $R_1 = 10\text{k}\Omega$, $R_2 = 20\text{k}\Omega$, $R_3 = 60\text{k}\Omega$, $R_4 = 20\text{k}\Omega$, $R_x = 3\text{k}\Omega$, and $V_s = 15\text{V}$.
 (c) Find the power absorbed by the resistor R_2 .

THE WHEATSTONE BRIDGE!!!

The trick to this problem is rather simple, do not think too much into the problem you cannot reduce this circuit, the resistors are neither in parallel or series! Start by labeling your nodes, then draw your current directions. Next, use your KCL's and solve the current through each resistor with nodal analysis. Simplify. Find I_x , V_x , P_{R_2} .

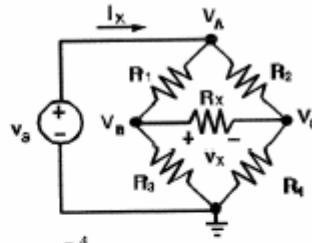3-8 (a)

$$\begin{pmatrix} 1 & 0 & 0 \\ -G_1 & G_1 + G_X + G_3 & -G_X \\ -G_2 & -G_X & G_2 + G_X + G_4 \end{pmatrix} \begin{pmatrix} v_A \\ v_B \\ v_C \end{pmatrix} = \begin{pmatrix} v_S \\ 0 \\ 0 \end{pmatrix}$$



(b) $G_1 := (10^4)^{-1}$ $G_2 := (2 \cdot 10^4)^{-1}$ $G_3 := (6 \cdot 10^4)^{-1}$

$G_4 := (2 \cdot 10^4)^{-1}$ $G_X := (3 \cdot 10^3)^{-1}$ $v_S := 15$ $G_X = 3.333 \times 10^{-4}$

$$\begin{pmatrix} v_A \\ v_B \\ v_C \end{pmatrix} := \begin{pmatrix} 1 & 0 & 0 \\ -G_1 & G_1 + G_X + G_3 & -G_X \\ -G_2 & -G_X & G_2 + G_X + G_4 \end{pmatrix}^{-1} \begin{pmatrix} v_S \\ 0 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} v_A \\ v_B \\ v_C \end{pmatrix} = \begin{pmatrix} 15 \\ 10.728 \\ 9.983 \end{pmatrix} \quad v_X := v_B - v_C \quad i_X := (v_A - v_B) \cdot G_1 + (v_A - v_C) \cdot G_2$$

$$v_X = 0.745 \quad i_X = 6.78 \times 10^{-4}$$

(c) $P_{R2} := (v_A - v_C)^2 \cdot G_2$ $P_{R2} = 1.2583 \times 10^{-3} \text{ W}$

Therefore, **V_a = 15; V_b = 10.72; V_c = 9.98; and P_{R2} = 1.26mW.**

(3-10) (a) Formulate mesh current equations for the circuit in Figure P3-10.

(b) Use these equations to find V_x and I_x.

These problems end to being a lot of algebra and reducing but they get the job done. The main key that many students forget in these type of mesh problems is where the center 2kΩ resistor when finding the mesh equation for A, the voltage through the 2kΩ resistor is (I_a – I_b) * 2kΩ. For finding mesh equation for B, the voltage through the 2kΩ resistor is (I_b – I_a) * 2kΩ

3-10 (a)


$$\begin{pmatrix} 2000 + 2000 + 2000 & -2000 \\ -2000 & 2000 + 4000 + 4000 \end{pmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 5 - 15 \\ 15 \end{pmatrix}$$

(b)

$$\begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 2000 + 2000 + 2000 & -2000 \\ -2000 & 2000 + 4000 + 4000 \end{pmatrix}^{-1} \begin{pmatrix} -10 \\ 15 \end{pmatrix}$$

$$\begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} -1.25 \times 10^{-3} \\ 1.25 \times 10^{-3} \end{pmatrix}$$

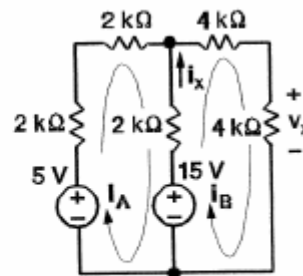$v_X := i_B \cdot 4000$ $i_X := i_B - i_A$ $v_X = 5$ $i_X = 2.5 \times 10^{-3}$



Therefore, **I_x = I_b – I_a = 2.5mA; V_x = I_b*4000 = 5V**

- (3-12) (a) Formulate mesh current equations for the circuit in the Figure P3-12
 (b) Solve for V_x and I_x using $R_1 = 200\Omega$, $R_2 = 500\Omega$, $R_3 = 60\Omega$, $R_4 = 240\Omega$, $R_5 = 200\Omega$, $I_s = 50\text{mA}$, and $V_s = 15\text{V}$.
 (c) Find the total power dissipated in the circuit

This is a good type of problem to apply the super node, but does not have to be solve that way. Simple nodal voltage equations will solve this one also.

3-12 Assign mesh currents as shown


(a) by KCL $i_2 - i_1 = i_s$ Super Mesh:

$$(R_1 + R_2) \cdot i_1 + (R_3 + R_4 + R_5) \cdot i_2 = v_s$$

(b) $R_1 := 200$ $R_2 := 500$ $R_3 := 60$

$R_4 := 240$ $R_5 := 200$

$v_s := 15$ $i_s := 0.05$

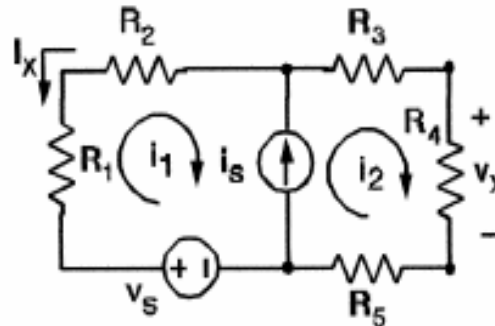

$$i_1 := \frac{-(i_s \cdot R_3 + i_s \cdot R_4 + i_s \cdot R_5 - v_s)}{(R_1 + R_2 + R_3 + R_4 + R_5)} \quad i_2 := \frac{(i_s \cdot R_1 + i_s \cdot R_2 + v_s)}{(R_1 + R_2 + R_3 + R_4 + R_5)} \quad \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} -8.333 \times 10^{-3} \\ 4.167 \times 10^{-2} \end{pmatrix}$$

$$i_x := -i_1 \quad i_x = 8.333 \times 10^{-3} \quad v_x := R_4 \cdot (i_2) \quad v_x = 10$$

(c) $P_{\text{total}} := (R_3 + R_4 + R_5) \cdot (i_2)^2 + (R_1 + R_2) \cdot i_1^2 \quad P_{\text{total}} = 0.917 \quad \text{W}$

Remember, $P = VI \rightarrow P = R \cdot I \cdot I \rightarrow P = RI^2$

Therefore, **$I_x = 8.33\text{mA}$; $V_x = 10$; $P_{\text{tot}} = 917\text{mW}$**

(3-19) Find the node voltages V_a and V_b in the Figure P3-19.

This problem seems to be quite troublesome at first but consider your KCL equations first and use common sense to solve the nodal equations.

At node B, there is a 12mA supply entering the node and two current leaving the node (look at the figure). The 20V source divided by the addition of the $2\text{k}\Omega$ and the $8\text{k}\Omega$ is one of the current leaving node B.

At node A, the node equation can be solved simply by using voltage division.

After equations are found solve for V_a and V_b .

3-19 Writing one mesh equation


$$(2000 + 4000 + 8000) \cdot i_A + 4000 \cdot 12 \cdot 10^{-3} = -20$$

solving for i_A $i_A := -4.857 \cdot 10^{-3}$

$$v_A := -8000 \cdot i_A \quad v_A = 38.856$$

$$v_B := (i_A + 12 \cdot 10^{-3}) \cdot 4000 \quad v_B = 28.572$$

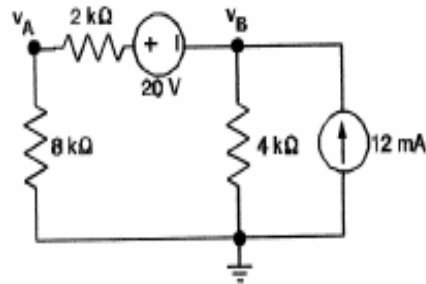Checking $(2000 + 4000 + 8000) \cdot i_A + 4000 \cdot (12 \cdot 10^{-3}) = -19.998$ \leftarrow checks the mesh equation



Therefore, $v_A = -8000 \cdot i_A = \underline{38.9}$; $v_B = \underline{28.57}$