
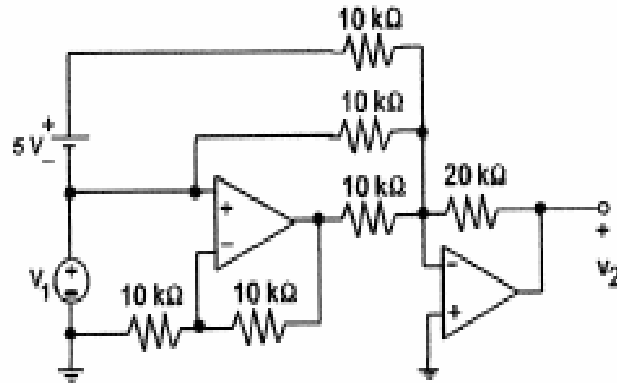


## Homework Solutions 8

4-32

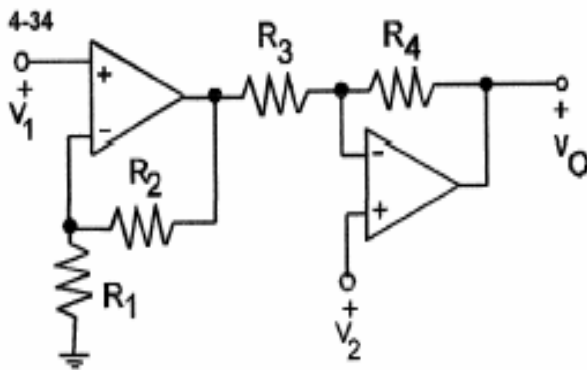

$$v_2 = \left(\frac{-20}{10}\right) \cdot (v_1 + 5) + \left(\frac{-20}{10}\right) \cdot v_1 + \left(\frac{-20}{10}\right) \cdot \left(\frac{10 + 10}{10} \cdot v_1\right) = -8 \cdot v_1 - 10$$




$$v_2 \text{ off} \quad v_{O1} = \left(\frac{R_2 + R_1}{R_1}\right) \cdot \left(\frac{-R_4}{R_3}\right) \cdot v_1$$

$$v_1 \text{ off} \quad v_{O2} = \left(\frac{R_4 + R_3}{R_3}\right) \cdot v_2$$

Using superposition

$$v_O = \left(\frac{R_4 + R_3}{R_3}\right) \cdot v_2 - \left(\frac{R_2 + R_1}{R_1}\right) \cdot \left(\frac{R_4}{R_3}\right) \cdot v_1$$


4-46  $v_S := -15, -14.9, 15$

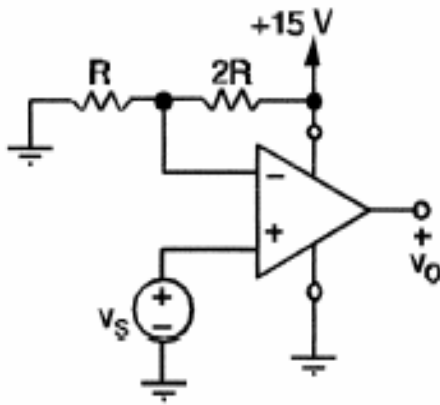

(a)  $v_P = v_S$   $v_n := 5$   $V_{OH} := 15$   $V_{OL} := 0$

$$v_O(v_S) := \begin{cases} V_{OH} & \text{if } v_S > v_n \\ V_{OL} & \text{if } v_S < v_n \end{cases}$$


(b)

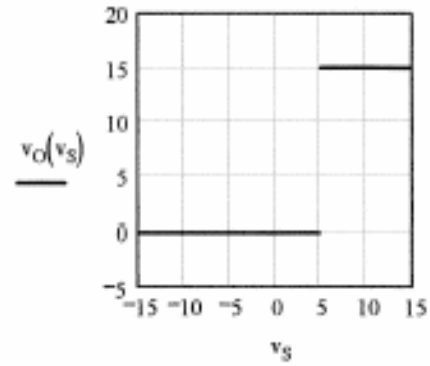

4-47  $V_{OH} := 10$   $V_{OL} := 0$

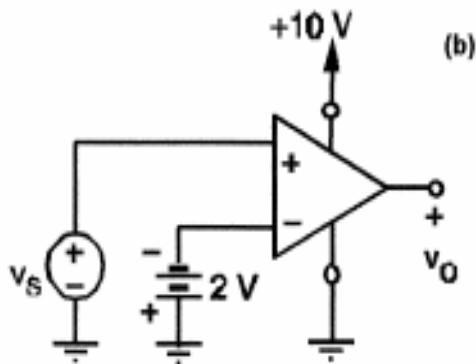(a)  $v_P = v_S$   $v_n := -2$

$$v_O(v_S) := \begin{cases} V_{OH} & \text{if } v_S > v_n \\ V_{OL} & \text{if } v_S < v_n \end{cases}$$



(b)

