

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 2

9/6/03

Name (Section): Solutions

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK

Problem 1 (10 points)
Complete this table.


QUANTITY	SYMBOL	UNIT
Power	P	W (Watt)
Charge	Q	C (Coulomb)
Current	I	A (Amp)
Voltage	V	V (Volt)
Resistance	R	Ω (Ohm)

Note: lower case is preferred for variables
(p, q, i, v), while upper case is used
for constants (P, Q, I, V)

(over)

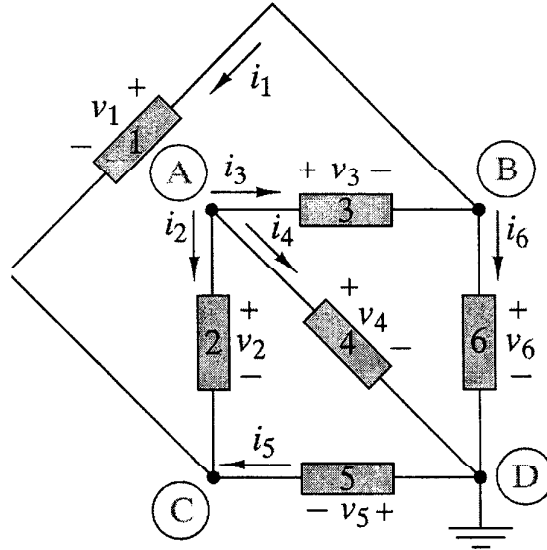Problem 2 (10 points)

Write the KCL equations for this circuit, then solve for the unknown currents. Complete the tables.



NODE	KCL EQUATION
A	$i_2 + i_3 + i_4 = 0$
B	$i_1 + i_6 - i_3 = 0$
C	$i_1 + i_2 + i_5 = 0$

ELEMENT	CURRENT
1	$i_1 = 1 \text{ A}$
2	$i_2 = 2 \text{ A}$
3	$i_3 = 3 \text{ A}$
4	$i_4 = -5 \text{ A}$
5	$i_5 = -3 \text{ A}$
6	$i_6 = 2 \text{ A}$

(over)