

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 5


10/03/03

Name (Section): Solutions

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK

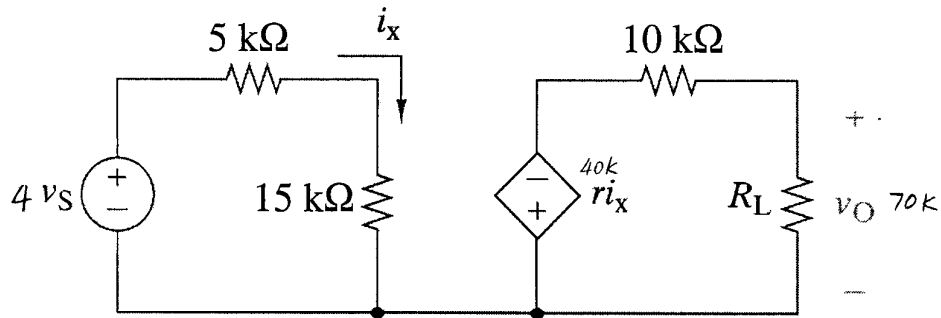Problem 1 (10 points)

Calculate i_x , v_o , and p_o (the power dissipated by R_L) given $v_s = 4\text{ V}$, $r = 40\text{ k}\Omega$, and $R_L = 70\text{ k}\Omega$. Complete the table.



VARIABLE	VALUE FOR $V_s = 4\text{ V}$, $R = 40\text{ k}\Omega$, AND $R_L = 70\text{ k}\Omega$
i_x	0.2 mA
v_o	-7 V
p_o	0.7 mW


Given v_s and r as above, choose the value of R_L that give maximum p_o , and calculate this value of p_o . Complete the table.

VARIABLE	VALUE FOR MAXIMUM POWER
R_L	$10\text{ k}\Omega$
p_o	1.6 mW

(over)

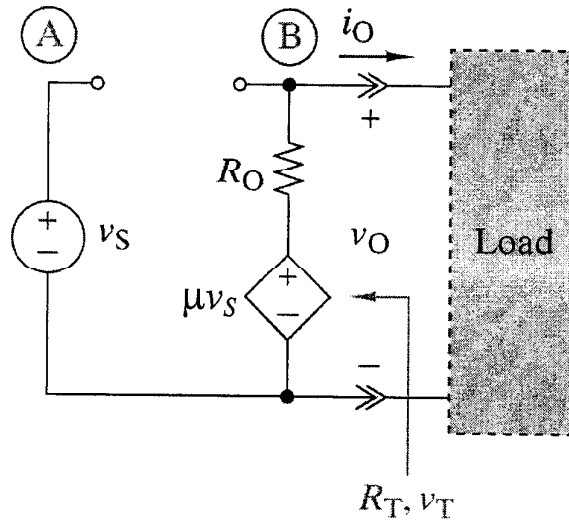Problem 2 (10 points)

Find the Thevenin and Norton equivalent circuit parameters for interface v_O in this circuit. Complete the table.



ELEMENT	VALUE
v_T	μv_s
R_T	R_o
i_N	$\frac{\mu v_s}{R_o}$
R_N	R_o

(over)