
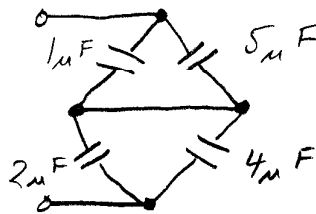


SOLUTIONS




6-36)

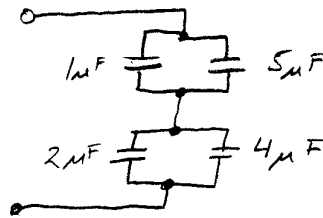


=





=

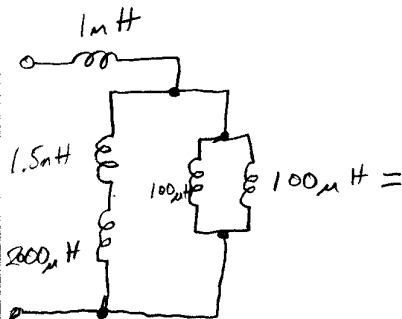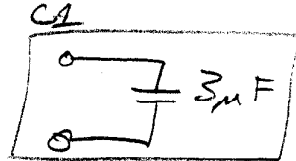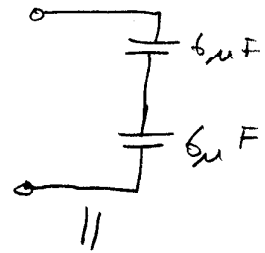


=

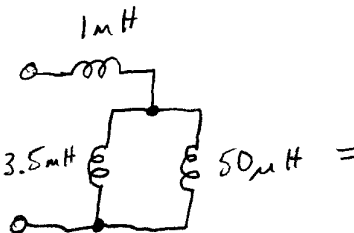

=

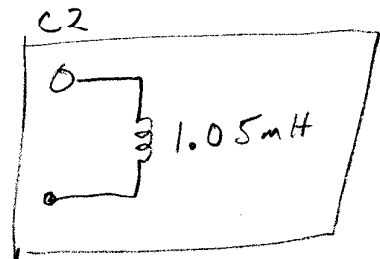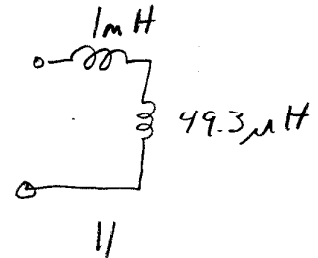

6-48) a)

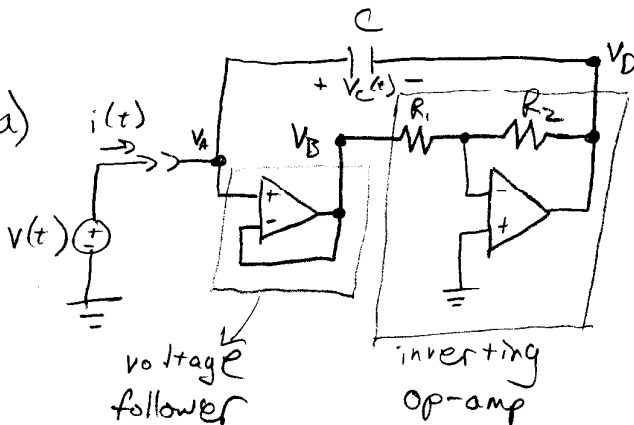

$$V_B = V_A = v(t)$$

$$V_D = -\frac{R_2}{R_1} V_B = -\frac{R_2}{R_1} V_A = -\frac{R_2}{R_1} v(t)$$

$$V_C = V_A - V_D$$

$$= v(t) + \frac{R_2}{R_1} v(t)$$

$$= v(t) \left[1 + \frac{R_2}{R_1} \right]$$

$$i(t) = C \frac{d}{dt} V_C(t) = C \frac{d}{dt} \left[v(t) \left(1 + \frac{R_2}{R_1} \right) \right] = C \left(1 + \frac{R_2}{R_1} \right) \frac{d}{dt} v(t)$$

$$\boxed{i(t) = C_{EQ} \frac{d}{dt} v(t) \text{ where } C_{EQ} = \left(1 + \frac{R_2}{R_1} \right) C \text{ q.e.d.}}$$

$$b) v_c(0) = v(0) \left(1 + \frac{R_2}{R_1}\right) = V_0$$

$$\boxed{v(0) = \frac{V_0}{1 + \frac{R_2}{R_1}}} = \frac{R_1 V_0}{R_1 + R_2}$$

$$c) w_c(0) = \frac{1}{2} C v_c^2(0) = W_0$$

$$\frac{1}{2} C v^2(0) \left(1 + \frac{R_2}{R_1}\right)^2 = W_0$$

$$v^2(0) = \frac{2 W_0}{C \left(1 + \frac{R_2}{R_1}\right)^2}$$

want $w_{eq}(0) = \frac{1}{2} C_{eq} \dot{v}(0)$

$$W_{eq}(0) = \frac{1}{2} C_{eq} v^2(0)$$

$$= \frac{1}{2} \left(1 + \frac{R_2}{R_1}\right) C \cdot \frac{2 W_0}{\left(1 + \frac{R_2}{R_1}\right)^2}$$

$$\boxed{W_{eq}(0) = \frac{W_0}{1 + \frac{R_2}{R_1}}} = \frac{R_1 W_0}{R_1 + R_2}$$

3
7-2)


$$10^{-4} \frac{d}{dt} i(t) + 10^{-1} i(t) = 0 \quad i(0) = -20 \text{ mA}$$

$$10^{-3} \frac{d}{dt} i(t) + i(t) = 0$$

Natural response: $i_n(t) = K e^{-t \cdot 1000}$
 Forced response: $i_f(t) = 0$

$$i(0) = K e^0 = K = -20 \text{ mA}$$
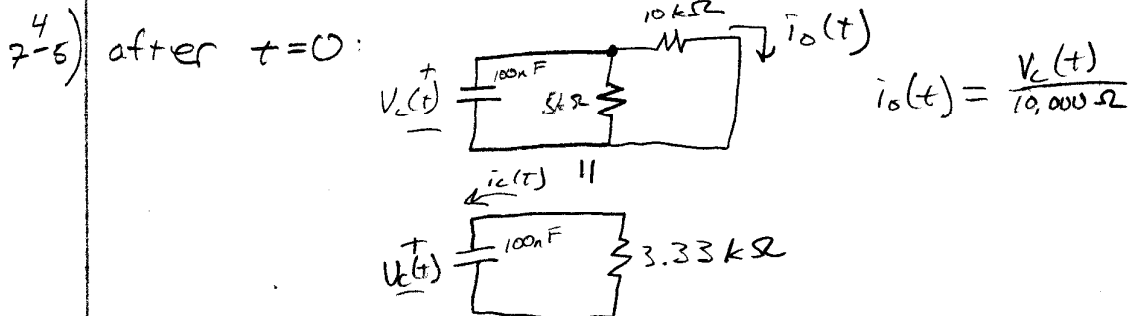
$$\boxed{i(t) = -20 \text{ mA} \cdot e^{-1000t}}$$



$$i_c(t) = C \frac{d}{dt} v_c(t) = -\frac{v_c(t)}{3.33 \text{ k}\Omega}$$

$$C R_{eq} \frac{d}{dt} v_c(t) + v_c(t) = 0$$

$$v_c(t) = K e^{-\frac{t}{C R_{eq}}} = K e^{-3000t}$$

WTF

since $v_L(0) = 15V$

$$v_L(t) = 15V \cdot e^{-3000t}$$

$$i_o(t) = \frac{15V}{10k\Omega} e^{-3000t}$$

$$i_o(t) = 1.5mA \cdot e^{-3000t}$$

7-10)

$$v_s(t) = v_L(t) + v_o(t) \quad v_o(t) = Ri(t)$$

since inductor, easier to solve for $i(t)$

since step function, easier to use initial and final conditions

$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{t}{T_L}} \quad T_L = \frac{L}{R}$$

initially zero-state: $i_L(0) = 0$

as $t \rightarrow \infty$ inductor acts like short, so:

$$i(\infty) = \frac{V_A}{R}$$

$$i(t) = \frac{V_A}{R} - \frac{V_A}{R} e^{-\frac{t}{\tau_R}}$$

$$i(t) = \frac{V_A}{R} - \frac{V_A}{R} e^{-\frac{Rt}{L}}$$

$$v_o(t) = \underbrace{V_A}_{\text{forced}} - \underbrace{V_A e^{-\frac{Rt}{L}}}_{\text{natural}}$$