

ENGR 210
FALL 2003
HOMEWORK #1
SOLUTIONS

1
of
3

- 1-2) a) 22 mV
b) 23 nF
c) $56 \text{ k}\Omega$
d) 752 kJ or 0.752 MJ
e) $235 \mu\text{H}$ or 0.235 mH

- $P = v \cdot i$
2-21) a) 72.6 W from B to A
b) 14.4 mW " A " B
c) 1.5 W " A " B
d) 645 mW " A " B

- 3-28) a) to recharge, requires $75 \text{ A} \cdot 6 \text{ h} = 450 \text{ A} \cdot \text{h}$

$$\text{efficiency} = \frac{\text{output}}{\text{input}} = \boxed{88.9\%}$$

$$b) w = \int p dt = \int v \cdot i dt$$

$V \& i$ constant ($V = 24 \text{ V}$, $i = 75 \text{ A}$), so
need Δt in seconds!
 $= V \cdot i \cdot \Delta t$
 $= 24 \text{ V} \cdot 75 \text{ A} \cdot 6 \text{ h} \cdot \frac{60 \text{ min}}{1 \text{ hr.}} \cdot \frac{60 \text{ s}}{1 \text{ min.}}$
 $= \boxed{38.88 \text{ MJ}}$

4
2-10) Ohm's Law:
 $v = i \cdot R$

Given:

$$R = 0.3 T_c + 100$$

$$i = 1 \text{ mA}$$


$$T_c = 400^\circ \text{C}$$

$$= 1 \text{ mA} \cdot (0.3 \cdot 400 + 100) \Omega$$

$$= (120 + 100) \text{ mV}$$

$$= \boxed{220 \text{ mV or } 0.22 \text{ V}}$$

6)
2-17)

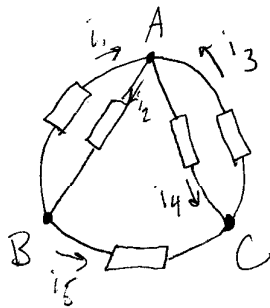

Given: $i_1 = 2 \text{ A}$

$$i_2 = -5 \text{ A}$$

$$i_3 = 4 \text{ A}$$

KCL at node B:

$$-i_1 + i_2 - i_5 = 0$$

$$i_5 = i_2 - i_1$$

$$= -5 \text{ A} - 2 \text{ A}$$

$$\boxed{i_5 = -7 \text{ A}}$$

KCL at node C:


$$-i_3 + i_4 + i_5 = 0$$

$$i_4 = i_3 - i_5$$

$$= 4 \text{ A} - (-7 \text{ A})$$


$$\boxed{i_4 = 11 \text{ A}}$$

7
2-18)

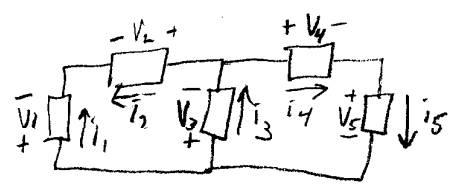

one other possibility:
Reverse ~~ALL~~ voltage signs AND
ALL current directions

5
2-16)

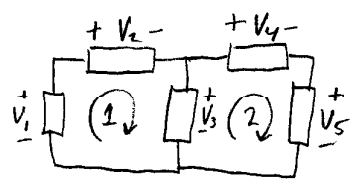

KVL around loop 1

$$-V_1 + V_2 + V_3 = 0$$

$$V_2 = V_1 - V_3$$

$$= 5V - (-10V)$$

$$\boxed{V_2 = 15V}$$

Given: $V_1 = 5V$

$$V_3 = -10V$$

$$V_4 = 10V$$

KVL around loop 2

$$-V_3 + V_4 + V_5 = 0$$

$$V_5 = V_3 - V_4$$

$$= -10V - 10V$$

$$\boxed{V_5 = -20V}$$