

$$\begin{aligned} 3-10) \text{ a) } A: (2k\Omega + 2k\Omega + 2k\Omega)i_A - 2k\Omega i_B &= 5V - 15V \\ 6k\Omega i_A - 2k\Omega i_B &= -10V \\ B: (2k\Omega + 4k\Omega + 4k\Omega)i_B - 2k\Omega i_A &= 15V \\ -2k\Omega i_A + 10k\Omega i_B &= 15V \end{aligned}$$

$$\begin{aligned} \text{b) from } A: i_B &= 5mA + 3i_A \\ \text{into } B: -2k\Omega i_A + 10k\Omega (5mA + 3i_A) &= 15V \\ -2k\Omega i_A + 50V + 30k\Omega i_A &= 15V \\ 28k\Omega i_A &= -35V \\ i_A &= -\frac{5}{4}mA = -1.25mA \\ i_B &= 5mA + 3\left(-\frac{5}{4}mA\right) \\ &= 5mA - \frac{15}{4}mA \\ &= \frac{5}{4}mA = 1.25mA \end{aligned}$$


$$\begin{aligned} V_X &= 4k\Omega \cdot i_B \\ &= 4k\Omega \cdot 1.25mA \end{aligned}$$

$$\boxed{V_X = 5V}$$

$$\begin{aligned} i_X &= i_B - i_A \\ &= 1.25mA - (-1.25mA) \end{aligned}$$

$$\boxed{i_X = 2.5mA}$$

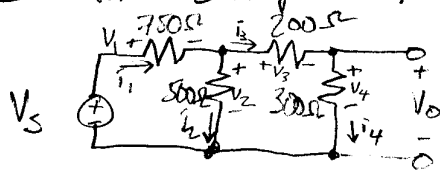2) 3-27 use unit output method: let $V_o = 1V$



$$\text{KVL } V_1 = V_o = 1V$$

$$\text{Ohm's } i_4 = \frac{1V}{300\Omega} = 3.33mA$$

$$\text{KCL } i_3 = i_4 = 3.33mA$$

$$\text{Ohm's } V_3 = i_3 \cdot 200\Omega = 667mV$$

$$\text{KVL } V_2 = V_3 + V_4 = 1.67V$$

$$\text{Ohm's } i_2 = \frac{V_2}{500\Omega} = 3.33mA$$

$$\text{KCL } i_1 = i_2 + i_3 = 6.67mA$$

$$\text{Ohm's } V_1 = i_1 \cdot 750\Omega = 5V$$




$$\text{KVL } V_s = V_1 + V_2 = 6.67V$$

$$K = \frac{V_o}{V_s}$$

$$\boxed{K = .15}$$

3-28)

due to voltage source:

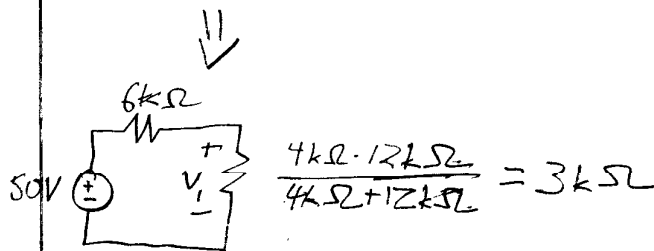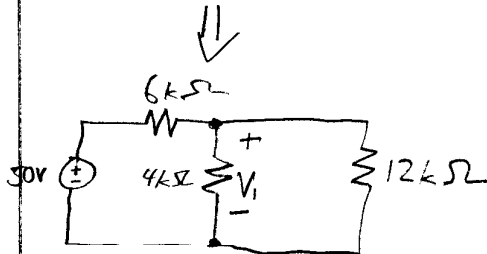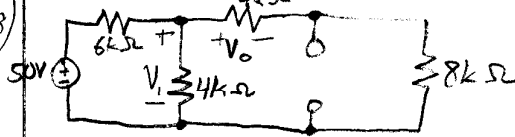

Voltage Division $V_1 = 50V \cdot \frac{3k\Omega}{3k\Omega + 6k\Omega}$
 $= 16.67V$




Voltage Division $V_0 = 16.67V \cdot \frac{4k\Omega}{4k\Omega + 12k\Omega}$
 $= 5.56V$

$V_0 = 5.56V - 10V$

$V_0 = -4.44V$

3-28

due to current source:

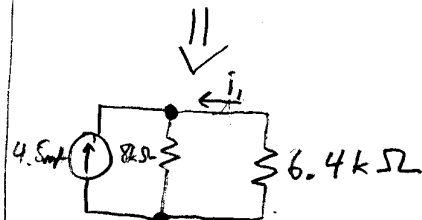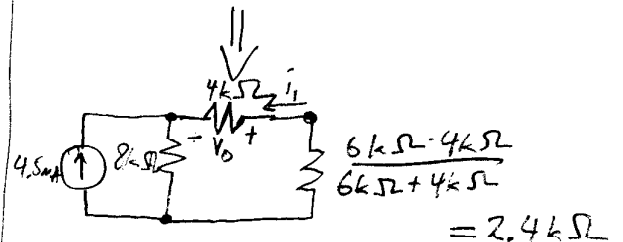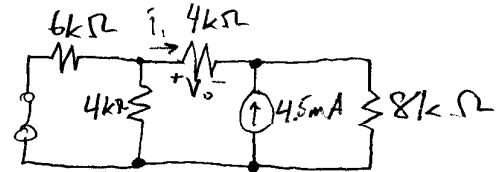

Current Division: $-i_1 = 4.5mA \cdot \frac{8k\Omega}{8k\Omega + 6.4k\Omega}$
 $i_1 = -2.5mA$

$V_0 = -2.5mA \cdot 4k\Omega$
 $= -10V$

4) Answer is not 4.25W because superposition applies to currents + voltages, not power

$$P_1 = i_1^2 \cdot R$$

$$250 \text{ mV} = i_1^2 \cdot 100 \Omega$$

$$2500 (\text{mA})^2 = i_1^2$$

$$i_1 = 50 \text{ mA}$$

$$P_2 = i_2^2 R$$

$$i_2^2 \cdot 100 \Omega = 4 \text{ W}$$



$$i_2^2 = .04 (\text{A})^2$$

$$i_2 = .2 \text{ A}$$

$$i = i_1 + i_2 = 250 \text{ mA}$$

$$P = i^2 R$$



$$P = 6.25 \text{ W}$$

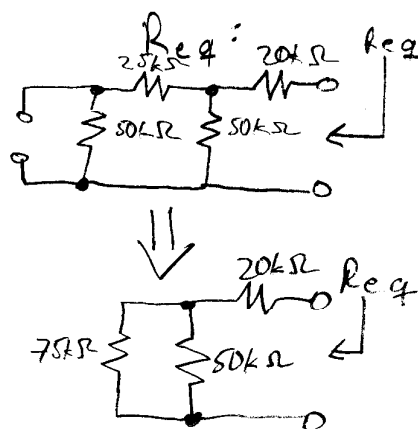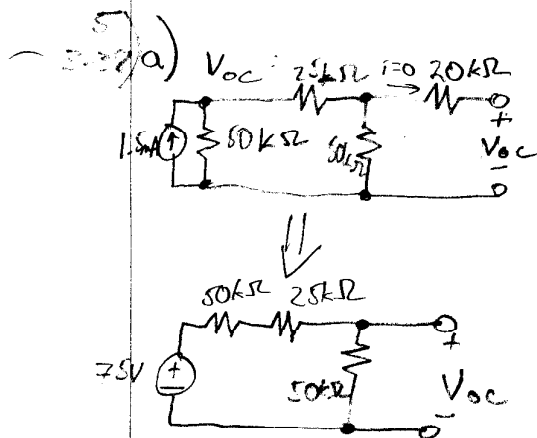

Voltage Division:

$$V_{oc} = 75 \text{ V} \cdot \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 25 \text{ k}\Omega + 50 \text{ k}\Omega}$$

$$= 30 \text{ V} = V_T$$

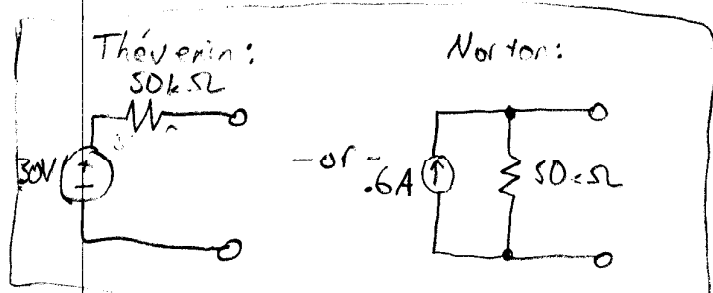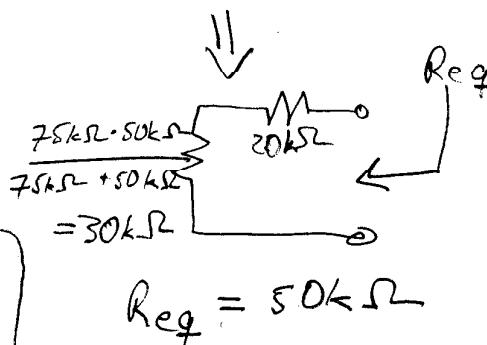

5
3-38
cont.

b) by voltage division: $V_L = V_T \frac{R_L}{R_T + R_L}$
 $= 30V \cdot \frac{R_L}{50k\Omega + R_L}$

$10k\Omega: V_L = 5V$

$25k\Omega: V_L = 10V$

$50k\Omega: V_L = 15V$

$100k\Omega: V_L = 20V$

6)
3-43

knowing $V = V_T - i R_T$
 $i R_L = V_T - i R_T$

$9V = V_T - .03A \cdot R_T$ and $10V = V_T - .02A \cdot R_T$

$-9V = -V_T + .03A \cdot R_T$


$1V = .01A \cdot R_T$

$100\Omega = R_T$

$10V = V_T - .02A \cdot 100\Omega$

$= V_T - 2V$

$V_T = 12V$

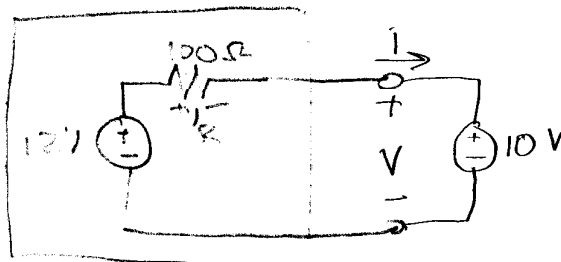

KVL: $12V = V_R + 10V$

$V_R = 2V$

Ohm's: $i = \frac{V_R}{100\Omega}$

$i = 20mA$