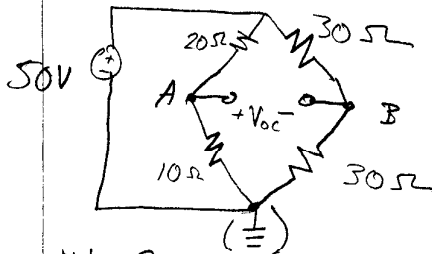


3-5) find V_{oc} :

R_{eq} :



Voltage Division:



$$V_A = 50V \cdot \frac{10\Omega}{10\Omega + 20\Omega} = 16.7V$$

$$V_B = 50V \cdot \frac{30\Omega}{30\Omega + 30\Omega} = 25V$$

$$V_{oc} = -8.3V = V_T$$

$$P_{max} = \frac{V_T^2}{4R_T}$$

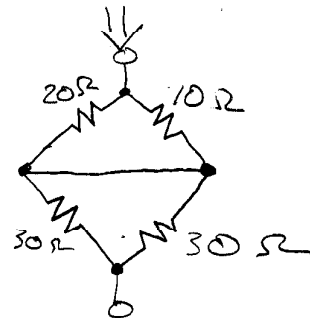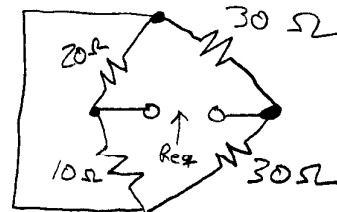
$$P_{max} = 0.801W \quad \text{for } R_L = R_{eq} = 21.67\Omega \quad R_{eq} = 21.67\Omega = R_T$$



$$20\Omega \parallel 10\Omega = 6.67\Omega$$

$$30\Omega \parallel 30\Omega = 15\Omega$$

3-7) a)

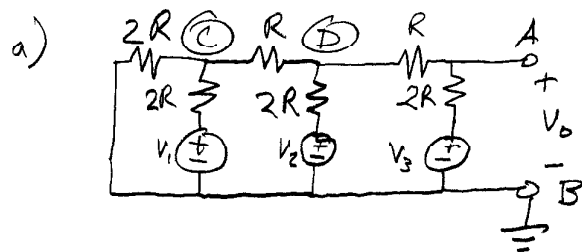

central nodes can be ignored, have node-voltage of adjacent source

$$A: \left(\frac{1}{R} + \frac{1}{2R}\right)V_o - \frac{1}{R}V_D - \frac{1}{2R}V_3 = 0$$

$$C: \left(\frac{1}{2R} + \frac{1}{2R} + \frac{1}{R}\right)V_C - \frac{1}{R}V_D - \frac{1}{2R}V_1 = 0$$

$$D: -\frac{1}{R}V_o - \frac{1}{R}V_C + \left(\frac{1}{R} + \frac{1}{2R} + \frac{1}{R}\right)V_D - \frac{1}{2R}V_2 = 0$$

2
OF
4

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{2R} & 0 & -\frac{1}{R} \\ 0 & \frac{1}{2R} + \frac{1}{2R} + \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & -\frac{1}{R} & \frac{1}{R} + \frac{1}{2R} + \frac{1}{R} \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{2R} V_3 \\ \frac{1}{2R} V_1 \\ \frac{1}{2R} V_2 \end{bmatrix}$$

Cramer's Rule: $V_0 = \frac{\Delta_{V_0}}{\Delta}$

$$\Delta_{V_0} = \begin{vmatrix} \frac{V_3}{2R} & 0 & -\frac{1}{R} \\ \frac{V_1}{2R} & \frac{2}{R} & -\frac{1}{R} \\ \frac{V_2}{2R} & -\frac{1}{R} & \frac{5}{2R} \end{vmatrix} = \frac{10V_3}{4R^3} + 0 + \frac{V_1}{2R^3} + \frac{2V_2}{2R^3} - \frac{V_3}{2R^3} - 0$$



$$= \frac{2V_1 + 4V_2 + 8V_3}{4R^3} = \frac{V_1 + 2V_2 + 4V_3}{2R^3}$$



$$\Delta = \begin{vmatrix} \frac{3}{2R} & 0 & -\frac{1}{R} \\ 0 & \frac{2}{R} & -\frac{1}{R} \\ -\frac{1}{R} & -\frac{1}{R} & \frac{5}{2R} \end{vmatrix} = \frac{30}{4R^3} + 0 + 0 - \frac{2}{R^3} - \frac{3}{2R^3} - 0$$

$$= \frac{8}{2R^3}$$

$$V_0 = \frac{V_1 + 2V_2 + 4V_3}{8}$$
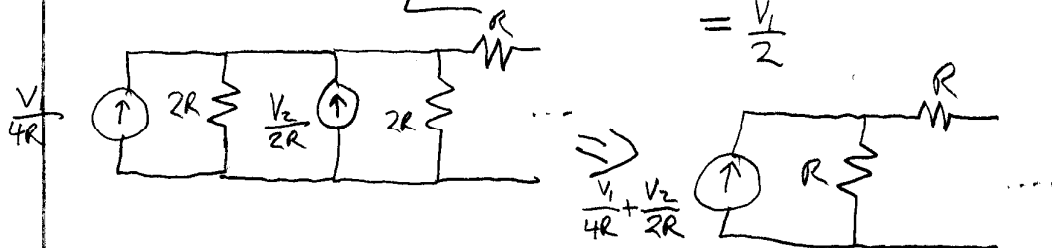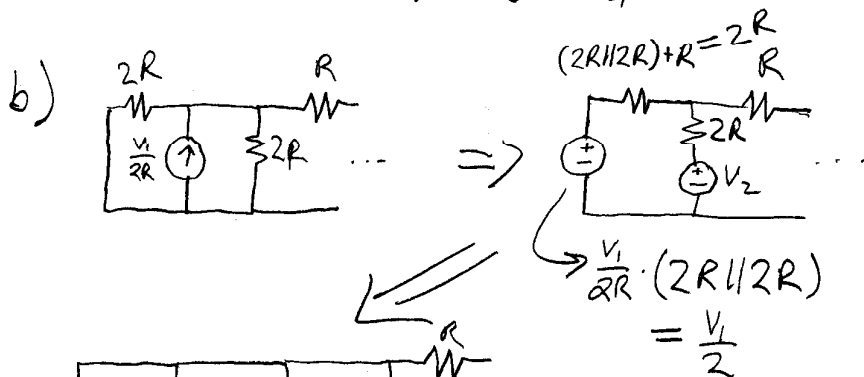
$$= \frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2} \quad \text{g.e.d.}$$



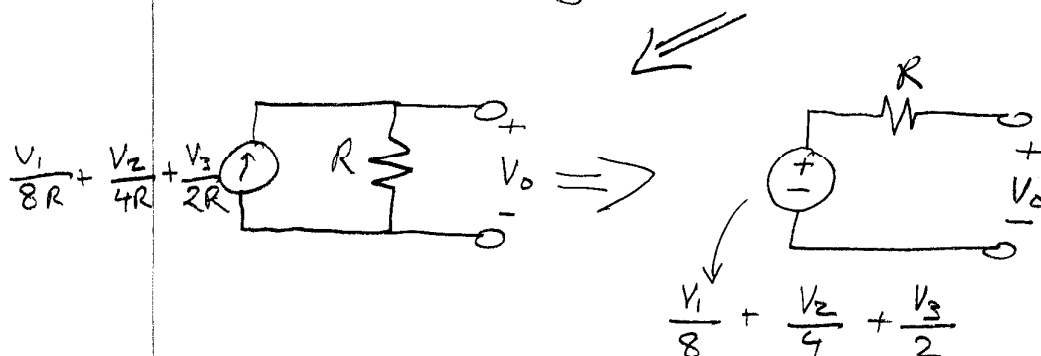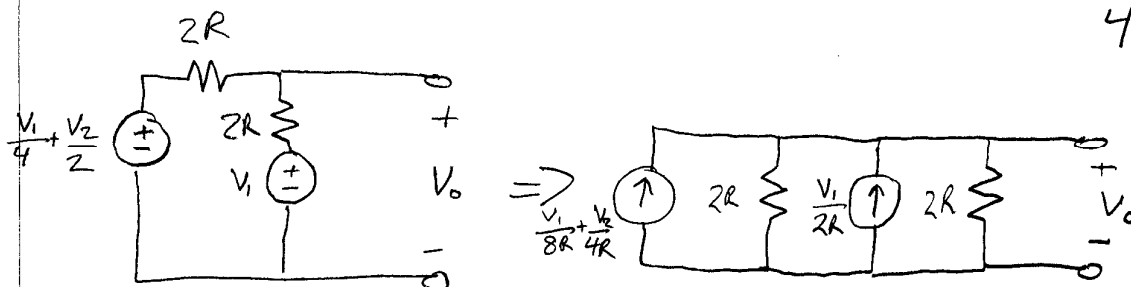

Since no load (open circuit)

$$V_0 = \frac{V_1}{8} + \frac{V_2}{4} + \frac{V_3}{2}$$
 g.e.d.

c) either is acceptable, with explanation

$$\begin{aligned} 3) \\ 4-2) \quad V_1 &= i_1 \cdot 100 \Omega \\ &= i_s \cdot 50 \Omega \end{aligned}$$

$$\begin{aligned} \text{current division: } i_1 &= i_s \frac{100 \Omega}{100 \Omega + 100 \Omega} \\ &= \frac{i_s}{2} \end{aligned}$$

$$\begin{aligned} V_0 &= i_0 \cdot 2 \text{ k}\Omega \\ &= -i_s \cdot 3.33 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \text{current division: } i_0 &= -10 i_1 \cdot \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 2 \text{ k}\Omega} \\ &= -3.33 i_1 \\ &= -1.67 i_s \end{aligned}$$

$$\boxed{\frac{i_0}{i_s} = -1.67}$$

$$\frac{V_0}{V_s} = \frac{-3.33 \text{ k}\Omega}{50 \Omega}$$

$$\boxed{\frac{V_0}{V_s} = -66.7}$$

$$\begin{aligned} p &= i v \\ &= i_s^2 \cdot 50 \Omega \end{aligned}$$

$$\boxed{P = 200 \mu\text{W}} \\ \text{supplied}$$

$$= i_s^2 \cdot 5.56 \text{ k}\Omega$$

$$\boxed{P = 22.2 \text{ mW}} \\ \text{delivered}$$

4-5) a) by KVL: $V_1 = V_{RE}$
 by Ohm's Law: $(i_s - i_x) 5k\Omega = (i_x + 199i_x) 450\Omega$
 $5000i_s - 5000i_x = 90000i_x$
 $5000i_s = 95000i_x$
 $i_x = \frac{i_s}{19}$

$i_2 = -199i_x$

$i_2 = -262\mu A$

$V_2 = i_2 \cdot 1k\Omega = -262mV$
 $V_1 = (i_s - i_x) 5k\Omega = 118mV$

$\frac{V_2}{V_1} = -2.21$

b) $i_1 = i_x = 1.32\mu A$

$R_{in} = 90k\Omega$

5-12) by KVL: $V_s = V_x - \mu V_x$
 $V_x(1 - \mu) = V_s$
 $V_x = \frac{V_s}{1 - \mu}$

$V_{oc} = -\mu V_x = \frac{-\mu V_s}{1 - \mu}$

$i_{sc} = -\frac{\mu V_x}{R_o}$

$R_T = \frac{V_{oc}}{i_{sc}}$
 $= \frac{-\mu V_x}{-\mu V_x / R_o}$
 $= R_o$

