
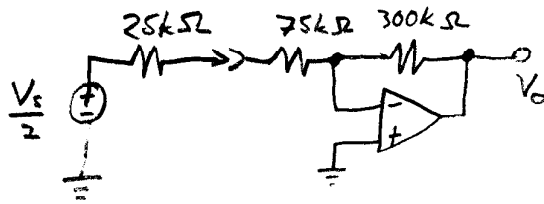


102) 4-21) first, reduce circuit:

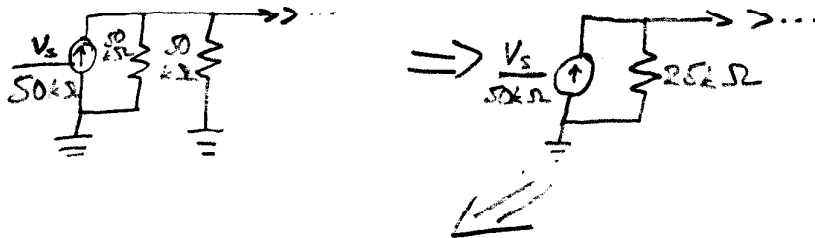

with $25k\Omega$ and $75k\Omega$ in series (100k),

Inverter:

$$V_o = K \frac{V_s}{2}$$

$$K = - \frac{300k\Omega}{100k\Omega}$$

$$= -3$$

$$V_o = -\frac{3}{2} V_s$$

3) 4-27) since no current into positive terminal, can treat

$$V_p = V_{s2} + V_{R2}$$

$$= V_{s2} + (V_{s1} - V_{s2}) \frac{R_2}{R_1 + R_2}$$

$$= V_{s2} \left(\frac{R_1 + R_2}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} \right) + V_{s1} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$= \frac{V_{s1} R_2 + V_{s2} R_1}{R_1 + R_2} = V_N$$


$V_{s1} - V_{s2}$ as voltage divider

again, along top:

$$V_N = V_o \cdot \frac{R_3}{R_3 + R_4}$$

$$V_o = \frac{R_3 + R_4}{R_3} \left(\frac{V_{s1} R_2 + V_{s2} R_1}{R_1 + R_2} \right)$$



4)
4-29) redraw:

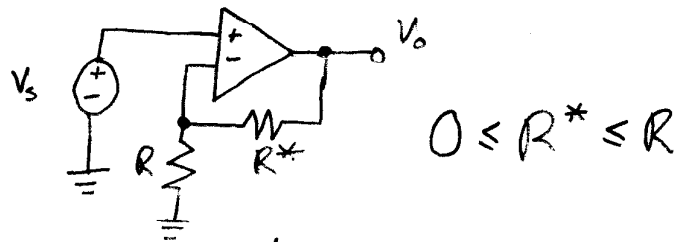

$$0 \leq R^* \leq R$$


gain Non inverter:
 $K = \frac{R^* + R}{R}$

$$1 \leq K \leq 2$$

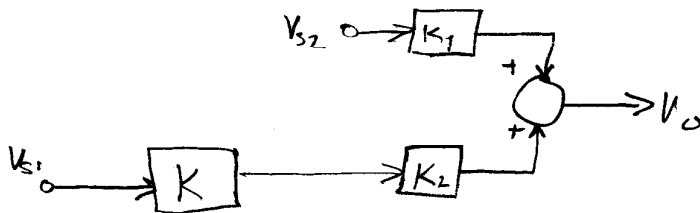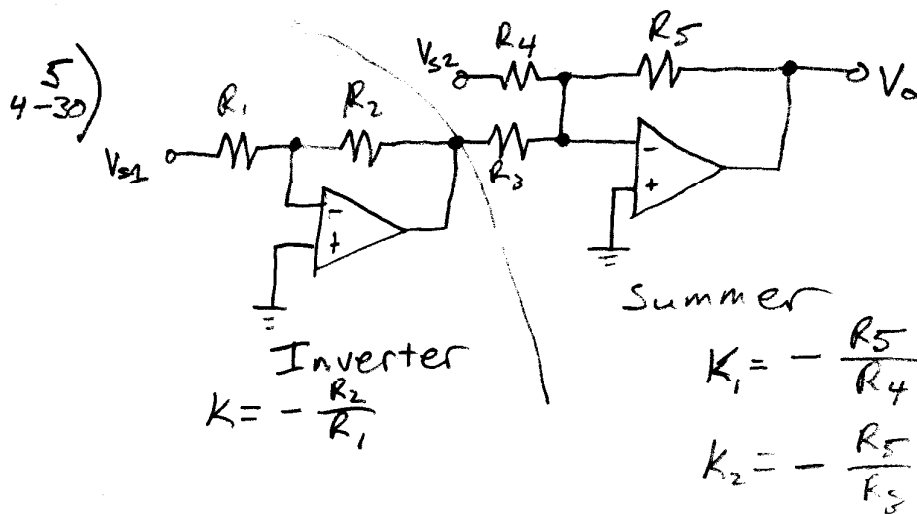

$$V_o = \frac{R_2 R_5}{R_1 R_3} V_{s1} - \frac{R_5}{R_4} V_{s2}$$

W07W

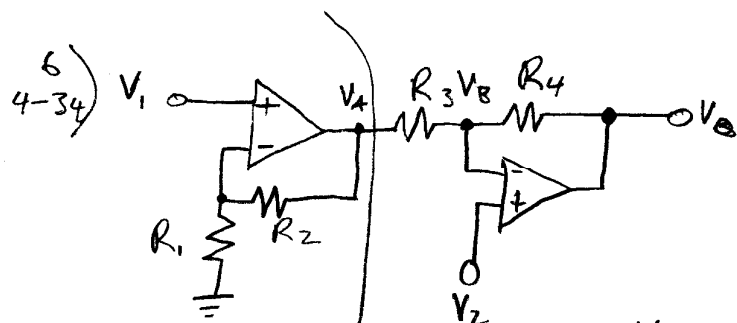

Non inverter

$$K = \frac{R_1 + R_2}{R_1}$$

NOT an Inverter

$$V_A = \frac{R_1 + R_2}{R_1} V_1 \quad V_B = V_2$$

Voltage division:

$$V_B - V_A = (V_0 - V_A) \left(\frac{R_3}{R_3 + R_4} \right)$$

$$V_B - V_A = V_0 \left(\frac{R_3}{R_3 + R_4} \right) - V_A \left(\frac{R_3}{R_3 + R_4} \right)$$

$$V_B + V_A \left(\frac{R_3}{R_3 + R_4} - \frac{(R_3 + R_4)}{R_3 + R_4} \right) = V_0 \frac{R_3}{R_3 + R_4}$$

$$V_B - V_A \frac{R_4}{R_3 + R_4} = V_0 \frac{R_3}{R_3 + R_4}$$

$$V_0 = V_B \frac{R_3 + R_4}{R_3} - V_A \frac{R_4}{R_3}$$

$$V_0 = V_2 \frac{R_3 + R_4}{R_3} - V_1 \frac{R_1 + R_2}{R_1} \frac{R_4}{R_3}$$