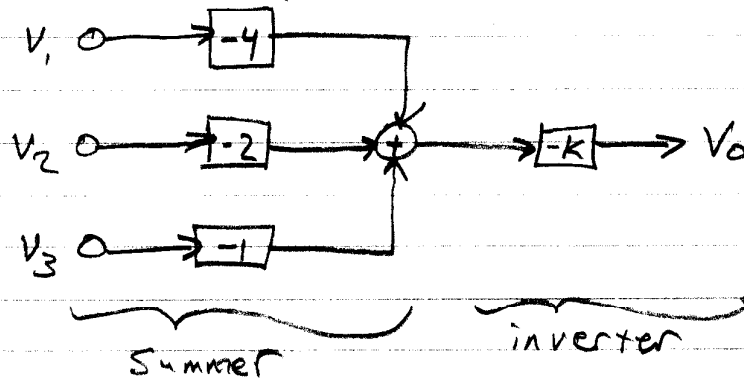


ENGR 210
FALL 2003
HOMEWORK #7 1 OF 3
SOLUTIONS

4-41) basic set-up:




want max $V_0 = 10V \Rightarrow$ occurs when all $v_{iA} = 5V$

$$\begin{aligned} 10V &= K(4 \cdot 5V + 2 \cdot 5V + 5V) \\ &= K(20V + 10V + 5V) \\ &= K(35V) \end{aligned}$$

$$K = \frac{2}{7}$$

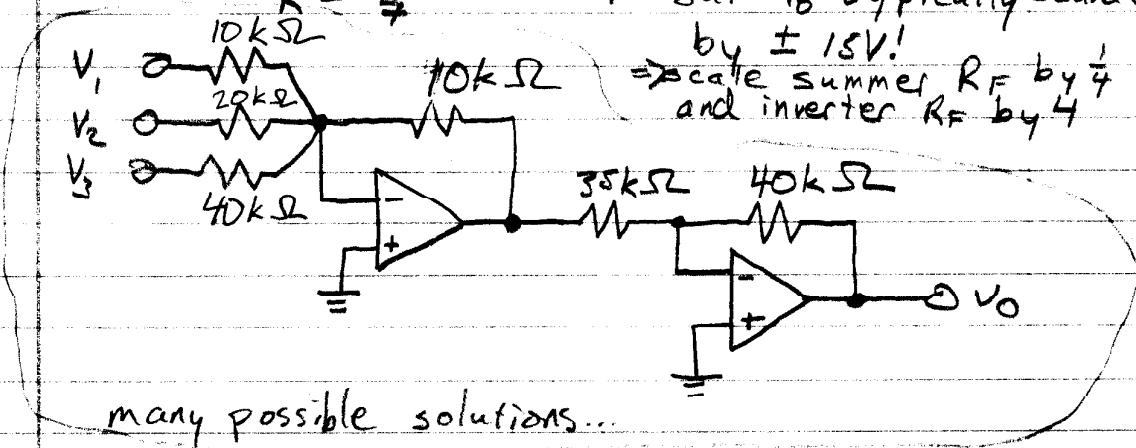but V_0 typically bounded by $\pm 15V!$
 $\Rightarrow$ scale summer R_F by $\frac{1}{4}$ and inverter R_F by 4



4-45) non-inverting Amp

for both open, R_0, R_1, R_2 in series, and

$$K = 10 = \frac{R_0 + R_1 + R_2 + R_3}{R_3}$$

for lower switch (actual S2) closed, R_2 shorted, and

$$K = 5 = \frac{R_0 + R_1 + R_3}{R_3}$$

for upper switch (S_1) closed, R_1 & R_2 shorted, regardless of actual S_2 's state, and

$$K = 2 = \frac{R_0 + R_3}{R_3}$$

$$2R_3 = R_0 + R_3$$

$$R_0 = R_3$$

$$5 = \frac{R_3 + R_1 + R_3}{R_3}$$

$$5R_3 = 2R_3 + R_1$$

$$R_1 = 3R_3$$

$$10 = \frac{R_3 + 3R_3 + R_2 + R_3}{R_3}$$

$$10R_3 = 5R_3 + R_2$$

$$R_2 = 5R_3$$

one possible set:

$$R_0 = 10 \text{ k}\Omega$$

$$R_1 = 30 \text{ k}\Omega$$

$$R_2 = 50 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$


$$V_N = -2 \text{ V}$$

a) $V_o = V_{OH}$ for $V_s > V_N$


$$V_o = V_{OH} \text{ for } V_s > -2 \text{ V}$$

$$V_o = V_{OL} \text{ for } V_s < -2 \text{ V}$$


b)

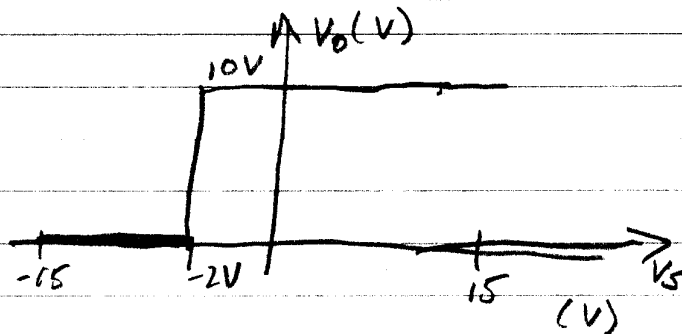

4)
4-57)

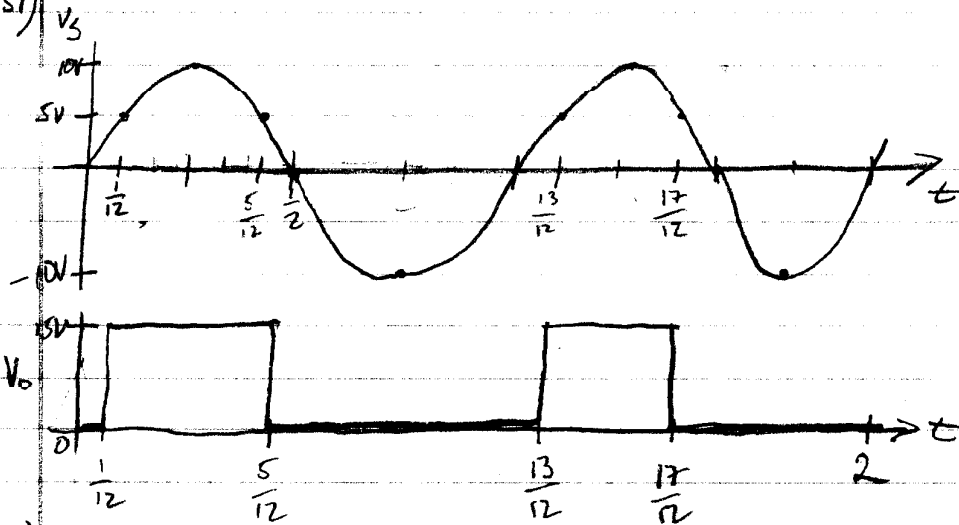

5)
4-58)

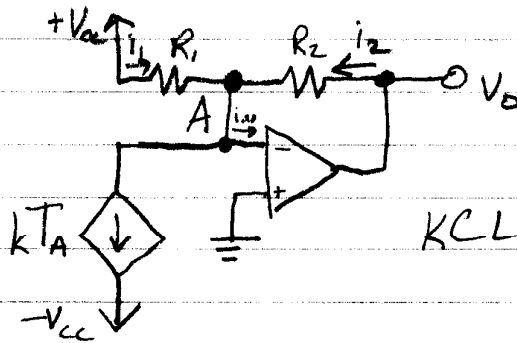

$$V_P = V_N = 0V$$

$$KCL @ A: i_1 + i_2 = kT_A + 0$$

$$\frac{V_{cc}}{R_1} + \frac{V_o}{R_2} = kT_A$$

$$\Delta V_o = k R_2 \Delta T_A$$

$$\frac{\Delta V_o}{\Delta T_A} = k R_2$$

$$\text{at } T_A = 0^\circ C = 273 K$$

$$V_o = 0V$$

$$\frac{V_{cc}}{R_1} + \frac{0V}{R_2} = kT_A$$

$$R_1 = \frac{V_{cc}}{kT_A}$$

$$= \frac{10V}{1\mu A \cdot 273K}$$

$$= \frac{10}{273} \frac{V}{\mu A}$$

$$\approx 0.0366 M\Omega$$

$$\approx 36.6 k\Omega$$

$$R_2 = \frac{\Delta V_o}{\Delta T_A} \cdot \frac{1}{k}$$

$$= \frac{100mV}{0.2} \cdot \frac{1}{1\mu A}$$

$$= 100 k\Omega$$

$$R_1 \approx 36.6 k\Omega$$

$$R_2 = 100 k\Omega$$