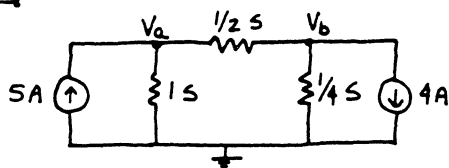


Chapter 4

Exercises

Ex. 4-1



KCL at V_a :

$$\begin{aligned} -5 + V_a + \frac{1}{2}(V_a - V_b) &= 0 \\ \underline{3V_a - V_b = 10} \quad (1) \end{aligned}$$


$$\text{KCL at } V_b: \frac{1}{2}(V_b - V_a) + \frac{1}{4}V_b + 4 = 0$$

$$\underline{-2V_a + 3V_b = -16} \quad (2)$$

Solving (1) & (2) simultaneously yields

$$\underline{V_a = 2\text{V}, V_b = -4\text{V}}$$

Ex. 4-2

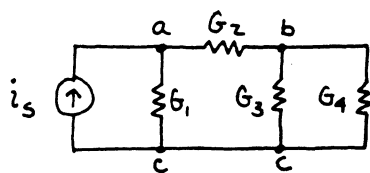

$$(1) \text{ KCL at } a: V_a(G_1 + G_2) - V_b G_2 - V_c G_1 = i_s$$

$$(2) \text{ KCL at } b: -V_a G_2 + V_b(G_2 + G_3 + G_4) - V_c(G_3 + G_4) = 0$$


$$(3) \text{ KCL at } c: -V_a G_1 - (G_3 + G_4)V_b + (G_1 + G_3 + G_4)V_c = -i_s$$

$$\text{To get (1)} \Rightarrow (1) = -(2) - (3)$$

$$\text{" " (2)} \Rightarrow (2) = -(1) - (3)$$

$$\text{" " (3)} \Rightarrow (3) = -(1) - (2)$$

Ex. 4-3

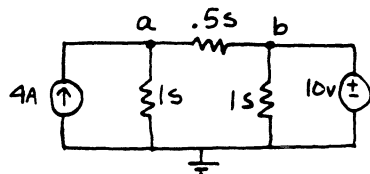


KCL at a :

$$-4 + V_a + .5(V_a - V_b) = 0$$

$$\Rightarrow V_a = \frac{.5V_b + 4}{1.5} = \frac{.5(10) + 4}{1.5} = \underline{6\text{V}}$$

Ex. 4-4

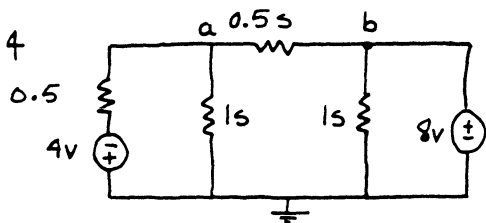


$$V_b = 8\text{V}$$

$$\text{KCL at } a: 0.5(V_a + 4) + V_a + 0.5(V_a - V_b) = 0$$

$$2V_a + 2 - (.5)(8) = 0$$

$$\Rightarrow \underline{V_a = 2/2 = 1\text{V}}$$

Ex. 4-5

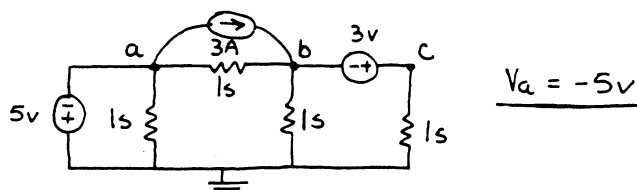


$$\text{KCL at } b: -3 + (V_b - V_a) + V_b + (V_b + 3) = 0$$

$$\text{With } V_a = -5 \Rightarrow \underline{V_b = -5/3 \text{ V}}$$

$$\text{also } V_c - V_b = 3 \Rightarrow \underline{V_c = 3 + V_b = 4/3 \text{ V}}$$

Ex. 4-6

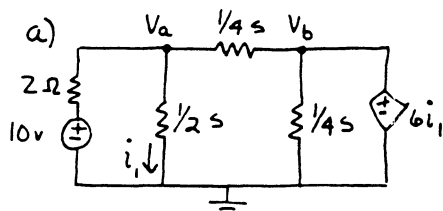

$$V_b = 6i_1 \quad (1)$$

$$V_a = 2i_1 \quad (2)$$

$$\text{KCL at } V_a: \frac{1}{2}(V_a - 10) + i_1 + \frac{1}{4}(V_a - V_b) = 0$$

$$\hookrightarrow 3V_a - V_b + 4i_1 - 20 = 0 \quad (3)$$

Solving (1), (2) & (3) simultaneously yields $V_b = 30 \text{ V}$

b) for element as current source, $i_s = 3V_a$

$$V_b = 6i_1 \quad (1)$$

$$V_a = 2i_1 \quad (2)$$


$$\text{KCL at } V_a: \frac{1}{2}(V_a - 10) + i_1 + i_s = 0$$

$$\hookrightarrow \frac{1}{2}(V_a - 10) + i_1 + 3V_a = 0$$

$$\hookrightarrow 4V_a + 4i_1 - 20 = 0 \quad (3)$$

Solving (1), (2) & (3) simultaneously yields $V_b = 15/4 \text{ V}$

Ex. 4-7

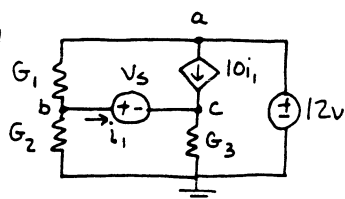

$$\text{KCL at } b: G_1(V_b - 12) + i_1 + G_2 V_b = 0 \quad (1)$$

$$\text{KCL at } c: -i_1 - 10i_1 + G_3 V_c = 0$$


$$\Rightarrow i_1 = \frac{G_3 V_c}{11} \quad (2)$$

$$\text{also } V_b - V_c = V_s \Rightarrow V_b = V_c + V_s \quad (3)$$

$$(2) \text{ into } (1) \text{ yields } (G_1 + G_2)V_b + \frac{G_3 V_c}{11} = 12 G_1 \quad (4)$$

$$(3) \text{ into } (4) \text{ and solving for } V_c \Rightarrow \underline{V_c = \frac{12 G_1 - (G_1 + G_2)V_s}{G_1 + G_2 + G_3/11}}$$

Ex. 4-8

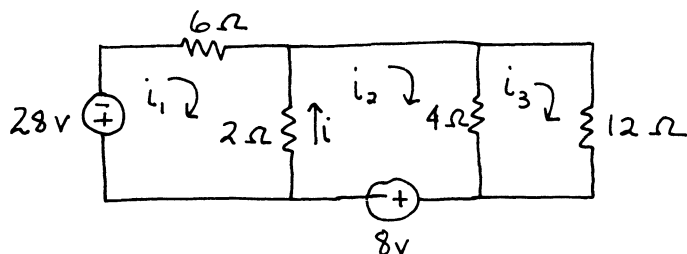

$$\text{KVL loop 1} \quad 28 + 6i_1 + 2(i_1 - i_2) = 0 \quad (1)$$

$$\text{KVL loop 2} \quad 2(i_2 - i_1) + 4(i_2 - i_3) + 8 = 0 \quad (2)$$


$$\text{KVL loop 3} \quad 12i_3 + 4(i_3 - i_2) = 0 \quad (3)$$

solving (1) - (3) simultaneously yields

$$i_1 = -\frac{13}{3} \text{ A}, \quad i_2 = -\frac{10}{3} \text{ A}, \quad i_3 = -\frac{5}{6} \text{ A}$$

$$\Rightarrow i = i_2 - i_1 = -\frac{10}{3} - \left(-\frac{13}{3}\right) = \underline{1 \text{ A}}$$

Ex. 4-9

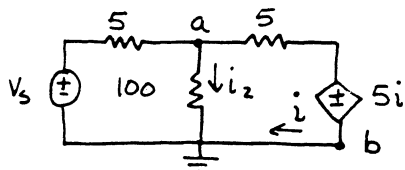

$$V_{ab} = 5i + 5i = 10i$$

$$\therefore P_{\text{motor}} = (V_{ab})i = 10i^2 = 150$$


$$\Rightarrow i = \sqrt{15} \text{ A}$$

$$\therefore V_{ab} = (10)(\sqrt{15}) \text{ V}$$

$$\Rightarrow i_2 = \frac{V_{ab}}{100} = \frac{\sqrt{15}}{10} \text{ A}$$

$$\text{KCL at a: } (V_{ab} - V_s)/5 + i_2 + i = 0 \Rightarrow \underline{V_s = \frac{31}{2}\sqrt{15} = 60.03 \text{ V}}$$

Ex. 4-10

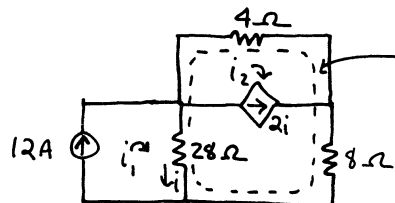

Supermesh

$$i_1 = 12 \text{ A} \quad (1)$$

KVL supermesh:

$$4i_2 + 8i_3 + 28(i_3 - 12) = 0 \quad (2)$$

$$\text{also: } 2i = i_3 - i_2 \quad (3)$$


solving (1) $\rightarrow$ (3) yields $i_3 = 9 \text{ A}$

$$\therefore \underline{i = 12 - 9 = 3 \text{ A}}$$

Ex. 4-11 (a) Nodal analysis since the other node is known ($=V_s$) thus only need one node eqn. at a.

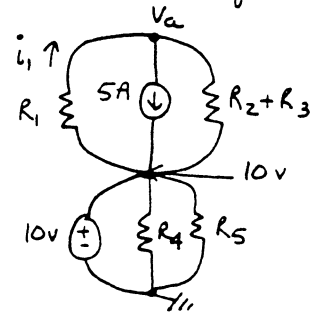
(b) Nodal analysis since when the circuit is redrawn (shown below), only one node eqn. at V_a is required.

Mesh analysis would require
4 mesh currents
 $\Rightarrow$ 4 unknowns.



Problems

P. 4-1

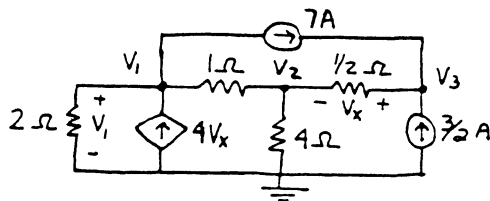

$$\text{KCL at } V_1 : \frac{V_1}{2} - 4V_x + 7 + (V_1 - V_2) = 0 \Rightarrow \underline{3V_1 - 2V_2 - 8V_x + 14 = 0} \quad (1)$$


$$\text{KCL at } V_2 : (V_2 - V_1) + \frac{V_2}{4} - 2V_x = 0 \Rightarrow \underline{-4V_1 + 5V_2 - 8V_x = 0} \quad (2)$$

$$\text{KCL at } V_3 : -7 + 2V_x - \frac{3}{2} = 0 \Rightarrow \underline{4V_x - 17 = 0} \quad (3)$$

Solving (1), (2) and (3) simultaneously yields

$$\underline{V_1 = 24 \text{ V}}$$

P. 4-2

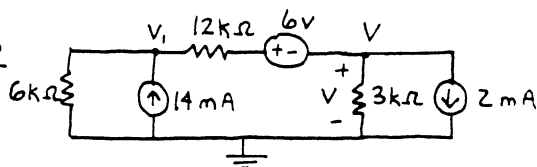


$$\begin{aligned} \text{KCL at } V_1 : \frac{V_1}{6} - 14 + \frac{(V_1 - 6 - V)}{12} &= 0 \\ \Rightarrow \underline{3V_1 - V - 174} &= 0 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{KCL at } V : -\frac{(V_1 - 6 - V)}{12} + \frac{V}{3} + 2 &= 0 \\ \Rightarrow \underline{-V_1 + 5V + 30} &= 0 \end{aligned} \quad (2)$$

solving (1) & (2) simultaneously yields $\underline{V = 6 \text{ volts}}$

P. 4-3

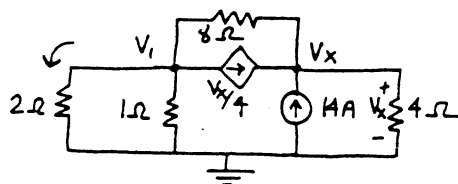

$$\text{KCL at } V_1: V_1/2 + V_1/1 + (V_1 - V_x)/8 + V_x/4 = 0$$

$$\Rightarrow 13V_1 + V_x = 0 \quad (1)$$


$$\text{KCL at } V_x: (V_x - V_1)/8 - V_x/4 - 4 + V_x/4 = 0$$

$$\Rightarrow -V_1 + V_x - 112 = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields $V_x = 104 \text{ V}$
and $V_1 = -8 \text{ V}$

$$\therefore P_{2\Omega} = \frac{V_1^2}{R} = \frac{(8)^2}{2} = 32 \text{ W}$$

P. 4-4

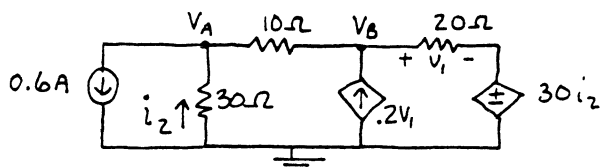


$$\text{KCL at } V_A: 6 - i_2 + \frac{(V_A - V_B)}{10} = 0 \quad (1)$$

$$\text{KCL at } V_B: \frac{(V_B - V_A)}{10} - 0.2V_1 + V_1/20 = 0 \quad (2)$$

$$\text{also } V_B - 30i_2 = V_1 \quad (3) \text{ and } V_A = -30i_2 \quad (4)$$

Solving (1) through (4) simultaneously yields
 $V_1 = 72/19 \text{ V}$, $i_2 = 3/95 \text{ A}$

P. 4-5

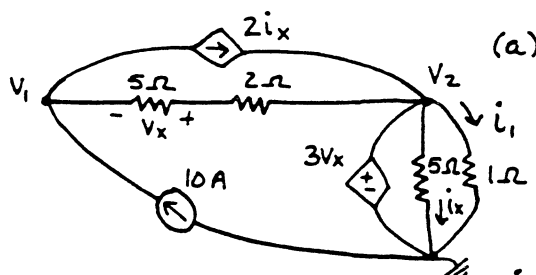

$$\text{KCL at } V_1: 10 - 2i_x + V_x/5 = 0$$

$$\Rightarrow V_x - 10i_x + 50 = 0 \quad (1)$$

$$\text{also } 3V_x = 5i_x \quad (2)$$

$\therefore$ solving for i_x & V_x
 $i_x = 6 \text{ A}$, $V_x = 10 \text{ V}$

P. 4-5 (continued)


$$(b) \ i_1 = \frac{V_2}{1} = 5i_x = 30A$$

$$\therefore P_{1\Omega} = i_1^2 R = (30)^2 (1) = \underline{900W}$$

$$\text{from KVL: } V_1 = 3V_x - V_x - 2(V_x/5) = 16V \quad \therefore \text{source is supplying power}$$

$$\therefore P_{\text{absorbed of source}} = -V_1 i_1 = - (16)(10) = \underline{-160W}$$

P. 4-6

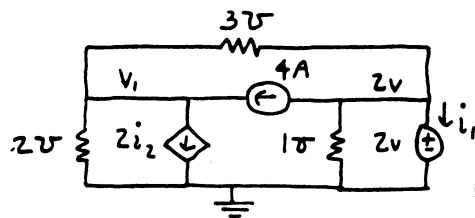

$$\text{KCL at } V_1: 2V_1 + 2i_2 - 4 + i_2 = 0$$

$$\downarrow \underline{2V_1 + 4i_2 - 4 = 0} \quad (1)$$

$$\text{KCL at } 2V: -i_2 + 4 + 2 + i_1 = 0$$


$$\downarrow \underline{-i_2 + 6 + i_1 = 0} \quad (2)$$

$$\text{also } \underline{3(V_1 - 2) = i_2} \quad (3)$$

Solving (1), (2) & (3) simultaneously yields

$$\underline{i_1 = -6A}$$

P. 4-7

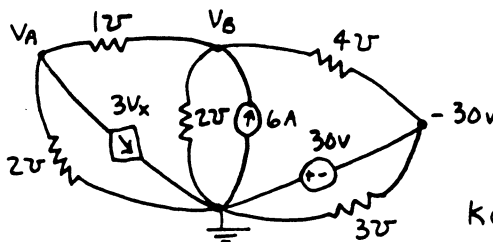

$$\text{KCL at } V_A: 2V_A + 3V_x + V_x = 0$$

$$\downarrow \underline{V_A + 2V_x = 0} \quad (1)$$

$$\text{KCL at } V_B: -V_x + 2V_B - 6 + 4(V_B + 30) = 0$$

$$\downarrow \underline{-V_x + 6V_B + 114 = 0} \quad (2)$$

$$\text{also } \underline{V_A - V_B = V_x} \quad (3)$$

Solving (1), (2) & (3) simultaneously yields

$$\underline{V_x = 6V}$$

P. 4-8

kVL around mesh i_1 & i_3 combined $\Rightarrow$

$$-3 + (i_1 - i_2) + 4(i_3 - i_2) + i_3 = 0$$

$$\Rightarrow \underline{3 - i_1 + 5i_2 - 5i_3 = 0} \quad (1)$$


kVL around mesh i_2 $\Rightarrow$

$$i_2 - i_1 + 2i_2 + 4(i_2 - i_3) = 0$$

$$\Rightarrow \underline{i_1 - 7i_2 + 4i_3 = 0} \quad (2)$$

also $\underline{i_1 - i_3 = 2} \quad (3)$

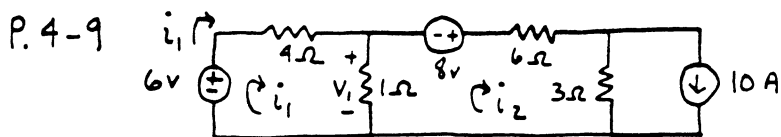solving (1), (2) & (3) simultaneously yields $\underline{i_1 = 3 \text{ mA}}$



kVL mesh i_1 : $-6 + 4i_1 + (i_1 - i_2) = 0 \Rightarrow \underline{-6 + 5i_1 - i_2 = 0} \quad (1)$

kVL mesh i_2 : $(i_2 - i_1) - 8 + 6i_2 + 3(i_2 - 10) = 0$

$$\Rightarrow \underline{-38 - i_1 + 10i_2 = 0} \quad (2)$$

solving (1) & (2) simultaneously yields $\underline{i_1 = 2 \text{ A}}$
and $i_2 = 4 \text{ A}$

$\therefore \underline{V_1 = 1(i_1 - i_2) = -2 \text{ V}}$

P. 4-10

kVL mesh i_1 : $2i_1 + 16 + 4i_x + 3(i_1 + i_x) = 0$

$$\Rightarrow \underline{5i_1 + 7i_x + 16 = 0} \quad (1)$$

kVL mesh i_2 : $-4i_x + 2i_2 - 8 = 0 \quad (2)$


kVL outer loop : $\underline{2i_1 + 16 + 2i_2 + 8i_4 - 6i_x = 0} \quad (3)$

also KCL bottom node : $\underline{i_4 + i_x - 1 = 0} \quad (4)$

solving (1), (2), (3) & (4) simultaneously $\Rightarrow \underline{i_x = 2 \text{ mA}}, i_2 = 8 \text{ mA}, i_4 = -1 \text{ mA}$

$\therefore i_{\text{thru } 8\text{V}} = i_2 - i_4 = 9 \text{ mA} \therefore P_{\text{supplied by } 8\text{V}} = V i = (8)(9) = \underline{72 \text{ mW}}$

P. 4-11

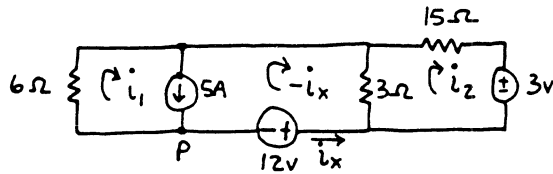


$$\text{KVL mesh } i_1, -i_x \text{ (P)}: 6i_1 + 3(-i_x - i_2) + 12 = 0 \quad (1)$$

$$\begin{aligned} \text{KVL mesh } i_2: 3(i_2 + i_x) + 15i_2 + 3 &= 0 \\ 18i_2 + 3i_x + 3 &= 0 \end{aligned} \quad (2)$$

$$\text{from KCL at P: } i_1 + i_x = 5 \quad (3)$$

solving (1), (2) & (3) simultaneously yields $i_x = 5A$

P. 4-12

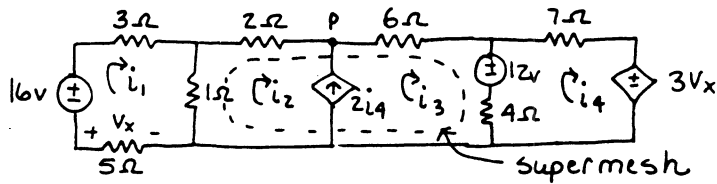


$$\begin{aligned} \text{KVL mesh } i_1 \text{ (P)}: -16 + 3i_1 + 1(i_1 - i_2) + 5i_1 &= 0 \\ \Rightarrow -9i_1 + i_2 &= -16 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{KVL supermesh (P)}: 1(i_2 - i_1) + 2i_2 + 6i_3 + 12 + 4(i_3 - i_4) &= 0 \\ \Rightarrow i_1 - 3i_2 - 10i_3 + 4i_4 &= 12 \end{aligned} \quad (2)$$

$$\begin{aligned} \text{KVL mesh } i_4 \text{ (P)}: 7i_4 + 3V_x + 4(i_4 - i_3) - 12 &= 0 \quad \text{also } V_x = -5i_1 \\ \Rightarrow 15i_1 + 4i_3 - 11i_4 &= -12 \end{aligned} \quad (3)$$

$$\text{KCL at P: } i_2 + 2i_4 - i_3 = 0 \quad (4)$$

P. 4-13

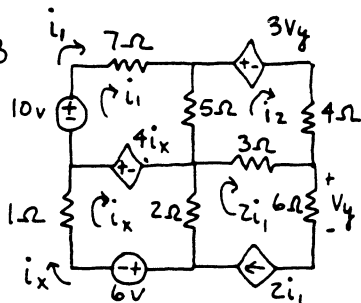


$$\begin{aligned} \text{mesh } i_1 \text{ (P)}: -10 + 7i_1 + 5(i_1 - i_2) - 4i_x &= 0 \\ \Rightarrow 12i_1 - 5i_2 - 4i_x &= 10 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{mesh } i_2 \text{ (P)}: 3V_y + 4i_2 + 3(i_2 - 2i_1) + 5(i_2 - i_1) &= 0 \\ \text{with } V_y = 12i_1 \\ \Rightarrow 25i_1 + 12i_2 &= 0 \end{aligned} \quad (2)$$

$$\begin{aligned} \text{mesh } i_x \text{ (P)}: i_x + 4i_x + 2(i_x - 2i_1) + 6 &= 0 \\ \Rightarrow 4i_1 - 7i_x &= 6 \end{aligned} \quad (3)$$


P. 4-14

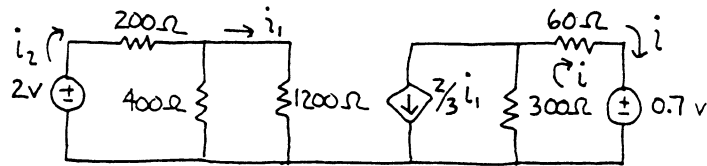

from voltage divider $1200i_1 = 2 \left(\frac{400 \parallel 1200}{400 \parallel 1200 + 200} \right) = 2 \left(\frac{3}{5} \right) = 1.2$
 $\therefore i_1 = .001 \text{ A}$

KVL mesh i : $60i + .7 + 300(i + \frac{3}{5}i_1) = 0$
 $\Rightarrow \underline{i = -.0025 \text{ A}}$

P. 4-15

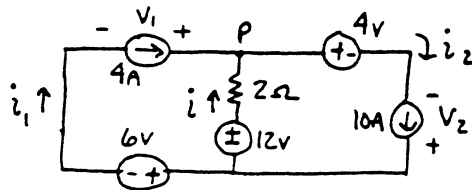

KCL at P: $i = i_2 - i_1$
 $i = 10 - 4 = 6 \text{ A}$

KVL i_1 : $-V_1 - 2i + 12 + 6 = 0 \Rightarrow V_1 = 18 - 2(6) = 6 \text{ V}$

KVL i_2 : $4 - V_2 - 12 + 2i = 0 \Rightarrow V_2 = -8 + 2(6) = 4 \text{ V}$

$\therefore P_{6V} = V_1 i_1 = (6)(4) = \underline{24 \text{ W}}$

$P_{4A} = -V_1 i_1 = -(6)(4) = \underline{-24 \text{ W}}$

$P_{2\Omega} = i^2 R = (6)^2 (2) = \underline{72 \text{ W}}$


$P_{12V} = -V i = -(12)(6) = \underline{-72 \text{ W}}$

$P_{4V} = V i_2 = (4)(10) = \underline{40 \text{ W}}$

$P_{10A} = -V_2 i_2 = -(4)(10) = \underline{-40 \text{ W}}$

Power absorbed

P. 4-16

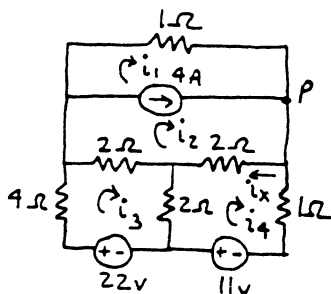

use mesh analysis

KVL i_3 : $4i_3 + 2(i_3 - i_2) + 2(i_3 - i_4) - 22 = 0$
 $\hookrightarrow \underline{2i_2 - 8i_3 + 2i_4 + 22 = 0} \quad (1)$

KVL i_4 : $2(i_4 - i_2) + i_4 - 11 + 2(i_4 - i_3) = 0$
 $\hookrightarrow \underline{2i_2 + 2i_3 - 5i_4 + 11 = 0} \quad (2)$

KVL i_1 & i_2 : $i_1 + 2(i_2 - i_4) + 2(i_2 - i_3) = 0$

$\Rightarrow \underline{i_1 + 4i_2 - 2i_3 - 2i_4 = 0} \quad (3)$


P. 4-16 continued

also $\underline{i_1 - i_2 + 4 = 0} \quad (4)$

and $\underline{i_2 - i_4 - i_x = 0} \quad (5)$

Solving (1) $\rightarrow$ (5) simultaneously yields $\underline{i_x = -1A}$

P. 4-17

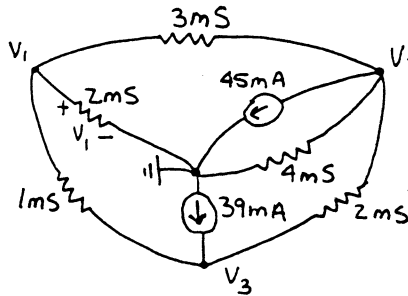


KCL at V_1 : $(V_1 - V_3) + 2V_1 + 3(V_1 - V_2) = 0$
 $\downarrow$ $\underline{6V_1 - 3V_2 - V_3 = 0} \quad (1)$

KCL at V_2 : $3(V_2 - V_1) + 45 + 4V_2 + 2(V_2 - V_3) = 0$
 $\downarrow$ $\underline{3V_1 - 9V_2 + 2V_3 - 45 = 0} \quad (2)$

KCL at V_3 : $(V_3 - V_1) - 39 + 2(V_3 - V_2) = 0 \Rightarrow \underline{V_1 + 2V_2 - 3V_3 + 39 = 0} \quad (3)$

Solving (1), (2) & (3) simultaneously yields $\underline{V_1 = 1V}$

P. 4-18

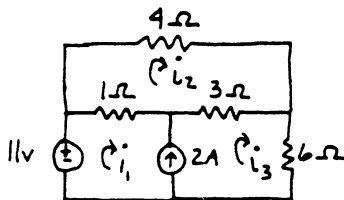


KVL mesh i_1 & i_3
 $-11 + (i_1 - i_2) + 3(i_3 - i_2) + 6i_3 = 0$
 $\downarrow$ $\underline{i_1 - 4i_2 + 9i_3 - 11 = 0} \quad (1)$

KVL mesh i_2 : $4i_2 + 3(i_2 - i_3) + (i_2 - i_1) = 0$
 $\downarrow$ $\underline{i_1 - 8i_2 + 3i_3 = 0} \quad (2)$

KCL at middle node: $\underline{i_1 + 2 - i_3 = 0} \quad (3)$

Solving (1), (2) & (3) simultaneously yields $\underline{i_1 = -1/2 A}$

P. 4-19

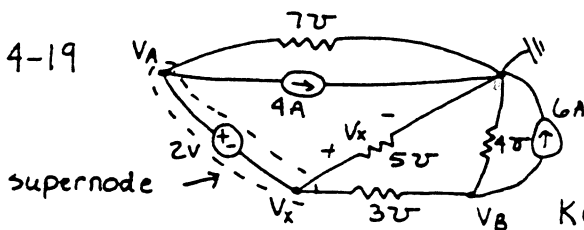


KCL supernode:
 $7V_A + 5V_x + 3(V_x - V_B) + 4 = 0$
 $\downarrow$ $\underline{7V_A - 3V_B + 8V_x + 4 = 0} \quad (1)$

KCL at V_B : $3(V_B - V_x) + 4V_B + 6 = 0$
 $\downarrow$ $\underline{7V_B - 3V_x + 6 = 0} \quad (2)$

also $\underline{V_A - V_x = 2} \quad (3)$

Solving (1), (2) & (3) simultaneously yields $\underline{V_x = -1.5V}$


P. 4-20

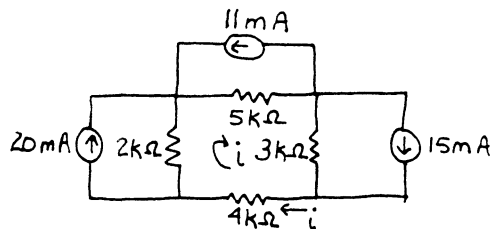

$$\text{KVL mesh } i: 2(i - 20) + 5(i + 11) + 3(i - 15) + 4i = 0$$

$$\downarrow 14i - 140 = 0 \Rightarrow \underline{i = 10\text{mA}}$$

P. 4-21

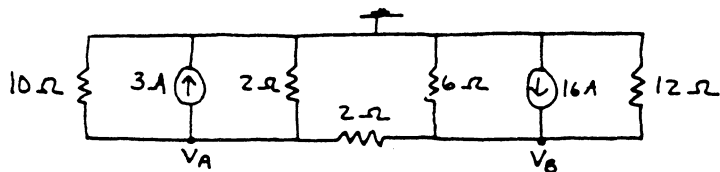

$$\text{KCL at } V_A: V_A/10 + 3 + V_A/2 + 1/2(V_A - V_B) = 0$$


$$\downarrow \underline{11V_A - 5V_B + 30 = 0} \quad (1)$$

$$\text{KCL at } V_B: V_B/12 - 16 + V_B/6 + 1/2(V_B - V_A) = 0$$

$$\downarrow \underline{2V_A - 3V_B + 64 = 0} \quad (2)$$

Solving (1) & (2) simultaneously yields $V_A = 10\text{V}$, $V_B = 28\text{V}$

P. 4-22

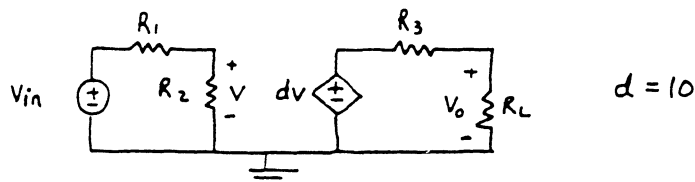


$$\text{from voltage divider } V = V_{in} \frac{R_2}{R_1 + R_2}$$

$$\text{from voltage divider } V_0 = dV \frac{R_L}{R_L + R_3}$$

$$= (10) V_{in} \frac{R_2}{R_1 + R_2} \cdot \frac{R_L}{R_L + R_3}$$

$$\therefore \underline{\underline{\frac{V_0}{V_{in}} = \frac{10 R_L R_2}{(R_L + R_3)(R_1 + R_2)}}}$$

P. 4-23

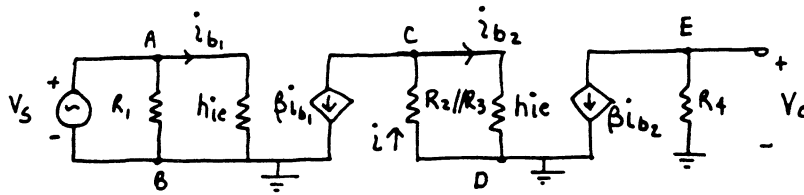

$$\text{KVL around ABA} \uparrow: h_{ie} i_{b1} - V_s = 0 \Rightarrow \underline{V_s = 1.3 i_{b1}} \quad (1)$$

$$\text{KCL at E: } V_o/R_4 + \beta i_{b2} = 0 \Rightarrow \underline{V_o = -(2)(50) i_{b2} = -100 i_{b2}} \quad (2)$$

$$\text{KCL at C: } i = \beta i_{b1} + i_{b2} = \underline{50 i_{b1} + i_{b2}} \quad (3)$$

$$\text{KVL around CDC} \uparrow: h_{ie} i_{b2} + i(R_2 \parallel R_3) = 0$$


$$\hookrightarrow 1.3 i_{b2} + (50 i_{b1} + i_{b2})(1.985) = 0$$

$$\hookrightarrow \underline{i_{b2} = -30.213 i_{b1}} \quad (4)$$

$$(4) \text{ into } (2) \text{ yields } i_{b1} = \frac{V_o}{3021.31}$$

$$\therefore \text{ from } (1) \text{ get } V_s = \frac{1.3}{3021.31} V_o \Rightarrow \underline{\frac{V_o}{V_s} = 2324.08}$$

P. 4-24

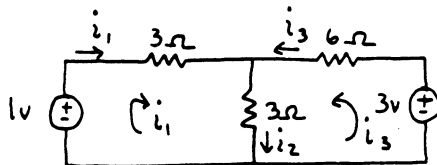

$$(a) \text{ KVL mesh } i_1: -1 + 3i_1 + 3(i_1 + i_3) = 0 \Rightarrow \underline{6i_1 + 3i_3 = 1} \quad (1)$$

$$\text{KVL mesh } i_3: 6i_3 + 3(i_3 + i_1) - 3 = 0 \Rightarrow \underline{i_1 + 3i_3 = 1} \quad (2)$$

$$\text{from KCL: } \underline{i_1 + i_3 = i_2} \quad (3)$$

$$\text{solving (1), (2) \& (3) simultaneously yields } \underline{i_1 = 0, i_2 = 1/3 \text{ A}} \\ \underline{i_3 = 1/3 \text{ A}}$$

(b) calculate power absorbed

$$P_{1V} = V i_1 = \underline{0}$$

$$P_{R_1} = i_1^2 R_1 = \underline{0}$$


$$P_{R_2} = i_2^2 R_2 = (1/3)^2 (3) = \underline{1/3 \text{ W}}$$

$$P_{R_3} = i_3^2 R_3 = (1/3)^2 (6) = \underline{2/3 \text{ W}}$$

$$P_{3V} = -V i_3 = -(3)(1/3) = \underline{-1 \text{ W}}$$

$$\text{see that } \Sigma P = 0$$

P. 4-25 simplify ckt.

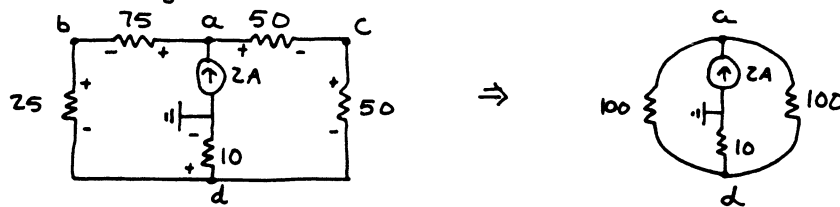

by symmetry 1A flows from a to b & 1A from a to c

$$\therefore V_{ab} = 75v \quad \text{and} \quad V_{ac} = 50v$$

$$V_{bd} = 25v \quad \text{and} \quad V_{cd} = 50v$$


with respect to ground

$$V_d = (10)(2A) = 20v$$

$$\text{from KVL: } V_b = V_d + V_{bd} = 45v$$

$$V_c = V_d + V_{cd} = 70v \quad \text{and} \quad V_a = V_b + V_{ab} = 120v$$

P. 4-26

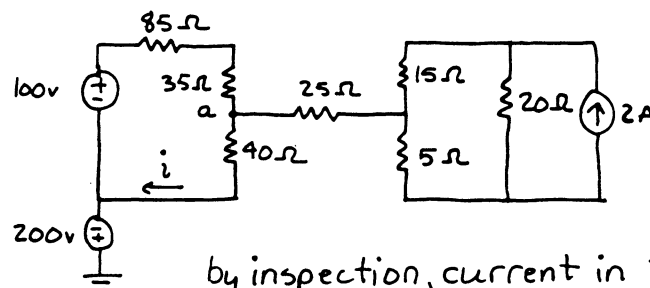

by inspection, current in $25\Omega = 0$


$$\therefore i = \frac{100v}{85+35+40} = \frac{100}{160} = 5/8 A$$

$$\text{from KVL: } V_A = -200 + 40i$$

$$= -200 + 40(5/8)$$

$$V_A = -175v$$

P. 4-27

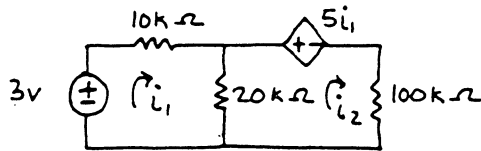

$$\text{KVL } i_1 \uparrow : -3 + 10i_1 + 20(i_1 - i_2) = 0 \Rightarrow \underline{30i_1 - 20i_2 = 3} \quad (1)$$


$$\text{KVL } i_2 \uparrow : 5i_1 + 100i_2 + 20(i_2 - i_1) = 0 \Rightarrow \underline{i_1 = 8i_2} \quad (2)$$

$$\text{solving (1) \& (2) simultaneously} \Rightarrow i_1 = \frac{6}{55} \text{ mA}, i_2 = \frac{3}{220} \text{ mA}$$

$$\begin{aligned} \therefore P_{\text{deliv. to } 5i_1 \text{ and } 100k\Omega} &= (5i_1)(i_2) + 100(i_2)^2 \\ &= 5\left(\frac{6}{55}\right)\left(\frac{3}{220}\right) + 100\left(\frac{3}{220}\right)^2 = 0.026 \text{ mW} \\ &= 2.6 \times 10^{-5} \text{ W} \end{aligned}$$

$$\begin{aligned} \therefore \text{Energy in 24 hr.} &= Pt = (2.6 \times 10^{-5})(24 \text{ hr})(3600 \text{ s/hr}) \\ &= \underline{2.25 \text{ J}} \end{aligned}$$

P. 4-28

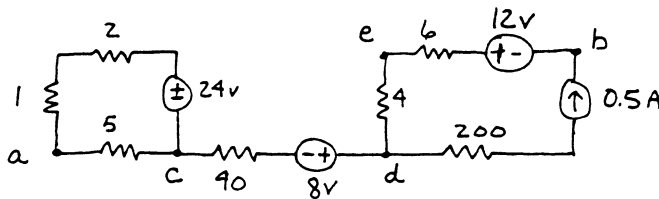

$$\text{KVL around } a c d e b a \uparrow : V_{ab} = V_{ac} + V_{cd} + V_{de} + V_{eb}$$

$$\text{by inspection current between } c-d \text{ is zero} \therefore V_{cd} = -8 \text{ V}$$


$$\text{from voltage divider } V_{ac} = 24 \left(\frac{5}{5+1+2} \right) = 15 \text{ V}$$

$$\text{and by inspection } V_{de} = (4)(-5) = -2 \text{ V}$$

$$V_{eb} = 6(-5) + 12 = 9 \text{ V}$$

$$\therefore \underline{V_{ab} = 15 - 8 - 2 + 9 = 14 \text{ V}}$$

P. 4-29

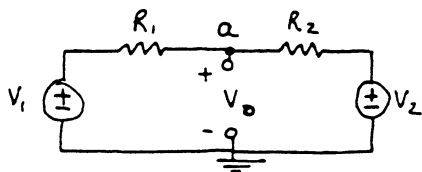


$$\text{KCL at } a : \frac{V_0 - V_1}{R_1} + \frac{V_0 - V_2}{R_2} = 0$$

$$\Rightarrow V_0 = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

$$\text{now want } \frac{R_2}{R_1 + R_2} = \frac{2}{3} \text{ and } \frac{R_1}{R_1 + R_2} = \frac{1}{3}$$

$$\text{solving the two above simultaneously yields}$$
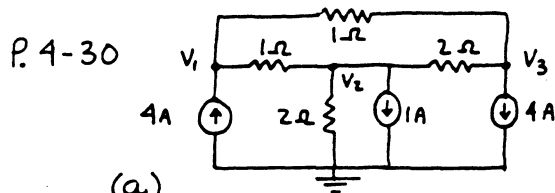
$$\underline{R_1 = 1\Omega \text{ and } R_2 = 2\Omega}$$



(a)

$$\text{KCL at } V_1: -4 + (V_1 - V_3)/1 + (V_1 - V_2)/1 = 0$$

$$\Rightarrow \underline{2V_1 - V_2 - V_3 = 4} \quad (1)$$

$$\text{KCL at } V_2: (V_2 - V_1)/1 + V_2/2 + 1 + (V_2 - V_3)/2 = 0$$

$$\Rightarrow \underline{-2V_1 + 4V_2 - V_3 + 2 = 0} \quad (2)$$

$$\text{KCL at } V_3: (V_3 - V_1)/1 + (V_3 - V_2)/2 + 4 = 0$$


$$\Rightarrow \underline{-2V_1 - V_2 + 3V_3 + 8 = 0} \quad (3)$$

Solving (1), (2) & (3) simultaneously $\Rightarrow$

$V_1 = -1\text{V}$
$V_2 = -2\text{V}$
$V_3 = -4\text{V}$

(b) $P_{\text{absorbed}} = V_i = -V_2(1) = -(2)(1) = \underline{-2\text{W}}$

P. 4-31

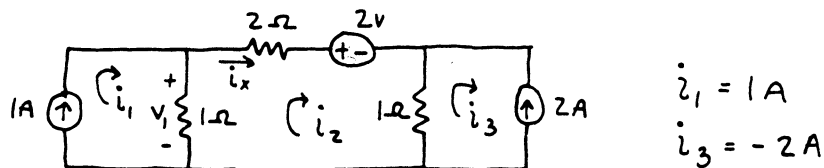

$$\text{KVL mesh } i_2: 1(i_2 - i_1) + 2i_2 + 2 + 1(i_2 - i_3) = 0$$


$$\Rightarrow \underline{i_2 = -3/4\text{A} = i_x}$$

now $V_1 = 1(i_1 - i_2) = 1 + 3/4 = \underline{1.75\text{V}}$

P. 4-32 KCL: $-1 + \frac{V_a}{1} + \frac{V_a}{3} + \frac{V_a - 6}{2} = 0$

$$\Rightarrow \underline{V_a = 24/11 = 2.18\text{V}}$$

P 4-33

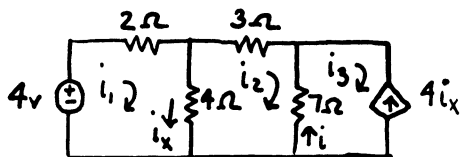

$$\text{mesh 1: } 6i_1 - 4i_2 = 4 \quad (1)$$

$$\text{mesh 2: } -4i_1 + 14i_2 - 7[4(i_2 - i_1)] = 0 \quad (2)$$


$$\text{where } 4i_x = 4(i_1 - i_2)$$

solving (1) & (2) yields: $i_1 = -14/3 \text{ A}$, $i_2 = -8 \text{ A}$

$$\text{now note } i_3 = 4(i_2 - i_1) = 4(-8 + 14/3) = -40/3 \text{ A}$$

$$\Rightarrow i = i_3 - i_2 = -16/3 = -5.33 \text{ A}$$

P 4-34

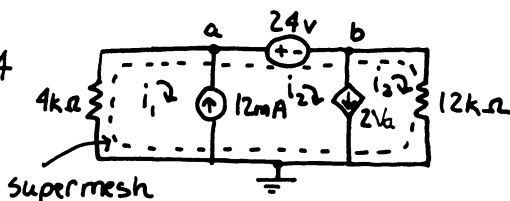

$$\text{Supermesh: } 4i_1 + 24 + 12i_3 = 0 \quad (1)$$

$$\text{also: } i_2 - i_1 = 12 \quad (2)$$


$$\text{and: } -i_3 + i_2 = 2V_a \quad (3)$$

$$\text{and: } V_a = -4i_1 \quad (4)$$

a) mesh

solving (1) - (4) simultaneously yields $V_a = 6 \text{ V}$

b) nodal

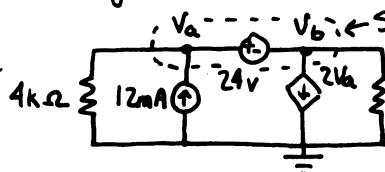

inside supernode


$$V_b = V_a - 24 \quad (1)$$

$$\text{KCL at supernode: } \frac{V_a}{4} - 12 + 2V_a + \frac{V_b}{12} = 0 \quad (2)$$

plugging (1) into (2) and multiplying by 12 yields

$$27V_a - 144 + V_a - 24 = 0 \Rightarrow V_a = 6 \text{ V}$$

P 4-35

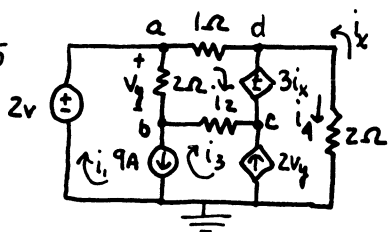

a) mesh analysis

combine loop 1, 3 & 4 into supermesh

$$\Rightarrow -2 + (i_1 - i_2)2 + (i_3 - i_2) - 3i_x + 2i_4 = 0 \quad (1)$$

$$\text{loop } i_2: -2i_1 + 4i_2 - i_3 + 3i_x = 0 \quad (2)$$

$$\text{also: } i_1 - i_3 = 9 \quad (3)$$

$$i_4 - i_3 = 2V_y \quad (4)$$

$$2(i_1 - i_2) = V_y \quad (5)$$

$$\text{and } V_c = -2i_x - 3i_x \quad (6)$$

$$i_4 = -i_x \quad (7)$$

solving (1) - (7) simultaneously yields

$$i_x = -1 \text{ A}, \quad V_c = 5 \text{ V}$$

P 4-35 (continued)

b) nodal analysis

$$V_d = 2v$$

$$\text{KCL at } b: 9 + \frac{V_b - V_c}{1} + \frac{V_b - 2}{2} = 0 \Rightarrow 3V_b - 2V_c = -16 \quad (1)$$

form supernode around nodes c & d, then KCL yields

$$\frac{V_d - 2}{1} + \frac{V_d}{2} - 2V_y + \frac{V_c - V_b}{1} = 0$$

with $V_y = 2 - V_b$ & multiplying above thru by 2 yields


$$2V_b + 2V_c + 3V_d = 12 \quad (2)$$

$$\text{also: } V_d - V_c = 3i_x = 3(-V_d/2) \Rightarrow -V_c + 2.5V_d = 0 \quad (3)$$

Solving (1) - (3) yields

$$\underline{V_c = 5v} \quad \text{and} \quad V_d = 2v \Rightarrow \underline{i_x = -\frac{V_d}{2} = -1A}$$

P 4-36

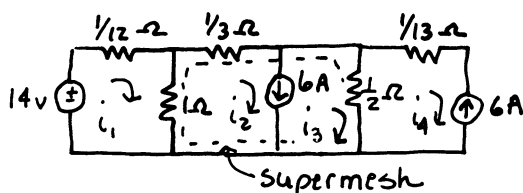

$$\text{mesh (1): } -14 + \frac{1}{12}i_1 + 1(i_1 - i_2) = 0 \quad (1)$$

supermesh:

$$1(i_2 - i_1) + \frac{1}{3}i_2 + \frac{1}{3}i_3 + \frac{1}{2}(i_3 - i_4) = 0 \quad (2)$$

$$\text{also } i_2 - i_3 = 6 \quad (3) \quad \text{and} \quad i_4 = -6 \quad (4)$$


plugging (3) and (4) into (2) yields

$$(i_2 - i_1) + \frac{1}{3}i_2 + \frac{1}{3}(i_2 - 6) + \frac{1}{2}[(i_2 - 6) + 6] = 0 \quad (5)$$

solving (1) and (5) simultaneously yields

$$\underline{i_1 = 22.89A}, \quad \underline{i_2 = 10.79A}$$

P 4-37

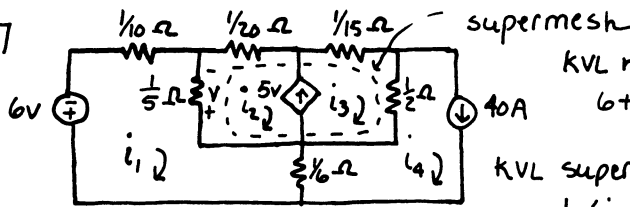

supermesh

KVL mesh 1:

$$6 + \frac{i_1}{10} + \frac{1}{5}(i_1 - i_2) + \frac{1}{6}(i_1 - 40) = 0 \quad (1)$$

KVL supermesh:

$$\frac{1}{5}(i_2 - i_1) + \frac{1}{20}i_2 + \frac{1}{15}i_3 + \frac{1}{2}(i_3 - i_4) = 0 \quad (2)$$


$$\text{also note: } i_3 - i_2 = 5V = 5 \frac{(i_2 - i_1)}{5} \Rightarrow i_3 = 2i_2 - i_1 \quad (3)$$

$$\text{and note: } i_4 = 40 \quad (4)$$

Solving (1) - (4) simultaneously leads to

$$i_1 = 10A, i_2 = 20A, i_3 = 30A$$

P 4-38

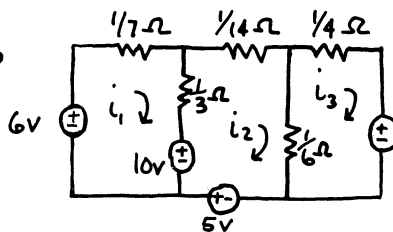


$$\text{KVL loop 1: } \left(\frac{1}{7} + \frac{1}{3}\right)i_1 - \frac{1}{3}i_2 + 10 - 6 = 0 \quad (1)$$

$$\text{loop 2: } -\frac{1}{3}i_1 + \left(\frac{1}{3} + \frac{1}{14} + \frac{1}{6}\right)i_2 - \frac{1}{6}i_3 - 10 - 5 = 0 \quad (2)$$

$$\text{loop 3: } -\frac{1}{6}i_2 + \left(\frac{1}{6} + \frac{1}{4}\right)i_3 + 2 = 0 \quad (3)$$

$$\text{Solving (1) - (3) simultaneously yields } i_1 = 21A, i_2 = 42A, i_3 = 12A$$

P 4-39

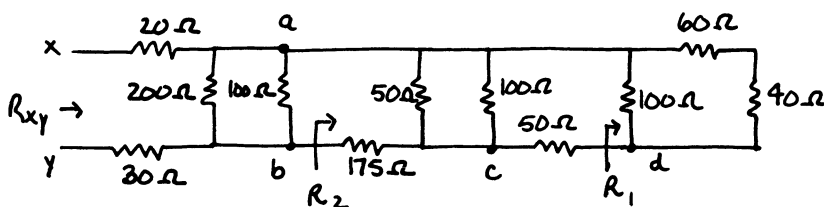


$$R_1 = \frac{1}{\frac{1}{100} + \frac{1}{60+40}} = 50\Omega$$

$$R_2 = 175 + \frac{1}{\frac{1}{50} + \frac{1}{100} + \frac{1}{50+R_1}} = 175 + \frac{1}{\frac{1}{50} + \frac{1}{100} + \frac{1}{100}} = 200\Omega$$

$$R_{xy} = 20 + 30 + \frac{1}{\frac{1}{200} + \frac{1}{100} + \frac{1}{R_2}} = 20 + 30 + \frac{1}{\frac{1}{200} + \frac{1}{100} + \frac{1}{200}} = 100\Omega$$

P 4-40

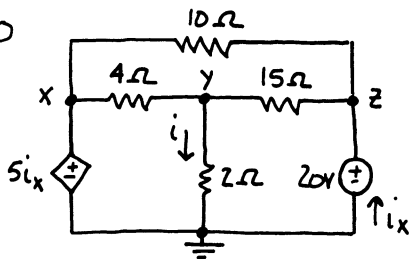

by inspection : $V_x = 5i$, $V_z = 20V$, $i = \frac{V_y}{2}$


$$\text{KCL at } y : \frac{V_y - 5i_x}{4} + \frac{V_y}{2} + \frac{V_y - 20}{15} = 0 \quad (1)$$

$$\text{KCL at } z : \frac{20 - 5i_x}{10} + \frac{20 - V_y}{15} - i_x = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields $V_y = 4.713V$

$$\Rightarrow i = \frac{V_y}{2} = \frac{4.713}{2} = \underline{2.356A}$$

P 4-41

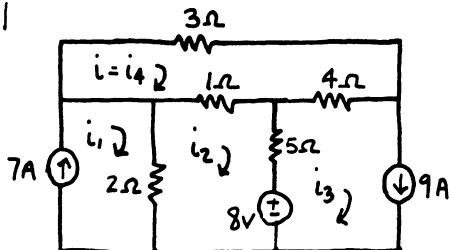


$i_1 = 7A$, $i_3 = 9A$

$$\text{mesh } i_2 : 1(i_2 - i_4) + 5(i_2 - 9) + 8 + 2(i_2 - 7) = 0 \quad (1)$$

$$\text{mesh } i_4 : 3i_4 + 4(i_4 - 9) + 1(i_4 - i_2) = 0 \quad (2)$$

Solving (1) & (2) simultaneously yields : $i = i_4 = \underline{5.38A}$

P 4-42

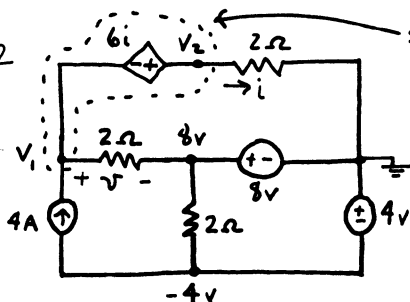

supernode

note : $V_2 = V_1 + 6i$

(1)

KCL at supernode :


$$-4 + \frac{V_1 - 8}{2} + \frac{V_1 + 6i}{2} = 0 \quad (2)$$

$$\text{also : } i = \frac{V_2}{2} \quad (3)$$

Solving (1) - (3) simultaneously yields : $V = \underline{24V}$

Advanced Problems

AP 4-1

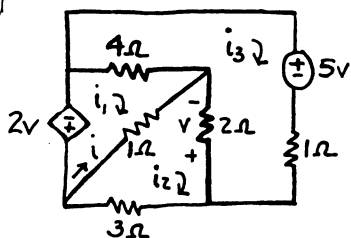

$$V = 2(i_3 - i_2) \quad (1)$$

$$\text{loop 1: } 2V + 4(i_1 - i_3) + 1(i_1 - i_2) \quad (2)$$


plugging (1) into (2) yields:

$$4(i_3 - i_2) + 4(i_1 - i_3) + i_1 - i_2 = 0 \Rightarrow i_1 = i_2$$

$$\text{now } i = i_2 - i_1 = i_2 - i_2 = 0$$

AP 4-2

a) model

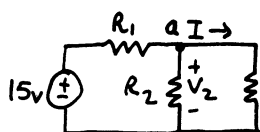

need to keep V_2 across R_2 as $4.8 \leq V_2 \leq 5.4$

$I = .3$ or $.1A$ depending on whether
 ↑ display is active ↑ not active

$$\text{KCL at } a: \frac{V_2 - 15}{R_1} + \frac{V_2}{R_2} + I = 0$$

$$\Rightarrow V_2' = 4.8V \quad (I' = .3A) \quad ; \quad V_2'' = 5.4V \quad (I'' = .1A)$$

assumed that maximum I results in minimum V_2 and visa-versa

now plug in V_2' & V_2'' into KCL eqn. to generate 2 eqns and then solve for R_1 & R_2 $\Rightarrow \underline{R_1 = 7.89\Omega}, \underline{R_2 = 4.83\Omega}$


$$b) I_{R_1 \max} = \frac{15 - 4.8}{7.89} = 1.292A \Rightarrow P_{R_1 \max} = (1.292)^2 (7.89) = 13.17W$$

$$I_{R_2 \max} = \frac{5.4}{4.83} = 1.119A \Rightarrow P_{R_2 \max} = \frac{(5.4)^2}{4.83} = 6.03W$$

$$I_{15V \max} = 1.292A$$

c) No; if the supply voltage (15V) were to rise or drop, the voltage at the display at the display would drop below 4.8V or rise above 5.4V. The power dissipated in the resistors is excessive. Most of the power from the supply is dissipated in the resistors, not the display.

AP 4-3

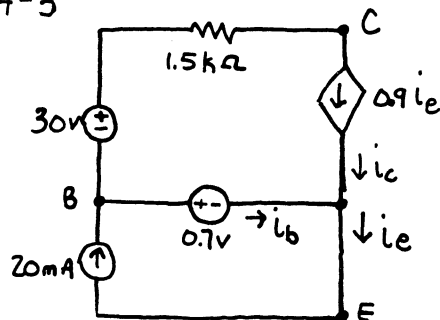


$$i_e = 20\text{mA}$$

$$i_c = 0.9i_e = 18\text{mA}$$

$$i_b = i_e - i_c = 2\text{mA}$$

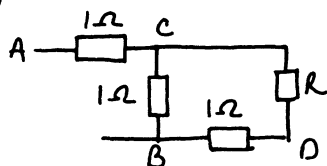
AP 4-4 The resistance R looking to the right from A to B is the same as the resistance looking to the right from C to D. So the right half of the network can be represented by the figure below:



$$\text{Thus } R = 1 + \frac{1(R+1)}{1+R+1} = \sqrt{3} \Omega$$

With the left half of the network included, the resistance between A and B is $\sqrt{3}/2$ or $.866 \Omega$.

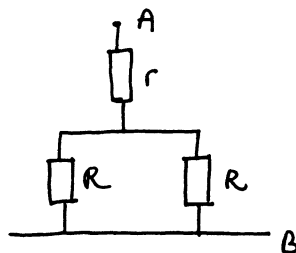
AP 4-5 Notice that if R is the resistance between A and B, the network can be drawn like :



$$\text{so } R = r + R/2$$


$$\text{or } \underline{R = 2r}$$

AP 4-6 The portion of the network to the right of C and D is the same as the original network with every resistance doubled. So the original network can be represented by the figure below. If R is the resistance between A and B, then have
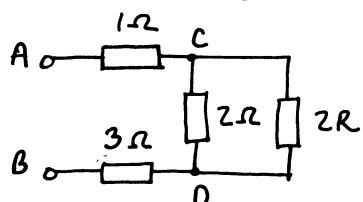
$$R = 4 + \frac{4R}{2 + 2R} \quad \text{and} \quad R = \frac{5 + \sqrt{41}}{2} = 5.70 \Omega$$


Design Problems

DP 4-1 simplify to

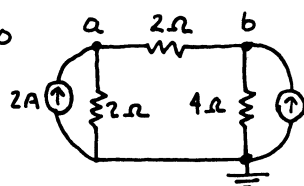

KCL at node a: $V_a(\frac{1}{2} + \frac{1}{2}) - \frac{1}{2}V_b - 2 = 0$ (1)


at node b: $-\frac{1}{2}V_a + (\frac{1}{2} + \frac{1}{4})V_b - i_s = 0$ (2)

now $V_{ba} = 3 = V_b - V_a \Rightarrow V_b = 3 + V_a$ (3)

plugging (3) into (1) yields: $V_a = 7V$ & $V_b = 10V$

thus from (2) get: $i_s = 4A$

DP 4-2

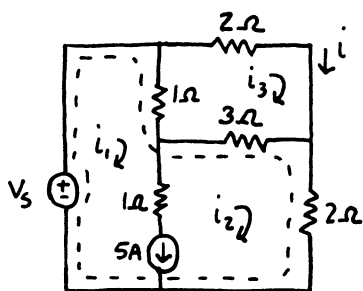

$i_3 = i = 3A$

Supermesh: $-V_s + 1(i_1 - i_3) + 3(i_2 - i_3) + 2i_2 = 0$

$\hookrightarrow -V_s + i_1 + 5i_2 = 12$ (1)

mesh 3: $1(i_3 - i_1) + 2i_3 + 3(i_3 - i_2) = 0$


$\hookrightarrow i_1 + 3i_2 = 18$ (2)

also $i_1 - i_2 = 5$ (3)

combining (2) & (3) yields $i_2 = 3.25A$, $i_1 = 8.25A$

from (1) $V_s = 12.5V$

DP 4-3

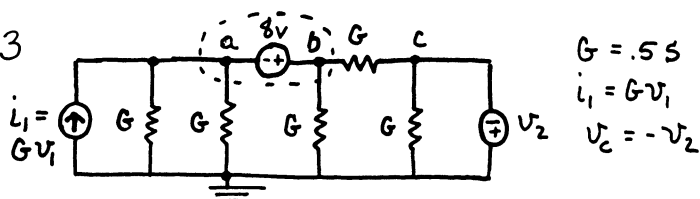

Supernode : $v_a(G+G) + v_b(G+G) - Gv_c = i_1$ (1)

also : $v_b - v_a = 8$ (2)

Combining (1) & (2) yields $v_a + (8 + v_a) + .5v_c = .5v_1$


$2v_a = .5v_1 - .5v_c - 8$

$\Rightarrow v_a = \frac{.5v_1 - .5v_c - 8}{2} = 0$

$\therefore .5v_1 - .5v_c = 8$

so let $v_c = 2v$ and $v_1 = 18v$ one solution

DP 4-4

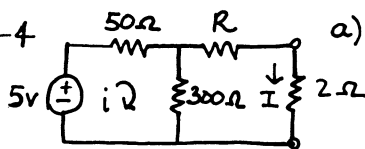

a) KVL left mesh : $-5 + 50i + 300(i - I) = 0$ (1)

right mesh : $(R + 2)I + 300(I - i) = 0$ (2)

Solving (1) & (2) for I $\Rightarrow I = \frac{150}{1570 + 35R}$ (3)

so if $R = 100$, then $I = 29.59 \text{ mA} \Rightarrow$ lamp will not light


b) from (3) note that as $R \downarrow I \uparrow$, so try $R = 50 \Omega \Rightarrow I = 45 \text{ mA}$ (won't light)

try $R = 25 \Omega \Rightarrow I = 61 \text{ mA} \Rightarrow$ will light


now check if $R \pm 10\%$ will light and not burn out

$-10\% \rightarrow 22.5 \Omega \rightarrow I = 63.63 \text{ mA}$
 $+10\% \rightarrow 27.5 \Omega \rightarrow I = 59.23 \text{ mA}$ } lamp will stay on

DP 4-5

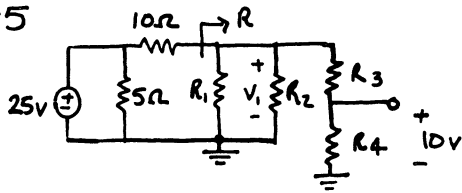
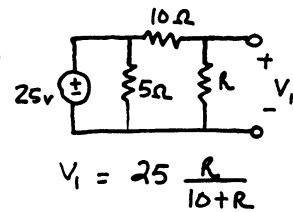
$$R = R_1 \parallel R_2 \parallel (R_3 + R_4)$$



using voltage divider


$$10 = \frac{R_4}{R_3 + R_4} V_1 = \frac{R_4}{R_3 + R_4} \frac{(R_1 \parallel R_2 \parallel (R_3 + R_4))}{10 + (R_1 \parallel R_2 \parallel (R_3 + R_4))} 25$$

choose $R_1 = R_2 = 25\Omega \rightarrow 10 = \frac{R_4}{20} \frac{(12.5 \parallel 20)}{10 + (12.5 \parallel 20)} 25 \Rightarrow R_4 = 18.4\Omega$

one solution

$$R_3 + R_4 = 20 \Rightarrow R_3 = 1.6\Omega$$

DP 4-6

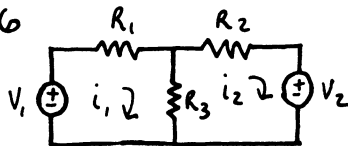

$$\text{mesh } i_1: (R_1 + R_3)i_1 - R_3i_2 - V_1 = 0 \quad (1)$$

$$\text{mesh } i_2: -R_3i_1 + (R_2 + R_3)i_2 + V_2 = 0 \quad (2)$$

from (1) & (2) get:
$$i_1 = \frac{\begin{bmatrix} V_1 & -R_3 \\ -V_2 & (R_2 + R_3) \end{bmatrix}}{\Delta} \quad i_2 = \frac{\begin{bmatrix} (R_1 + R_3) & V_1 \\ -R_3 & -V_2 \end{bmatrix}}{\Delta}$$

where $\Delta = (R_1 + R_3)(R_2 + R_3) - R_3^2$

now if $R_1 = R_2 = R_3 = 1K$ where K represents 1000

$$\text{then } \Delta = 4 - 1 = 3K^2$$

so have $i_1 = \frac{[2V_1 - V_2]}{3K^2} K, \quad i_2 = \frac{[-2V_2 + V_1]}{3K^2} K$


$$\Rightarrow i = i_1 - i_2 = \frac{V_1 + V_2}{3K}$$

if $V_1 = V_2 = 1V \Rightarrow i = 2/3mA$ okay

if $V_1 = V_2 = 2V \Rightarrow i = 4/3mA$ okay

Spice Problems

SP 4-1

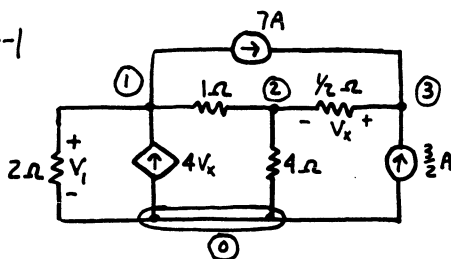

ans. $V_1 = 24V$


input file:

```

R1 1 0 2
R2 1 2 1
R3 2 0 4
R4 2 3 .5
G1 0 1 3 2 4
I1 1 3 7
I2 0 3
.print dc V(1)
.END

```


SP 4-2

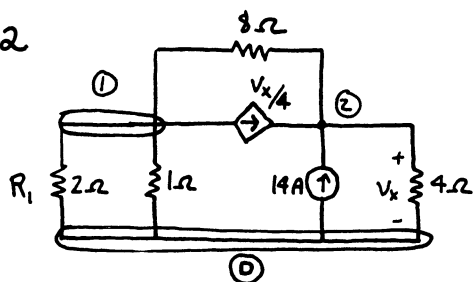

input file :

```
R1 1 0 2
R2 1 0 1
R3 1 2 8
R4 2 0 4
G1 1 2 2 0 .25
I1 0 2 14
.DC I1 14 14 1
.PRINT DC V(1) V(2) I(R1)
.END
```


Ans. $V_x = V_2 = 104V$

$V_1 = -8V$

$\Rightarrow P_{2\Omega} = \frac{(8)^2}{2} = 32W$

Also $I(R1) = -4A$

SP 4-3

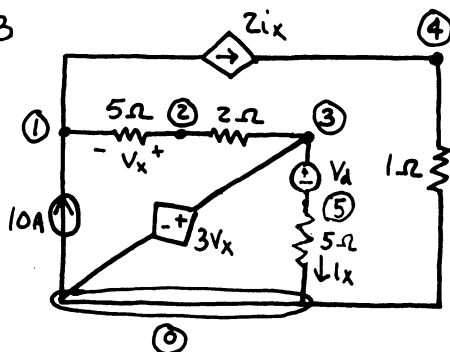

input file

```
R1 1 2 5
R2 2 3 2
R3 5 0 5
R4 4 0 1
I1 0 1 10
```

```
VOUDDY 3 5 DC 0 ; Note the dummy source was
F1 1 4 VOUDDY 2 ; Necessary because the format
E1 3 0 2 1 3 ; of F(ccecs) requires the
.DC I1 10 10 1 ; current source to be dependant
.PRINT DC I(R3) V(2,1) V(1) ; on a voltage source
.END
```


Ans. $i_x = i_{R3} = 6A$

$V(2,1) = V_x = V_2 - V_1 = 10V$

$P_{1\Omega} = I^2 2i_x = 12W$

$P_{10A} = -(10A)V_1 = -160W$

SP 4-4

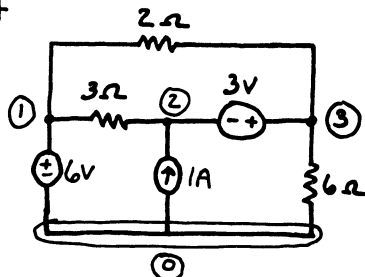

input file


```
V1 1 0 DC 6
I1 0 2 1
V2 3 2 3
R1 1 2 3
R2 1 3 2
R3 3 0 6
.END
```

Ans. $V_1 = 6V$

$V_2 = 4V$

$V_3 = 7V$

SP 4-7

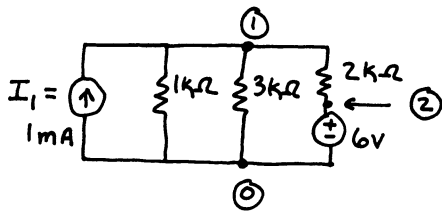

input file

*uses .OP Default

```
I1 0 1 DC 1m
V1 2 0 DC 6
R1 1 0 1k
R2 1 2 2k
R3 1 0 3k
.PRINT DC V(1) V(2)
.END
```


Output: $V(1) = 2.1818 \text{ V}$

$V(2) = 6.00 \text{ V}$

Current through voltage source $V(1)$

$$I(V1) = -1.909 \times 10^{-3} \text{ A}$$

SP 4-8

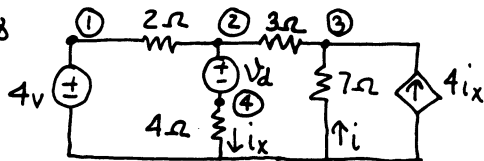

$V_d = 0$ measures i_x for CCCS

input file:

```
V1 1 0 DC 4
VD 2 4 DC 0
F1 0 3 VD 4
R1 1 2 2
R2 4 0 4
R3 2 3 3
R4 0 3 7 ; I flows 0 to 3
.DC V1 4 4 1
.PRINT DC V(1) I(R4)
.END
```


output:

$V(1) = 4.00 \text{ V}$

$I(R4) = 8.00 \text{ A}$

then $i = 8.0 \text{ A}$

SP 4-9

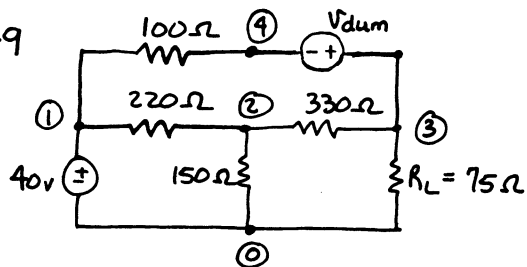


input file

```
V1 1 0 DC 40
R1 1 2 220
R2 2 0 150
R3 2 3 330
R4 3 0 75
R5 1 4 100
VDUM 3 4
.DC 40 40 1
.PRINT DC V(1)
.END
```

output: $V(3) = 17.0569 \text{ V}$

SP 4-10

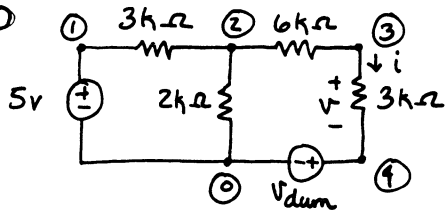






input file

```
R3 2 3 6000
R1 1 2 3k
R2 3 4 3k
R4 2 0 2k
V1 1 0 DC 5
VDum 4 0 0
.PRINT DC V(3)
.END
```

output: $V(3) = 0.5882 \text{ V}$
 $I(V_{dum}) = 1.961 \text{ E-4 A}$

Chapter 5


Exercises

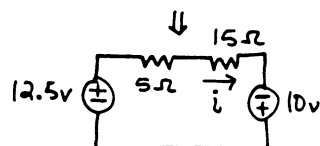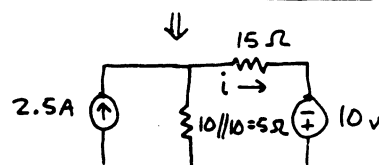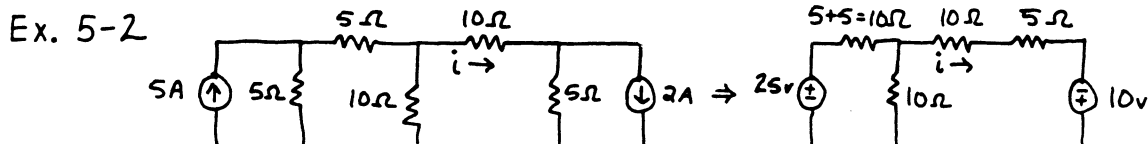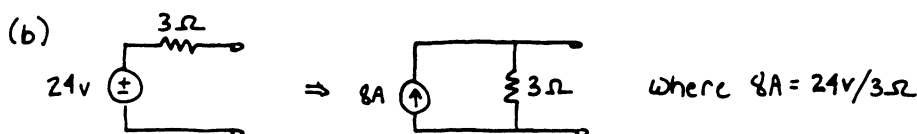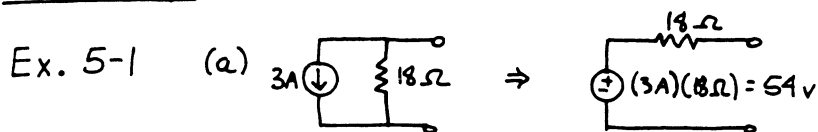

∴ from KVL

$$\tilde{i} = \frac{10V + 12.5V}{5\Omega + 15\Omega} = \underline{1.125 A}$$

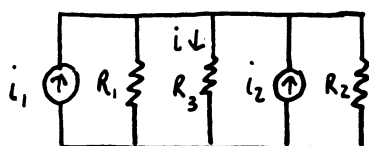Ex 5-3 Using the method of voltage source transform, we change the two voltage sources into two current sources




where $i_1 = \frac{V_1}{R_1} = -\frac{1}{2}e^{-t} (A)$

$i_2 = \frac{V_2}{R_2} = \frac{1}{2}e^{-2t} (A)$

because $R_1 = R_2 = R_3 = 2\Omega \Rightarrow i = \frac{1}{2+2+2} (i_1 + i_2) = \underline{\underline{\frac{1}{6}(e^{-2t} - e^{-t}) A}}$

Ex 5-4

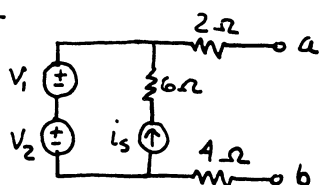


terminals a-b are open

$\Rightarrow$ no current in the 2Ω & 4Ω resistors


∴ $\underline{V_{ab} = V_1 + V_2}$

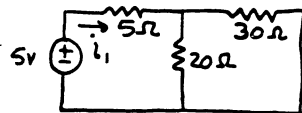Ex. 5-5 consider 5v source only (short 3v source)



$$i_1 = \frac{5v}{5 + 20 \parallel 30} = \frac{5}{5 + 12} = \underline{0.294 A}$$

consider 3v source (short 5v source)

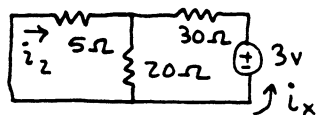


$$i_x = \frac{3v}{30 + 20 \parallel 5} = \frac{3}{30 + 4} = 0.088 A$$

$$\therefore \text{from current divider } i_2 = -i_x \left(\frac{20}{20+5} \right) = \underline{-0.071 A}$$

$$\therefore i = i_1 + i_2 = 0.294 - 0.071 = \underline{0.223 A}$$

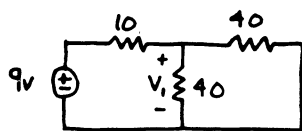
Ex. 5-6 consider 9v source only (short 12v source)



voltage divider $\Rightarrow$

$$V_1 = 9v \left(\frac{40 \parallel 40}{10 + 40 \parallel 40} \right) = 9 \left(\frac{20}{10+20} \right) = \underline{6v}$$

consider 12v source (short 9v source)

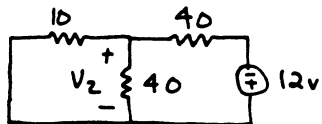


voltage divider $\Rightarrow$

$$V_2 = -12v \left(\frac{40 \parallel 10}{40 + 40 \parallel 10} \right) = \underline{-2v}$$

$$\therefore V = V_1 + V_2 = 6 - 2 = \underline{4v}$$

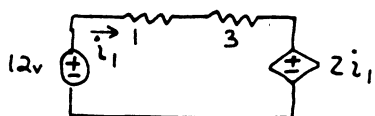
Ex. 5-7 consider 12v source only (open 6A source)



$$\text{KVL } \uparrow: -12 + i_1(1+3) + 2i_1 = 0$$

$$\Rightarrow \underline{i_1 = 2A}$$

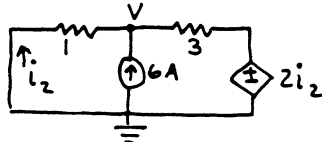consider 6A source only (short 12v source)



$$\text{KCL at } V: -i_2 - 6 + (V - 2i_2)/3 = 0$$


$$\text{also } V = -(1)i_2$$

$$\therefore \text{solve for } \underline{i_2 = -3A}$$

$$\therefore i = i_1 + i_2 = 2 - 3 = \underline{-1A}$$

Ex. 5-8

find V_{oc}

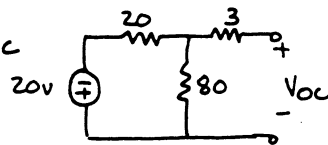


no current flows through 3Ω


$\therefore$ from Voltage divider

$$V_{oc} = -20V \left(\frac{80\Omega}{80\Omega + 20\Omega} \right) = \underline{-16V}$$

to find R_T , kill 20V source

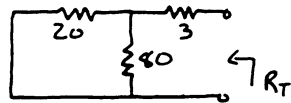


$$R_T = 20\Omega \parallel 80\Omega + 3 = \underline{19\Omega}$$

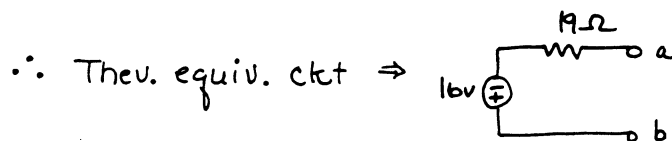

Ex. 5-9


find V_{oc}

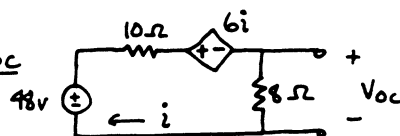

$$\text{KVL } \circlearrowleft: -48 + 10i + 6i + 8i = 0 \Rightarrow i = 2A$$

$$\therefore V_{oc} = 8i = \underline{16V}$$


find i_{sc}

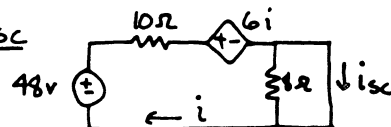


Since no current flows through $8\Omega \Rightarrow i_{sc} = i$

$$\text{KVL } \circlearrowleft: -48 + 10i_{sc} + 6i_{sc} = 0 \Rightarrow \underline{i_{sc} = 3A}$$

$$\therefore R_T = V_{oc}/i_{sc} = \underline{16/3\Omega}$$

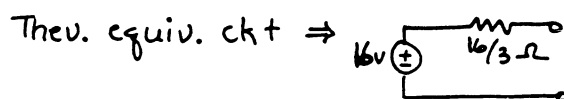

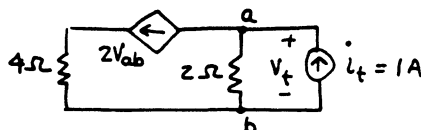
Ex. 5-10 no independent sources $\therefore V_{oc} = i_{sc} = 0 \Rightarrow$ apply 1A test source




$$V_{ab} = V_t$$

$$\text{KCL at } a: 2V_t + V_t/2 - 1 = 0 \Rightarrow V_t = \underline{2/5V}$$

$$\therefore R_T = \frac{V_t}{i_t} = \underline{2/5\Omega}$$

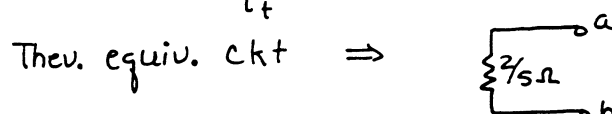

Ex. 5-11 find i_{sc}

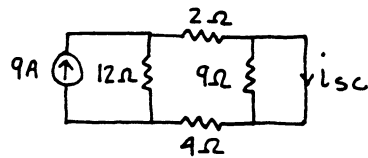

no current flows through 9Ω

$\therefore$ from current divider


$$i_{sc} = 9 \left(\frac{12}{12+6} \right) = 6A$$

open 9A source to find R_T

$$\therefore R_T = 9 \parallel (2+4+12) = \frac{(9)(18)}{9+18} = 6\Omega$$

$\therefore$ Norton equiv. ckt $\Rightarrow$

Ex. 5-12 find V_{oc}

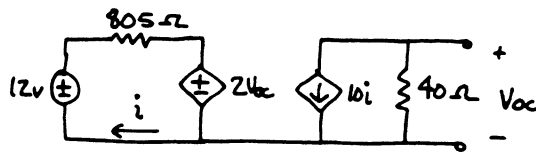


$$\text{KVL around left mesh: } \uparrow -12 + 805i + 2V_{oc} = 0 \quad (1)$$

$$\text{from right loop: } V_{oc} = -10i(40) = -40i \quad (2)$$

$$\text{solving (1) and (2) simultaneously } \Rightarrow \underline{V_{oc} = -960V}$$

find i_{sc}

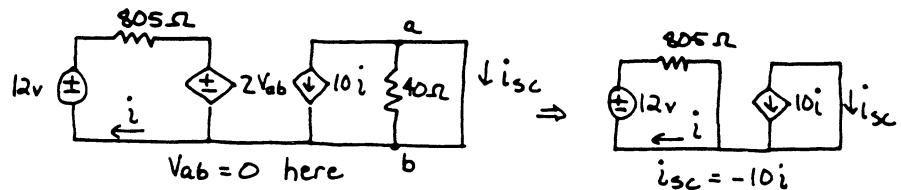


$$\text{from left loop: } i = 12V / 805\Omega = -i_{sc} / 10$$

$$\therefore \underline{i_{sc} = -0.149A}$$

$$\therefore R_T = V_{oc} / i_{sc} = \frac{-960}{-0.149} = 6.44 \times 10^3 \Omega = \underline{6.44 k\Omega}$$

Norton equiv. ckt $\Rightarrow$


Ex 5-13

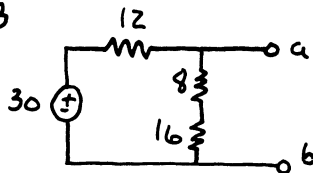

$$R_T = \frac{12 \times 24}{12+24} = \frac{12 \times 24}{36} = 8\Omega$$


$$V_{oc} = \frac{24}{12+24} 30 = 20V$$

so have

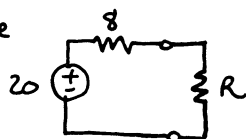

$$i = \frac{20}{8+R} A$$



Ex. 5-14 find V_{oc}

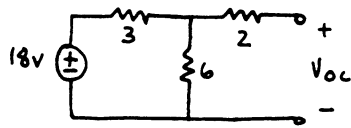

from voltage divider

$$V_{oc} = 18V \left(\frac{6}{6+3} \right) = \underline{12V}$$


find R_T (short 18V source)

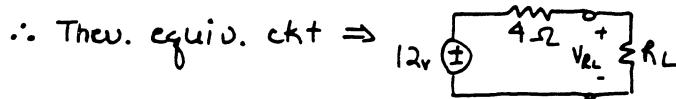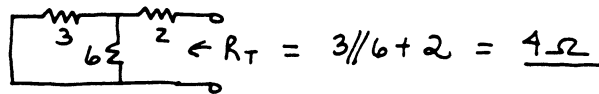

for max power to $R_L \Rightarrow R_L = R_T = 4\Omega$

$$\therefore P_{\max \text{ to } R_L} = \frac{(V_{R_L})^2}{R_L} = \frac{(6)^2}{4} = \underline{9W}$$

Ex. 5-15 find i_{sc}


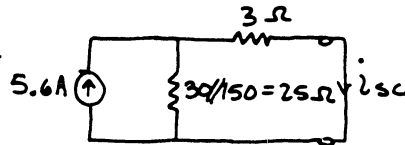


from current divider

$$i_{sc} = 5.6A \left(\frac{25}{25+3} \right)$$

$$\underline{i_{sc} = 5A}$$


find R_T (open 5.6A source)

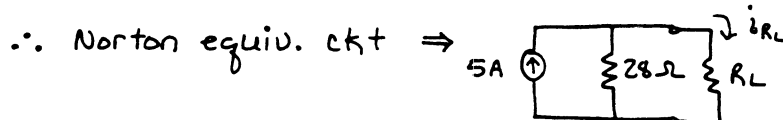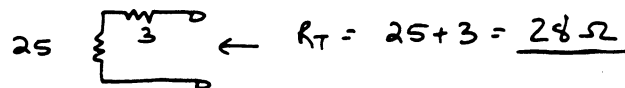

for max power $R_L = R_T = 28\Omega$

$$\therefore P_{L \max} = (i_{R_L})^2 R_L = (5/2)^2 (28) = \underline{175W}$$

Ex. 5-16

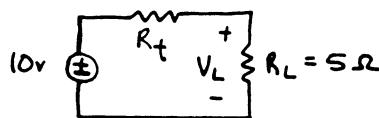


$$P_{L \max} = \frac{V_{L \max}^2}{R_L} = \frac{\left[10V \left(\frac{5}{5+R_t} \right) \right]^2}{R_L}$$

now for V_L to be maximized R_t must be minimized

$\therefore$ choose $R_t = 1\Omega$

$$\therefore P_{L \max} = \frac{\left[10 \left(\frac{5}{6} \right) \right]^2}{5} = \underline{13.9W}$$

Ex 5-17

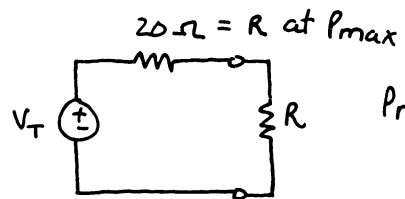


$$P_{\max} = 5 = \left(\frac{V_T}{40}\right)^2 20 = \frac{V_T^2}{80}$$

$$\Rightarrow \underline{V_T = \sqrt{400} = 20 \text{ V}}$$

Problems


P. 5-1

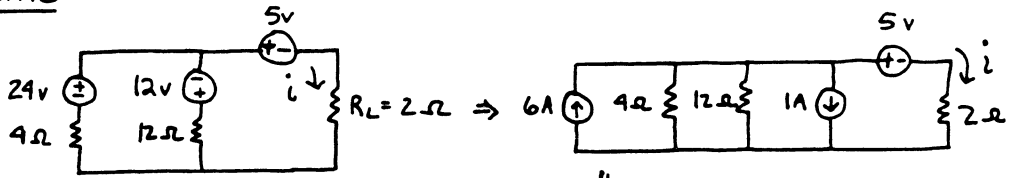

$$i = \frac{15V - 5V}{3\Omega + 2\Omega} = 2A$$


$$P_{R_L} = i^2 R_L = (2)^2 (2) = 8W$$

P. 5-2




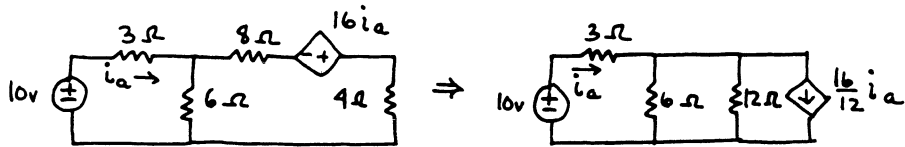


$$\text{KVL } \uparrow: -10 + 3i_a + 4i_a + \frac{16}{3}i_a = 0$$

$$\Rightarrow \underline{i_a = 6A}$$




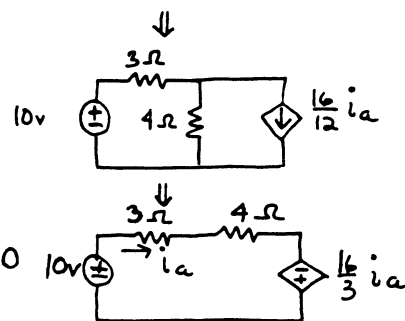


P. 5-3

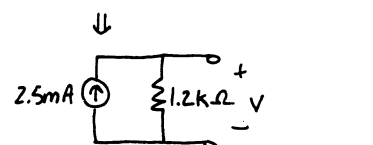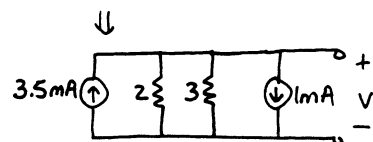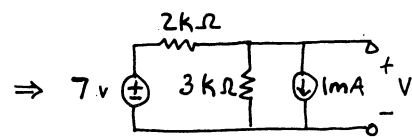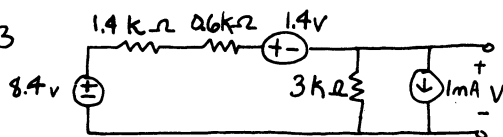

$$V = (1.2k\Omega)(2.5mA) = 3 \text{ Volts}$$


P. 5-4

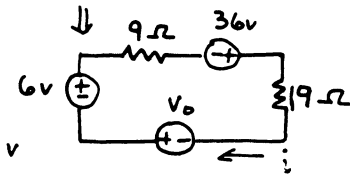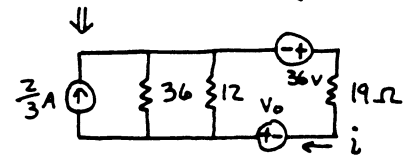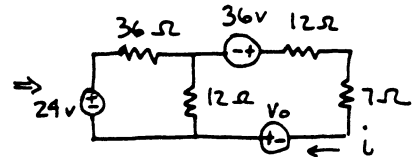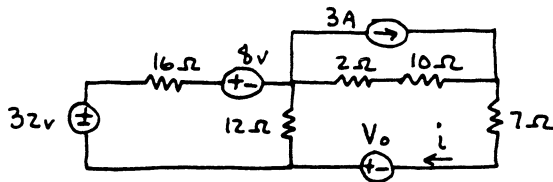

$$\text{KVL } \uparrow: -6 + i(9+19) - 36 - V_o = 0$$

$$\Rightarrow V_o = -42 + 28(5/2) = 28\text{V}$$

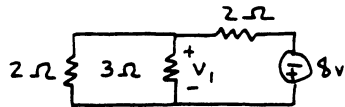
P. 5-5 consider 8V source only (short 4V source)



from voltage divider

$$V_1 = -8\text{V} \left[\frac{2/3}{2/3 + 2} \right] = (-8) \left(\frac{1.2}{3.2} \right) = -3\text{V}$$

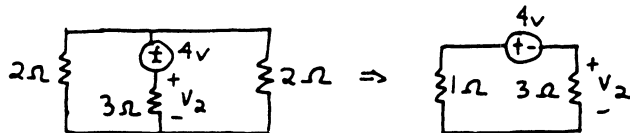consider 4V source only (short 8V source)




Voltage divider

$$V_2 = -4\text{V} \left(\frac{3}{3+1} \right) = -3\text{V}$$

$$\therefore V = V_1 + V_2 = -3 - 3 = -6\text{ volts}$$

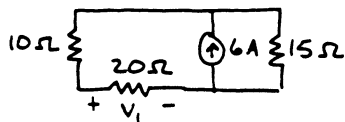
P. 5-6 consider 6A source only (open 9A source)



from current divider

$$V_1/20 = 6 \left[\frac{15}{15+30} \right] \Rightarrow V_1 = 40\text{V}$$

consider 9A source only (open 6A source)

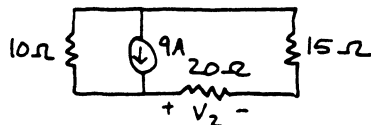


current divider :


$$V_2/20 = 9 \left[\frac{10}{10+35} \right] \Rightarrow V_2 = 40\text{V}$$

$$\therefore V = V_1 + V_2 = 40 + 40 = 80\text{V}$$

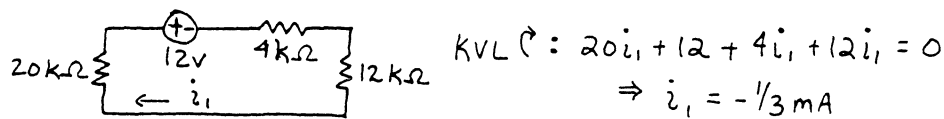
P.5-7 consider 12v source only (open both current sources)



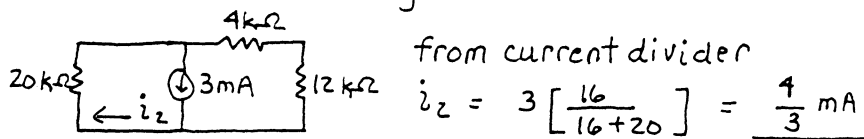consider 12mA source only (short 12v and open 6mA sources)




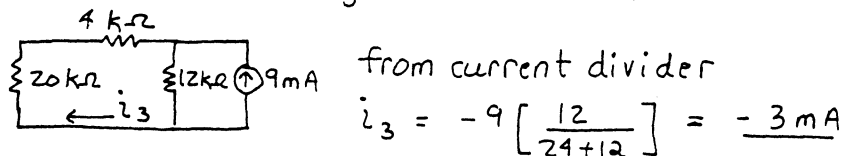consider 9mA source only (short 12v and open 12mA sources)



$$\therefore i = i_1 + i_2 + i_3 = -1/3 + 4/3 - 3 = -2 \text{ mA}$$

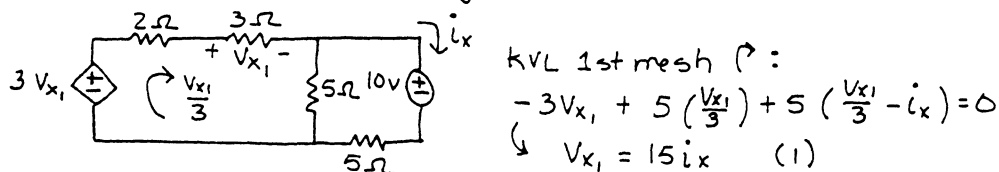
P.5-8 consider 10v source only (open 4A source)



$$\text{KVL 2nd mesh } \uparrow: 5(i_x - V_{x1}/3) + 10 + 5i_x = 0 \quad (2)$$

Solving (1) and (2) simultaneously $\Rightarrow V_{x1} = 10 \text{ V}$

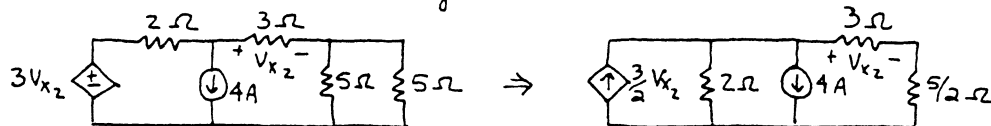consider 4A source only (short 10v source)




using current divider

$$\frac{V_{x2}}{3} = \left(\frac{3}{2}V_{x2} - 4 \right) \left(\frac{2}{2+3+5/2} \right) \Rightarrow V_{x2} = 16 \text{ V}$$

$$\therefore V_x = V_{x1} + V_{x2} = 10 + 16 = 26 \text{ V}$$

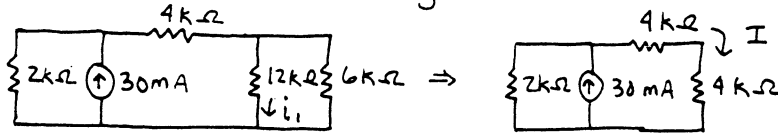
P.5-9 consider 30mA source only (open 15mA and short 60v sources)



$$\text{current divider} \Rightarrow I = 30 \left(\frac{2}{2+8} \right) = 6 \text{ mA}$$

$$\therefore i_1 = I \left(\frac{6}{6+12} \right) = \underline{2 \text{ mA}}$$

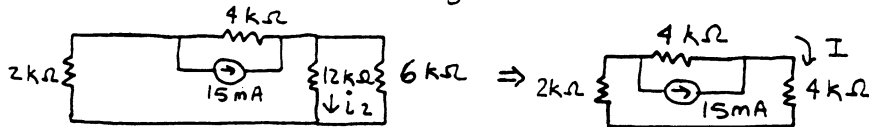
consider 15mA source only (open 30mA source and short 60v source)



$$\text{current divider} \Rightarrow I = 15 \left(\frac{4}{4+6} \right) = 6 \text{ mA}$$

$$\therefore i_2 = I \left(\frac{6}{6+12} \right) = \underline{2 \text{ mA}}$$

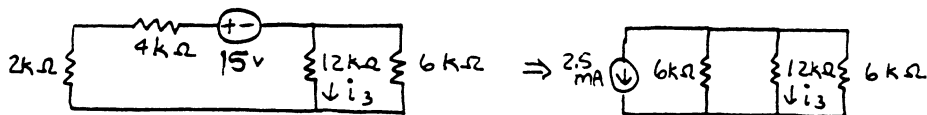consider 15v source only (open both current sources)





from current divider


$$i_3 = -2.5 \left(\frac{6//6}{6//6+12} \right) = -10 \left(\frac{3}{3+12} \right) = \underline{-0.5 \text{ mA}}$$

$$\therefore i = i_1 + i_2 + i_3 = 2 + 2 - 0.5 = \underline{3.5 \text{ mA}}$$

P.5-10 use source transformations

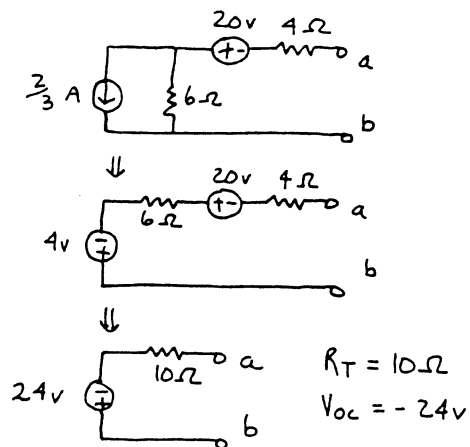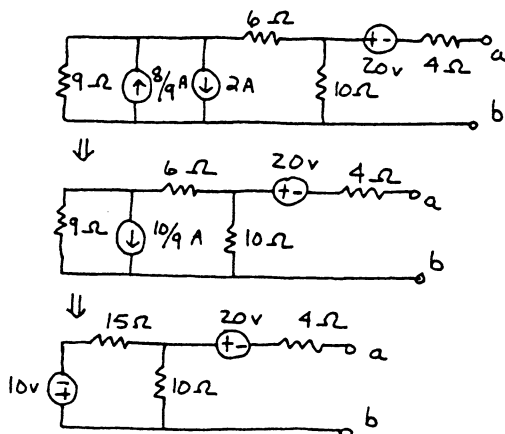

P. 5-11 find V_{oc}

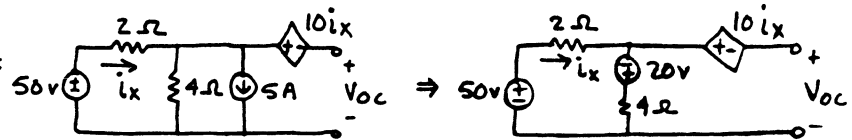


$$\text{KVL around 1st mesh } \Rightarrow -50 + 2i_x - 20 + 4i_x = 0 \Rightarrow i_x = 70/6 \text{ A}$$

$$\text{KVL around 2nd mesh } \Rightarrow -4i_x + 20 + 10i_x + V_{oc} = 0$$

$$\Rightarrow \underline{V_{oc} = -90\text{V}}$$

find i_{sc}

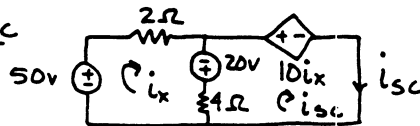

$$\text{KVL } i_x \text{ mesh } \Rightarrow -50 + 2i_x - 20 + 4(i_x - i_{sc}) = 0$$

$$\downarrow \underline{6i_x - 4i_{sc} - 70 = 0} \quad (1)$$

$$\text{KVL } i_{sc} \text{ mesh } \Rightarrow 4(i_{sc} - i_x) + 20 + 10i_x = 0$$

$$\downarrow \underline{6i_x + 4i_{sc} + 20 = 0} \quad (2)$$


$$\text{solving (1) and (2) simultaneously } \Rightarrow \underline{i_{sc} = -45/4 \text{ A}}$$

$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \underline{8\Omega}$$

Thev equiv. ckt:



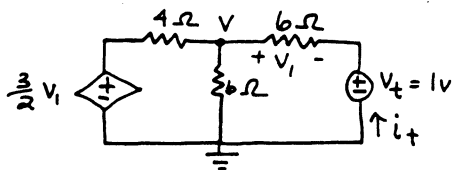P. 5-12 since no independent sources $V_{oc} = i_{sc} = 0 \therefore$ apply test source



$$V = V_1 + V_t$$


$$\text{KCL at } V: (V - \frac{3}{2}V_1)/4 + V/6 + V_1/6 = 0 \quad \text{with } V = V_1 + 1$$

$$\downarrow \underline{V_1 = -2\text{A}}$$

$$\text{now } i_T = -\frac{V_1}{6} = \underline{1/3 \text{ A}}$$

$$\therefore R_T = \frac{V_t}{i_t} = \frac{1}{1/3} = \underline{3\Omega}$$

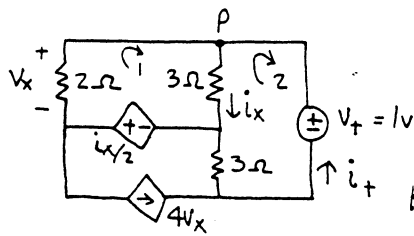P.5-13 since only have dependent sources, $V_{oc} = i_x = 0$, $\therefore$ use test source



$$\text{KVL (mesh 1): } -V_x + 3i_x - 1/2 i_x = 0$$

$$\downarrow V_x = 5/2 i_x \quad (1)$$

$$\text{KVL (mesh 2): } 1 + 3(-i_T + 4V_x) - 3i_x = 0$$


$$\downarrow 12V_x - 3i_T - 3i_x + 1 = 0 \quad (2)$$

$$\text{KCL at P: } V_x/2 + i_x - i_T = 0 \quad (3)$$

solving (1), (2) & (3) simultaneously yields $i_T = -1/9 \text{ A}$

$$\therefore R_T = \frac{V_T}{i_T} = \frac{1}{-1/9} = -9\Omega$$

P.5-14 find V_{oc}

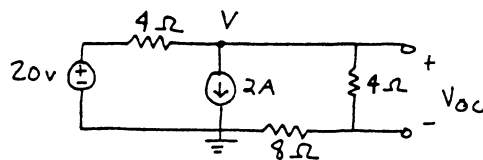


$$\text{KCL at V: } (V-20)/4 + 2 + V_{oc}/4 = 0$$

$$\downarrow V + V_{oc} - 12 = 0 \quad (1)$$

$$\text{voltage divider: } V_{oc} = V \left(\frac{4}{4+8} \right) = V \left(\frac{1}{3} \right) \quad (2)$$


solving (1) & (2) simultaneously $\Rightarrow V_{oc} = 3\text{V}$

find R_T (kill all sources)

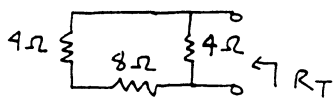


$$R_T = 4 \parallel 8 = 3\Omega$$

Thev. equiv. ckt $\Rightarrow$

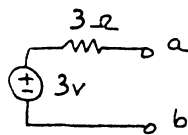

P. 5-15 find V_{oc}

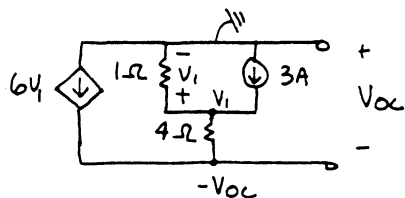

$$\text{KCL at } V_1: V_1 - 3 + (V_1 + V_{oc})/4 = 0$$


$$\Rightarrow 5V_1 + V_{oc} - 12 = 0 \quad (1)$$

$$\text{KCL at } -V_{oc}: -6V_1 + (-V_{oc} - V_1)/4 = 0$$

$$\Rightarrow -25V_1 = V_{oc} \quad (2)$$

solving (1) & (2) simultaneously $\Rightarrow V_{oc} = 15V$

find i_{sc}

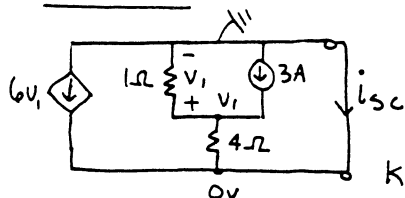

$$\text{KCL at } V_1: V_1 - 3 + (V_1)/4 = 0$$

$$\Rightarrow V_1 = 12/5 V$$


$$\text{KCL at } 0V: -6V_1 - V_1/4 - i_{sc} = 0$$

$$\Rightarrow i_{sc} = -15A$$

$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{15}{-15} = -1\Omega$$



P. 5-16 (a) find V_{oc}

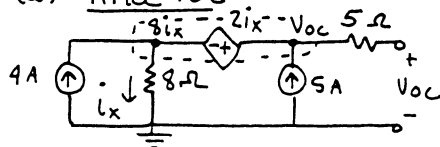


$$\text{KCL at supernode: } -4 + i_x - 5 = 0$$

$$\Rightarrow i_x = 9A$$

$$V_{oc} = 8i_x + 2i_x = 10i_x = 90V$$

find i_{sc}

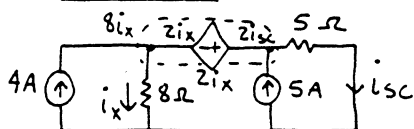


$$\text{KCL at supernode: } -4 + i_x - 5 + i_{sc} = 0$$

$$\Rightarrow i_x + i_{sc} = 9 \quad (1)$$


$$5i_{sc} = 10i_x \quad (2)$$

solving (1) & (2) simultaneously $\Rightarrow i_{sc} = 6A$

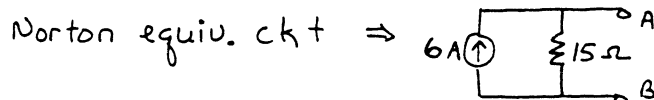
$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{90}{6} = 15\Omega$$




P. 5-16 continued

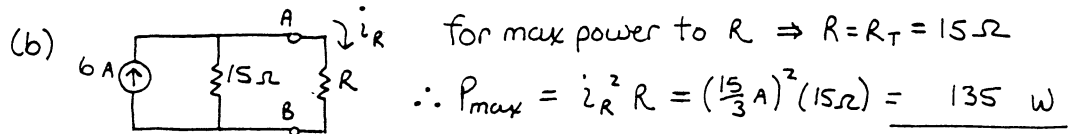


P. 5-17 find V_{oc}

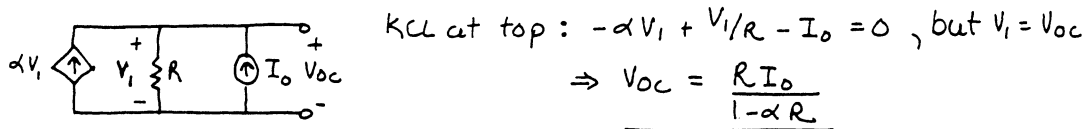


find i_{sc}

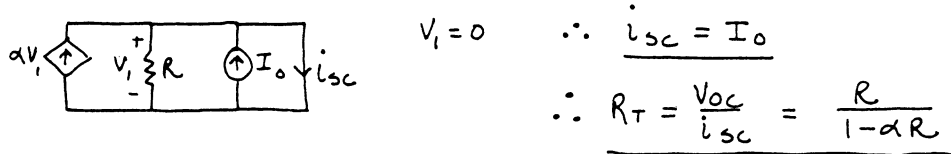


Norton equiv.

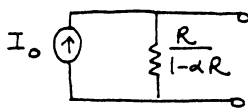


Thev. equiv.

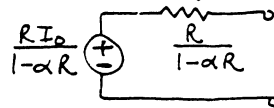

P. 5-18 find V_{oc}

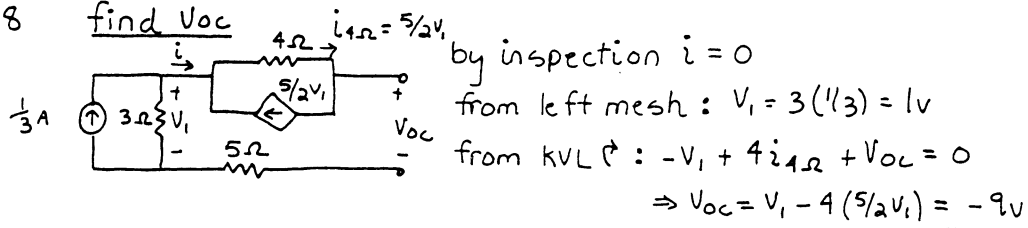

find i_{sc}

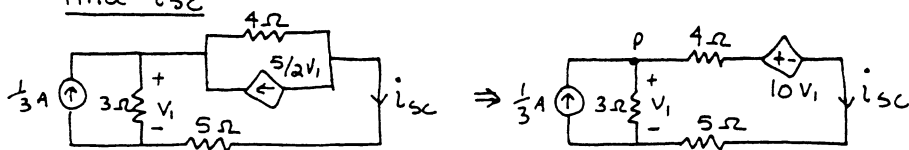


from KVL $\uparrow$: $-V_1 + 4i_{sc} + 10V_1 + 5i_{sc} = 0$
 $\hookrightarrow 9V_1 + 9i_{sc} = 0 \quad (1)$


from KCL at P: $-\frac{1}{3} + \frac{V_1}{3} + i_{sc} = 0 \quad (2) \quad (1) \text{ \& } (2) \text{ yields } \underline{i_{sc} = \frac{1}{2}A}$

$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{-9}{1/2} = \underline{-18\Omega}$

Norton equiv. ckt:

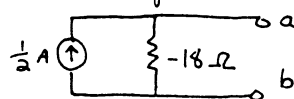

P. 5-19 find V_{oc}

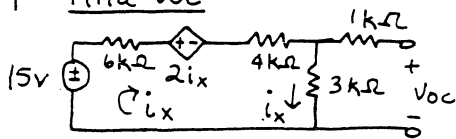


$$\text{KVL } \uparrow i_x: -15 + i_x(6+4) + 2i_x + 3i_x = 0$$

$$\Rightarrow i_x = 1\text{mA}$$

$$\therefore V_{oc} = 3i_x = 3\text{V}$$

find i_{sc}

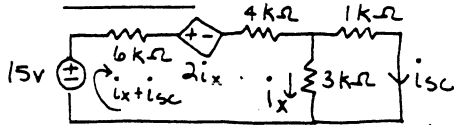


$$\text{KVL } \uparrow i_x + i_{sc}: -15 + 2i_x + 10(i_x + i_{sc}) + 3i_x = 0$$

$$\downarrow -15 + 15i_x + 10i_{sc} = 0 \quad (1)$$


$$\text{KVL } \uparrow i_{sc}: -3i_x + i_{sc} = 0 \quad (2)$$

solving (1) & (2) simultaneously yields: $i_{sc} = 1\text{mA}$
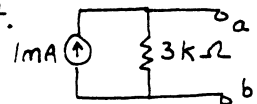
$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{3}{1} = 3\text{k}\Omega \quad \text{Norton equiv. ckt.}$$



P. 5-20 find V_{oc}

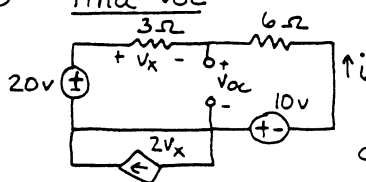


$$\text{KVL left mesh } \uparrow: -20 + V_x + V_{oc} = 0 \quad (1)$$

$$\text{KVL right mesh } \uparrow: -V_{oc} - 6i - 10 = 0 \quad (2)$$

$$\text{also } V_x = -3i \quad (3)$$

solving (1), (2) & (3) simultaneously yields $\Rightarrow V_{oc} = 10\text{V}$

find i_{sc}

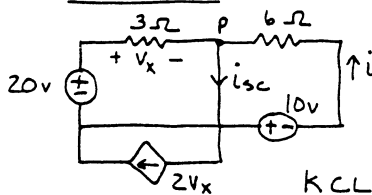

$$\text{KVL left mesh}: -20 + V_x = 0 \Rightarrow V_x = 20\text{V} \quad (1)$$


$$\text{KVL right mesh}: 6i + 10 = 0 \quad (2)$$

$$\text{KCL at P}: -V_x/3 - i + i_{sc} = 0 \quad (3)$$


(1), (2) & (3) yield: $i_{sc} = 5\text{A}$

$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{10}{5} = 2\Omega$$

Norton equiv. ckt.

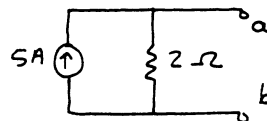

P.5-21 find V_{oc}

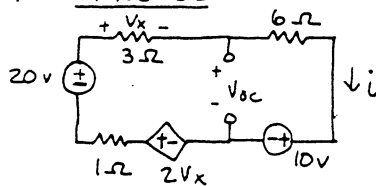

$$\text{KVL } \uparrow \text{ entire loop: } -20 + V_x + 6i + 10 - 2V_x + i = 0$$


$$\Rightarrow 7i - V_x - 10 = 0 \quad (1)$$

$$\text{KVL } \uparrow \text{ right loop: } -V_{oc} + 6i + 10 = 0 \quad (2)$$

$$\text{also } V_x = 3i \quad (3)$$

$$\text{solving (1), (2) \& (3) yields } \Rightarrow \underline{V_{oc} = 25V}$$

find i_{sc}

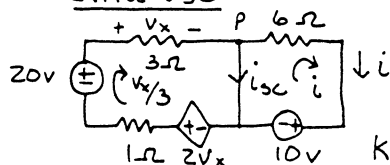


$$\text{KVL } \uparrow V_x/3 \text{ mesh: } -20 + V_x - 2V_x + V_x/3 = 0$$

$$\Rightarrow \underline{V_x = -30V}$$

$$\text{KVL } \uparrow i \text{ mesh: } 6i + 10 = 0 \Rightarrow \underline{i = -5/3 A}$$


$$\text{KCL at P: } -V_x/3 + i_{sc} + i = 0 \Rightarrow \underline{i_{sc} = V_x/3 - i = -25/3 A}$$
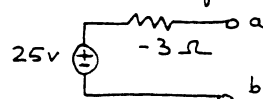
$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{25}{-25/3} = \underline{-3\Omega} \quad \text{Thev. equiv. ckt}$$




P.5-22 (a) for max power need $R_L = R_T$ $\therefore$ find R_T

kill current source

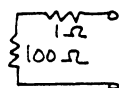

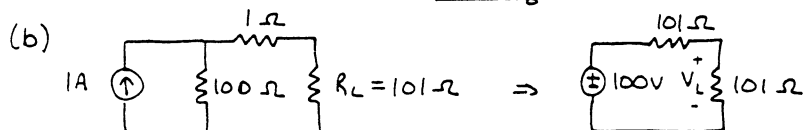
$$\leftarrow \underline{R_T = 101\Omega = R_L}$$




$$\underline{P_{max} = V_L^2 / 101 = (50)^2 / 101 = 24.75W}$$

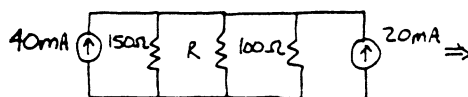P.5-23 (a) use source transformations to reduce ckt.




Norton equiv. where $R_T = 60\Omega$

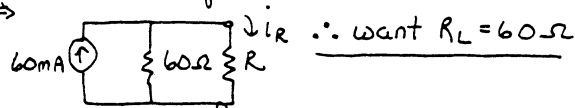

$$(b) \underline{P_{max} = i_R^2 (R) = (30)^2 (60) = 54,000\mu W = 54mW}$$

P. 5-24

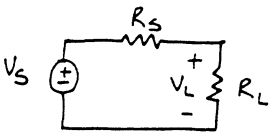


$$V_L = V_s \left[\frac{R_L}{R_s + R_L} \right]$$

$$\therefore P_L = \frac{V_L^2}{R_L} = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$

By inspection,
 P_L is max when you vary R_s to get the smallest denominator. $\therefore$ set $R_s = 0$

P. 5-25 find $R_T = V_{oc}/i_{sc}$


find V_{oc}

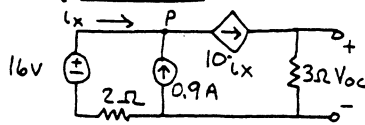

$$\text{KCL at P: } -i_x - .9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$$

$$\therefore V_{oc} = 3(10i_x) = 3 \text{ V}$$


find i_{sc}

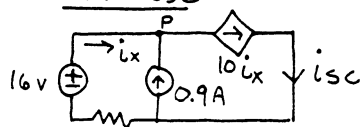

$$\text{KCL at P: } -i_x - .9 + 10i_x = 0 \Rightarrow i_x = 0.1 \text{ A}$$


$$\therefore i_{sc} = 10i_x = 1 \text{ A}$$
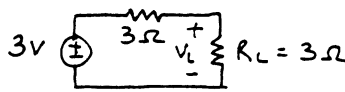
$$\therefore R_T = V_{oc}/i_{sc} = 3 \Omega = R_L \text{ for max power}$$



$$P_{L_{max}} = \frac{V_L^2}{R_L} = \frac{(1.5)^2}{3} = 0.75 \text{ W}$$

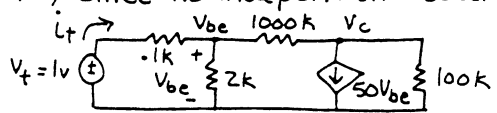P. 5-26 (a) since no independent sources apply test source



$$\text{KCL at } V_{be}: -i_t + \frac{1}{2} V_{be} + (V_{be} - V_c)/1000 = 0$$

$$(1) \quad \downarrow -1000i_t + 50V_{be} - V_c = 0$$

$$\text{KCL at } V_c: (V_c - V_{be})/1000 + 50V_{be} + V_c/100 = 0$$

$$\downarrow 11V_c + 50000V_{be} = 0 \quad (2)$$


$$\text{also } (1 - V_{be})/.1 = i_t \quad (3)$$

solving (1), (2) & (3) simultaneously yields $i_t = 3.35 \text{ mA}$

$$\therefore R_{in} = \frac{V_t}{i_t} = \frac{1 \text{ V}}{3.35 \text{ mA}} = .299 \text{ k}\Omega = 299 \Omega$$

P. 5-26 continued

(b) apply test source

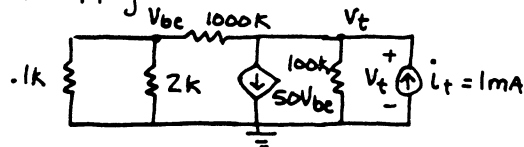

$$\text{KCL at } V_{be} : V_{be}/1 + V_{be}/2 + (V_{be} - V_t)/1000 = 0$$

$$\hookrightarrow 10501 V_{be} = V_t \quad (1)$$


$$\text{KCL at } V_t : (V_t - V_{be})/1000 + 50V_{be} + V_t/100 - 1 = 0$$

$$\hookrightarrow 11V_t + 49999V_{be} - 1000 = 0 \quad (2)$$


solving (1) & (2) yields : $V_t = 63.5 \text{ v}$

$$\therefore R_{out} = V_t / i_t = 63.5 \text{ v} / 1 \text{ mA} = 63.5 \text{ k}\Omega$$


P. 5-27 redraw the ckt.

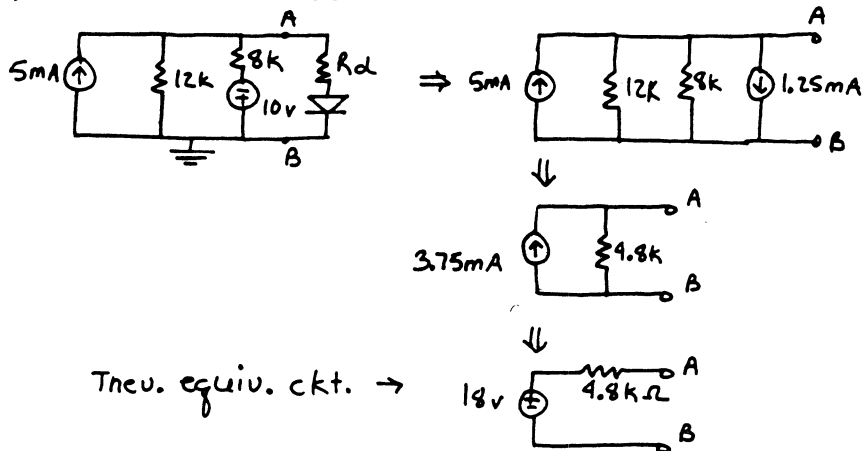

P. 5-28 redraw ckt as:

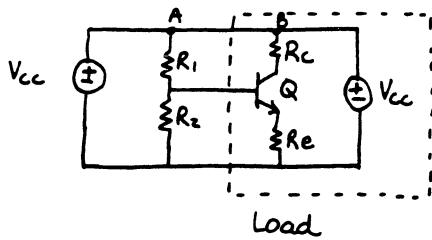

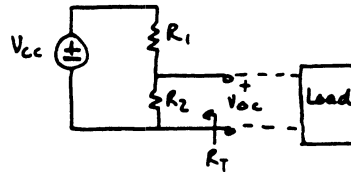
since points A & B are at same potential virtually no current exists between A-B $\therefore$ open ckt.



find R_T : kill V_{cc} source $\Rightarrow R_T = R_1 // R_2 = R_1 R_2 / (R_1 + R_2)$

find V_{oc} : voltage divider $V_{oc} = V_{cc} \left(\frac{R_2}{R_1 + R_2} \right)$

$\therefore$ can replace above ckt as:

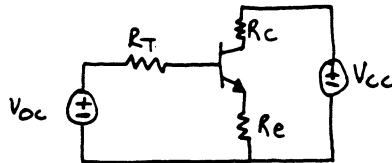


where $V_{oc} = V_{cc} \left(\frac{R_2}{R_1 + R_2} \right)$

$$R_T = \frac{R_2 R_1}{R_2 + R_1}$$

P. 5-29 (a) for max power $R_L = R_T$

find V_{oc}

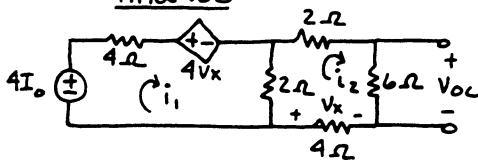

$$\text{KVL } i_1: -4I_o + 4i_1 + 4V_x + 2(i_1 - i_2) = 0$$

$$\hookrightarrow 6i_1 - 2i_2 + 4V_x - 4I_o = 0 \quad (1)$$


$$\text{KVL } i_2: 2i_2 + 6i_2 - V_x + 2(i_2 - i_1) = 0$$

$$\hookrightarrow -2i_1 + 10i_2 - V_x = 0 \quad (2)$$

$$\text{also } V_x = -4i_2 \quad (3) \quad \text{and } V_{oc} = 6i_2 \quad (4)$$

solving (1), (2), (3) & (4) yields $V_{oc} = I_o$

find i_{sc}

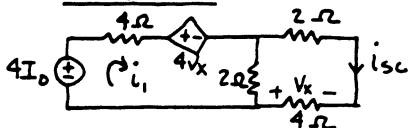

$$\text{KVL } i_1: -4I_o + 4i_1 + 4V_x + 2(i_1 - i_{sc}) = 0$$

$$\hookrightarrow 6i_1 - 2i_{sc} + 4V_x - 4I_o = 0 \quad (1)$$

$$\text{KVL } i_{sc}: 2i_{sc} + 4i_{sc} + 2(i_{sc} - i_1) = 0$$

$$\hookrightarrow -2i_1 + 8i_{sc} = 0 \quad (2)$$


$$\text{also } V_x = -4i_{sc} \quad (3)$$

solving (1), (2) & (3) yields $i_{sc} = \frac{2}{3}I_o$ $\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{3}{2}\Omega = R_L$

$$(b) P_{Lmax} = 54 \text{ W} = \frac{(V_{oc}/2)^2}{R_L} = I_o^2/6$$

$$\Rightarrow I_o = 18 \text{ A}$$

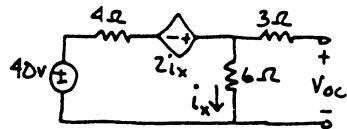P.5-30 (a) find V_{oc} (transform current source)




$$\text{KVL } \uparrow: -40 + 4i_x - 2i_x + 6i_x = 0$$

$$\Rightarrow i_x = 5A$$

$$\therefore V_{oc} = 6i_x = 30V$$

find i_{sc}

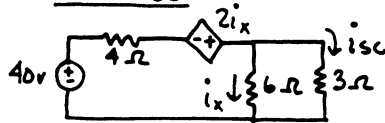

$$\text{KVL } \uparrow: -40 + 4(i_x + i_{sc}) - 2i_x + 6i_x = 0$$


$$\downarrow -40 + 8i_x + 4i_{sc} = 0 \quad (1)$$

$$\text{also } 6i_x = 3i_{sc} \quad (2)$$

Solving (1) & (2) yields $i_{sc} = 5A$


$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{30}{5} = 6\Omega$$

Thev. equiv. ckt :

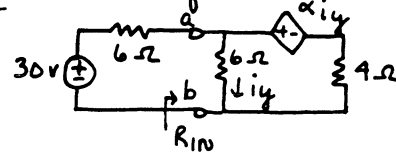

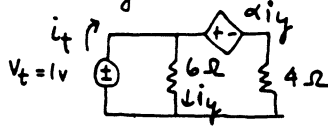(b) for max power $R_{LN} = R_T = 6\Omega$

apply a test source since no independent sources present



$$R_{LN} = \frac{V_t}{i_t}$$


$$i_y = \frac{1}{6}$$

$$\text{KVL } \uparrow: \alpha(1/6) + 4(i_t - 1/6) - 1 = 0$$

$$\downarrow \alpha + 24i_t - 10 = 0 \quad (1)$$

from (1) and $R_{LN} = 1/i_t = 6$ yields $\alpha = 6$


P.5-31 consider V_2 source only

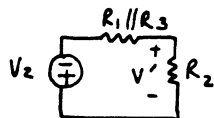

$$\text{voltage divider: } V' = -V_2 \left[\frac{R_2}{R_2 + R_1 // R_3} \right]$$

$$V' = -V_2 \left[\frac{R_2(R_1 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$$

consider V_1 source only

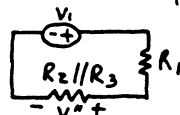

$$\text{voltage divider } V'' = V_1 \left[\frac{R_2 // R_3}{R_2 // R_3 + R_1} \right]$$

$$V'' = V_1 \left[\frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right]$$


consider i_1 source only



$$V''' = 0 \text{ since no current flows through } R_2, R_3 \text{ and } R_1.$$

$$\therefore V = V' + V'' + V''' = \frac{V_1 R_2 R_3 - V_2 (R_2 (R_1 + R_3))}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$



P. 5-32 find V_{oc}

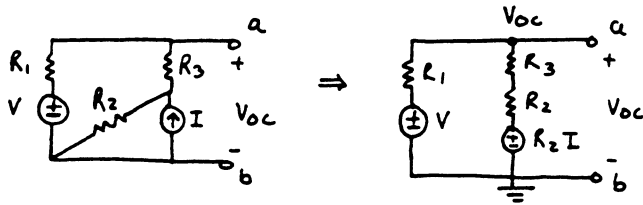

$$\text{KCL at } V_{oc} : (V_{oc} - V)/R_1 + (V_{oc} - R_2 I)/R_2 + R_3 = 0$$


$$\Rightarrow V_{oc} = \frac{V(R_2 + R_3) + R_1 R_2 I}{R_1 + R_2 + R_3}$$

find R_T (kill sources)

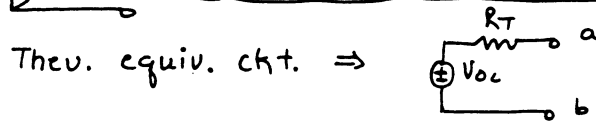
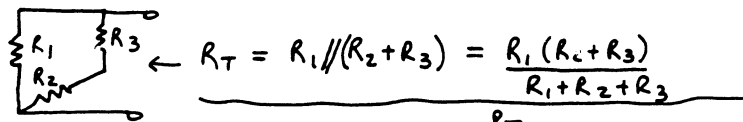


P. 5-33 From the graph, when $V_{ab} = V = 0 \Rightarrow i = i_{sc} = 20 \text{ mA}$
 when $i = 0 \Rightarrow V = V_{oc} = -3 \text{ V}$

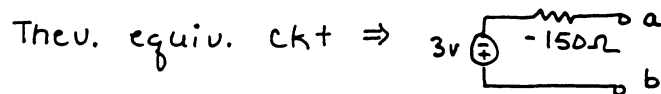
$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{-3 \text{ V}}{20 \text{ mA}} = -150 \Omega = -150 \Omega$$



P. 5-34 use source transformations

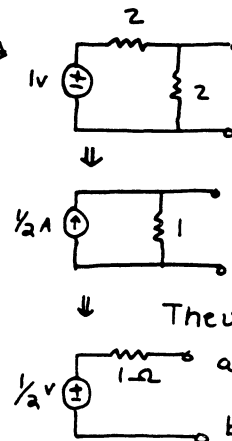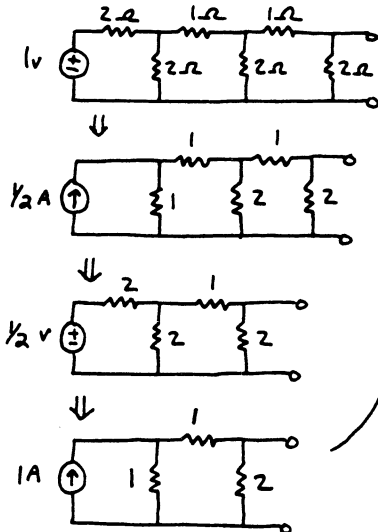

P. 5-35

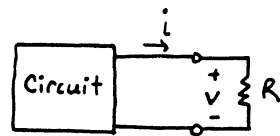


with R absent (open ckt): $V = 1.5\text{v} \Rightarrow i = V/\infty = 0$

with $R = 10\text{k}\Omega$: $V = 0.25\text{v} \Rightarrow i = V/R = 0.025\text{mA}$

with $R = 100\text{k}\Omega$: $V = 1.0\text{v} \Rightarrow i = 0.01\text{mA}$

plot i vs V

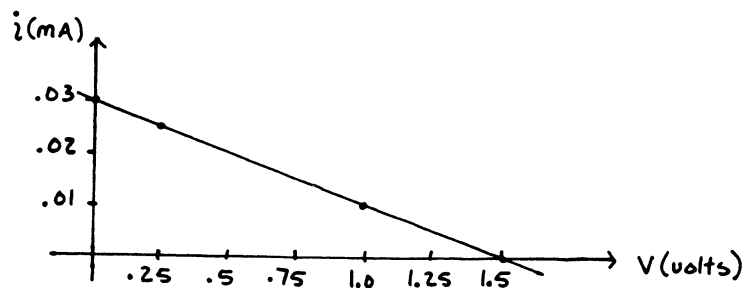

Since i vs V is linear $\Rightarrow$ circuit is linear


$V_{oc} = 1.0\text{v}$ (when $i = 0$, terminals opened)

$i_{sc} = 0.03\text{mA}$ (when $V = 0$, terminals shorted)

$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = \frac{1.0\text{v}}{0.03\text{mA}} = 33.3\text{k}\Omega$$

Thev. equiv. ckt $\Rightarrow$


p 5-36 for i_{sc} :

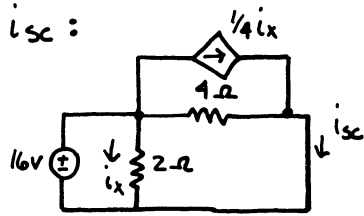

$$i_x = \frac{16}{2} = 8 \text{ A}$$


$$\therefore i_{sc} = \frac{16}{4} + \frac{8}{4} = 6 \text{ A}$$

to find R_n , turn off 16V source

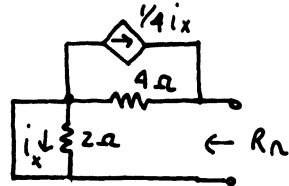


note: $i_x = 0 \Rightarrow R_{eq} = R_n = 4 \Omega$

Norton equiv.

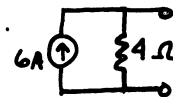

p 5-37 for V_{oc} :

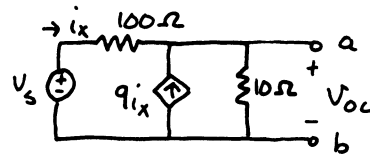


$$i_x = \frac{V_s - V_{oc}}{100}$$

KCL at terminal a:

$$\frac{1}{100} (V_{oc} - V_s) - 9 \left[\frac{1}{100} (V_s - V_{oc}) \right] + \frac{1}{10} V_{oc} = 0$$

$$\Rightarrow V_{oc} = \frac{1}{2} V_s$$

use current source at a-b to find R_T :

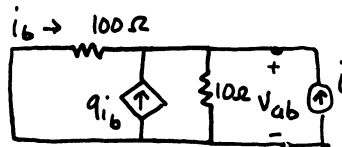


$$i_b = -\frac{V_{ab}}{100}$$


$$\text{KCL: } \frac{1}{100} V_{ab} - 9 \left[\frac{1}{100} (-V_{ab}) \right] + \frac{1}{10} V_{ab} - i = 0$$

$$\Rightarrow i = \frac{1}{5} V_{ab} \quad \therefore R_T = \frac{V_{ab}}{i} = 5 \Omega$$

so Thev. equiv.

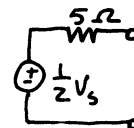

P 5-38 find i_{sc} :

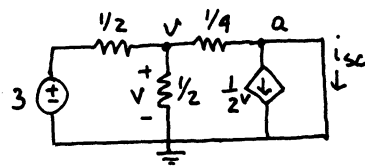


$$\text{KCL at } v: \frac{v-3}{1/2} + \frac{v}{1/2} + \frac{v}{1/4} = 0$$

$$\Rightarrow v = 3/4 \text{ V}$$

$$\text{KCL at } a: i_{sc} = \frac{v}{1/4} - \frac{v}{2} = \underline{\underline{\frac{21}{8} \text{ A}}}$$

to find R_T set source = 0

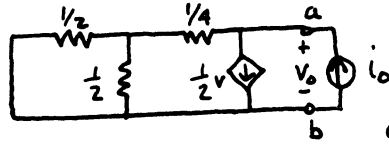


$$\text{at } v: \frac{v}{1/2} + \frac{v}{1/2} + \frac{v-V_o}{1/4} = 0 \Rightarrow v = \frac{V_o}{2}$$

$$\text{at } a: i_o = \frac{1}{2} v + \frac{V_o - v}{1/4} = \frac{9}{4} V_o$$

$$\therefore R_T = \frac{V_o}{i_o} = \underline{\underline{\frac{4}{9} \Omega}}$$


P 5-39 1) 10V source

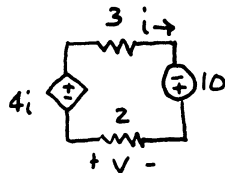

$$\text{KVL: } -4i + 3i - 10 + 2i = 0 \Rightarrow i = 10 \text{ A}$$

$$\text{so } \underline{\underline{V = -2(10) = -20 \text{ V}}}$$


2) 8A source

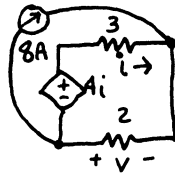

$$\text{KVL: } 3i - 4i + 2(8+i) = 0 \Rightarrow i = -16 \text{ A}$$

$$\text{so } \underline{\underline{V = -2(8+i) = 16 \text{ V}}}$$

3) 2A source

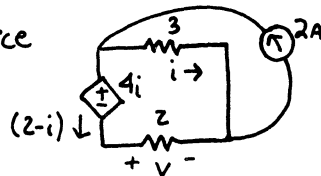


$$\text{KVL: } 3i - 2(2-i) - 4i = 0 \Rightarrow i = 4 \text{ A}$$

$$\text{so } \underline{\underline{V = 2(2-i) = -4 \text{ V}}}$$

$$\therefore \underline{\underline{V_T = -20 + 16 - 4 = -8 \text{ V}}}$$

P 5-40 find V_{oc} :

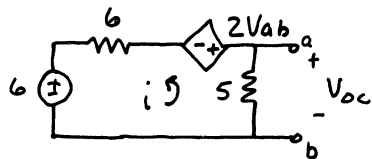


$$KVL: 6 + 11i + 2V_{ab} = 0$$

$$\Downarrow 6 + 11i + 2(5(-i)) = 0 \Rightarrow i = -6A$$

$$\therefore V_{oc} = -i(5) = \underline{30V}$$


find R_T :

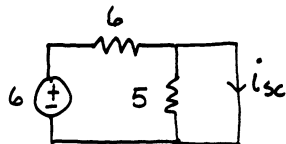



$$-6 + 6i_{sc} = 0 \quad \text{so } i_{sc} = 1A$$

$$\therefore R_T = V_{oc}/i_{sc} = \underline{30\Omega}$$

so have

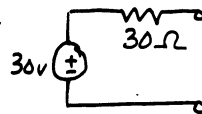


P 5-41 find R_T :

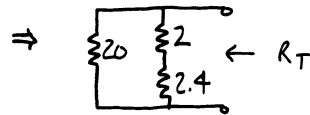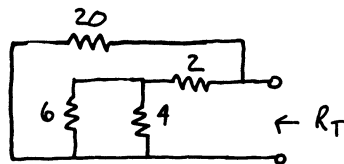

$$R_T = \frac{20(2+2.4)}{20+2+2.4} = \underline{3.61\Omega}$$

find V_T :

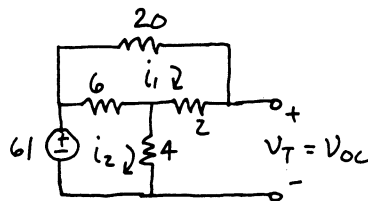

$$V_T = 2i_1 + 4i_2$$


$$\text{mesh } i_1: 28i_1 - 6i_2 = 0 \quad (1)$$

$$\text{mesh } i_2: -6i_1 + 10i_2 - 6 = 0 \quad (2)$$

$$\text{solving (1) \& (2) yields: } i_1 = 1.5A, i_2 = 7A$$

$$\therefore V_T = 3 + 28 = \underline{31V}$$

P 5-42

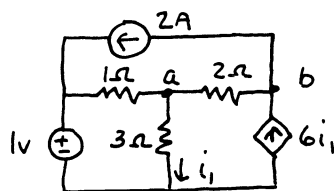

$$KCL \text{ at } b: i + 6i_1 - 2 = 0$$

$$\Rightarrow i_1 = 1/3 - 1/6 i \quad (1)$$


$$KVL \text{ around left lower mesh:}$$

$$1(i_1 + i) + 3i_1 - 1 = 0 \quad (2)$$

$$\text{plugging (1) into (2)} \Rightarrow \underline{i = -1A}$$


P 5-43 first find V_{oc} by superposition

12V source

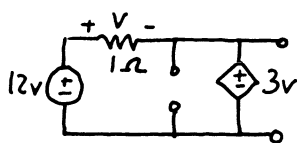

$$\begin{aligned} \text{KVL: } V + 3V - 12 &= 0 \\ \Rightarrow V &= 3\text{volts} \\ \therefore V_{oc} &= 3V = 9\text{volts} \end{aligned}$$


i source

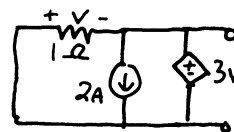


$$\begin{aligned} \text{KVL: } V + 3V &= 0 \\ \Rightarrow V &= 0 \\ \therefore V_{oc} &= 0 \end{aligned}$$

so total $V_{oc} = 9 + 0 = 9\text{volts}$


find R_T

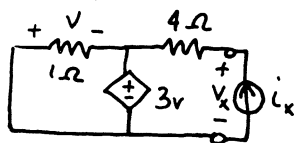
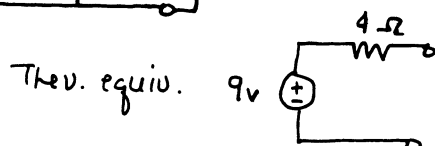
$$\begin{aligned} \text{KVL: } 4i_x + 3V &= V_x \quad \text{also } V = -3V \Rightarrow V = 0 \\ \text{so } V_x &= 4i_x \Rightarrow R_T = V_x / i_x = 4\Omega \end{aligned}$$




P 5-44 find V_{oc} :

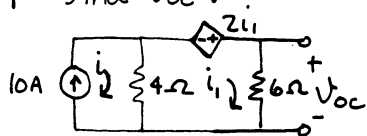

$$\begin{aligned} i &= 10A; \text{KVL 2nd mesh: } 4i_1 - 2i_1 + 6i_1 - 4i_1 = 0 \\ &\Rightarrow i_1 = 5A \\ \text{so } V_{oc} &= 6i_1 = 30V \end{aligned}$$

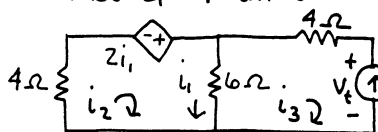find $R_T \Rightarrow$ kill 10A source & drive terminals a-b with current source



$$i_3 = -i_t \quad \text{KVL } i_2: 4i_2 + 2i_1 + 6(i_1 + i_t) = 0 \quad (1)$$


$$\text{also: } i_2 = i_1 - i_t \quad (2)$$

(1) & (2) yields $i_t = -6i_1$

now $V_t = 6i_1 + 4i_t = -i_t + 4i_t = 3i_t$


$\therefore R_T = \frac{V_t}{i_t} = 3\Omega$

P 5-45 find V_{oc}

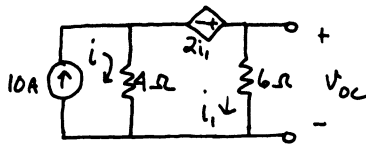

$$\begin{aligned} \text{KVL: } 4i_1 - 2i_1 + 6i_1 - 4i_1 &= 0 \quad \text{and } i_1 = 10A \\ \Rightarrow i_1 &= 40/8 = 5A \\ \therefore V_{oc} &= 6i_1 = 30V \end{aligned}$$

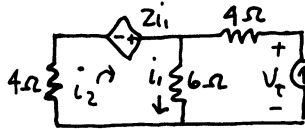find $R_T \Rightarrow$ kill 10A source & drive terminals a-b



$$\text{KVL left loop: } 4i_2 + 2i_1 + 6(i_1 + i_t) = 0 \quad (1)$$


$$\text{also: } i_2 = i_1 - i_t \quad (2)$$

$$\text{from (1) \& (2) } \Rightarrow i_1 = -1/6 i_t$$

$$\text{now } V_t = 6i_1 + 4i_t = -i_t + 4i_t = 3i_t \Rightarrow R_T = \frac{V_t}{i_t} = 3\Omega$$

Advanced Problems

AP 5-1 apply test source to output

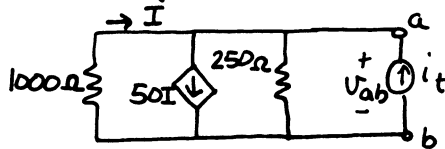

$$\text{KCL: } -I + 50I + \frac{V_{ab}}{250} - i_t = 0 \quad (1)$$

$$\text{also: } I = \frac{V_{ab}}{1000} \quad (2)$$

$$(1) \& (2) \text{ yield } i_t = \frac{53}{1000} V_{ab} \quad \text{or } R_{out} = \frac{V_{ab}}{i_t} = \frac{1000}{53} = 18.9\Omega$$

AP 5-2 all 24A flows thru 10Ω so $V = 10(24) = 240V$


current is .05A = 12A

So the voltage across 12Ω $\Rightarrow V_{12} = 12(12) = 144V$

then $V_T = 240 - 144 = 96V$

to find R_T apply 1A at output:

Thev. equiv.

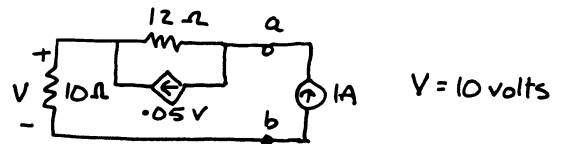


so current source = .5A

$\therefore$ have .5A thru 12Ω $\therefore V_{12\Omega} = 6V$

$\Rightarrow V_{ab} = 6 + 10 = 16V \Rightarrow R_T = 16\Omega$

AP 5-3


- 1) disconnect R_L
open circuit a-b

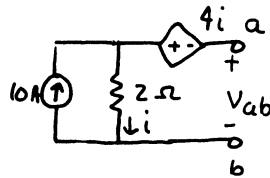

$$\text{KVL: } -V_{ab} - 4i + 2i = 0, \quad i = 10 \text{ A}$$

$$\Rightarrow V_T = V_{ab} = -2i = \underline{-20 \text{ V}}$$

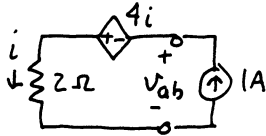- 2) set independent source = 0 and place 1A source at a-b




$$\text{KVL: } -V_{ab} - 4i + 2i = 0, \quad i = 1 \text{ A}$$

$$\Rightarrow V_{ab} = -2 \text{ A}$$

$$\therefore R_T = V_{ab}/1 \text{ A} = \underline{-2 \Omega}$$

- 3) Connect $R_L = 2.2 \Omega$

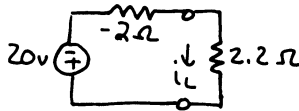


$$i_L = \frac{-20}{-2 + R_L} = \frac{-20}{0.2} = \underline{-100 \text{ A}}$$

AP 5-4

$$P_{\max} = V_T^2 / 4R_T$$

find $R_T \Rightarrow$ kill i source

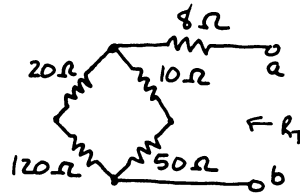

$$R_T = 8 + (20 + 120) // (10 + 50)$$

$$= 50 \Omega$$

find V_{OC} :

$$i_{10\Omega} = \frac{120 + 50}{120 + 50 + 20 + 10} 20 \text{ A}$$


$$= 17 \text{ A}$$

$$\therefore V_{10\Omega} = 10(17) = 170 \text{ V}$$


$$V_{50\Omega} = 50(17 - 20) = -150 \text{ V}$$

$$\Rightarrow V_{OC} = V_{10\Omega} + V_{50\Omega} = 170 - 150 = \underline{20 \text{ V}}$$

$$\therefore P_{\max} = \frac{20^2}{4(50)} = \underline{2 \text{ W}}$$

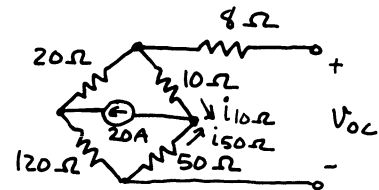

AP 5-5

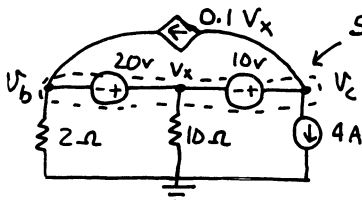



Supernode KCL: $\frac{V_b}{2} + \frac{V_x}{10} + 4 = 0$ (1)

also $V_b = V_x - 20$ (2)

(1) & (2) yields $\underline{V_x = 10 \text{ V}}$

AP 5-6 When the terminals of the boxes are open-circuited, no current flows in Box A, but the resistor in Box B dissipates 1 watt. Box B is therefore warmer than Box A. If you short the terminals of each box, the resistor in Box A will draw 1 amp and dissipate 1 watt. The resistor in Box B will be shorted, draw no current and dissipate no power. Then Box A will warm up and Box B will cool off.

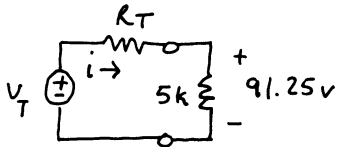AP 5-7 a)  $i = \frac{91.25}{5 \times 10^3} \Rightarrow V_T = \left(\frac{91.25}{5 \times 10^3} \right) R_T + 91.25 \quad (1)$

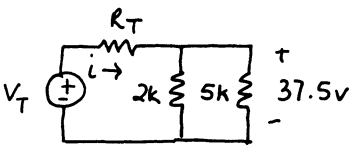b)  $i = \frac{37.5}{10/7 \times 10^3} \Rightarrow V_T = \frac{37.5}{10/7 \times 10^3} R_T + 37.5 \quad (2)$


solving (1) & (2) to get $R_T = 6.72 \text{ k}\Omega$ & $V_T = 213.9 \text{ V}$

AP 5-8 When $0 < V < V_p$ it works as a pure resistor
so $R = V_p / I_p$ $V_{oc} = 0$ 

when $V_p < V < V_m$ it is linear but shows negative resistance characteristic

$$\Rightarrow V_{oc} = V_{oc}|_{I=0} = V_1$$

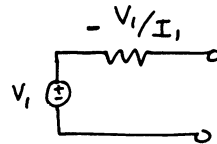
$$R = \frac{V_{oc}}{I_{sc}} = -\frac{V_1}{I_1}$$



when $V_m < V < V_f$ it is linear


$$\text{so } V_{oc} = V|_{I=0} = V_2$$
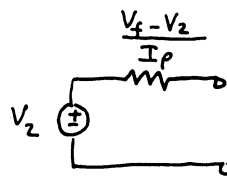
$$R = \frac{V_{oc}}{I_{sc}} = \frac{V_f - V_2}{I_p}$$



AP 5-9 We are asked to vary $R = R_t$, not R_{load} .
Thus $R_t = R_{load}$ is not the optimal solution.
Clearly when $R = 0$, maximum current and voltage (hence maximum power) are delivered to the load.

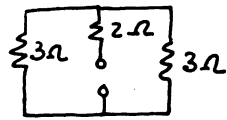AP 5-10 find $R_T \rightarrow$ kill sources



$$R_T = 2 + 3//3 = 3.5 \Omega$$

find V_{oc} :

supernode KCL: $\frac{V_b}{3} - 2 + \frac{V_a}{3} = 0$ (1)

also: $V_a - V_b = 5$ (2)

solving (1) & (2) yields: $V_a = 5.5V$

now $V_{oc} = V_a + 2(2) = 5.5 + 4 = 9.5V$

$\therefore P_{max} = V_{oc}^2 / 4R_T = (9.5)^2 / 4(3.5) = 6.45W$

AP 5-11 (a) $V_o = -g R_L V$ and $V = \frac{R_2}{R_1 + R_2} V_i \Rightarrow \frac{V_o}{V_i} = -g \frac{R_L R_2}{R_1 + R_2}$

(b) so have $\frac{V_o}{V_i} = -g \frac{(5 \times 10^3)(10^3)}{1.1 \times 10^3} = -170$

$\Rightarrow \underline{g = 0.0374 S}$

Design Problems

DP 5-1 find Thev. equiv. with R_L disconnected

$$R_T = 6 + \frac{5(20)}{25} = 10 \Omega$$

$$V_T = V_{oc} = \frac{20}{25}(100) = 80V$$

$$\text{now } P = i^2 R_L = \left(\frac{V_T}{R_L + R_T} \right)^2 R_L = \frac{80^2 R_L}{(R_L + 10)^2} = 150$$

$$\Rightarrow R_L^2 + \left(20 - \frac{6400}{150} \right) R_L + 100 = 0 \Rightarrow R_L = 11.335 \pm 5.333$$

$$\therefore \underline{R_L = 6.00 \Omega \text{ or } 16.67 \Omega}$$

DP 5-2 Thev. equiv.

$I = 10^{-2} A$

$V_T = -30(500)I = -150V$

deactivate source $\Rightarrow I = 0 \therefore R_T = 500 \Omega$

so set $R_L = 500 \Omega$ then $P_{max} = V_T^2 / 4R_L = \frac{(150)^2}{4(500)} = 11.25W$


DP 5-3 at terminal a-b : $R_o = R_T = V_{oc}/i_{sc}$

short circuit output $\Rightarrow V_{ab} = 0$


then $dV_{ab} = 0$

$$\therefore I = \frac{1}{2 \times 10^3} = .5 \text{ mA}$$
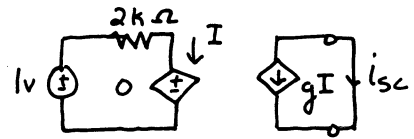
$$\text{so } -g \frac{(10)^{-3}}{2} = i_{sc}$$



find V_{oc} :

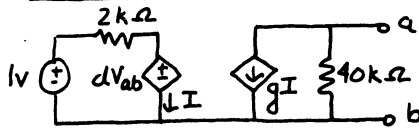

$$\text{right mesh: } V_{ab} = (-gI)(40,000) \quad (1)$$

$$\text{left mesh: } 2000I + .0004 V_{ab} = 1 \quad (2)$$


$$\text{from (1) and (2) get } I = 1/(2000 - 16g)$$

$$\text{now } R_o = 50,000 = V_{oc}/i_{sc} = \frac{V_{oc}}{-g \cdot 10^{-3}/2} \quad (3)$$

$$\text{also } V_{oc} = -g(40,000)I = -g \frac{(40,000)}{(2000 - 16g)} \quad (4)$$

$$\text{solving (3) \& (4) yields } \underline{g = 25}$$

DP 5-4

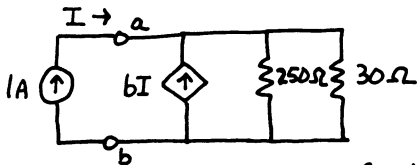

let $I = 1 \text{ A}$, then total current to R_p is

$$I_{R_p} = 1 + bI \quad \text{where } R_p = \frac{250(30)}{250 + 30} = 26.79 \Omega$$

$$\therefore V_{ab} = (1 + bI)(26.79)$$

$$\text{now } R_{in} = 2705 = (1 + bI)(26.79)/1 \text{ A} \Rightarrow 1 + bI = 100.99 \approx 101$$


$$\therefore \underline{b = 100}$$

DP 5-5 desire $R_T = 64 \Omega$

find V_{oc} : with open circuit $i = 8 \text{ A}$, so current thru 12Ω is $i_{12} = d \cdot 8$

$$\therefore V_{oc} = 8 \times 4 + 8d \times 12 = 32(1 + 3d)$$

find i_{sc} :

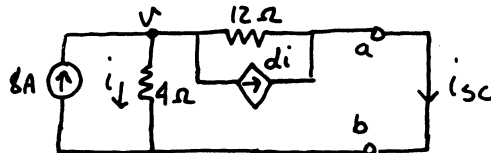


$$\text{KCL at node } v : v/4 + v/12 + d(v/4) = 8 \Rightarrow v = \frac{96}{4 + 3d} \quad (1)$$

$$\text{also: } i_{sc} = d \cdot v/4 + v/12 \quad (2)$$

$$\text{plugging (1) into (2) yields } \Rightarrow i_{sc} = \frac{8(3d + 1)}{4 + 3d}$$

$$\therefore R_T = 64 = \frac{V_{oc}}{i_{sc}} = 4(4 + 3d) \text{ so } \underline{d = 4} \quad \text{thus } \underline{V_T = V_{oc} = 716 \text{ V}}$$


DP5-6

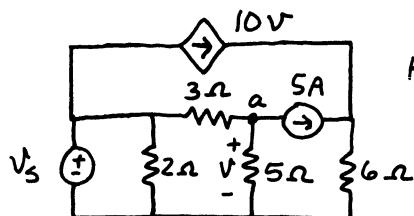

KCL at node a: $V(\frac{1}{5} + \frac{1}{3}) + 5 - \frac{V_s}{3} = 0$

so if $V=0$ then $\underline{V_s = 15V}$


DP 5-7

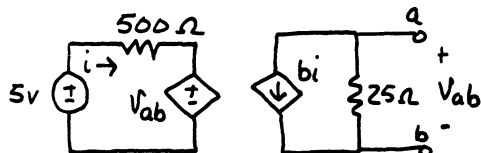

find i_{sc} : $V_{ab} = 0 \therefore i = 5/500 = 10mA$
 $\therefore i_{sc} = -bi = -10^{-2}b$

find V_{oc} : KVL left loop: $-5 + 500i + V_{ab} = 0$ (1)
 also $V_{ab} = -25(bi)$ (2) $\Rightarrow V_{ab} = \frac{5}{(1-20/b)}$

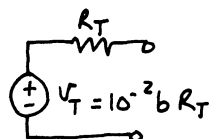
$\therefore R_T = \frac{V_{ab}}{i_{sc}} = \frac{-500}{(b-20)}$




need $60 < R_T < 70 \Omega$

so if $b = 12.5 \Rightarrow \underline{R_T = 66.66 \Omega}$ and $\underline{|V_T| = 8.33V}$

DP 5-8

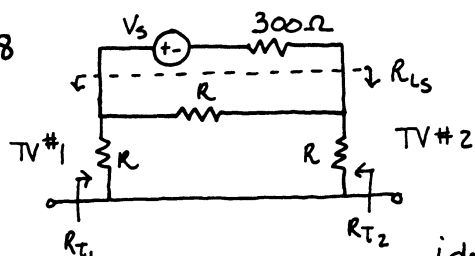

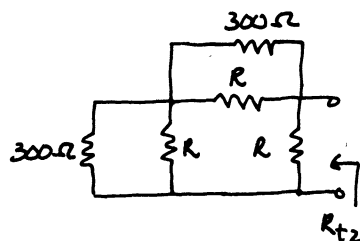
For maximum power to each TV, require $R_{T1} = 300\Omega$, $R_{T2} = 300\Omega$. Furthermore, for the source (antenna) to deliver maximum power, we require R_{Ls} (seen by antenna) $= 300\Omega$. Note that calculation of R_{Ls} , R_{T1} , R_{T2} leads to identical circuits, hence consider R_{T2} (kill V_s)



$R_{T2} = R // [(300 // R) + (300 // R)]$
 $= \frac{2R \left(\frac{R300}{R+300} \right)}{R + R300/R+300} = 300$
 $\Rightarrow \underline{R = 600 \Omega}$

Spice Problems

SP 5-2

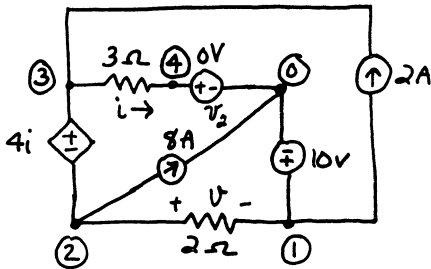

ans. $i = I(V2) = -2.00A$

$V = V(2,1) = -8.00V$


input file

```

V1 1 0 DC 10
V2 4 0
R1 3 4 3
R2 2 1 2
I1 1 3 DC 2
I2 2 0 DC 8
H1 3 2 V2 4
.DC V1 10 10 1
.PRINT DC V(2,1) I(V2)
.END

```

SP 5-5

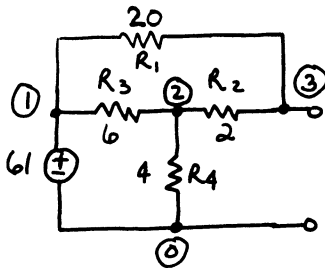

ans. $\frac{V(3)}{V1} = 5.082E-01$

so $V_T = 31V$ $\therefore R_T = \text{output resistance} = \underline{3.62 \Omega}$


input file

```

R2 2 3 2
R4 2 0 4
R3 1 2 6
R1 1 3 20
V1 1 0 DC 6
.TF V(3) V1
.END

```

SP 5-6

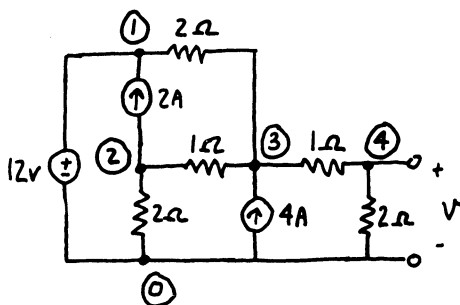

ans. $V(4) = 4.9524$


input file

```

R1 1 3 2
R2 2 0 2
R3 2 3 1
R4 3 4 1
R5 4 0 2
V1 1 0 DC 12
I1 2 1 DC 2
I2 0 3 DC 4
.DC V1 12 12 1
.PRINT DC V(4)
.END

```

SP 5-8

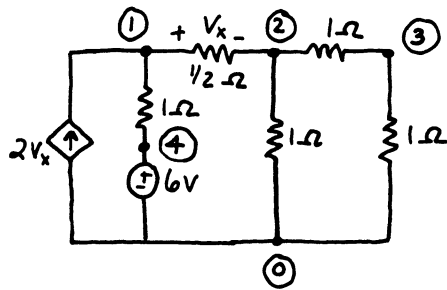


ans. $V(3) = 1.714 \text{ V}$

input file

```
R1 1 4 1
R2 1 2 .5
R3 2 0 1
R4 2 3 1
R5 3 0 1
V1 4 0 DC 6
G1 0 1 1 2 2
.DC V1 6 6 1
.PRINT DC V(3)
.END
```

SP 5-9

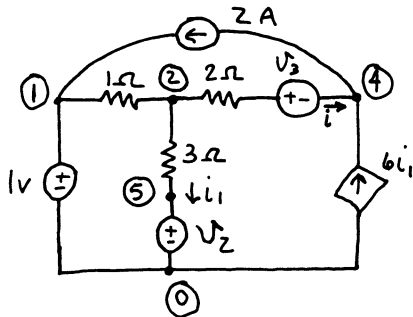


ans. $I(V3) = -1.000 \text{ A} = i$

input file

```
V1 1 0 DC 1
R1 1 2 1
R2 2 5 3
R3 2 3 2
IS 4 1 DC 2
V2 5 0 0
V3 3 4 0
F1 0 4 V2 6
.DC V1 1 1 1
.PRINT DC I(V3)
.END
```

SP 5-10

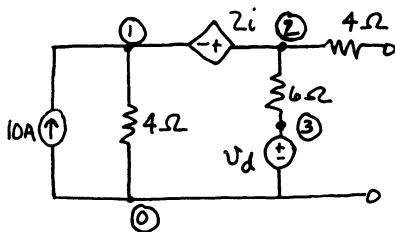


input file

```
I1 0 1 DC 10
R1 1 0 4
H1 2 1 VD 2
R2 2 3 6
VD 3 0 DC 0
.TF V(2) I2
.END
```

SPICE Output : $V(2) = 30.00 \text{ V}$



output resistance = 3.00Ω

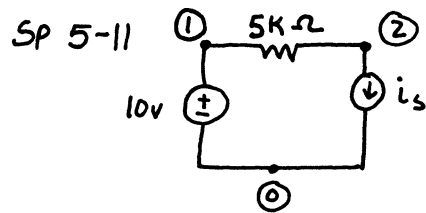$\therefore \underline{V_T = 30 \text{ V}} \quad \& \quad \underline{R_T = 3 + 4 = 7 \Omega}$



input file
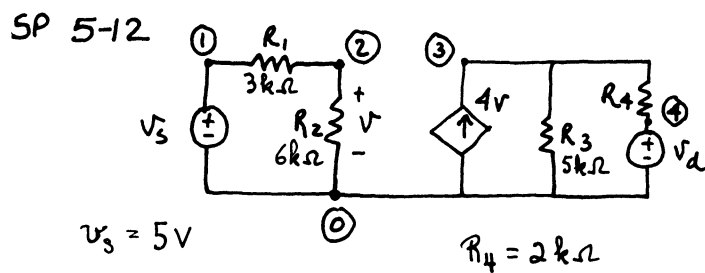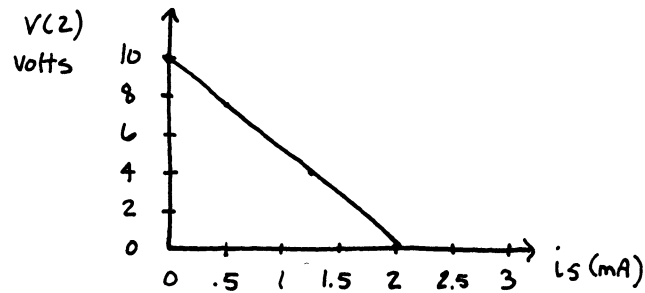
```
vleft 1 0 dc 10v
R1 1 2 5k
iS 2 0 dc 1mA
.dc iS 0 2e-3 0.2e-3
.probe V(2)
.options nopage
.end
```




input file

```
* Amplifier
VS 1 0 DC 5
R1 1 2 3k
R2 2 0 6k
G1 0 3 2 0 4
R3 3 0 5k
R4 3 4 2k
VD 4 0 DC 0
.DC VS 5 5
.PRINT I(VD)
.END
```

Chapter 6

Exercises

Ex 6-1

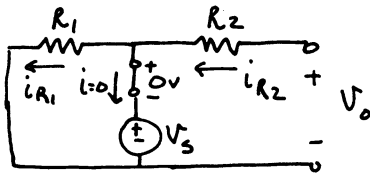

$$V_1 = V_s$$

$$i_{R1} = \frac{V_s}{R_1} \text{ and } i_{R2} = \frac{V_o - V_s}{R_2}$$

$$\text{now } i_{R1} = i_{R2} \therefore \frac{V_s}{R_1} = \frac{V_o - V_s}{R_2}$$

$$\text{or } \frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}$$

Ex. 6-2 referring to figure 12-10(b)

$$\text{from voltage divider : } V_1 = \frac{R_1}{R_1 + R_2} V_o \Rightarrow \frac{V_o}{V_1} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o}{V_1} = 1 + \frac{40}{10} = 5$$


$$\text{from KVL : } V_s + V_i = V_1, \quad V_i = -\frac{V_o}{A}$$

$$\Rightarrow V_s = V_1 + \frac{V_o}{A}$$

$$\frac{V_s}{V_o} = \frac{V_1}{V_o} + \frac{1}{A} = \frac{1}{5} + \frac{1}{10^6} \approx 1/5$$

$$\therefore \frac{V_o}{V_s} = 5$$

Ex 6-3 use op amp model

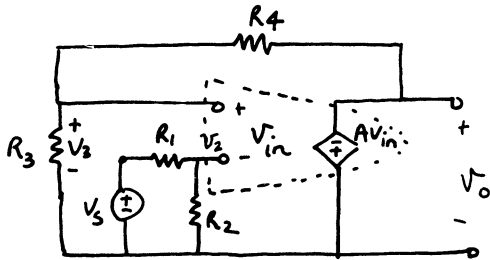

$$V_3 = \frac{R_3}{R_3 + R_4} V_o$$

$$V_2 = \frac{R_2}{R_2 + R_1} V_s$$

$$V_{in} = V_3 - V_2 = \frac{R_3}{R_3 + R_4} V_o - \frac{R_2}{R_2 + R_1} V_s \quad (1)$$


$$\text{now } V_o = -A V_{in} \text{ or } V_{in} = -\frac{V_o}{A} \quad (2)$$

equating (1) & (2) and solving for V_o/V_s yields

$$\frac{V_o}{V_s} = \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3} \right)$$

$$\text{if } R_2 \gg R_1 \Rightarrow \frac{V_o}{V_s} = 1 + \frac{R_4}{R_3}$$

Ex. 6-4

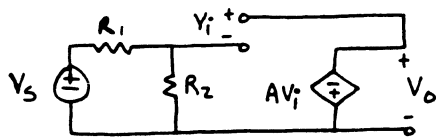

from voltage divider

$$V_i = V_s \left(\frac{R_2}{R_1 + R_2} \right) = V_o - V_i$$

$$\Rightarrow V_i = V_o - V_s \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\text{also } V_o = -A V_i$$

$$= -A \left(V_o - V_s \left(\frac{R_2}{R_1 + R_2} \right) \right)$$

$$\Rightarrow \frac{V_o}{V_s} = \left(\frac{R_2}{R_1 + R_2} \right) \frac{A}{1 + A} = \frac{k A}{1 + A}$$

Ex 6-5 from example 6-2

$$k = \frac{R_1}{R_1 + R_2} = \frac{50}{50 + 100} = \frac{1}{3}$$

$$\frac{V_o}{V_s} = \frac{-A(1-k)}{1 + A k} = \frac{-10^4(1-1/3)}{1 + 10^4(1/3)} = \underline{-1.9994}$$

compared to approximation when $A \gg 1$

$$\text{then } \frac{V_o}{V_s} = -2.0$$

Ex. 6-6 Assume $i_1 \ll i_{i_L} \Rightarrow i = i_L \therefore V_o = V_s + V_i$

$$\text{KVL (rt. mesh): } V_o = -A V_i - R_o i$$

$$= -A V_i - R_o (V_o / R_L)$$

$$V_o = -A(V_o - V_s) - R_o (V_o / R_L)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 + \frac{R_o}{R_L} + A} = \frac{10^4}{1 + .1 + 10^4} = \underline{0.99989}$$

$$\text{now } R_{in} = \frac{V_s}{i_1} = -\frac{V_s}{V_i / R_i} = -\frac{V_s R_i}{V_i} = -\frac{V_s R_i}{-\frac{V_o}{A} \left(1 + \frac{R_o}{R_L} \right)}$$

$$\Rightarrow R_{in} = \left(\frac{V_s}{V_o} \right) \frac{R_i A}{1 + R_o / R_L} = (0.99989)^{-1} \frac{(10^5)(10^4)}{1 + .1} = \underline{909 \text{ M}\Omega}$$

Ex. 6-7 w/o the buffer

$$V_o = \frac{R_L}{R_1 + R_L} V_s = \frac{500}{1500} V_s = \frac{1}{3} V_s$$

$$\Rightarrow P_1 = \frac{V_o^2}{R_L} = \frac{1}{9} \frac{V_s^2}{R_L}$$


with the buffer

$$V_o = \frac{R_L}{R_o + R_L} V_s \quad \Rightarrow \text{with gain} = 1.0 \text{ of buffer}$$

$$\begin{aligned} \Rightarrow P_2 &= \frac{V_o^2}{R_L} = \frac{V_s^2}{R_L} \frac{R_L^2}{(R_o + R_L)^2} \\ &= \frac{V_s^2}{R_L} \frac{(500)^2}{(510)^2} = .961 \frac{V_s^2}{R_L} \end{aligned}$$

$$\therefore \frac{P_2}{P_1} = \frac{.961}{1/9} = 8.65$$

Ex 6-8

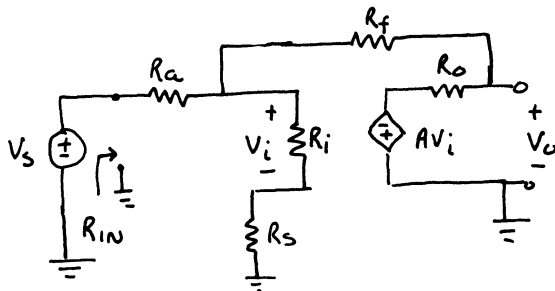

$$\text{Answers : } A_v = \frac{V_o}{V_s} = \frac{R_o(R_i + R_s) + A R_i R_f}{(R_f + R_o)(R_i + R_s) + R_a(R_f + R_o + R_i + R_s) - A R_i R_a}$$

$$R_{in} = R_a + \frac{(R_f + R_o)(R_i + R_s)}{(R_f + R_o + R_i + R_s) - A R_i}$$

$$R_{out} = \frac{R_o[R_a(R_f + R_i + R_s) + R_f(R_i + R_s)]}{-A R_i R_a}$$

if the op amp is ideal (A very large, R_i large, R_o small)


$$A_v = \frac{V_o}{V_s} \approx \frac{A R_i R_f}{(1-A) R_i R_a} \approx -\frac{R_f}{R_a}$$

$$R_{in} \approx R_a \quad \text{and} \quad R_{out} \approx \frac{R_o(R_a R_i + R_f R_i)}{-A R_i R_a} = -\frac{R_o(R_a + R_f)}{A R_a}$$

$$\text{if } R_f = 10 R_a \text{ then } \Rightarrow R_{out} = -\frac{11 R_o}{A} \rightarrow 0$$

Problems

P. 6-1

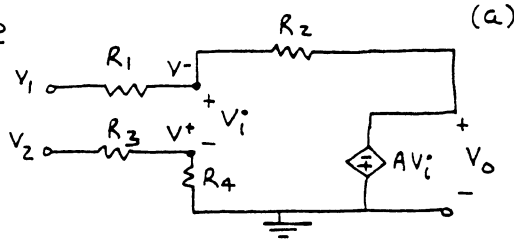

(a) Voltage divider yields

$$V^+ = \frac{R_4}{R_3 + R_4} V_2 \quad (1)$$

KCL at V^- yields

$$\frac{V^- - V_1}{R_1} = \frac{V_0 - V^-}{R_2}$$

$$\Rightarrow V^- = \frac{R_1}{R_1 + R_2} V_0 + \frac{R_2}{R_1 + R_2} V_1 \quad (2)$$

now $V_0 = -A V_i$

$$V_0 = -A(V^- - V^+) = -A \left[\frac{R_1}{R_1 + R_2} V_0 + \frac{R_2}{R_1 + R_2} V_1 - \frac{R_4}{R_3 + R_4} V_2 \right]$$

$$\Rightarrow V_0 \left[-\frac{1}{A} - \frac{R_1}{R_1 + R_2} \right] = \frac{R_2}{R_1 + R_2} V_1 - \frac{R_4}{R_3 + R_4} V_2$$

let $A \rightarrow \infty$ and solve for V_0

$$\therefore V_0 = -\frac{R_2}{R_1} V_1 + \frac{1 + R_2/R_1}{1 + R_3/R_4} V_2$$

(b) want $V_0 = 4V_2 - 11V_1$


$$\therefore \frac{R_2}{R_1} = 11 \quad \text{and} \quad \frac{1 + R_2/R_1}{1 + R_3/R_4} = 4$$

$$1 + 11 = 4(1 + R_3/R_4)$$


$$\Rightarrow \frac{R_3}{R_4} = 2$$

$$\text{let } R_1 = 10k\Omega \Rightarrow R_2 = 11R_1 = 110k\Omega$$
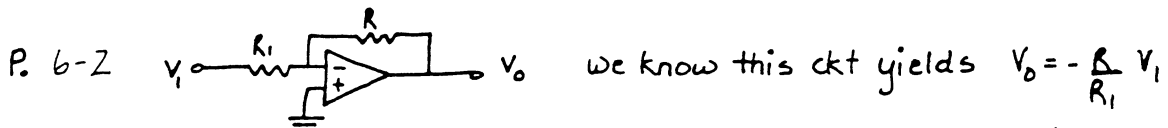
$$\text{let } R_3 = 20k\Omega \Rightarrow R_4 = \frac{1}{2} R_3 = 10k\Omega$$



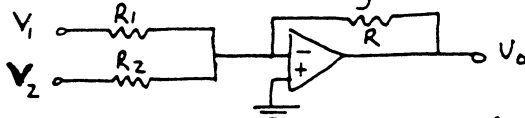
so consider adding another input lead into the neg. terminal



with $V_i = 0$, KCL at neg. input yields

$$-V_1/R_1 - V_2/R_2 = V_0/R \Rightarrow V_0 = -\frac{R}{R_1} V_1 - \frac{R}{R_2} V_2$$

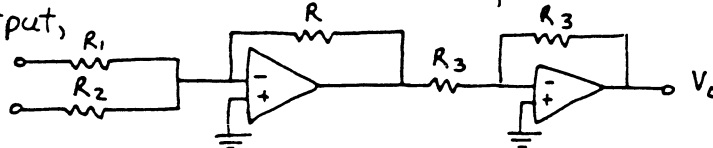See that need to invert answer, so add an inverter to the output,




$$\text{let } R_3 = 10k\Omega$$

$$\text{now } \frac{R}{R_1} = 6 \quad \text{and} \quad \frac{R}{R_2} = 2 \quad \therefore \text{let } R = 60k\Omega$$

$$R_1 = 10k\Omega$$

$$R_2 = 30k\Omega$$

P. 6-3

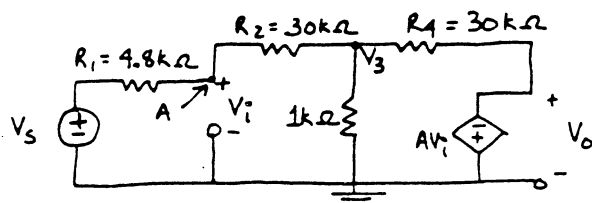

$$\text{KCL at A: } (V_i - V_s)/4.8 = (V_3 - V_i)/30 \Rightarrow V_3 = 7.25V_i - 6.25V_s$$

$$\text{KCL at } V_3: (V_3 - V_i)/30 + V_3 + (V_3 - V_o)/30 = 0$$

$$\Rightarrow 32V_3 = V_i + V_o$$


$$32(7.25V_i - 6.25V_s) = V_i + V_o$$

$$\text{using } V_i = -\frac{V_o}{A}$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{200}{1 + \frac{232}{A}}$$

$$\text{for } A \rightarrow \infty \quad \frac{V_o}{V_s} = -200$$

P. 6-4

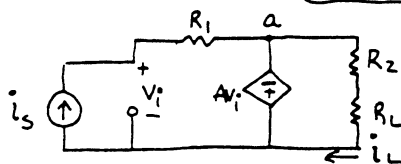


$$\text{if } A \gg 1 \text{ and } V_i \approx 0 \Rightarrow V_a = -i_s R_1$$

$$\text{then } i_L = \frac{V_a}{R_2 + R_L} = -\frac{R_1 i_s}{R_2 + R_L}$$

$$\approx -\frac{R_1 i_s}{R_2} \quad \text{if } R_2 \gg R_L$$

$$\text{so } \frac{i_L}{i_s} = -\frac{R_1}{R_2} = -100$$

P. 6-5

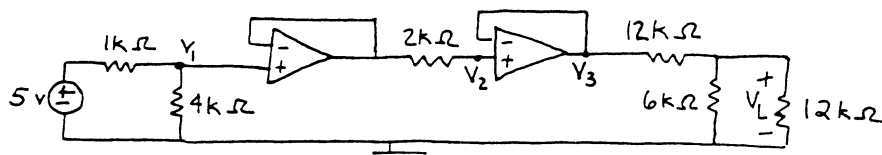

no current into the buffers


$$\therefore V_1 = 5 \left[\frac{4}{1+4} \right] = 4 \text{ V}$$

$$V_2 = V_1 \quad (\text{since buffer has gain} = 1)$$

$$V_2 = V_3$$

$$\Rightarrow V_L = V_3 \left[\frac{12/6}{12/6 + 12} \right] = \frac{1}{4} V_3 = \frac{1}{4} V_1 = 1 \text{ V}$$

P 6-6

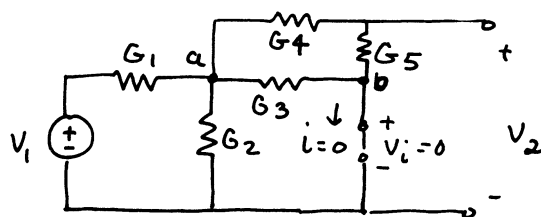


$$V_b \rightarrow 0$$

$$\text{KCL node a: } (G_1 + G_2 + G_3 + G_4)V_a - G_1 V_1 - G_4 V_2 = 0 \quad (1)$$

$$\text{KCL node b: } G_3 V_a + G_5 V_2 = 0 \quad (2)$$

$$\text{from (1) \& (2) } \Rightarrow \frac{V_2}{V_1} = \frac{-G_1 G_3}{G_5 (G_1 + G_2 + G_3 + G_4) + G_3 G_4}$$

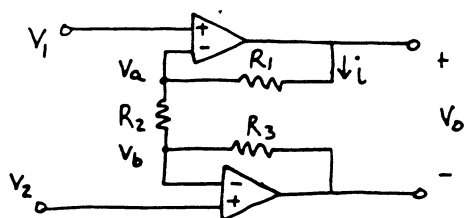P. 6-7 Assume $A = \infty$ (no current into the operational amps.)




with the voltage across the input to the op amps $= 0$, then have $V_a = V_1$ and $V_b = V_2$

$$\therefore \text{from KVL: } V_o - iR_3 - iR_2 - iR_1 = 0$$

$$\Rightarrow V_o = i(R_1 + R_2 + R_3)$$

$$\text{also: } i = \frac{V_a - V_b}{R_2} = \frac{V_1 - V_2}{R_2} \Rightarrow V_o = \frac{(R_1 + R_2 + R_3)(V_1 - V_2)}{R_2}$$

P. 6-9

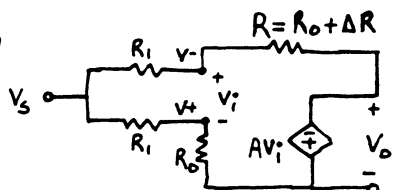

$$\text{from voltage divider: } V^+ = \frac{R_0}{(R_0 + R_1)} V_s \quad (1)$$

$$\text{KCL at } V^-: (V - V_s)/R_1 = (V_o - V^-)/R \Rightarrow V^- = \frac{R}{R_1 + R} V_s + \frac{R_1}{R_1 + R} V_o \quad (2)$$

$$\text{now } V_o = -AV_i = -A(V - V^+) \quad (3) \Rightarrow \text{plugging (1) \& (2) into (3) yields}$$

$$V_o \left(-\frac{1}{A} - \frac{R}{R_1 + R} \right) = \left(\frac{R}{R_1 + R} - \frac{R_0}{R_0 + R_1} \right) V_s$$

$$\text{assuming } \frac{R_1}{R_1 + R} \gg \frac{1}{A} \Rightarrow -V_o \left(\frac{R_1}{R_1 + R} \right) = \left(\frac{R}{R_1 + R} - \frac{R_0}{R_0 + R_1} \right) V_s$$


$$\Rightarrow V_o = -\frac{V_s}{R_1} \left[R - \frac{R_0(R_1 + R)}{R_0 + R_1} \right]$$

$$= -\frac{V_s}{R_1} \left[\frac{(R_0 + \Delta R)(R_0 + R_1) - R_0(R_1 + R_0 + \Delta R)}{R_0 + R_1} \right]$$

$$= -\frac{V_s}{R_1} \frac{R_1 \Delta R}{(R_0 + R_1)}$$

$$V_o = -V_s \frac{R_0}{R_0 + R_1} \frac{\Delta R}{R_0}$$

P. 6-11

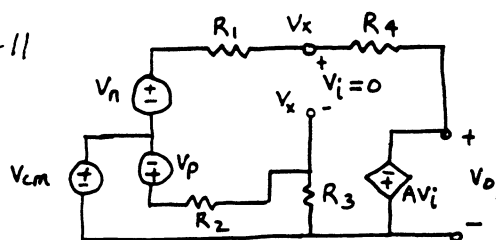

with $V_i = 0$, from voltage divider

$$V_x = (V_{cm} + V_p) \left(\frac{R_3}{R_2 + R_3} \right) \quad (1)$$

KCL at V_x (+ terminal)

$$\frac{(V_{cm} + V_p - V_x)}{R_1} = \frac{(V_x - V_o)}{R_4}$$

$$\Rightarrow V_o = V_x \left(1 + \frac{R_4}{R_1} \right) - \frac{R_4}{R_1} (V_{cm} + V_p) \quad (2)$$

when $R_3/R_2 = R_4/R_1$ eqn. (1) becomes : $V_x = (V_{cm} + V_p) \left(\frac{R_4/R_1}{1 + R_4/R_1} \right) \quad (3)$

plugging (3) into (2) yields

$$V_o = -R_4/R_1 (V_n - V_p)$$

P. 6-12 Select an inverting amplifier in which the gain is

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1} \quad (\text{see figure 12-12})$$

then $R_2 = 10R_1$


since the maximum current is 10mA through R_1

$$R_1 \geq \frac{1V}{10mA} = 0.1 k\Omega$$

$\therefore$ if $R_1 = 0.1 k\Omega$, then

$$R_2 = 10R_1 = 1 k\Omega$$


P. 6-13

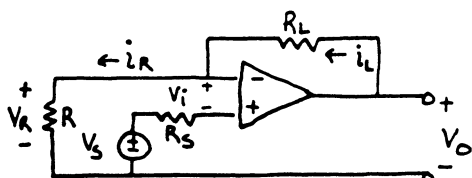

Assume that $V_i = 0$ and that the current entering the op amp is negligible.

$$\therefore V_R = V_s = i_L R \Rightarrow \frac{i_L}{V_s} = \frac{1}{R}$$

P. 6-14

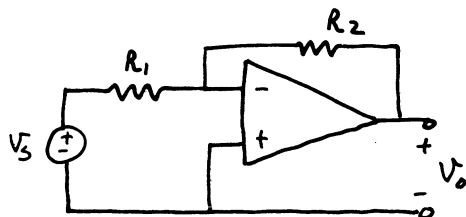


See table 6-3

for 741 : $A = 2 \times 10^5$ $R_i = 2 M\Omega$
 $R_o = 75 \Omega$

using ideal case $\frac{V_o}{V_s} = -\frac{R_2}{R_1}$

use $R_1 = 1000 \Omega = 1 k\Omega$ then $R_2 = 100 k\Omega$

P. 6-15

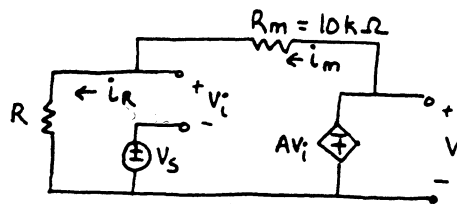

assume the op-amp draws no current $\Rightarrow i_R = i_m$

from KVL: $V_o = (R_m + R)i_R$ (1)

$V_i = i_R R - V_s$ (2)

also $V_o = -A V_i$ (3)

(2) into (3) $\Rightarrow V_o = A(V_s - i_R R)$ (4)


Solving for i_R in (1) and plugging into (4) yields

$$\frac{V_o}{V_s} = \frac{A}{1 + kA} \quad \text{where } k = \frac{R}{R + R_m}$$


for $A \gg 1 \Rightarrow \frac{V_o}{V_s} = \frac{1}{k} = \frac{R_m + R}{R}$

so $i_R = i_m = \frac{V_o}{R + R_m} = \frac{(R_m + R)V_s}{R(R + R_m)} = \frac{V_s}{R} \Rightarrow R = \frac{V_s}{i_R} = \frac{1V}{10^{-4}A} = 10k\Omega$

P. 6-16

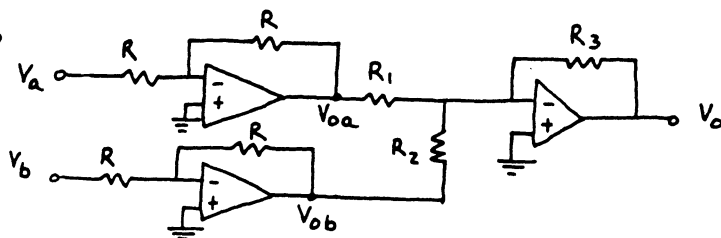

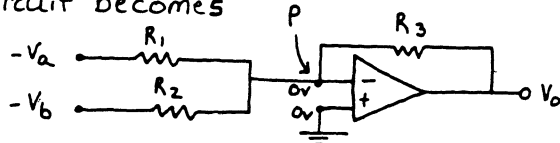
(a) assume ideal op-amps $\Rightarrow V_{oa} = -V_a$ and $V_{ob} = -V_b$
 $\therefore$ the circuit becomes




KCL at P: $V_a/R_1 + V_b/R_2 = V_o/R_3 \Rightarrow V_o = \frac{R_3}{R_1} V_a + \frac{R_3}{R_2} V_b$

(b) the circuit functions as a weighted adder

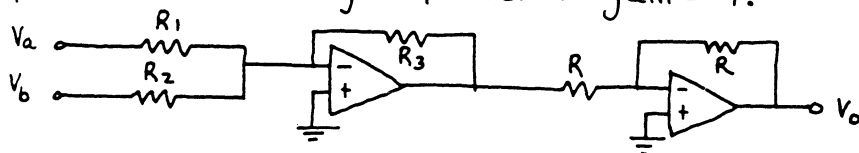(c) use above ckt. with input of $+V_a$ and $+V_b$ and then invert the output with an inverting amplifier of gain = -1.



P. 6-17

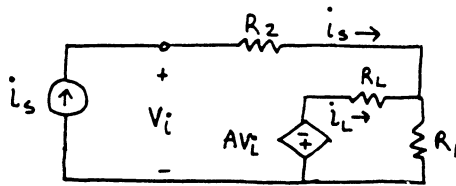


with $V_i = 0$, R_1 & R_2 are in parallel

$\therefore$ from current divider

$$i_s = -\frac{R_1}{R_1 + R_2} i_L$$

$$\Rightarrow \frac{i_L}{i_s} = -\frac{(R_1 + R_2)}{R_1}$$

P. 6-18

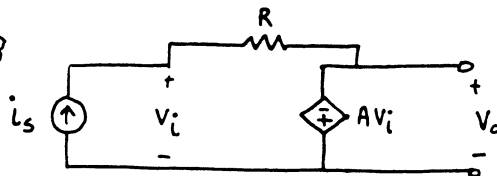


assume $V_i = 0$

$\therefore i_s$ flows through R

$$\text{from KVL: } -V_o - i_s R = 0 \Rightarrow \frac{V_o}{i_s} = -R$$

P. 6-19 (a)

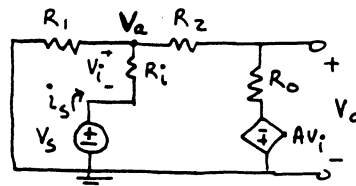

$$\text{KCL at } V_o: i_s + \frac{(-A V_i - V_o)}{R_2 + R_o} - \frac{V_o}{R_i} = 0 \quad (1)$$

$$\text{also: } V_o = V_s - i_s R_i \quad (2)$$

$$V_i = -i_s R_i \quad (3)$$


(3) and (2) into (1) yields

$$V_s \left[\frac{1}{R_i} + \frac{1}{R_2 + R_o} \right] = i_s \left[1 + \frac{A R_i}{R_2 + R_o} + \frac{R_i}{R_2 + R_o} + \frac{R_i}{R_i} \right]$$

$$\text{assuming } A \gg 1 \Rightarrow \frac{A}{R_2 + R_o} \gg \frac{1}{R_i}$$

$$\Rightarrow R_{in} = \frac{V_s}{i_s} = \left[\frac{A R_i}{R_1 + R_2 + R_o} \right] R_i$$

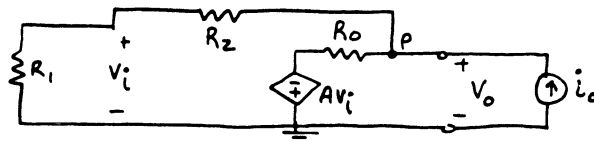(b) assume $R_i \gg R_2$ and set $V_s = 0$



$$\text{KCL at P: } i_o - V_o / (R_1 + R_2) - (V_o + A V_i) / R_o = 0 \quad (1)$$


$$\text{also: } V_i = V_o \left(\frac{R_1}{R_1 + R_2} \right) \quad (2)$$

$$(2) \text{ into } (1) \text{ yields } i_o = \frac{V_o}{R_1 + R_2} + \frac{V_o}{R_o} - \frac{V_o A R_1}{(R_1 + R_2) R_o}$$

$$\text{for } A \gg 1: i_o \approx \frac{V_o A R_1}{(R_1 + R_2) R_o}$$

$$\Rightarrow R_{out} = \frac{V_o}{i_o} = \frac{(R_1 + R_2) R_o}{A R_1}$$


P. 6-20

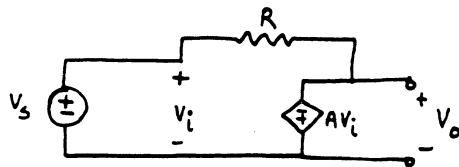

$$V_s = V_i$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{V_o}{V_i} = -\frac{AV_i}{V_i} = -A$$

P. 6-21

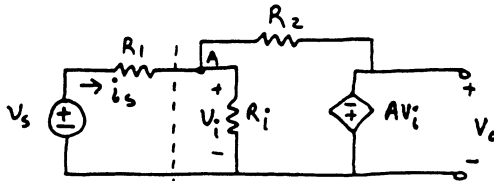

← find the T&E equiv. to right of dotted line and add R_T to R_1 to get total $R_{in} = V_s/i_s$


$$\text{KCL at A: } i_s = V_i/R_i + (V_i + AV_i)/R_2$$

$$\Rightarrow \frac{i_s}{V_i} = \frac{1}{R_i} + \frac{1}{R_2} + \frac{A}{R_2} \approx \frac{A}{R_2} \quad \text{for } A \gg 1$$

$$\therefore R_T = \frac{R_2}{A}$$

$$\text{Thus, the total input impedance} \Rightarrow R_{in} = R_1 + R_2/A \approx R_1$$

P. 6-22

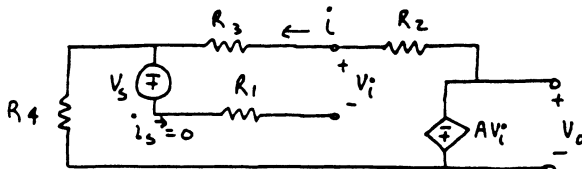

Since $i_s = 0$, from KVL

$$-V_s - V_i + R_3 i = 0$$

$$\Rightarrow i = (V_s + V_i)/R_3 \quad (1)$$

$$\text{also: } i = V_o/(R_4 + R_3 + R_2) \quad (2)$$


equating (1) and (2) and using $V_i = -V_o/A$ yields

$$V_o \left[\frac{1}{AR_3} + \frac{1}{R_2 + R_3 + R_4} \right] = \frac{V_s}{R_3}$$

assume $AR_3 \gg R_2 + R_3 + R_4$

$$\Rightarrow V_o = \frac{(R_3 + R_2 + R_4)}{R_3} V_s$$

Note: V_o is indep. of R_1

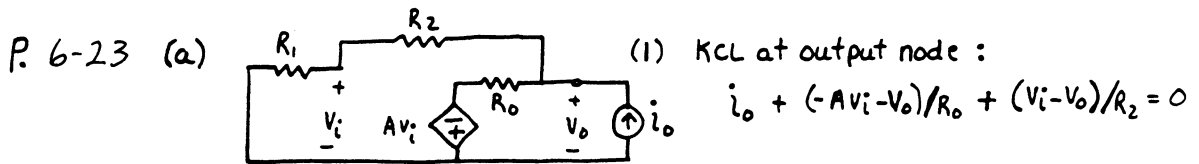

(2) also : $V_i = \frac{R_1 V_o}{R_1 + R_2} = k V_o$

(2) into (1) yields $i_o + (-A k V_o - V_o)/R_o + (k V_o - V_o)/R_2 = 0$

assume $A k \gg 1$


$$\Rightarrow i_o - \frac{A k V_o}{R_o} + \frac{(k-1)}{R_2} V_o = 0$$

assume $\frac{A k}{R_o} \gg \frac{(k-1)}{R_2} \Rightarrow R_{out} = \frac{V_o}{i_o} = \frac{R_o}{A k}$

(b) for $A = 10^5$, $k = 0.1$, $R_o = 1 \text{ k}\Omega$

$$\Rightarrow R_{out} = 0.1 \Omega$$

P. 6-24

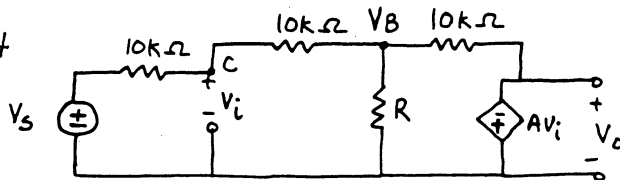

KCL at C : $(V_i - V_s)/10 + (V_i - V_B)/10 = 0 \Rightarrow V_B = 2 V_i - V_s$ (1)

KCL at V_B : $(V_B - V_i)/10 + V_B/R + (V_B - V_o)/10 = 0$ (2)

also : $V_i = -V_o/A$ (3)


plugging (3) and (1) into (2) yields

$$\Rightarrow -2(2 + 10/R)V_s = [1 + (3 + 20/R)/A] V_o$$

assume $(3 + 20/R)/A \ll 1$

$$\Rightarrow R = 10/(-V_o/V_s - 2) = 10/(100 - 2) = .02 \text{ k}\Omega = 102 \Omega$$

P. 6-25 (a)

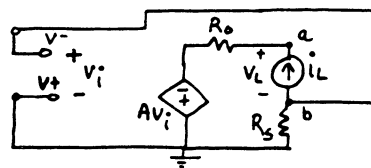

replace R_L with current source i_L and find $R = V_L/i_L$

set $V_s = 0$

now $V^+ = 0$ and $V_i = V^- - V^+ = -i_L R_s$

from KVL : $-V_L + i_L R_o - A V_i - V_i = 0$

$$\Rightarrow V_L = i_L R_o - (1+A)(-i_L R_s) = i_L [R_o + (1+A)R_s]$$

$$\therefore R_{out} = \frac{V_L}{i_L} = R_o + (1+A)R_s \approx A R_s \quad \text{for } A \gg 1$$

(b) $R_{out} = A R_s + R_o$

$$= (10^5)(10^4) + 10^3$$

$$R_{out} \approx 10^9 \Omega$$

P. 6-26 (a) without amplifier : $V_o/V_s = \frac{R_L}{R_s + R_L} = \frac{1}{2}$

with amplifier : $\frac{V_o}{V_s} = 1$ since $R_{in} \gg 500\Omega$
and $R_L \gg R_o$

(b) $P_a = V_o^2/R_L = V_s^2/R_L$

direct : $P_d = V_o^2/R_L = \frac{1}{4} V_s^2/R_L$

$\therefore$ power gain = $\frac{P_a}{P_d} = 4$

(c) desire $P_a/P_d = 16 = \frac{V_s^2/R_L}{\left(\frac{R_L}{R_s + R_L}\right)^2 V_s^2}$

$\therefore \frac{R_L}{R_s + R_L} = 1/\sqrt{16}$, with $R_s = 500\Omega \Rightarrow R_L = 167\Omega$

P. 6-27 assume ideal amps

KCL at V_s :


$V_s/10 + (V_s - V_1)/100 = 0$

$\Rightarrow V_1 = 11V_s$ (1)

also : $V_o = V_1 - V_2 = 2V_1$ (2)

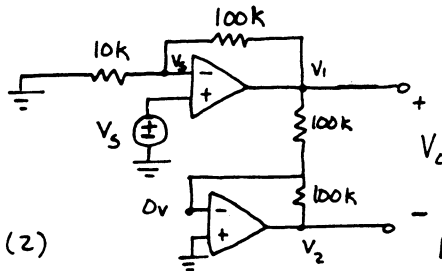(1) into (2) yields

$V_o = 22V_s \Rightarrow \underline{V_o/V_s = 22}$



by inspection
 $V_2 = -V_1$


P 6-28

see Exer 6-3

$$V_o = \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3}\right) V_1 - \frac{R_4}{R_3} V_2$$


$$= \frac{1}{3} (1 + 4) 6 - \left(\frac{20}{5}\right) 3$$

$$= 10 - 12 = -2V$$

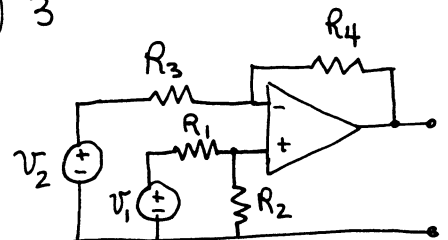

P 6-29 a) ideal $V_o = -\frac{10k\Omega}{1k\Omega} (1V) = \underline{-10V}$

b) non-ideal

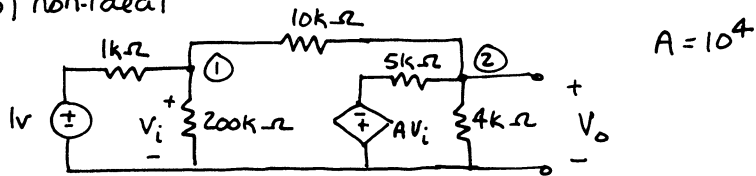


$$\text{KCL node 1: } \frac{V_i - 1}{1} + \frac{V_i}{200} + \frac{V_i - V_o}{10} = 0 \quad (1)$$

$$\text{node 2: } \frac{V_o - V_i}{10} + \frac{V_o + AV_i}{5} + \frac{V_o}{4} = 0 \quad (2)$$

from (1) and (2) get $\underline{V_o = -9.97V}$

P 6-30

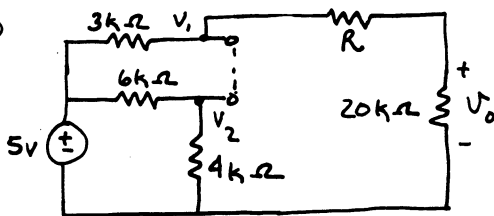


$$V_2 = \frac{4}{4+6} V_s \quad \text{and} \quad V_1 = V_2 \\ = 2V$$

$$\text{KCL at } V_1: \frac{5-2}{3k\Omega} + \frac{V_o-2}{R} = 0 \Rightarrow R = 2 - V_o \quad (R \text{ in } k\Omega)$$

at neg. value of $V_o = -14V$ get $R = 2 - (-14) = 16k\Omega$

so saturates at $\underline{R \geq 16k\Omega}$

P 6-31

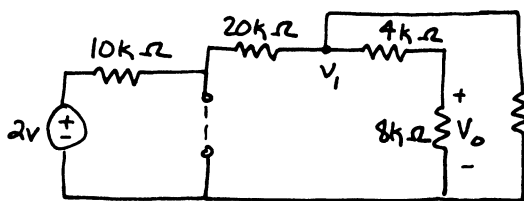

KCL into '-' terminal:


$$\frac{2}{10} + \frac{V_1}{20} = 0 \Rightarrow V_1 = -4V$$

$$\text{KCL node } V_1: \frac{V_1}{20} + \frac{V_1}{5} + \frac{V_1 - V_0}{4} = 0$$

$$\Rightarrow V_0 = -8V$$

$$\therefore I_0 = \frac{V_0}{8k\Omega} + \frac{V_0 - V_1}{4} = \underline{-2mA}$$

P 6-32

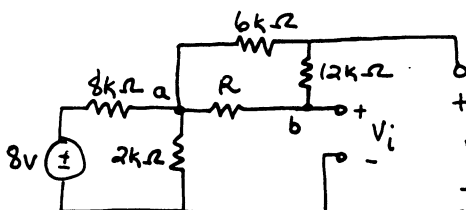

KCL node a:

$$\frac{V_a - 8}{8} + \frac{V_a - V_0}{6} + \frac{V_a}{2} + \frac{V_a - V_i}{R} = 0 \quad (1)$$

$$\text{KCL node b: } \frac{V_i - V_a}{R} + \frac{V_i - V_0}{12} = 0 \quad (2)$$

now let $V_i = 0$ and multiply (1) by 24 & (2) by -12

$$3(V_a - 8) + 4(V_a - V_0) + 12V_a + \frac{24V_a}{R} = 0 \quad (3)$$


$$\frac{12V_a}{R} + V_0 = 0 \quad (4)$$

$$\text{solving for } V_a \Rightarrow V_a = \frac{24}{\left[19 + \frac{24 + 48}{R}\right]}$$

$$\text{want } V_0 = -1.95V \text{ or } V_a = \frac{1.95R}{12}$$

$$\text{thus } \frac{1.95R}{12} = \frac{24}{\left[19 + \frac{72}{R}\right]} \Rightarrow \underline{R = 4k\Omega}$$

P 6-33

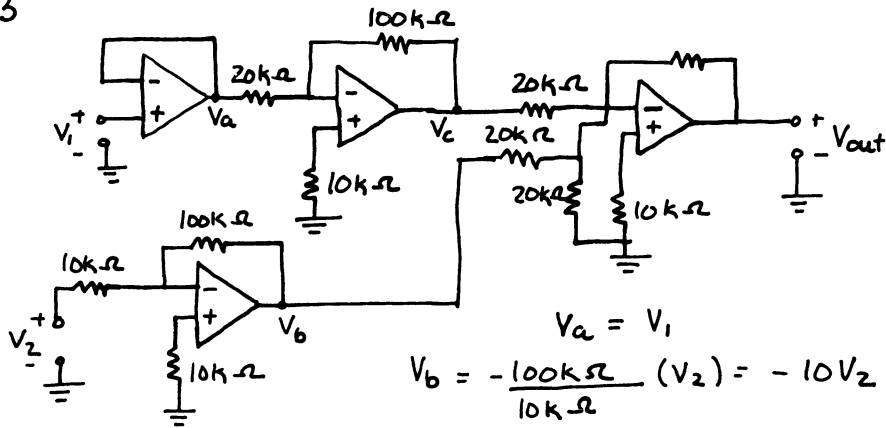


$$V_a = V_1$$

$$V_b = -\frac{100k\Omega}{10k\Omega} (V_2) = -10V_2$$

$$V_c = -\frac{100k\Omega}{20k\Omega} (V_a) = -5V_a = -5V_1$$

$$V_{out} = -80k\Omega \left(\frac{V_c}{20k\Omega} + \frac{V_b}{20k\Omega} \right) = -4V_c - 4V_b = \underline{20V_1 + 40V_2}$$

P 6-34

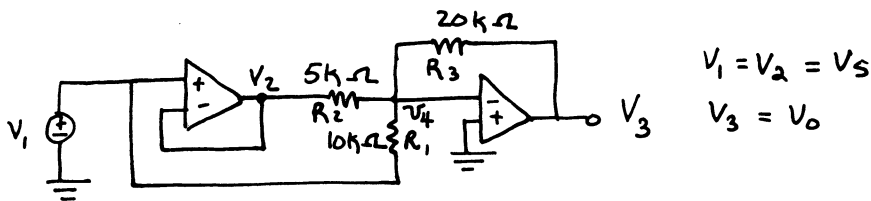

$$V_1 = V_2 = V_s$$


$$V_3 = V_o$$

$V_4 \rightarrow 0$
virtual ground

$$V_o = 20 \left(\frac{V_s}{10} + \frac{V_s}{5} \right) = 2V_s + 4V_s = \underline{6V_s}$$

since KCL at V_4 is $\frac{V_o}{20} = \frac{V_s}{10} + \frac{V_s}{5}$

P 6-35

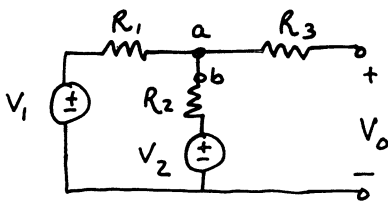


$$V_b = V_2 \text{ since no current}$$

$$V_a = V_b \text{ due to short so } V_a = V_b = V_2$$

$$\text{KCL: } \frac{V_1 - V_a}{R_1} + \frac{(V_o - V_a)}{R_3} = 0 \quad \text{so } \frac{V_1 - V_2}{R_1} + \frac{V_o - V_2}{R_3} = 0$$

$$\Rightarrow V_o = \left(1 + \frac{R_3}{R_1} \right) V_2 - \frac{R_3}{R_1} V_1$$

P 6-36

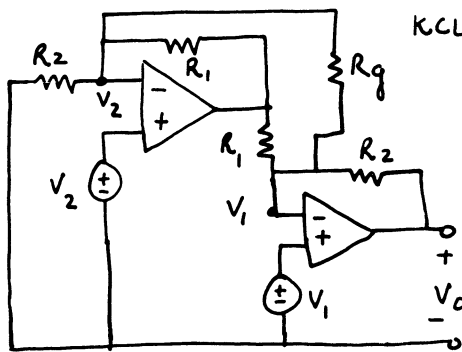

$$\text{KCL } V_1 : \frac{V_1 - V_0}{R_2} + \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_2}{R_g} = 0 \quad (1)$$

$$V_2 : \frac{V_2 - V_0}{R_1} + \frac{V_2 - V_1}{R_g} + \frac{V_2}{R_2} = 0 \quad (2)$$


solving (1), (2) for V_0 :

$$V_0 = \left(1 + \frac{R_2}{R_1} + \frac{2R_2}{R_g}\right)(V_1 - V_2)$$

let $R_g = 200 \text{ k}\Omega$, $R_2 = 50 \text{ k}\Omega$ then have $10 = \left(1 + \frac{50}{R_1} + \frac{100}{200}\right)$

so need $R_1 = 5.88 \text{ k}\Omega$

P 6-37

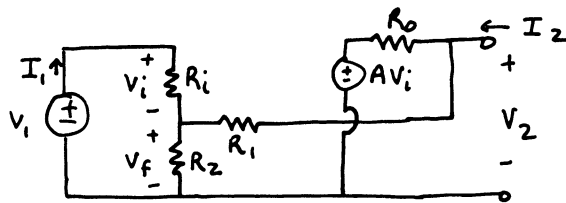

$$a) V_i = V_1 - V_f$$

$$V_2 = AV_i - A \left[\frac{R_2 R_i}{R_2 + R_i} \frac{V_2}{R_1 + \frac{R_2 R_i}{R_2 + R_i}} \right]$$

let $\beta \equiv R'_2 / (R'_2 + R_1)$ with $R'_2 = R_2 // R_i$

$$V_2 = AV_i - A\beta V_2 \quad \therefore \frac{V_2}{V_i} = \frac{A}{(1 + A\beta)}$$


Feedback eqn: $\frac{V_2}{V_i} = \frac{A}{1 + A\beta}$ $\left. \begin{array}{l} V_i = V_1 + V_f \\ I_1 = V_i / R_i \end{array} \right\} \begin{array}{l} V_i = V_2 / A \\ V_f = \beta V_2 \end{array}$

$$\therefore \frac{V_1}{I_1} = \frac{V_2 \left[\frac{1}{A} + \beta \right]}{V_2 / AR_i} = (1 + A\beta) R_i \quad \text{so } R_{in} = (1 + A\beta) R_i$$

b) $R'_2 = 10 // 100 = 9.09 \text{ k}\Omega \Rightarrow \beta = \frac{9.09}{9.09 + 10} = .476$

so $\frac{V_2}{V_1} = \frac{10^4}{1 + 10^4(.476)} = \underline{2.10}$; $R_{in} = [1 + 10^4(.476)] 100 = \underline{476 \text{ M}\Omega}$

P 6-39

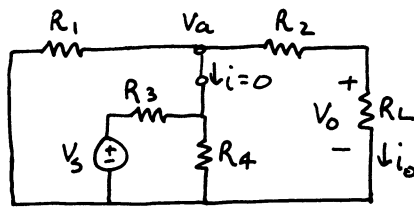

$$V_1 = \frac{R_4}{R_3 + R_4} V_s = a V_s, \quad V_a = V_1 = a V_s$$

$$i = -\frac{V_a}{R_1}, \quad i_o = \frac{V_a - V_o}{R_2}$$

$$\therefore -\frac{V_a}{R_1} = \frac{V_a - V_o}{R_2} \quad \text{or} \quad -\frac{a V_s}{R_1} = \frac{a V_s}{R_2} - \frac{V_o}{R_2}$$

$$\text{so } V_o = a \left(1 + \frac{R_2}{R_1}\right) V_s = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) V_s = \left(\frac{20}{30}\right) \left(1 + \frac{98}{7}\right) (1) = 1.0 \text{ V}$$

$$\text{so } i_o = \frac{V_o}{R_L} = \frac{1.0 \text{ V}}{2 \text{ k}\Omega} = 0.5 \text{ mA}$$

Advanced Problems

AP 6-1 1st op amp has -3V input and is inverting amplifier


$$V_{o1} = -\left(\frac{6}{2}\right)(-3) = 9 \text{ V}$$

Second op amp equiv. ckt:


KCL node a:

$$\frac{9-2}{2} + \frac{V_o-2}{4} = 0$$

$$\Rightarrow \underline{V_o = -12 \text{ V}}$$

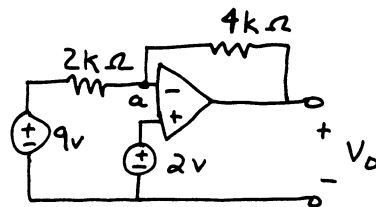


AP 6-2

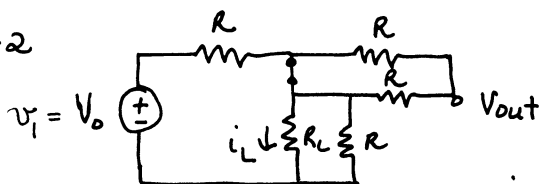


$$V_o = \text{constant}$$

$$\underline{i_L = \frac{V_o}{R}} \quad \text{if } R_L \ll R$$

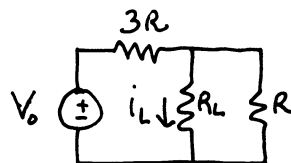

AP 6-3

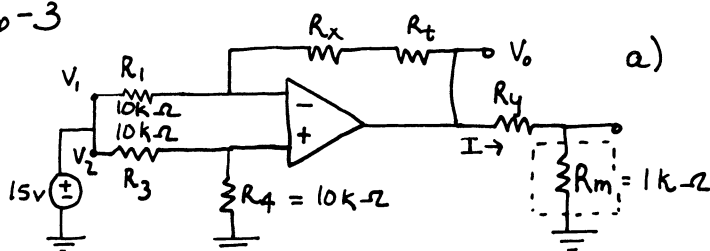

$V_1 = V_2 = 15V$ from result of problem 6-1

$$V_o = \frac{1 + (R_x + R_t)/R_1}{1 + R_3/R_4} (V_2) - \frac{R_x + R_t}{R_1} V_1$$

When $t = -55^\circ C$ $V_o = 0 \rightarrow R_t = 1000 e^{55/25} = 9.025 k\Omega$

$\therefore$ have $0 = \frac{(10 + R_x + 9.025)10(15)}{(10 + 10)(10)} - \frac{R_x + 9.025}{10}(15) \Rightarrow R_x = 988 k\Omega$

b) when $t = 125^\circ C$


$$R_t = 1000 e^{-125/25} = 6.74 \Omega$$

so $V_o = 6.75 V$

now because want $I = 1mA$ through the meter

$$R_y + R_m = \frac{V_o}{I} = \frac{6.75V}{1mA} = 6.75 k\Omega \Rightarrow R_y = 5.75 k\Omega$$

AP 6-4

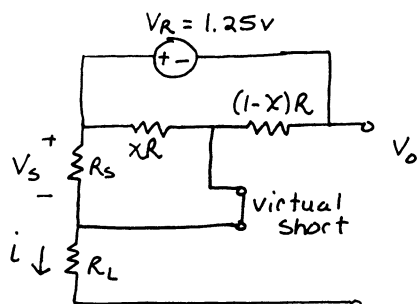


using voltage divider

$$V_s = \frac{xR}{xR + (1-x)R} V_R = x V_R$$

also $i = \frac{x V_R}{R_s}$

for $x = 1$, $i_{max} = \frac{(1)(1.25)}{1} = 1.25 A$ so $0 < i \leq 1.25 A$

AP 6-5

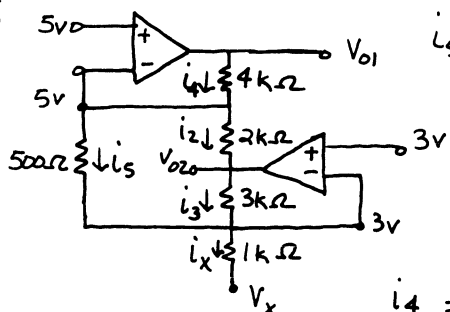

$$i_5 = \frac{5-3}{500} = 4mA, \quad i_x = \frac{3-V_x}{1}$$

$$\therefore i_3 = i_x - i_5 = -(1 + V_x) (mA)$$

$$V_{02} = (3k\Omega) i_3 + 3 = -3V_x (volts)$$

$$i_2 = \frac{5 - V_{02}}{2k} = \frac{(5 + 3V_x)}{2} (mA)$$

$$i_4 = i_2 + i_5 = \frac{5 + 3V_x}{2} + 4 = (6.5 + 1.5V_x) (mA)$$

$$V_{01} = (4k\Omega) i_4 + 5 = 26 + 6V_x + 5 = (31 + 6V_x) (volts)$$

so $V_{01} - V_{02} = 31 + 6V_x - (-3V_x) = 31 + 9V_x = 13V \Rightarrow V_x = -2V$

AP 6-6

The ladder structure uses the shunt resistors to generate n binary weighted currents. From the left we have $I_1 = \frac{V_R}{2R}$ $I_2 = I_1/2$, ..., $I_n = I_1/2^{n-1}$

Depending on the switch position, each current is diverted to the ground bus I^+ or to the virtual ground bus I^- . Use bit b_k to identify the status of the switch k . Then

$$V_o = -\frac{R_f}{R} V_R (b_1 2^{-1} + b_2 2^{-2} + \dots + b_{n-1} 2^{n-1} + b_n 2^{-n})$$

Design Problems


OP 6-1 $V_o = -\left[\frac{12}{4} V_1 + \frac{12}{6} (-10)\right]$

range is: $\pm 12 = -[3V_1 - 20]$

$$V_1 = \left(\frac{20 \pm 12}{3}\right), \text{ so } V_1^+ = \frac{32}{3} \text{ \& } V_1^- = \frac{8}{3}$$

so have $\underline{\frac{8}{3} < V_1 < \frac{32}{3}}$ linear range

DP 6-2

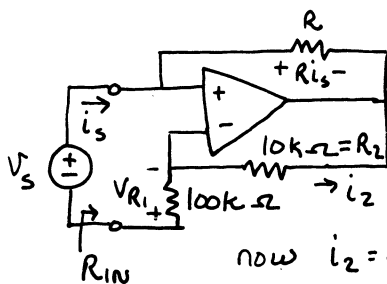

$$R_{in} = \frac{V_s}{i_s}$$

$$V_{R_2} = R_2 i_s \therefore i_2 = i_s R/R_2$$


now $i_2 = i_1$ so $V_{R_1} = i_1 R_1 = i_s \frac{R}{R_2} R_1$

KVL around left mesh: $V_s + V_{R_1} = 0$ or $V_s + i_s \frac{R R_1}{R_2} = 0$

$$\text{so } R_{in} = \frac{V_s}{i_s} = -\frac{R R_1}{R_2} = -\frac{R (100)}{10} = -10R$$

need $\left|\frac{V_s}{i_s}\right| = 1M\Omega$ or $\underline{R = 100k\Omega}$ * note it is a negative resistance

DP 6-3

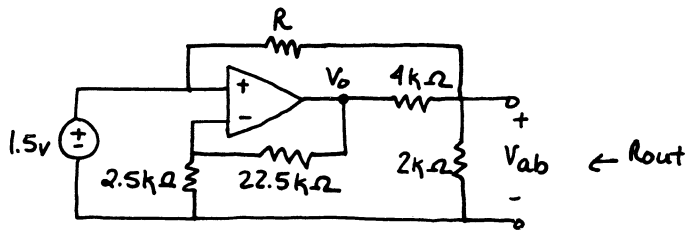

$$V_o = \left(1 + \frac{22.5}{2.5}\right) 1.5 = 15V$$

KCL at terminals a-b $\frac{V_{ab}}{2} + \frac{V_{ab}-1.5}{R} + \frac{V_{ab}-15}{4} = 0$ (1)

$$\Rightarrow V_{ab} = \frac{6+15R}{3R+4}$$


now find i_{sc} at a-b

$$i_{sc} = \frac{1.5}{R} + \frac{15}{4} \quad (2)$$

$$\text{now } R_{out} = \frac{V_{ab}}{i_{sc}} = \frac{\frac{6+15R}{3R+4}}{\frac{6+15R}{4R}} = \frac{4R}{3R+4} = .57k\Omega$$

$$\therefore R = 1k\Omega$$

DP 6-4

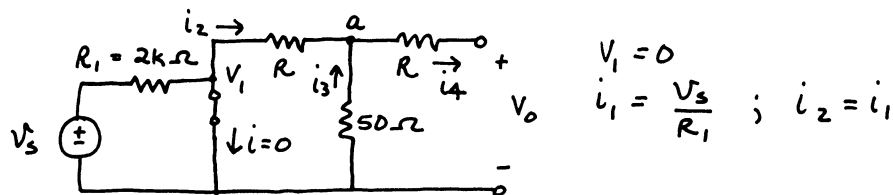

at a: $V_a = V_1 - i_2 R = -i_2 R = -\frac{V_s R}{R_1}$

$$i_3 = -\frac{V_a}{50} = \frac{V_s R}{50 R_1}$$

at a: $i_4 = i_2 + i_3 = \frac{V_s}{R_1} + \frac{R}{50 R_1} V_s = \frac{50+R}{50 R_1} V_s$

$$V_o = V_a - R i_4 = -\frac{R}{R_1} V_s = -\frac{R(50+R)}{50 R_1} V_s$$


$$\text{so } \frac{V_o}{V_s} = -\frac{R}{R_1} \left(1 + \frac{50+R}{50}\right)$$

given $R_1 = 2k\Omega$ find R if $V_o/V_s = -1000$

$$\Rightarrow -1000 = \frac{R}{2000} \left(1 + \frac{50+R}{50}\right) \text{ yields } R = 9950\Omega$$

DP 6-5 need gain $V_o/V_s = \frac{4}{20 \times 10^{-3}} = 200$


inverting ckt

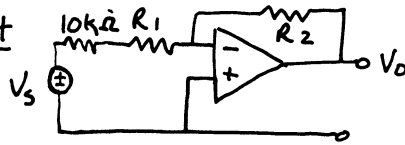

$$\frac{V_o}{V_s} = -\frac{R_2}{R_1 + R_m}$$

use $R_2 = 2 \text{ M}\Omega$, $R_1 = 0$
 $R_m = 10 \text{ k}\Omega$

non inverting ckt

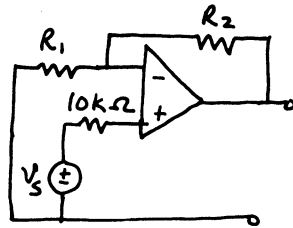

$$\frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1}\right)$$


$R_{in} = \text{higher}$ for noninverting compared to inverting

choose $(1 + R_2/R_1) = 200$ use $R_1 = 1 \text{ k}\Omega$, $R_2 = 199 \text{ k}\Omega$

so use non inverting for higher R_{in} for microphone

Spice Problems

SP 6-1

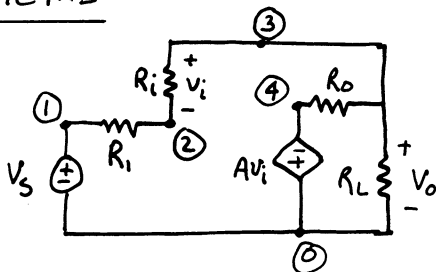

a) input file

```
VS 1 0 DC 10.0000768
R1 1 2 1K
Ri 2 3 10meg
RO 4 3 1e-99
RL 3 0 5K
EI 0 4 3 2 1meg
.TF V(3) VS
.END
```

b) input file

```
VS 1 0 DC 10.0000768
R1 1 2 1K
Ri 2 3 80K
RO 4 3 100
RL 3 0 5K
EI 0 4 3 2 1E4
.TF V(3) VS
.END
```

$$\Rightarrow V(3)/V_s = 1.0$$




$$V(3)/V_s = 0.9999$$

$$R_{in} = 7.8 \times 10^8 \Omega$$

$$R_{out} = 10 \text{ m}\Omega$$

SP 6-2

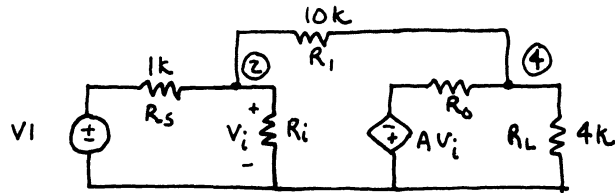

a) ideal

$$A = 10^9, R_i = 10M\Omega, R_o = 0$$

```

VI 1 0 DC 1
RS 1 2 1000
RI 2 0 10meg
R1 2 4 10k
EI 0 3 2 0 10meg
RO 3 4 0
RL 4 0 4k
.DC VI 1 1 1
.PRINT DC V(4)
.END

```

Ans. $V(4) = -9.9999V$

b) actual

$$A = 10^4, R_i = 200k\Omega, R_o = 5k\Omega$$

```

VI 1 0 DC 1
RS 1 2 1000
RI 2 0 200k
R1 2 4 10k
EI 0 3 2 0 1E04
RO 3 4 5k
RL 4 0 4k
.DC VI 1 1 1
.PRINT DC V(4)
.END

```

Ans. $V(4) = -9.9697V$

SP 6-3 See figure in SP 6-1

```


input file: VS 1 0 DC 10.0000768
R1 1 2 1k
Ri 2 3 100k
Ro 4 3 1000
RL 3 0 10k
EI 0 4 3 2 1e4
.TF V(3) VS
.END

```

Ans. $V(3) = 9.9990$, $R_{in} = 9.092E+08\Omega = 909\text{ Megaohm}$

$$V(3)/VS = .9999$$

SP 6-4

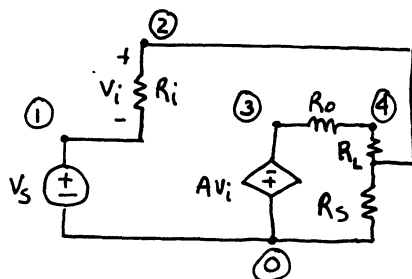

$$R_L = 10k\Omega$$


```

input file: RL 4 2 10k
VS 1 0 DC 1
RI 1 2 100k
EI 0 3 2 1 1E5
RO 3 4 1k
RS 2 0 10k
.TF V(4,2) VS
.END

```

answer: $V(4,2)/V(5) = 2$, $R_{out} = 10k\Omega$

SP 6-5

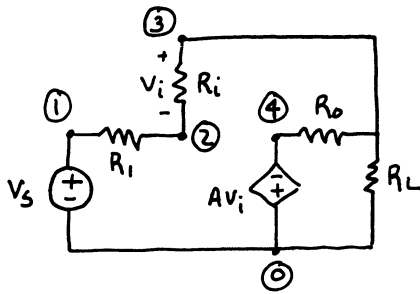


input file :

```

VS 1 0 DC 10.0000768
R1 1 2 10K
Ri 2 3 100K
Ro 4 3 100
RL 3 0 10K
EI 0 4 3 2 1E4
.TF V(3) VS
.END

```

SP 6-6

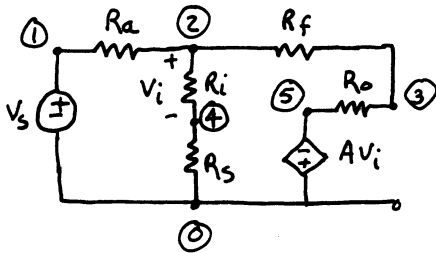

input file :


```

VS 1 0 DC 1
RA 1 2 25K
RF 2 3 50K
Ri 2 4 500K
Ro 5 3 100
RS 4 0 10K
EI 0 5 2 4 1E5
.TF V(3) VS
.END

```

	Ideal	Actual
V_o/V_s	-2	-2
R_{in}	25 k Ω	25 k Ω
R_{out}	0	3.2 m Ω

SP 6-7

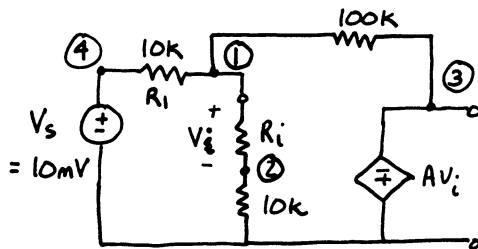

ideal op amp so let $A = 10^6$
 $R_i = 10^9 \Omega$

output :

$$\frac{V(3)}{V_s} = -1.00E+01$$

$R_{in} = 1.00E+04$

$R_{out} = 0.00E+00$

input resistance seen by V_s is 10 k Ω

```

VS 4 0 DC .01
R1 4 1 10K
R2 1 3 100K
R3 2 0 10K
RI 1 2 1E9
EI 0 3 1 2 1E6
.DC VS 10M 10M 1
.TF V(3) VS
.PRINT DC V(3)
.END

```

Chapter 7

Exercises

Ex. 7-1 $100\text{ms} = 0.1\text{s}$, $10\text{mA} = 0.01\text{A}$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(t) dt \Rightarrow v(.1) = 0 + \frac{1}{10^{-5}} \int_0^{.1} (.01) dt$$

$$\underline{v(.1) = 100\text{V}}$$

$$q(.1) = C v(.1) = 10^{-5}(100) = \underline{10^{-3}\text{C} = 1\text{mC}}$$

Ex. 7-2 break up into intervals

$$v(t) = \begin{cases} 10t & 0 < t < 1 \\ 10 & 1 < t < 2 \\ 10(3-t) & 2 < t < 3 \\ 0 & t > 3 \end{cases}$$

$$\text{now } i = C dv/dt = 10^{-6} \frac{dv}{dt}$$

$\therefore$ have

$$i(t) = \begin{cases} 10^{-6}(10) = 10^{-5}\text{A} & 0 < t < 1 \\ 0 & 1 < t < 2 \\ 10^{-6}(-10) = -10^{-5}\text{A} & 2 < t < 3 \\ 0 & t > 3 \end{cases}$$

Ex. 7-3 break up into intervals

$$i = \begin{cases} 0 & t < 1 \\ 1 & 1 < t < 2 \\ 0 & t > 2 \end{cases}$$


$$\text{now } v(t) = v(0) + \frac{1}{C} \int_0^t i dt = \frac{1}{10^{-4}} \int_0^t i dt$$

$$\therefore 0 < t < 1 \Rightarrow v(t) = 10^4 \int_0^t 0 dt = 0$$

$$1 < t < 2 \Rightarrow v(t) = v(1) + 10^4 \int_1^t 1 dt = 0 + 10^4 t = 10^4 t \text{ V}$$

$$t > 2 \Rightarrow v(t) = v(2) + 10^4 \int_2^t 0 dt = 10^4(2) = \underline{2 \times 10^4 \text{ V}}$$

Ex 7-4

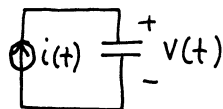

because $i(t) = 0$ when $t < 0$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt = \frac{1}{5} \int_0^t (2 + 2\cos 5t) dt + v(0) = \underline{\underline{\frac{2}{5}t + \frac{2}{25}\sin 5t + \frac{1}{5}v}}$$

Ex. 7-5

$$W = \frac{1}{2} C V^2 = \frac{1}{2} (2 \times 10^{-4}) (100)^2 = \underline{1\text{J}}$$

$$V_C(0^+) = V_C(0^-) = \underline{100\text{V}}$$