


CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 1

1/21/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

Problem 1 (10 points)
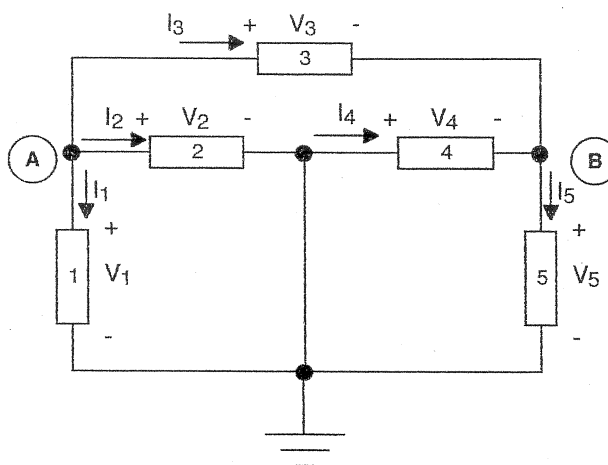
$$\frac{16}{20}$$


Consider the five element circuit shown above. You measure the electrical parameters shown below for each circuit element. Complete this table and indicate whether each device is absorbing (**A**) or delivering (**D**) power. Current is defined to be positive when it flows into the positive terminal of the device.

Device	Voltage	Current	Power	A/D
1	+30 V	-10 A	-300 W	D
2	+30 V	4 A	+120 W	A
3	+50 V	6 A	+300 W	A
4	+20 V	4 A	+80 W	A
5	-20 V	10 A	-200 W	D

$$P = IV \quad ① \quad i = \frac{P}{V} = \frac{-300}{30} = -10 \text{ A}$$

$$② \quad V = \frac{P}{i} = \frac{120}{4} = +30 \text{ V}$$

$$④ \quad V = \frac{P}{i} = \frac{80}{4} = +20 \text{ V}$$

$$⑤ \quad i_5 = i_4 + i_3 = 6 + 4 = 10 \text{ A}$$

$$P = IV = 10 \text{ A} \cdot -20 \text{ V} = -200 \text{ W}$$

Name : Jonathan Manuza Section: MA

CWRU e-mail: JMM57

Problem 2 (10 points)

- (a) An automobile battery is charged at a constant rate of 10000 milliamperes for 20 kiloseconds. Assume the charger keeps the battery voltage at a constant 0.012 kilovolts . What is the total energy in megajoules supplied to the battery?

$$W = \int p dt$$

ANSWER: .A megajoules

$$I = \frac{dq}{dt}$$

$$10000 \times 10^{-3} = \frac{Q}{2 \times 10^3}$$

$$Q = 2 \times 10^5$$

- (b) An electrical power plant supplies 0.800kilovolts and 12000 milliamperes to operate an electric motor. The power plant is supplying how many kilowatts?

ANSWER: 9.6 kilowatts

$$P = IV = 12000 \times 10^{-3} \cdot 800 \times 10^3$$

Name : Daniel Donato

Section: MN

CWRU e-mail: dpd11

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 1

1/21/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

Problem 1 (10 points)

20
20 *

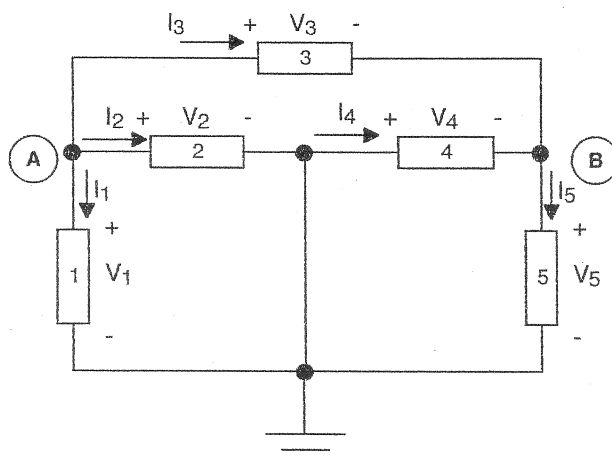

-20

Consider the five element circuit shown above. You measure the electrical parameters shown below for each circuit element. . Complete this table and indicate whether each device is absorbing (A) or delivering (D) power. Current is defined to be positive when it flows into the positive terminal of the device.

Device	Voltage	Current	Power	A/D
1	+30 V	-10 A	-300W	D
2	+30V	4 A	+ 120 W	A
3	+50 V	6 A	+300 W	A
4	20V	4 A	+80 W	A
5	-20 V	10A	-200W	D

$$I_5 = I_2 + I_4 =$$

Name: Daniel Donato Section: MN CWRU e-mail: dpd11

Problem 2 (10 points)

- (a) An automobile battery is charged at a constant rate of 10000 milliamperes for 20 kiloseconds. Assume the charger keeps the battery voltage at a constant 0.012 kilovolts. What is the total energy in megajoules supplied to the battery?

ANSWER: 2.4 megajoules

10A 20000S $P = 12 \cdot 10 = 120W$

$V = 12V$

$120 \cdot 20000$
2400000J

- (b) An electrical power plant supplies 0.800kilovolts and 12000 milliamperes to operate an electric motor. The power plant is supplying how many kilowatts?

ANSWER: 9.6 kilowatts

800V 12A

$$12(800) = 9600W = 9.6 \times 10^3$$

Name :

Chad Kaschke

Section:

MA

CWRU e-mail:

cwkl

CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering

Department of Electrical Engineering and Computer Science


ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 1

1/21/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

Problem 1 (10 points)

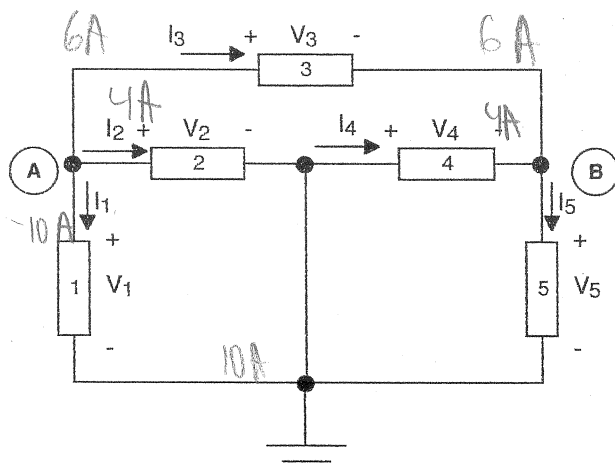17
20

Consider the five element circuit shown above. You measure the electrical parameters shown below for each circuit element. Complete this table and indicate whether each device is absorbing (A) or delivering (D) power. Current is defined to be positive when it flows into the positive terminal of the device.

$$P = iV$$

Device	Voltage	Current	Power	A/D
1	+30 V	-10 A	-300 W	D
2	+30 V	4 A	+120 W	A
3	+50 V	6 A	+300 W	A
4	+20 V	4 A	+80 W	A
5	-20 V	+10 A	-200 W	A

$$I_{in} = \int i dt$$

$$10 = 10 A$$

Name :

Chad Kaschube

Section:

MA

CWRU e-mail:

cwkl

Problem 2 (10 points)

$$i = 10 \text{ Amps} \quad 20,000 \text{ seconds}$$

$$V = 12 \text{ Volts}$$

- (a) An automobile battery is charged at a constant rate of 10000 milliamperes for 20 kiloseconds. Assume the charger keeps the battery voltage at a constant 0.012 kilovolts. What is the total energy in megajoules supplied to the battery?

ANSWER: 2.4 megajoules

$$10 \cdot 12 = 120 \text{ W}$$

$$120 (20,000) =$$

$$2,400,000 \text{ Joules}$$

$$\text{megajoules } 10^6$$

- (b) An electrical power plant supplies 0.800 kilovolts and 12000 milliamperes to operate an electric motor. The power plant is supplying how many kilowatts?

ANSWER: 9.6 kilowatts

$$V = 800 \text{ Volts}$$

$$I = 12 \text{ AMPs}$$

$$800 \cdot 12 = 9600 \text{ Watts} = 9.6 \text{ kilowatts}$$

Name : Kevin Engel Section: TA CWRU e-mail: kte1

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 1

1/28/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

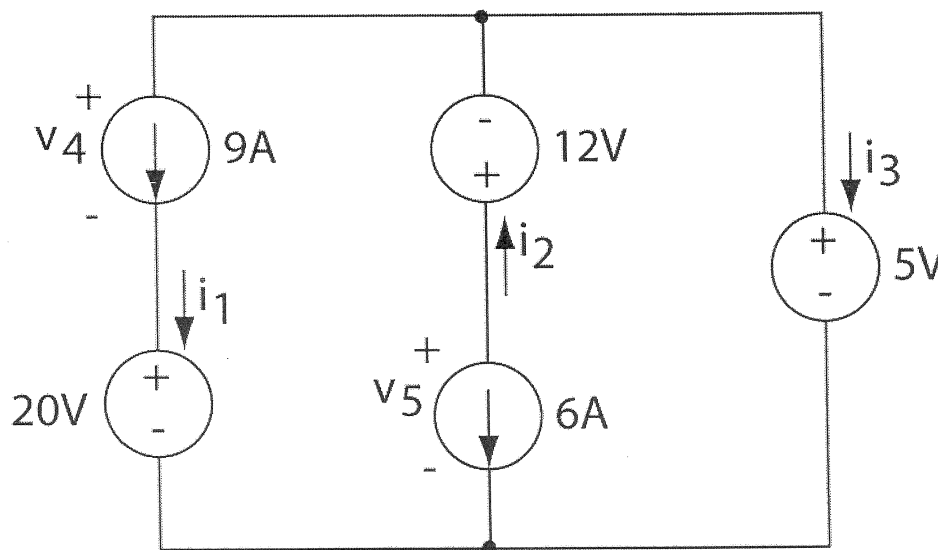Problem 1 (10 points) – CONNECTION CONSTRAINTS

Answer the following questions for the circuit below. Be sure to follow the sign conventions indicated.



19
20

(a) Determine the indicated currents through the voltage sources.

$i_1 =$ 9 A amperes

$i_2 =$ -6 A amperes

(b) What is the current through the 5 volt voltage source.


$i_3 =$ -15 amperes

(c) What is the voltage across each current source?

$v_4 =$ -15 volts

$v_5 =$ 17 volts

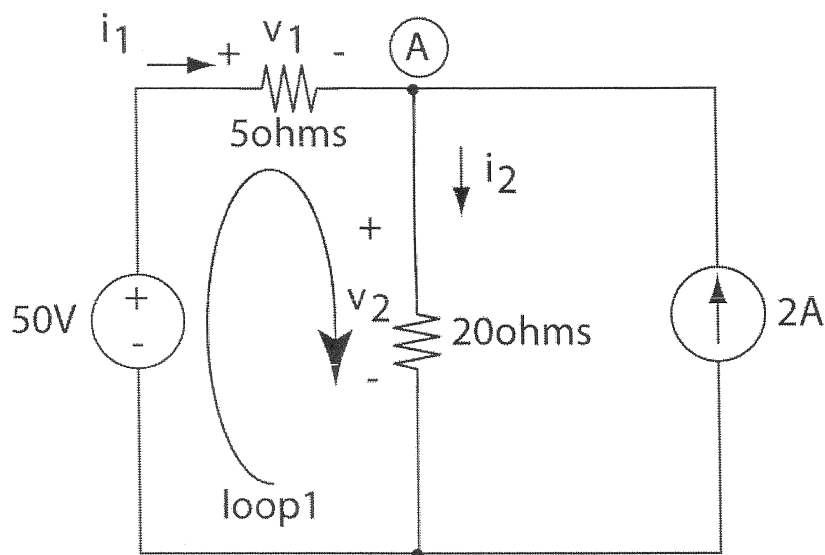Problem 2 (10 points) COMBINED CONSTRAINTS



(a) How many nodes are in the above circuit? # nodes = 3 ✓

(b) Write the Kirchoff's Current Law equation for all the currents at node A. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$2 + i_1 = i_2 \quad \checkmark$$

(c) Write the Kirchoff's Voltage Law equation for loop 1. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$-50 + v_1 + v_2 = 0 \quad \checkmark$$

(d) What are the values of i_1 and i_2 ?

$i_1 =$.4 amperes ✓

$i_2 =$ 2.4 amperes

$$\begin{aligned} v_1 + v_2 &= 50 \\ 5i_1 + 20i_2 &= 50 \end{aligned}$$

$$\begin{aligned} i_1 + 4i_2 &= 10 \\ i_2 - i_1 &= 2 \end{aligned}$$

$$i_2 = \frac{12}{5} \quad i_1 = \frac{2}{5}$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 1

1/28/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

Problem 1 (10 points) – CONNECTION CONSTRAINTS

Answer the following questions for the circuit below. Be sure to follow the sign conventions indicated.

13
20

$-9 + i_2 - i_3 = 0$
 $i_1 + 6A + i_3 = 0$
 $i_3 = -15A$
 $i_2 = 6$


(a) Determine the indicated currents through the voltage sources.
 $I_1 = \underline{9A}$ amperes
 $I_2 = \underline{-6A}$ amperes

(b) What is the current through the 5 volt voltage source.
 $I_3 = \underline{-15A}$ amperes

(c) What is the voltage across each current source?
 $V_4 = \underline{-15V}$ volts
 $V_5 = \underline{17V}$ volts

Handwritten work on the right:
 $i_2 - i_3 = 9$
 $i_1 + i_3 = -6$
 $(A) -i_2 + i_3 = 0$
 $(B) i_1 + i_2 + i_3 = 0$
 $-20 - V_4 - 12V + V_5 = 0$
 $-V_5 + 12V + 5V = 0$
 $V_5 = 17V$
 $V_4 = -15V$
 $-32 + 17 = -V_4$
 $-15 = V_4$

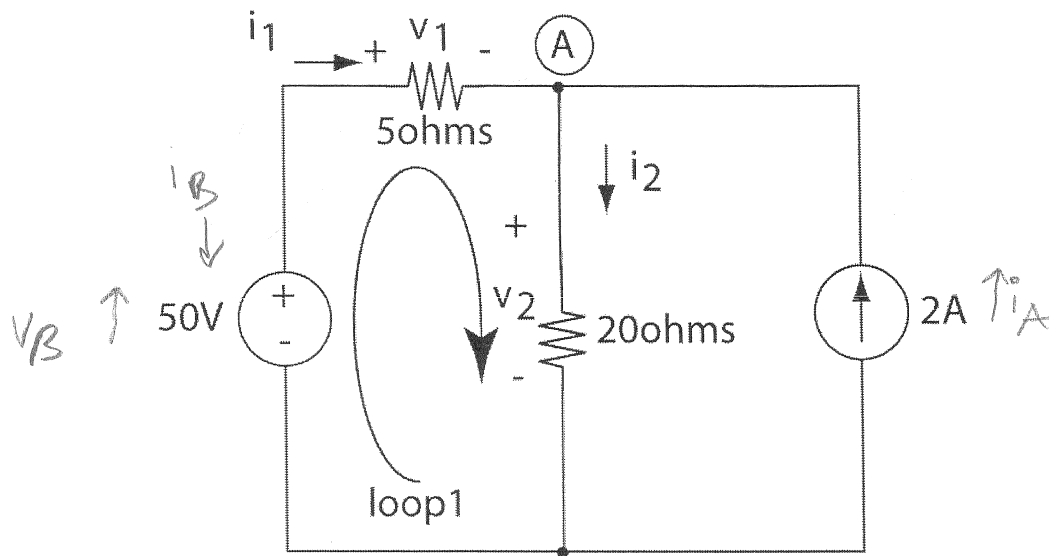Problem 2 (10 points) COMBINED CONSTRAINTS



(a) How many nodes are in the above circuit? # nodes = 3 ✓

(b) Write the Kirchoff's Current Law equation for all the currents at node A. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$i_1 - i_2 + \cancel{2} = 0$$

(c) Write the Kirchoff's Voltage Law equation for loop 1. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc. -2

$$\cancel{-V_B} + V_1 + V_2 = 0$$

(d) What are the values of i_1 and i_2 ?

$i_1 =$ ~~2~~ amperes

$i_2 =$ ~~2~~ amperes

$$V_1 + V_2 = 50V$$

$$i_1 R_1 + i_2 R_2 = 50V$$

$$i_1 - i_2 + 2 = 0$$

$$i_2 = i_1 + 2$$

$$i_2 - 2 + i_B = 0$$

$$25 = i_2$$

$$i_1 + i_B = 0$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 1

1/28/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

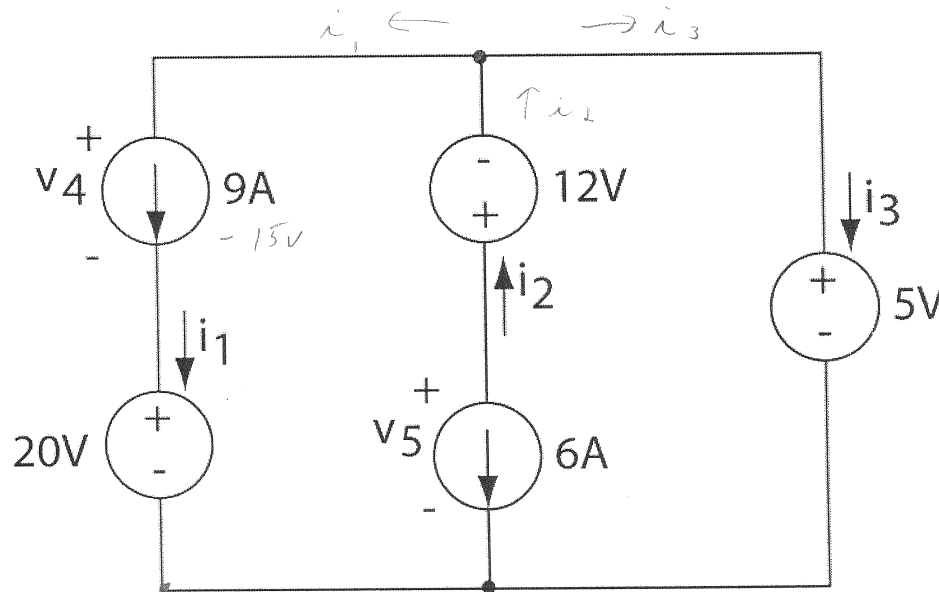Problem 1 (10 points) – CONNECTION CONSTRAINTS

Answer the following questions for the circuit below. Be sure to follow the sign conventions indicated.



(a) Determine the indicated currents through the voltage sources.

$i_1 =$ 9A amperes

$i_2 =$ -6A amperes

(b) What is the current through the 5 volt voltage source.

$i_3 =$ -15A amperes

(c) What is the voltage across each current source?

$V_4 =$ -15V volts

$V_5 =$ 17V volts

KCL

$$-i_1 + i_2 - i_3 = 0$$

$$-9A + -6A - i_3 = 0$$

$$i_3 = -15A$$

KVL


$$-20V - V_4 + 5V = 0$$

$$-15V = V_4$$

$$-20V + 15V - 12V + V_5 = 0$$

$$V_5 = 17V$$

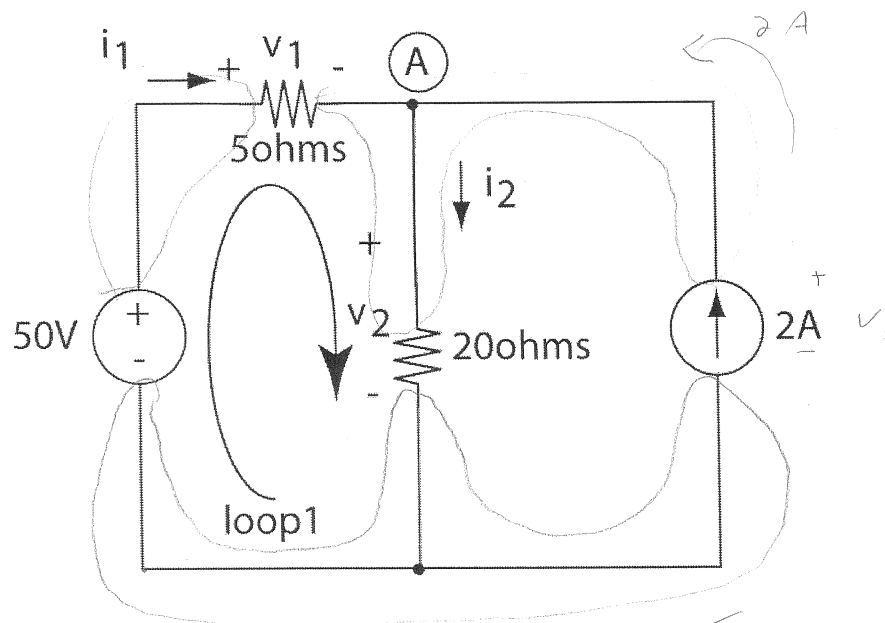Problem 2 (10 points) COMBINED CONSTRAINTS



- (a) How many nodes are in the above circuit? # nodes = 3 ✓
- (b) Write the Kirchoff's Current Law equation for all the currents at node A. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.

$$i_1 - i_2 + 2A = 0$$

- (c) Write the Kirchoff's Voltage Law equation for loop 1. Your answer should be in terms of given circuit parameters, i.e., i_1 , i_2 , etc.
 V_1, V_2

$$-50V + V_1 + V_2 = 0$$

- (d) What are the values of i_1 and i_2 ?

$i_1 =$ 0.4 amperes ✓

$i_2 =$ 2.4 amperes

KVL

$$-50V + i_1 \cdot 50\Omega + i_2 \cdot 20\Omega = 0$$

$$-50V + (i_2 - 2)50 + i_2 \cdot 20 = 0$$

$$-50V + 50i_2 - 100 + 20i_2 = 0$$

$$70i_2 = 150$$

$$i_2 = 2.14A$$

$$i_1 - 2.4 + 2 = 0$$

$$i_1 = 0.4A$$

Name : Stanley Shookens Section: ME

CWRU e-mail: SKLZ35

CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering

Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 3


2/4/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE
STATE ALL ASSUMPTIONS

EQUIVALENT CIRCUITS. VOLTAGE AND CURRENT DIVISION

1. (10 points) Determine the current i_2 going through the 20Ω resistor in the circuit shown below.


$i_2 =$ _____ amperes

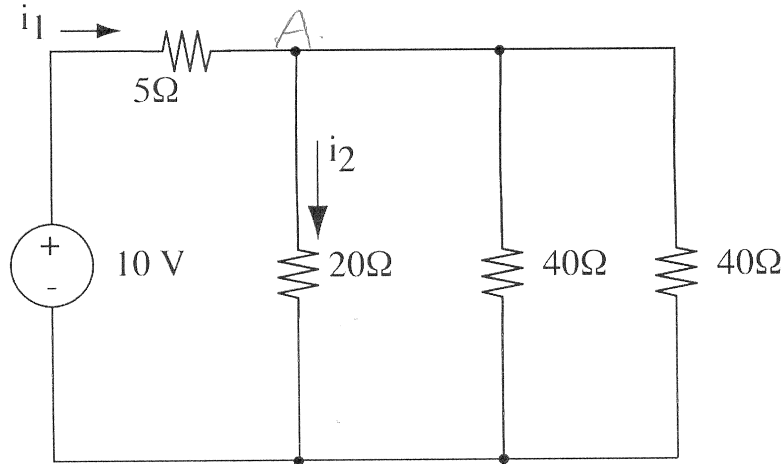

$$\frac{9}{20}$$

$$\frac{1}{x} = \frac{1}{20} + \frac{1}{40} + \frac{1}{40}$$
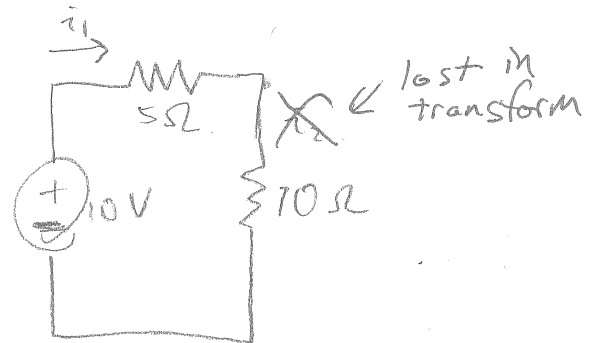
$$\frac{1}{x_{\text{req}}} = \frac{1}{10} = x_{\text{req}} = 10\Omega$$




$$V = IR$$

$$I = \frac{V}{R} = \frac{10V}{10\Omega} = 1A$$

COMBINED CONSTRAINTS

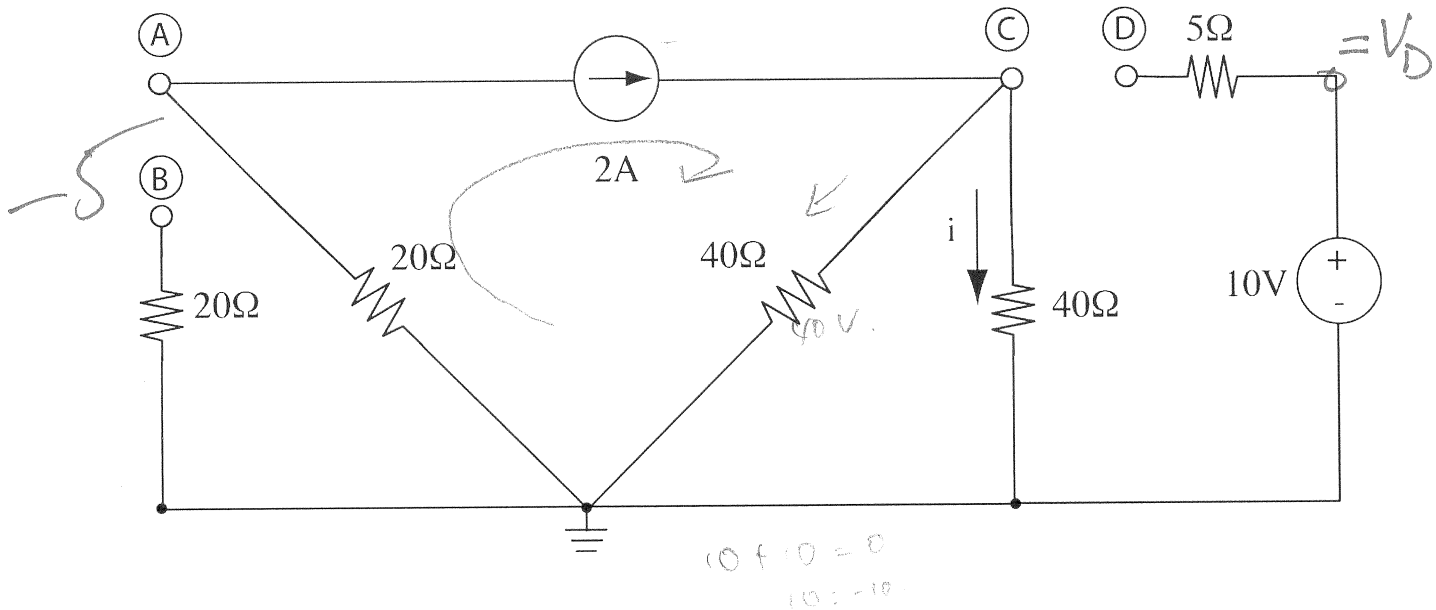2. (10 points) Determine the numerical values of the indicated parameters for the circuit shown below. Be sure to observe the indicated current direction and voltage polarity in your answer.



V_D , the voltage at point D with respect to ground	40V
i , the current through the vertical 40Ω resistor (note the indicated direction)	2A
V_C , the voltage at point C with respect to ground	40V
V_B , the voltage at point B with respect to ground	$\frac{1}{5}V = \cancel{0.2V}$
V_A , the voltage at point A with respect to ground	-40V

$$V_C = I R_{\text{eq}}$$

$$V_C = 2(20)$$

$$= 40V$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{40} + \frac{1}{40}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{20}$$

For KVL, $+V_C + V_A = 0$

$$40 + V_A = 0$$

$$V_A = -40$$

~~$V_D = V_C$~~ because V_D is not a close circuit, so current will not go there.

V_B is a open circuit, so no current go through.

But $V_B = \text{ground}; 0!!!$

$$V_B = I R_{\text{eq}} = 2 \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{40} \right)$$

$$= 2 \left(\frac{1}{10} \right)$$

$$V_B = \frac{2}{10}$$

Name: Jennifer M. AndySection: MECWRU e-mail: jma20**CASE WESTERN RESERVE UNIVERSITY**

Case School of Engineering

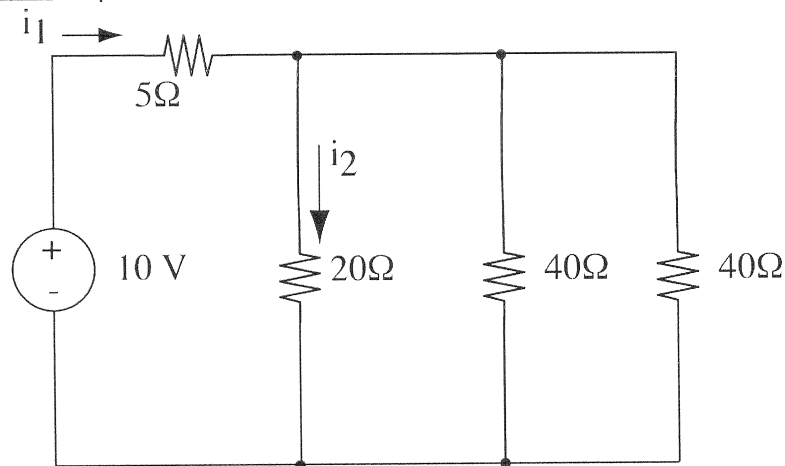
Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)



Quiz No. 3

2/4/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE
STATE ALL ASSUMPTIONS

EQUIVALENT CIRCUITS. VOLTAGE AND CURRENT DIVISION1. (10 points) Determine the current i_2 going through the 20Ω resistor in the circuit shown below. $i_2 = \frac{11}{20}$ amperes

$$i_1 = \frac{10V}{5\Omega} = 2A$$

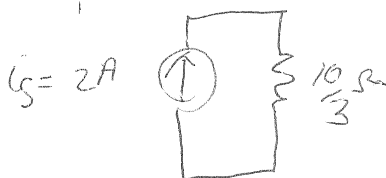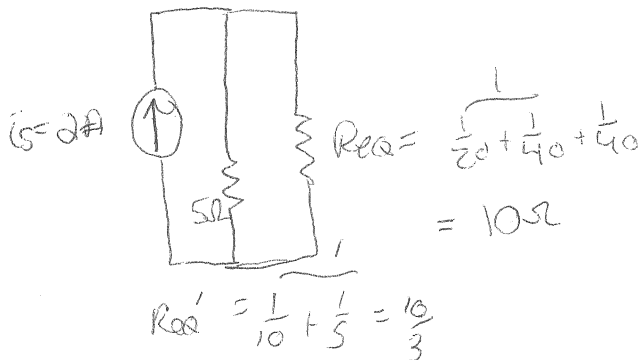

$$V = 20 \frac{1}{3} V$$

$$V = i_2 R$$


$$i_2 = \frac{(20 \frac{1}{3}) V}{20\Omega}$$

$$i_2 = \frac{11}{20} A$$


$$\frac{11}{20}$$

Name: Leah AndySection: MECWRU e-mail: jma 20**COMBINED CONSTRAINTS**

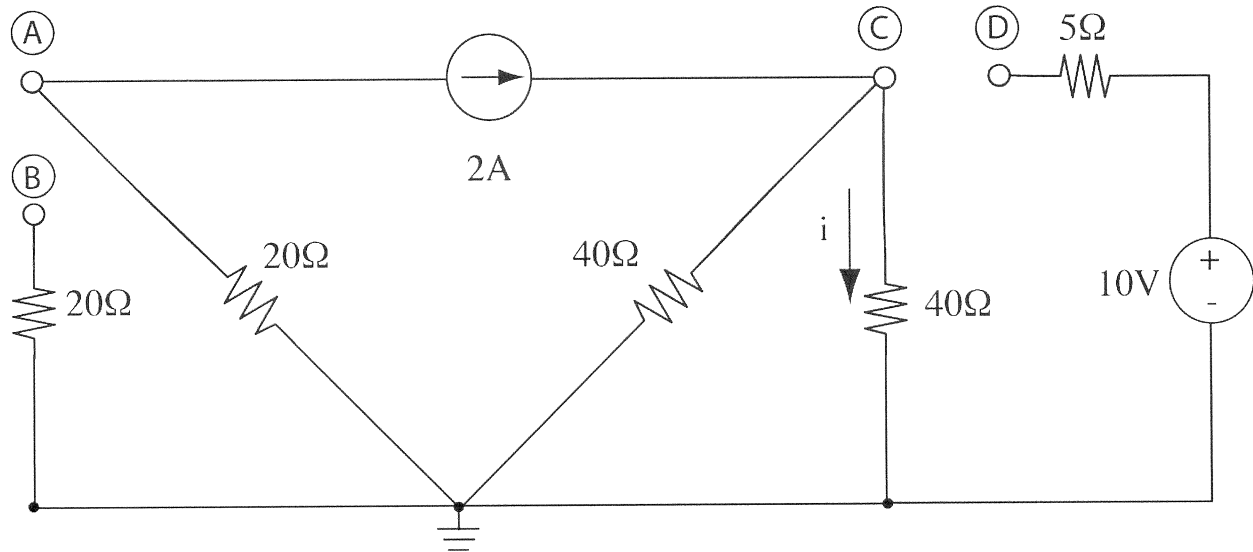2. (10 points) Determine the numerical values of the indicated parameters for the circuit shown below. Be sure to observe the indicated current direction and voltage polarity in your answer.




V_D , the <u>voltage</u> at point D with respect to ground	-5A
i , the current through the vertical 40Ω resistor (note the indicated direction)	$\frac{1}{3}A$
V_C , the voltage at point C with respect to ground	$\frac{40}{3}V$ (13.33V)
V_B , the voltage at point B with respect to ground	ϕ
V_A , the voltage at point A with respect to ground	-40V

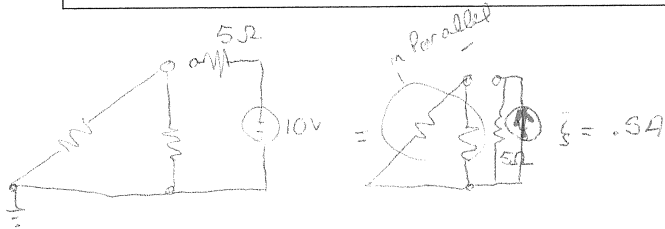

$$i = \frac{V_C}{R} = \frac{(40/3)}{40}$$

$$i = \frac{1}{3}A$$

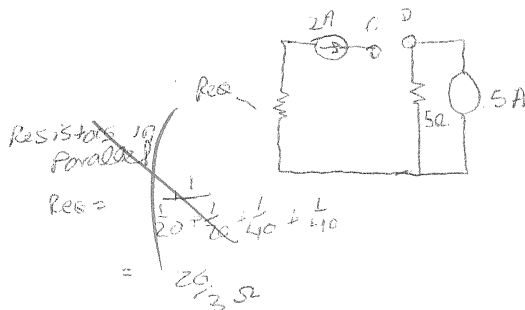

$$V_C = i R_{eq}$$

$$= (2A)(20/3)\Omega$$

$$V_C = 40/3V$$

Node A

$$KCL = i_A - 2A = 0$$

$$i_A = 2A$$

$$V_A = i_A R$$

$$= (2A)(20\Omega)$$

$$= 40V$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 3


2/4/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE
STATE ALL ASSUMPTIONS

EQUIVALENT CIRCUITS. VOLTAGE AND CURRENT DIVISION

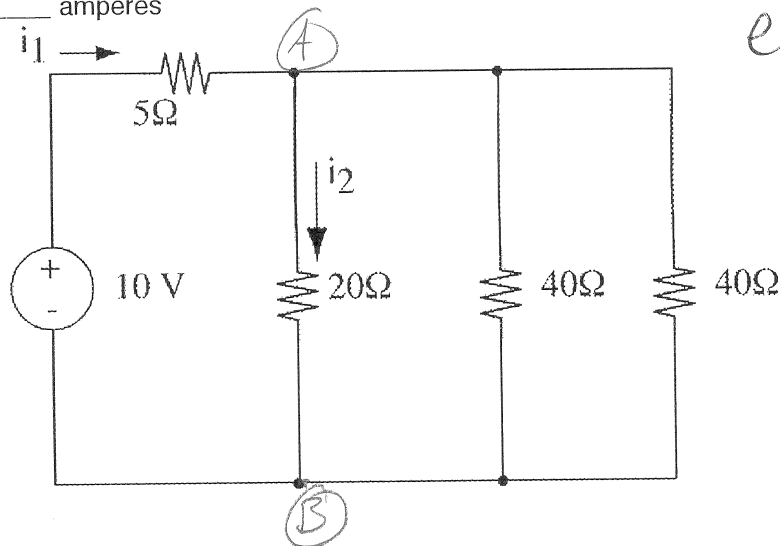
1. (10 points) Determine the current i_2 going through the 20Ω resistor in the circuit shown below.

$i_2 = \underline{\underline{\frac{1}{3}}}$ amperes



excellent

$$\frac{20}{20+40+40}$$

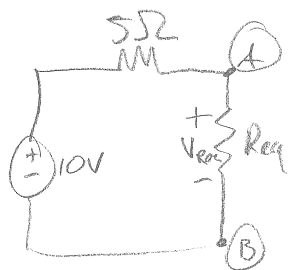

$$\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{40} + \frac{1}{40} = \frac{4}{40} = \frac{1}{10}$$

$$R_{eq} = 10\Omega$$

$$i_1 = \frac{V}{5+10} = 1.5 \text{ A}$$


$$V_{Req} = \frac{2}{3} \text{ V} = \frac{20}{3}$$

$$i_2 = \frac{V_{Req}}{20\Omega} = \frac{\frac{20}{3}}{20} = \boxed{\frac{1}{3} \text{ A}}$$

Name: Dan Pawlowski Section: ME CWRU e-mail: dfp9

COMBINED CONSTRAINTS

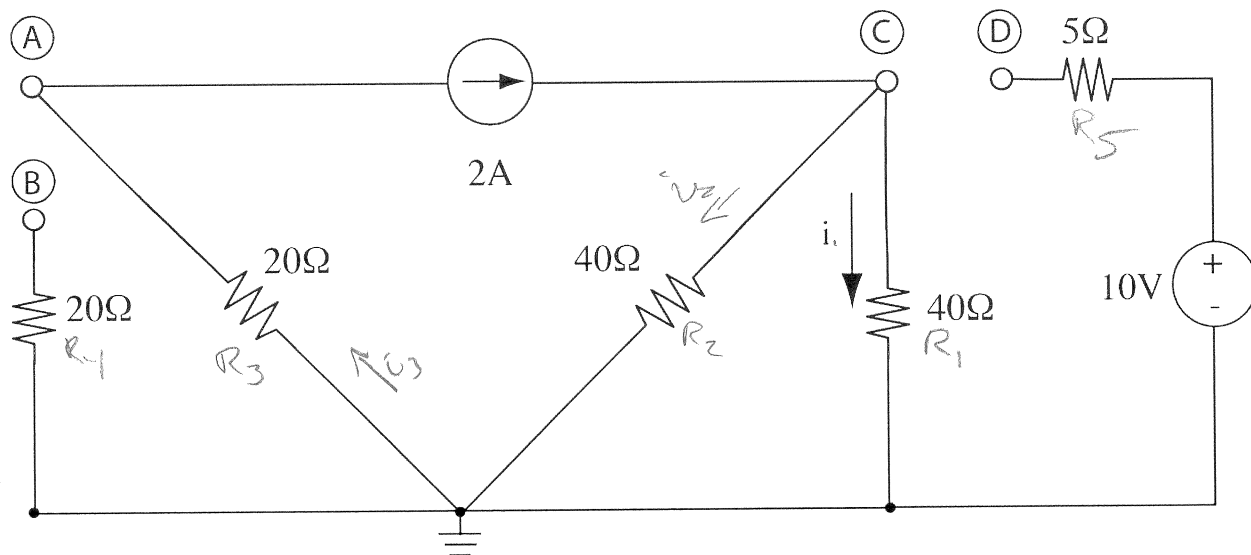2. (10 points) Determine the numerical values of the indicated parameters for the circuit shown below. Be sure to observe the indicated current direction and voltage polarity in your answer.



V_D , the voltage at point D with respect to ground	10 V
i_1 , the current through the vertical 40Ω resistor (note the indicated direction)	1 A
V_C , the voltage at point C with respect to ground	40 V
V_B , the voltage at point B with respect to ground	0 V
V_A , the voltage at point A with respect to ground	-40 V

$$C: 2A - i_1 - i_2 = 0 \quad i_1 = i_2$$

$$i_1 = 1A$$

$$V_C = i_1 R_1 = 40V$$

$$A: -2A + i_3 = 0$$

$$i_3 = 2A$$

$$-V_A = i_3 R_3 = (2A)(20\Omega)$$

Quiz No. 4

2/11/05


PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

STATE ALL ASSUMPTIONS

NODE VOLTAGE ANALYSIS

1. (10 points) Write node voltage equations for V_A , V_B and V_C for the following circuit given that

(4)

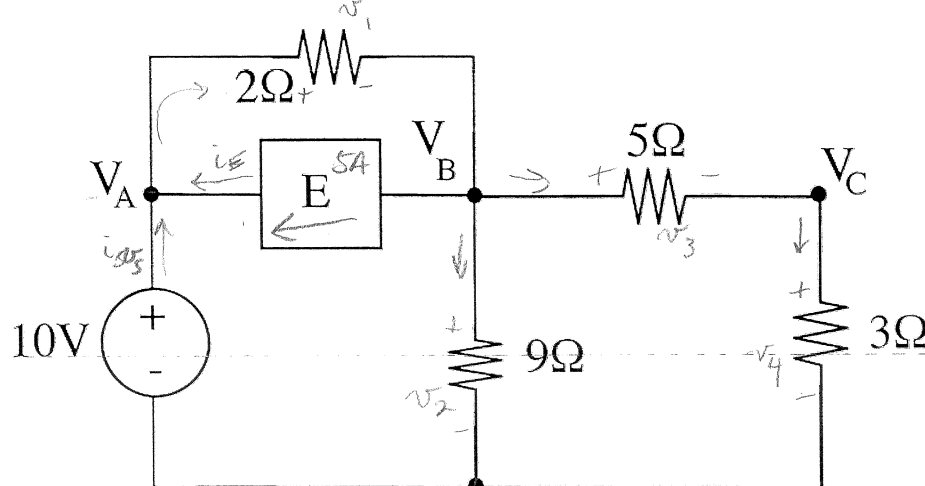

(a) E is a 5 volt voltage source with the plus reference on the left.

NODE	Node Voltage Equations
A	$-\frac{1}{2} V_A + (1 + \frac{1}{2}) V_B + 0 V_C = 0$
B	$\frac{1}{2} + 1 V_A + (\frac{1}{2} - \frac{1}{9} - \frac{1}{5}) V_B + \frac{1}{5} V_C = 0$
C	$0 V_A + \frac{1}{5} V_B + (\frac{1}{5} + \frac{1}{3}) V_C = 0$

A: $i_{v_5} + i_E = i_1$

$i_{v_5} + \frac{v_B - v_A}{R_1} = \frac{v_A - v_B}{R_1}$

B: $i_1 = i_E + i_2 + i_3$

$\frac{v_A - v_B}{R_1} = \frac{v_B - v_A}{R_1} + \frac{v_B - v_C}{R_2} + \frac{v_B - v_C}{R_3}$

C: $i_3 = i_4$

$\frac{v_B - v_C}{R_3} = \frac{v_C}{R_4}$

(b) E is a 5 ampere current source with the reference arrow pointing left.

NODE	Node Voltage Equations
A	$(\frac{1}{2}) V_A + (1 - \frac{1}{2}) V_B + 0 V_C = 0$
B	$(-\frac{1}{2} + 1) V_A + (\frac{1}{2} - \frac{1}{9} - \frac{1}{5}) V_B + (\frac{1}{5}) V_C = 0$
C	$0 V_A + \frac{1}{5} V_B + (\frac{1}{5} + \frac{1}{3}) V_C = 0$

$\frac{v_A + v_A}{R_1} = \frac{v_A - v_B}{R_1} + i_{v_5}$

A: $i_E + i_{v_5} = i_1$

$i_{v_5} = i_1 - i_E$

B: $i_1 = i_E + i_2 + i_3$

$\frac{v_B - v_A}{2} = \frac{v_B - v_A}{9} + \frac{v_B - v_C}{5}$


$v_A - 0 = \frac{v_B - v_A}{R_1} - (v_B - v_A)$

$v_A - \left(\frac{v_B - v_A}{R_1} \right) + (v_B - v_A) = 0$

MESH CURRENT ANALYSIS

2. (10 points) The circuit shown below is a DC model of a residential power distribution circuit. Use the mesh current method to write equations for the indicated currents.

(10)

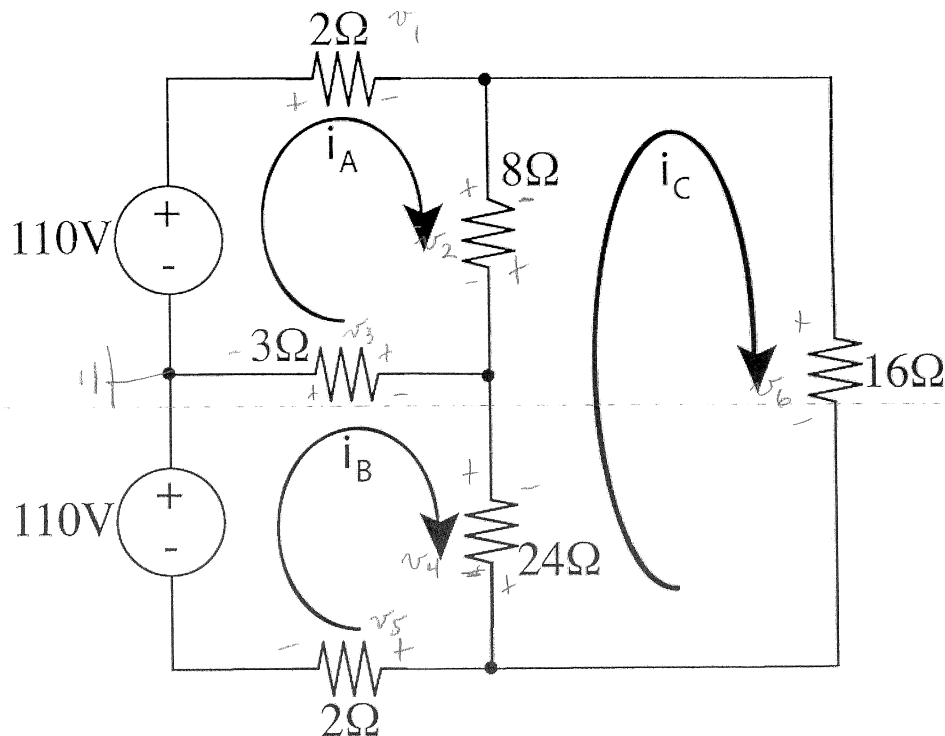

MESH	Mesh Current Equations
A	$13 i_A + (-3) i_B + (-8) i_C = 110$
B	$-3 i_A + 29 i_B + (-24) i_C = 110$
C	$-8 i_A + (-24) i_B + 48 i_C = 0$

A: $-110 + v_1 + v_2 + v_3 = 0$ B: $-110 + v_3 + v_4 + v_5 = 0$ C: $v_4 + v_2 + v_6 = 0$

A: $-110 + i_A 2 + i_A 8 - i_C 8 + i_A 3 - i_B 3 = 0$

$-110 + i_B 3 - i_A 3 + i_B 24 - i_C 24 + i_B 2$

$i_C 24 - i_B 24 + i_C 8 - i_A 8$

$+ i_C 16 = 0$

24
 8
 16

Quiz No. 4

2/11/05


PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE
STATE ALL ASSUMPTIONS

20/20

NODE VOLTAGE ANALYSIS


1. (10 points) Write node voltage equations for V_A , V_B and V_C for the following circuit given that

10

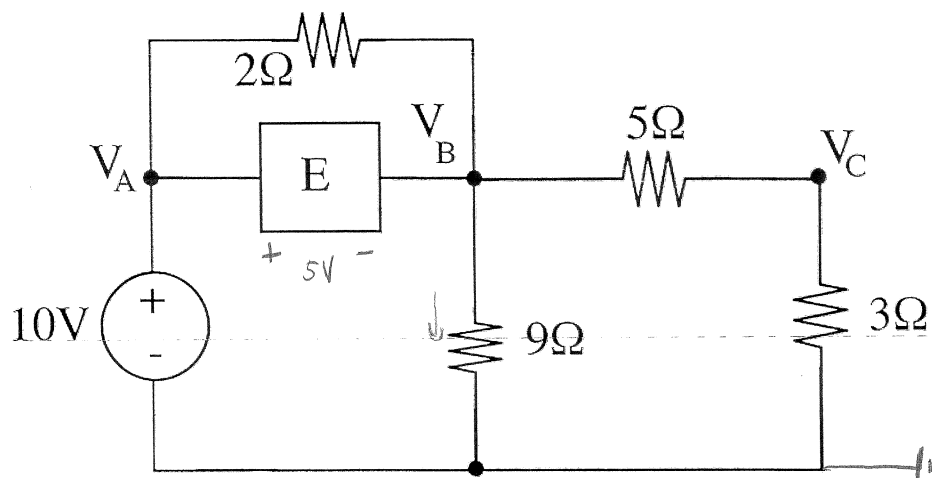

(a) E is a 5 volt voltage source with the plus reference on the left.

NODE	Node Voltage Equations
A	<u>1</u> V_A + <u>0</u> V_B + <u>0</u> V_C = <u>10V</u>
B	<u>1</u> V_A + <u>-1</u> V_B + <u>0</u> V_C = <u>-5V</u>
C	<u>0</u> V_A + <u>$-\frac{1}{5}S$</u> V_B + <u>$\frac{8}{15}S$</u> V_C = <u>0</u>

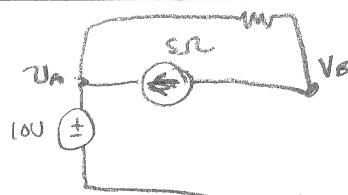

(b) E is a 5 ampere current source with the reference arrow pointing left.

NODE	Node Voltage Equations
A	<u>1</u> V_A + <u>0</u> V_B + <u>0</u> V_C = <u>10V</u>
B	<u>$\frac{1}{2}S$</u> V_A + <u>$\frac{73}{90}S$</u> V_B + <u>$-\frac{1}{5}S$</u> V_C = <u>-5A</u>
C	<u>0</u> V_A + <u>$-\frac{1}{5}S$</u> V_B + <u>$\frac{8}{15}S$</u> V_C = <u>0</u>

$$\frac{1}{5} + \frac{1}{9} + \frac{1}{2}$$

$$\frac{18}{90} + \frac{10}{90} + \frac{45}{90}$$


$$\frac{73}{90}$$

$$\frac{1}{5} + \frac{1}{3}$$

MESH CURRENT ANALYSIS

2. (10 points) The circuit shown below is a DC model of a residential power distribution circuit. Use the mesh current method to write equations for the indicated currents.

(10)

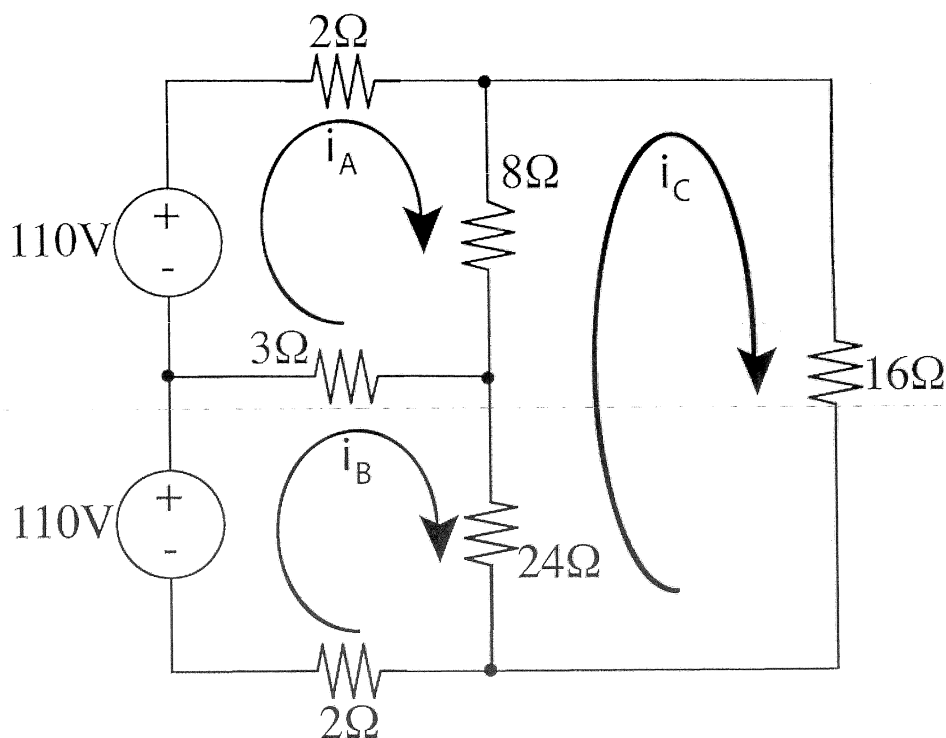

MESH	Mesh Current Equations
A	$13\Omega i_A + -3\Omega i_B + -8\Omega i_C = 110V$
B	$-3\Omega i_A + 29\Omega i_B + -24\Omega i_C = 110V$
C	$-8\Omega i_A + -24\Omega i_B + 48\Omega i_C = 0$


Name : Nick DenissenSection: TECWRU e-mail: nod11

Quiz No. 4

2/11/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE

STATE ALL ASSUMPTIONS

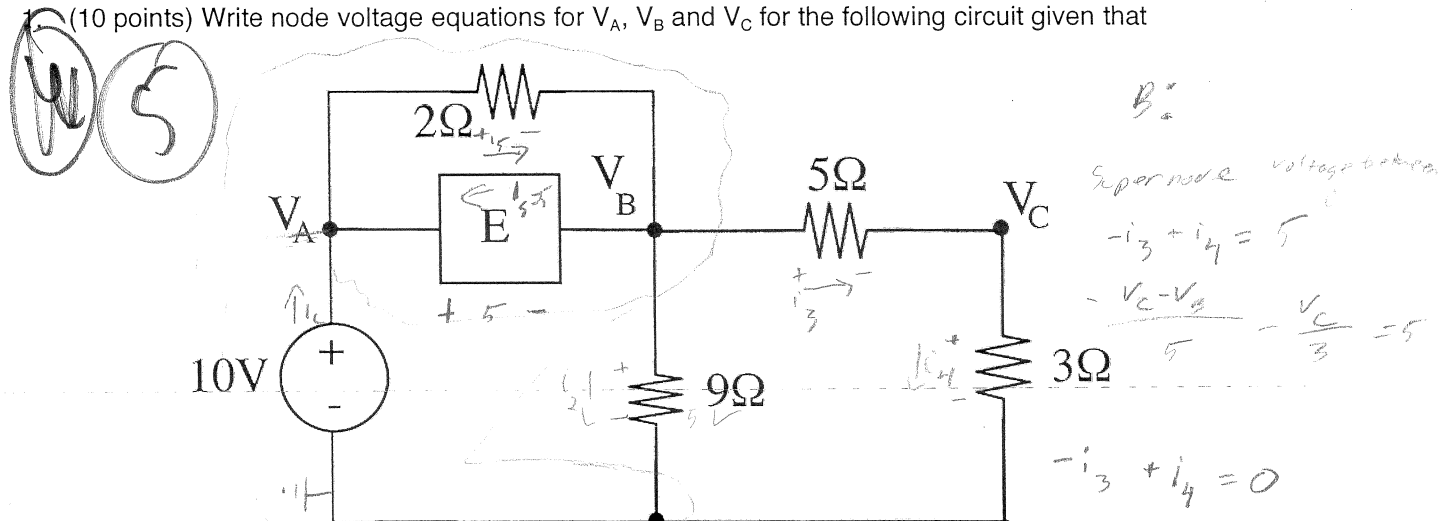NODE VOLTAGE ANALYSIS(10 points) Write node voltage equations for V_A , V_B and V_C for the following circuit given that

(a) E is a 5 volt voltage source with the plus reference on the left.

NODE	Node Voltage Equations			
A	$\frac{1}{2}$	$V_A +$	0	$V_B + 0 V_C = 10$
B	0	$V_A +$	$-\frac{1}{5}$	$V_B + \frac{2}{15} V_C = 5$
C	0	$V_A +$	$-\frac{1}{5}$	$V_B + \frac{8}{15} V_C = 0$

(b) E is a 5 ampere current source with the reference arrow pointing left.

NODE	Node Voltage Equations			
A	$\frac{1}{2}$	$V_A +$	0	$V_B + 0 V_C = 10$
B	$\frac{1}{2}$	$V_A +$	$\frac{2}{15}$	$V_B + \frac{1}{5} V_C = 5$
C	0	$V_A +$	$-\frac{1}{5}$	$V_B + \frac{8}{15} V_C = 0$

$$B: i_5 - i_5 - i_2 - i_3 = 0$$

$$C: i_3 = i_4$$

$$\frac{V_B - V_C}{5} = \frac{V_C}{3}$$


$$\frac{V_A - V_B}{2} - 5 - \frac{V_B - 0}{9} - \frac{V_B - V_C}{5} = 0$$

$$\frac{1}{2}V_A - \frac{1}{2}V_B - \frac{1}{9}V_B - \frac{1}{5}V_B + \frac{1}{5}V_C = 5$$

MESH CURRENT ANALYSIS

2. (10 points) The circuit shown below is a DC model of a residential power distribution circuit. Use the mesh current method to write equations for the indicated currents.

7

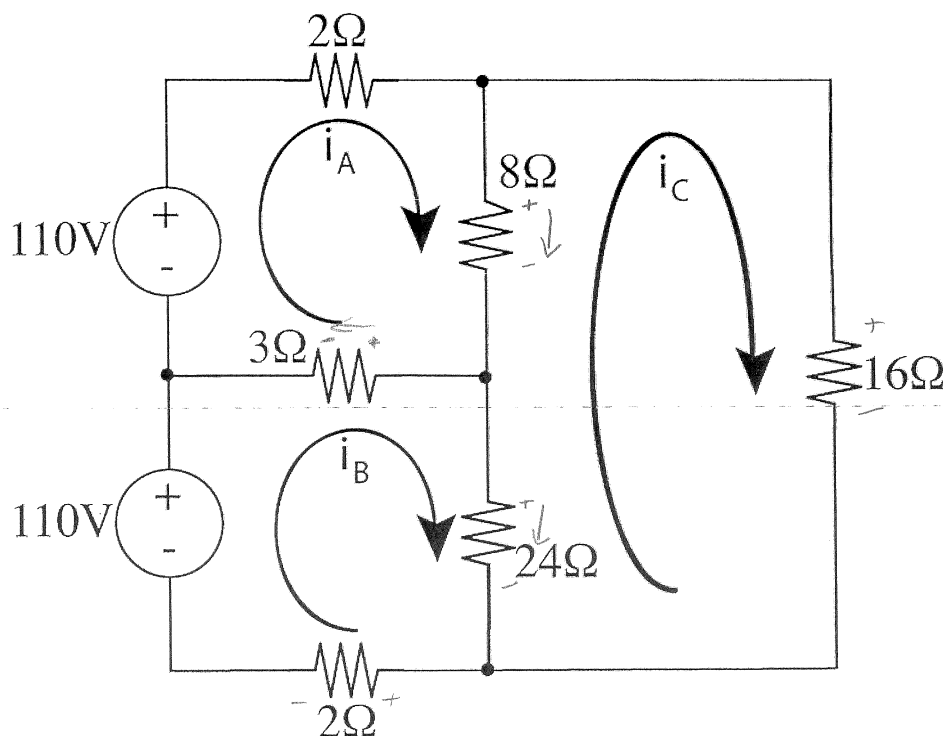

MESH	Mesh Current Equations
A	$110 - 2i_A + 8(i_A - i_C) + 3(i_A - i_B) = 0$
B	$-110 + 2i_B + 24(i_B - i_C) + 3(i_B - i_A) = 0$
C	$-8(i_C - i_A) - 24(i_C - i_B) + 16i_C = 0$

$$A: -110 + 2i_A + 8(i_A - i_C) + 3(i_A - i_B) = 0$$

$$2i_A + 8i_A - 8i_C + 3i_A - 3i_B = 110$$

$$13i_A - 3i_B - 8i_C$$

$$C: -24(i_C - i_B) - 8(i_C - i_A) + 16i_C = 0$$

$$B: -110 - 3(i_B - i_A) + 24(i_B - i_C) + 2i_B = 0$$

$$110 = 23i_B + 3i_A - 24i_C$$

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)



Quiz No. 5

2/20/04

17

 20


PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

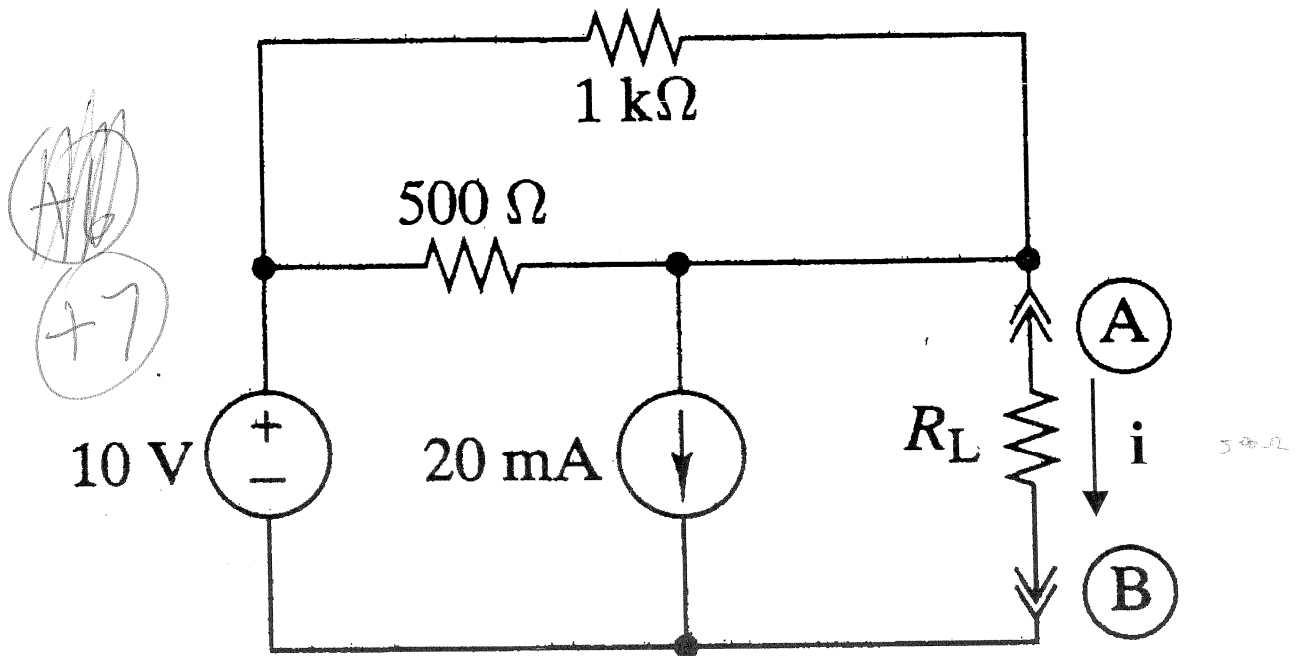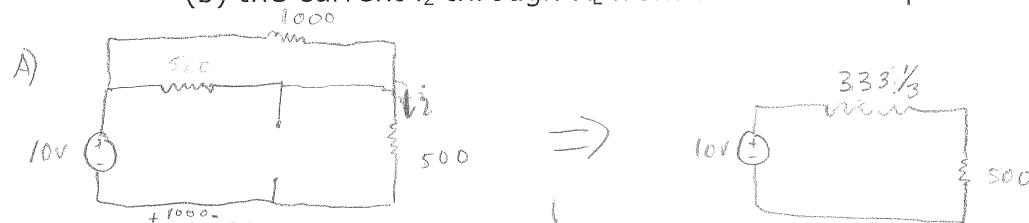LINEARITY - SUPERPOSITION1. (10 points) Assume $R_L = 500\Omega$. Using superposition determine(a) the current i_1 through R_L from the 10 volts source. $i_1 = \underline{.012 A}$ (b) the current i_2 through R_L from the 20 milliamper source. $i_2 = \underline{-.013 A}$ 

$$V_L = \frac{500}{500 + 333\frac{1}{3}} \cdot 10V = 6.0V$$

$$i_1 = \frac{V}{R} = \frac{6.0V}{500\Omega}$$

$$i_1 = .012 A$$

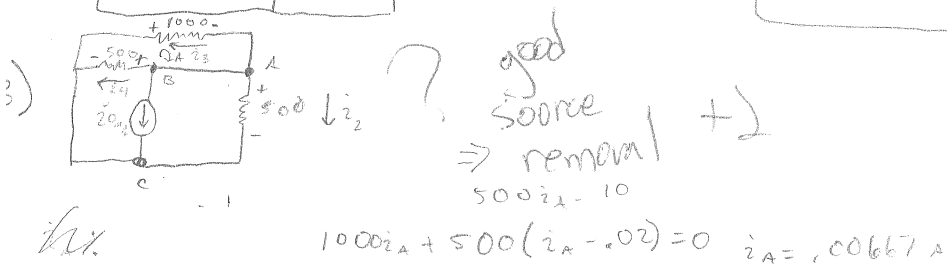

$$1000i_A + 500(i_A - .02) = 0 \quad i_A = .00667 A$$


$$500i_2 + 1000i_A = 0$$

$$i_2 = -2i_A$$





$$i_2 = -.013 A$$

2. (10 points) What is the Thevenin equivalent of the circuit shown below.

$V_T =$ 120 V $R_T =$ 10 Ω

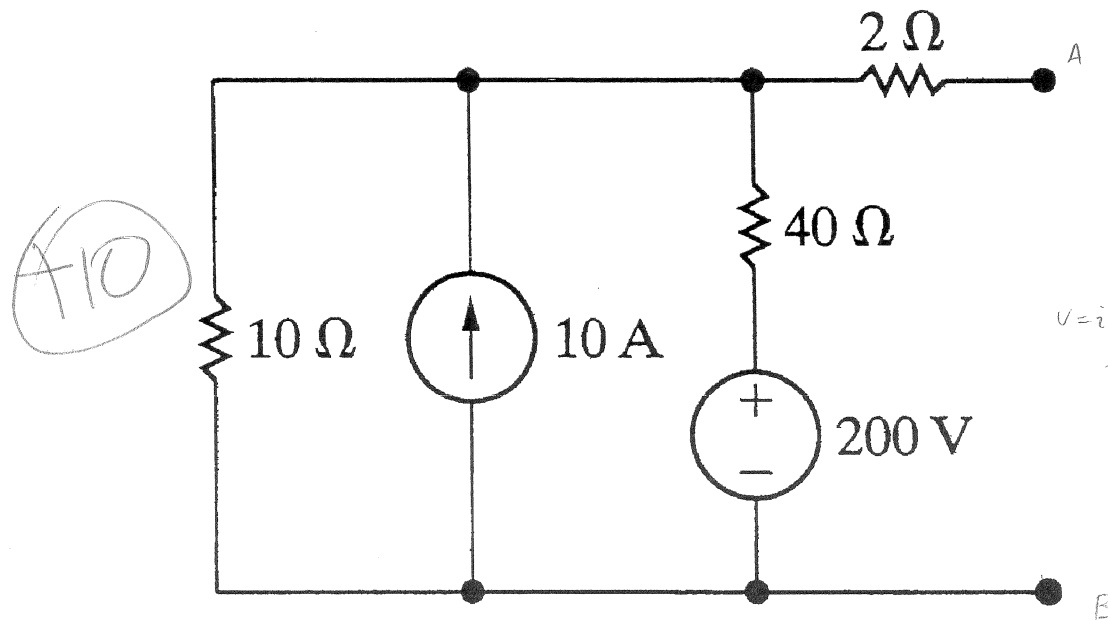

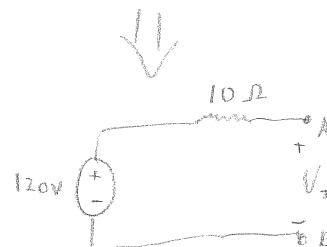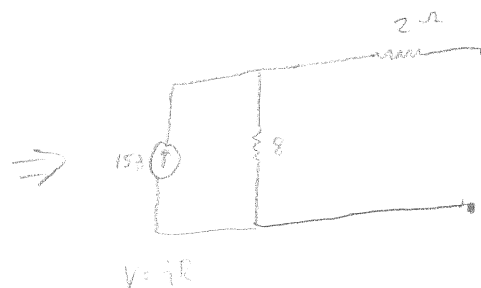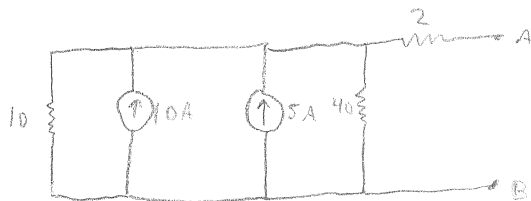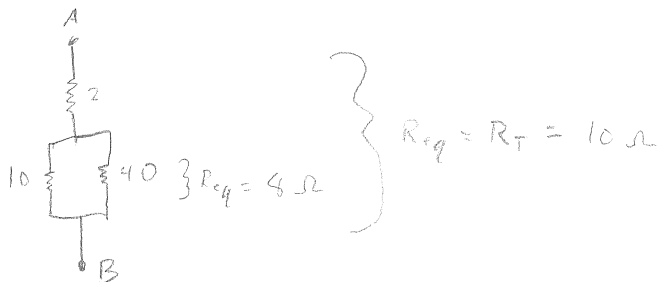$V = iR$
 $i = \frac{V}{R} = \frac{200}{40} = 5 \text{ A}$



CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)


Quiz No. 5

2/20/04

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS





LINEARITY - SUPERPOSITION

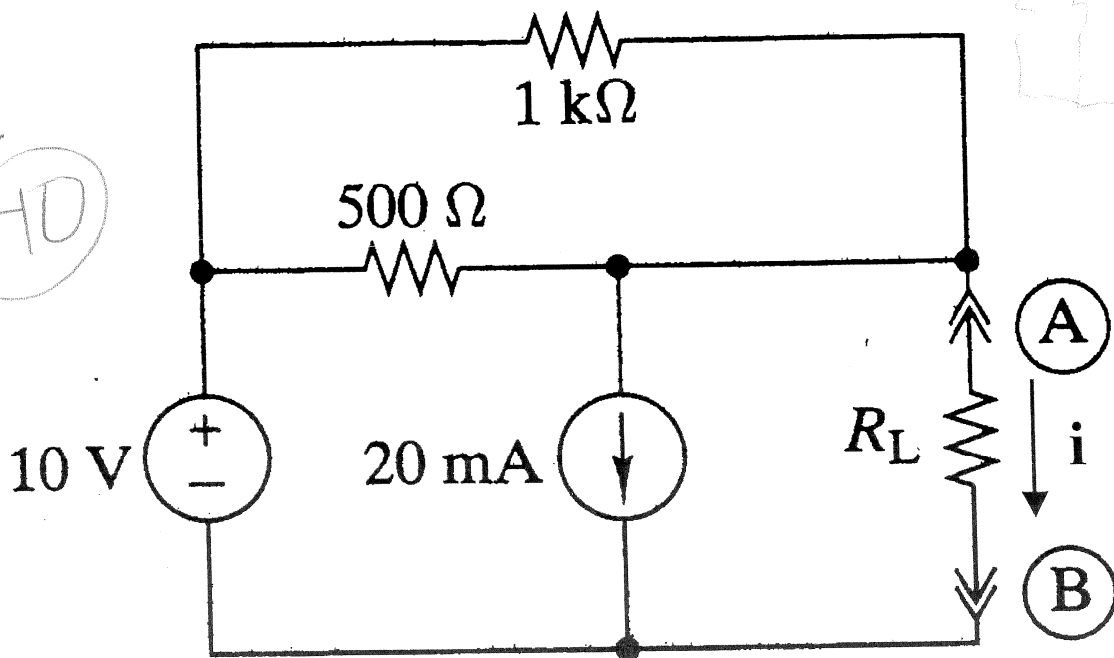1. (10 points) Assume $R_L = 500\Omega$. Using superposition determine



(a) the current i_1 through R_L from the 10 volts source. $i_1 = 12 \text{ mA}$

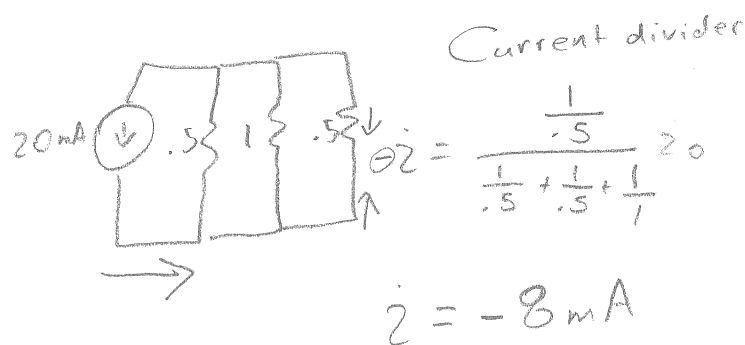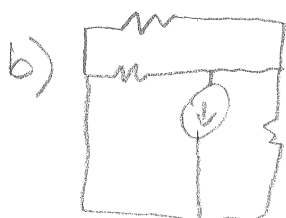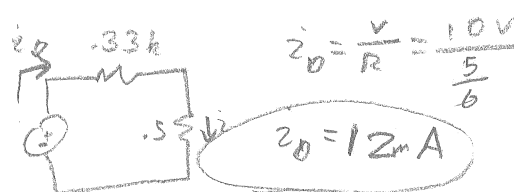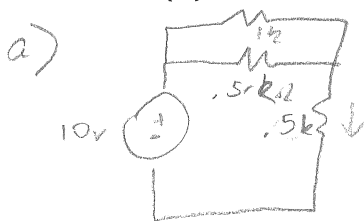(b) the current i_2 through R_L from the 20 milliamper source. $i_2 = -8 \text{ mA}$








Name: Perry Twyford Section: WA

CWRU e-mail: p++3

2. (10 points) What is the Thevenin equivalent of the circuit shown below.

$V_T =$ 120 V $R_T =$ 10 Ω

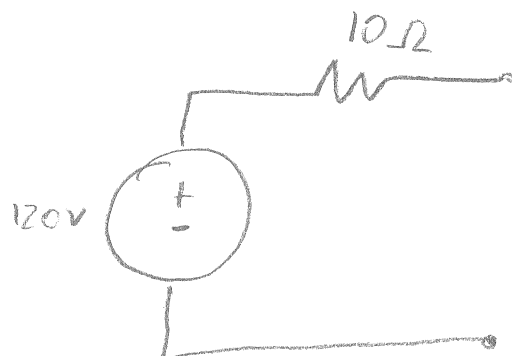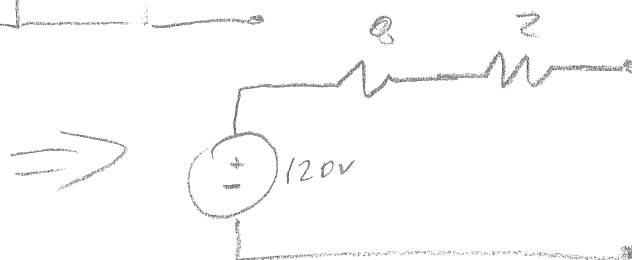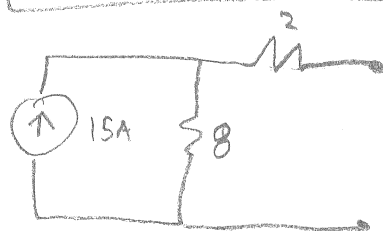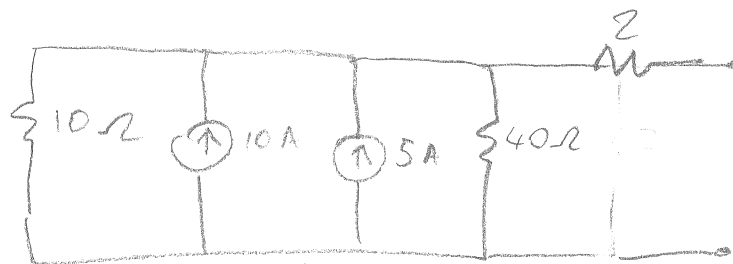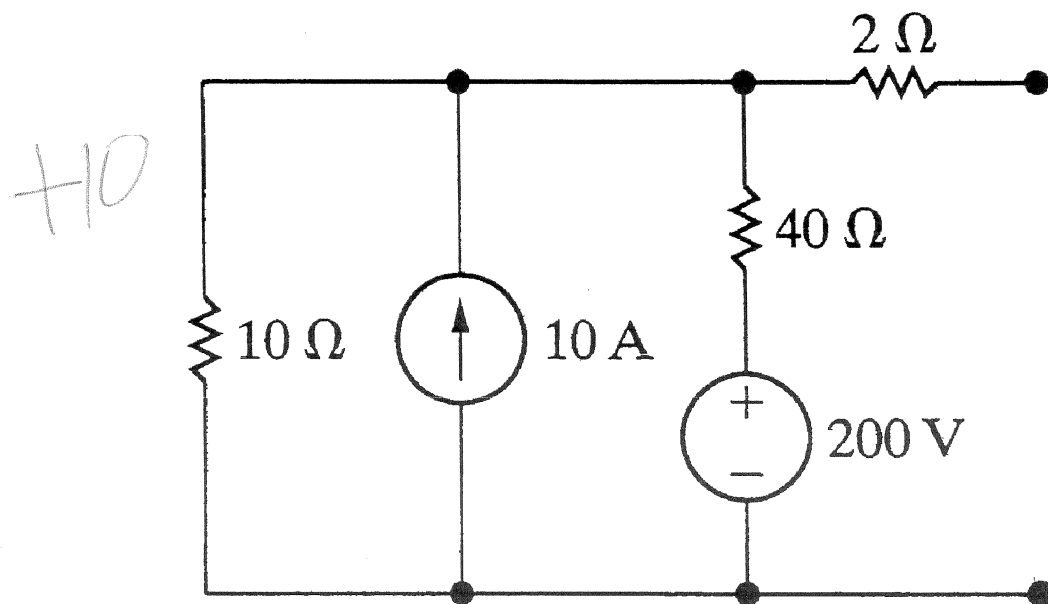

Name: Emily Sershan Section: WA

CWRU e-mail: ecs7

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Quiz No. 5


2/20/04

14 ~~14~~
20

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


LINEARITY - SUPERPOSITION

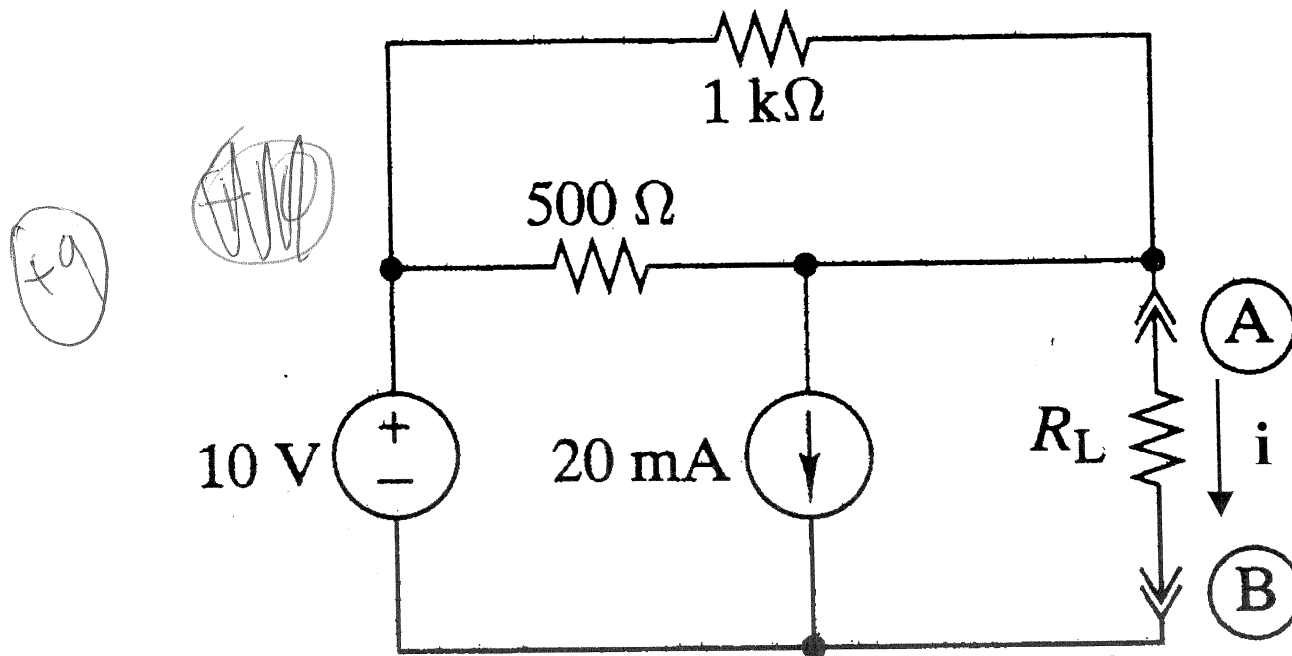1. (10 points) Assume $R_L = 500\Omega$. Using superposition determine



(a) the current i_1 through R_L from the 10 volts source. $i_1 = \underline{6V \Rightarrow 12mA}$



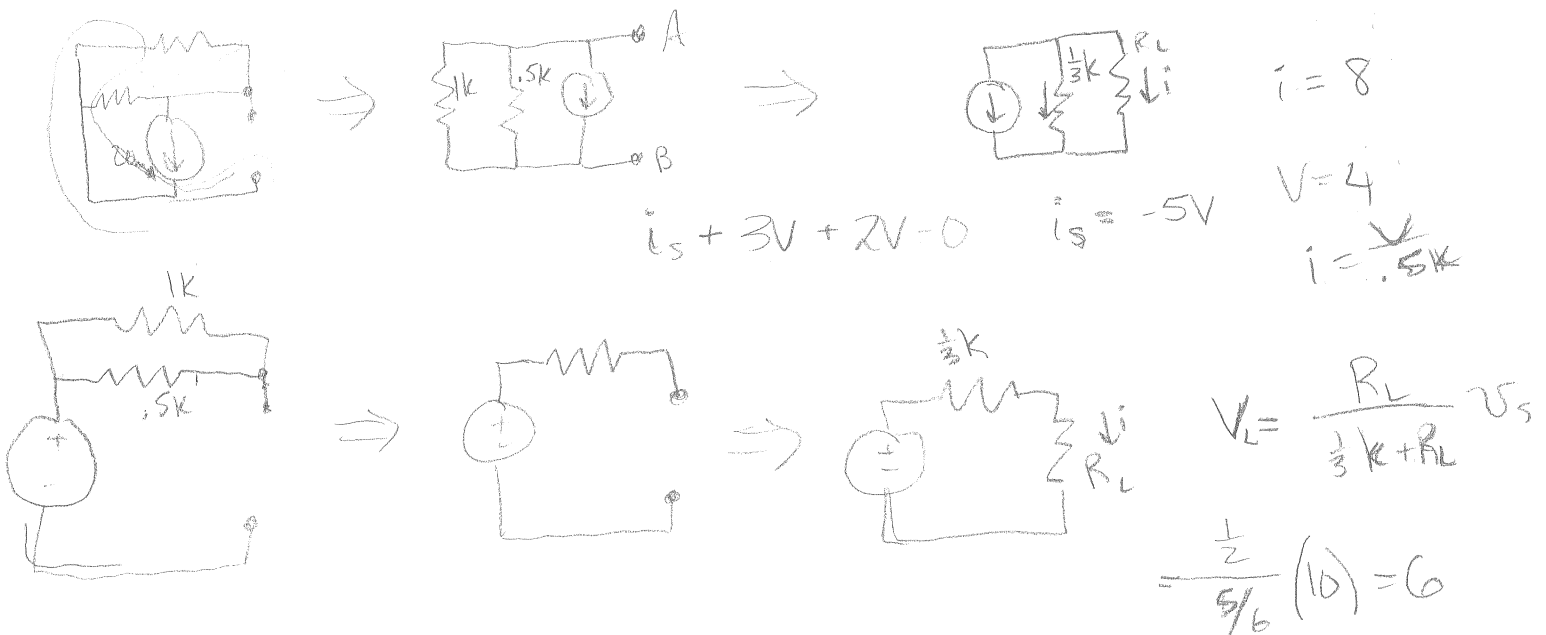
(b) the current i_2 through R_L from the 20 milliamper source. $i_2 = \underline{-8mA}$



2. (10 points) What is the Thevenin equivalent of the circuit shown below.

$V_T =$ 50V $R_T =$ $16/3 \Omega$

(15)

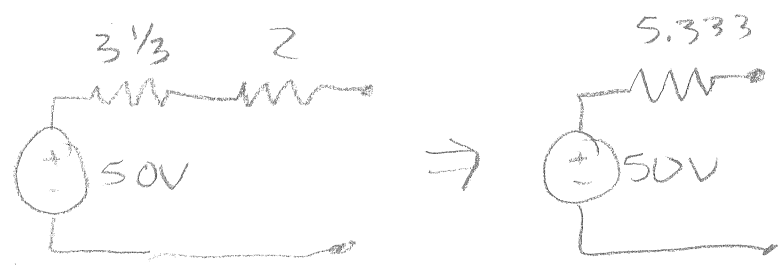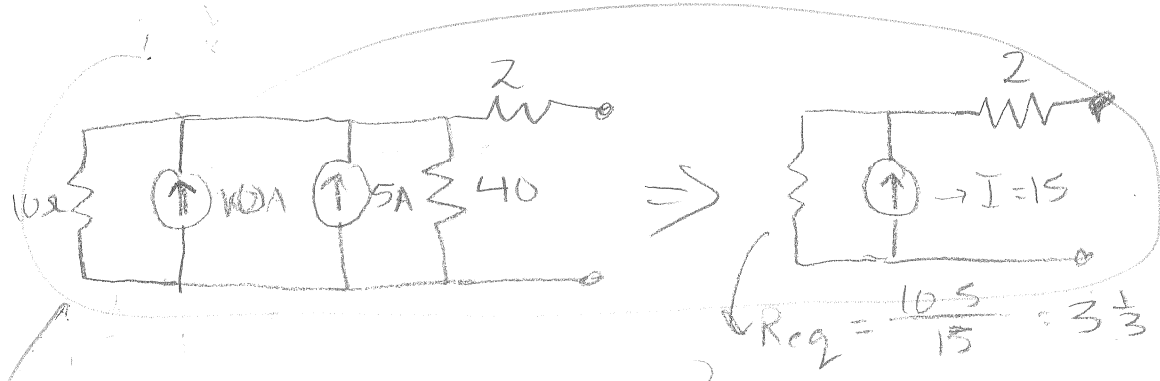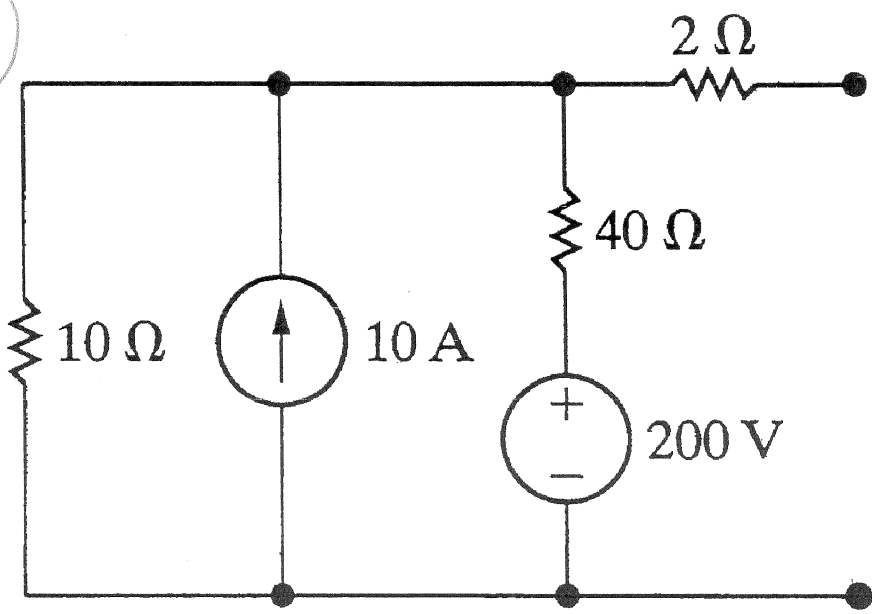

good idea,
check your
 R_{eq} equations & math
remember Norton/Thvenin
conversion rules