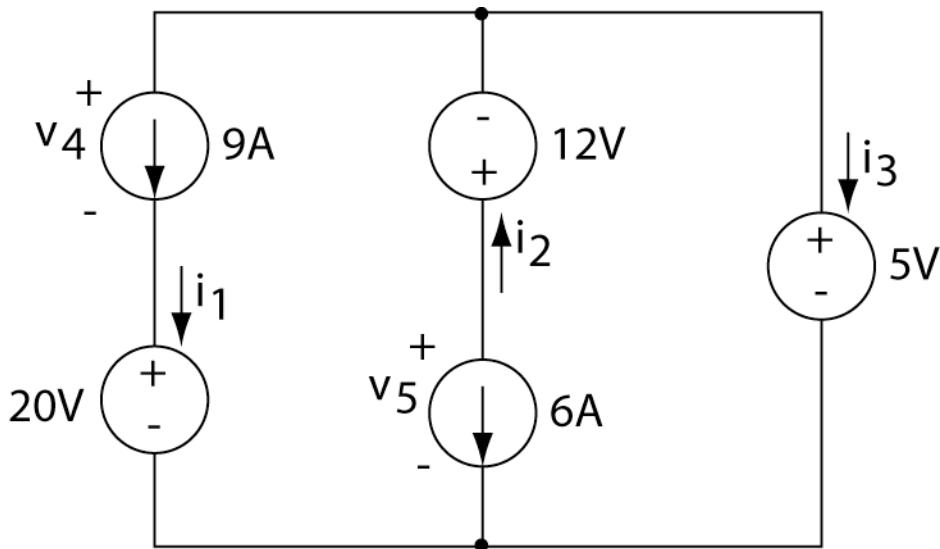


**CASE WESTERN RESERVE UNIVERSITY**  
Case School of Engineering  
Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

Quiz No. 2

1/28/05

**PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE****Problem 1 (10 points) – CONNECTION CONSTRAINTS**Answer the following questions for the circuit below. Be sure to follow the sign conventions indicated.

(a) Determine the indicated currents through the voltage sources.

 $i_1 = \underline{\hspace{2cm}}$  amperes $i_2 = \underline{\hspace{2cm}}$  amperes


(b) What is the current through the 5 volt voltage source.

 $i_3 = \underline{\hspace{2cm}}$  amperes

(c) What is the voltage across each current source?

 $V_4 = \underline{\hspace{2cm}}$  volts $V_5 = \underline{\hspace{2cm}}$  volts

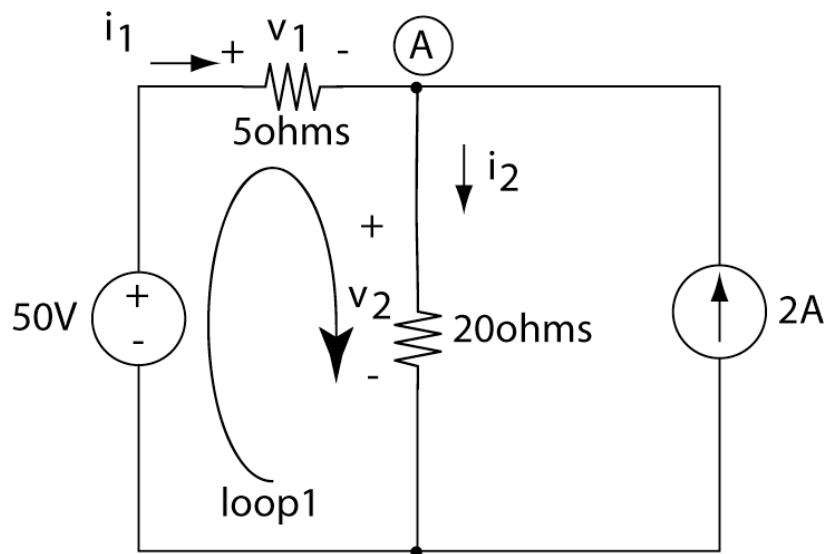**Problem 2** (10 points) COMBINED CONSTRAINTS



(a) How many nodes are in the above circuit? # nodes = \_\_\_\_\_

(b) Write the Kirchoff's Current Law equation for all the currents at node A. Your answer should be in terms of given circuit parameters, i.e.,  $i_1$ ,  $i_2$ , etc.

(c) Write the Kirchoff's Voltage Law equation for loop 1. Your answer should be in terms of given circuit parameters, i.e.,  $i_1$ ,  $i_2$ , etc.

(d) What are the values of  $i_1$  and  $i_2$ ?

$i_1$ =\_\_\_\_\_ amperes

$i_2$ =\_\_\_\_\_ amperes