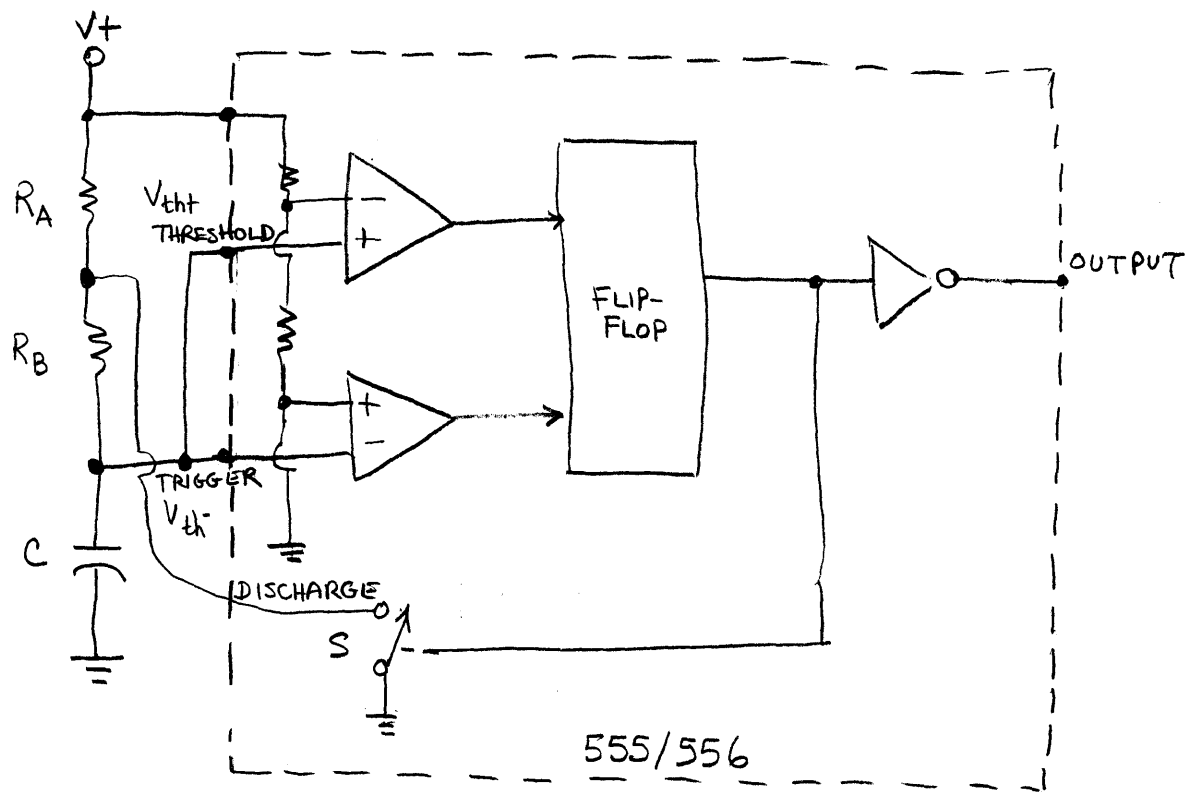



Basic 555/556 Timer Operation




DESIGNED IN 1972 24 transistors
15 resistors

- THRESHOLD - $\frac{2}{3} V_{cc}$ CAUSES OUTPUT TO GO LOW
- TRIGGER - $\frac{1}{3} V_{cc}$ CAUSES OUTPUT TO GO HIGH,
- DISCHARGE - SHORTS out capacitor to discharge it.
WHEN output is low

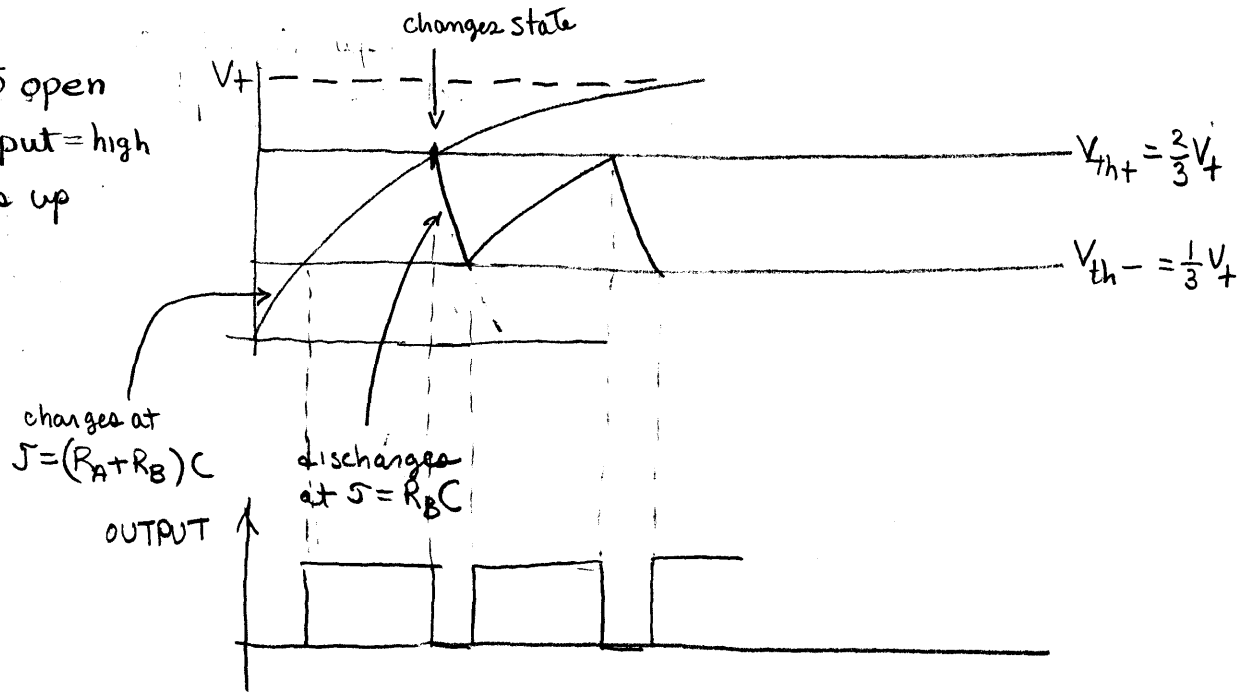① Assume S open
and output = high
⇒ C charges up



Fundamental exponential equation

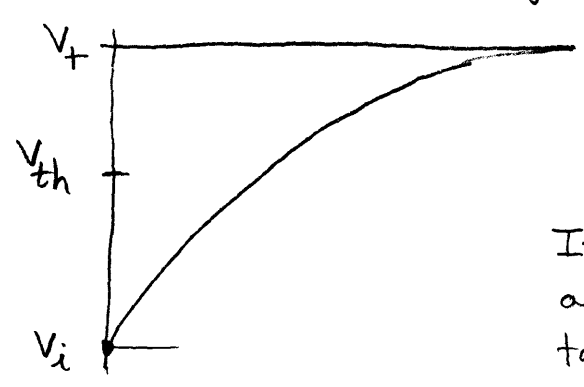

If exponential waveform starts at V_i and charges to V_+ how long T does it take to reach V_{th} ?

basic waveform $v(t) = (V_+ - V_i)(1 - e^{-t/\tau}) + V_i$

to reach V_{th} in T seconds

$$V_{th} = (V_+ - V_i)(1 - e^{-T/\tau}) + V_i$$

Solving for T

$$V_{th} - V_i = (V_+ - V_i)(1 - e^{-T/\tau})$$

$$\frac{V_{th} - V_i}{V_+ - V_i} = 1 - e^{-T/\tau}$$

$$e^{-T/\tau} = 1 - \frac{V_{th} - V_i}{V_+ - V_i} = \frac{V_+ - V_i - V_{th} + V_i}{V_+ - V_i} = \frac{V_+ - V_{th}}{V_+ - V_i}$$

take log.

$$\ln e^{-T/\tau} = \ln \left[\frac{V_+ - V_{th}}{V_+ - V_i} \right]$$

$$-T/\tau = \ln \left[\frac{V_+ - V_{th}}{V_+ - V_i} \right]$$

$$T = -\tau \ln \left[\frac{V_+ - V_{th}}{V_+ - V_i} \right] = \tau \ln \left[\frac{V_+ - V_i}{V_+ - V_{th}} \right]$$

For circuits $\tau = RC$

9

$$T = T_{\text{charge}} + T_{\text{discharge}}$$

$$= (R_A + R_B)C \ln \left[\frac{V_+ - \frac{1}{3}V_+}{V_+ - \frac{2}{3}V_+} \right] + R_B C \ln \left[\frac{0 - \frac{2}{3}V_+}{0 - \frac{1}{3}V_+} \right]$$

$$\text{for } V_{th} = \frac{2}{3}V_+$$

$$V_i = \frac{1}{3}V_+$$

final voltage V_+

$$\text{for } V_{th} = \frac{1}{3}V_+$$

$$V_i = \frac{2}{3}V_+$$

final voltage $V_+ = 0$

$$= (R_A + R_B)C \ln \left[\frac{\frac{2}{3}}{\frac{1}{3}} \right] + R_B C \ln \left[\frac{-\frac{2}{3}}{-\frac{1}{3}} \right]$$

$$= (R_A + R_B)C \ln 2 + R_B C \ln [2]$$

$$= (R_A + 2R_B)C \ln 2$$

$$= 0.693 (R_A + 2R_B)C$$