

We can substitute the element equations into the node equations and solve the problem.

$$@ B \quad i_1 - i_2 - i_4 = 0$$

$$\frac{v_A - v_B}{2R} - \frac{v_B - v_C}{2R} - \frac{v_B - 0}{R_{12}} = 0$$

$$\frac{1}{2R} v_A - \left( \frac{1}{2R} + \frac{1}{2R} + \frac{1}{R_{12}} \right) v_B + \left( \frac{1}{2R} \right) v_C = 0$$

$$@ C \quad i_3 + i_2 - i_5 = 0$$

$$\frac{v_A - v_C}{R_{12}} + \frac{v_B - v_C}{2R} - \left( \frac{v_C - 0}{R} \right) = 0$$

$$\left( \frac{1}{R_{12}} \right) v_A + \left( \frac{1}{2R} \right) v_B + \left( -\frac{1}{R} - \frac{1}{2R} - \frac{1}{R} \right) v_C = 0$$

Substituting  $v_A = v_s$  and putting into standard form,

$$@ C \quad \left( \frac{1}{2R} \right) v_B + \left( \frac{1}{R_{12}} - \frac{1}{2R} - \frac{1}{R} \right) v_C = -\frac{1}{R_{12}} v_s$$

$$@ B \quad \left( -\frac{1}{2R} - \frac{1}{2R} - \frac{1}{R_{12}} \right) v_B + \left( \frac{1}{2R} \right) v_C = -\frac{1}{2R} v_s$$

---


$$@ C \quad \frac{1}{2R} v_B - \frac{7}{2R} v_C = -\frac{2}{R} v_s$$

$$@ B \quad -\frac{3}{R} v_B + \frac{1}{2R} v_C = -\frac{1}{2R} v_s$$


---

$$\frac{1}{2} v_B - \frac{7}{2} v_C = -2 v_s$$

$$-3 v_B + \frac{1}{2} v_C = -\frac{1}{2} v_s$$

divided out all the R's

This can be solved by Cramer's Rule

$$v_B = \frac{\Delta_B}{\Delta} = \frac{\begin{bmatrix} -2v_s & -\frac{7}{2} \\ -\frac{1}{2}v_s & +\frac{1}{2} \end{bmatrix}}{\begin{bmatrix} \frac{1}{2} & -\frac{7}{2} \\ -3 & +\frac{1}{2} \end{bmatrix}} = \frac{(-v_s) - (\frac{7}{4}v_s)}{(\frac{1}{4}) - (\frac{21}{2})} = \frac{-4v_s - 7v_s}{1 - 42}$$

$$v_B = \frac{-11v_s}{-41} = 0.2683 v_s$$

$$v_c = \frac{\Delta_c}{\Delta} = \frac{\begin{bmatrix} \frac{1}{2} & -2v_s \\ -3 & -\frac{1}{2}v_s \end{bmatrix}}{\begin{bmatrix} \frac{1}{2} & -\frac{7}{2} \\ -3 & +\frac{1}{2} \end{bmatrix}} = \frac{(\frac{1}{4}v_s) - (6v_s)}{(\frac{1}{4}) - (\frac{21}{2})} = \frac{-v_s - 24v_s}{1 - 42}$$

$$v_c = \frac{-25v_s}{-41} = 0.60976 v_s$$

The input current is then given by

$$\begin{aligned} i_{in} &= i_1 + i_3 \\ &= \frac{v_A - v_B}{2R} + \frac{v_A - v_c}{R_2} = \frac{1}{R} \left[ \frac{v_s}{2} - \frac{0.2683v_s}{2} + \frac{v_s}{2} - \frac{0.60976v_s}{2} \right] \\ &= \frac{1}{R} \left[ 0.5v_s - 0.13415v_s + 2v_s - 1.2195v_s \right] \end{aligned}$$

$$i_{in} = \frac{1.1463}{R} v_s$$


$$R_{in} = \frac{v_s}{i_{in}} = \frac{v_s}{\frac{1.1463}{R} v_s} = 0.8723 R$$

## Example 3-6

For the circuit given below


(a) Formulate the node-voltage equations

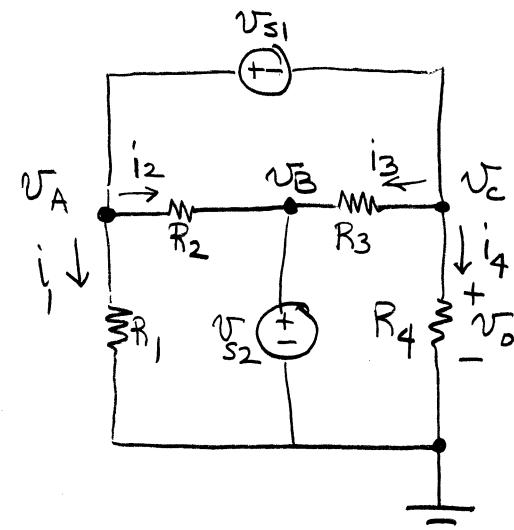(b) Solve for  $v_o$  using  $R_1 = R_4 = 2\text{k}\Omega$   
and  $R_2 = R_3 = 4\text{k}\Omega$ ,



This circuit cannot be solved since we cannot write a current for  $v_A$  or  $v_C$  through  $v_{S1}$ . We cannot use a source transformation on  $v_{S1}$  since it does not have a series resistance. We also cannot ground either node A or C since that would change the circuit. Therefore, we must use a "supermode".

Construct a supermode around  $v_{S1}$ .

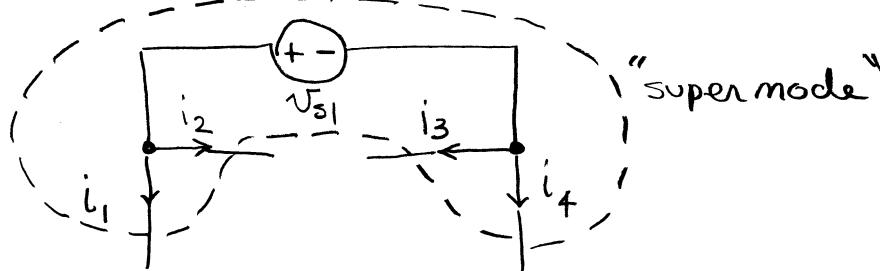

$$\text{For a supermode } \sum_{\text{out}} i = 0 \quad i_1 + i_2 + i_3 + i_4 = 0$$

$$i_1 = \frac{v_A - 0}{R_1}$$

$$i_2 = \frac{v_A - v_B}{R_2} \quad v_B = v_{S2}$$

$$i_3 = \frac{v_C - v_B}{R_3}$$

$$i_4 = \frac{v_C - 0}{R_4} \quad v_C = v_o$$

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\left(\frac{v_A}{R_1}\right) + \left(\frac{v_A - v_{S2}}{R_2}\right) + \left(\frac{v_C - v_{S2}}{R_3}\right) + \left(\frac{v_C}{R_4}\right) = 0$$

We have one other equation

$$v_A - v_C = v_{S1}$$

Rearranging  $\left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_A + \left(\frac{1}{R_3} + \frac{1}{R_4}\right)v_C = \left(\frac{1}{R_2} + \frac{1}{R_3}\right)v_{S2}$

$$v_A - v_C = v_{S1}$$

Putting in numerical values

$$\frac{1}{R_1} = .00050$$

$$\frac{1}{R_2} = .00025$$

$$\frac{1}{R_3} = .00025$$

$$\frac{1}{R_4} = .00050$$

$$(75 \times 10^{-5})v_A + (75 \times 10^{-5})v_C = (50 \times 10^{-5})v_{S2}$$

$$v_A - v_C = v_{S1}$$

$$3v_A + 3v_C = 2v_{S2}$$

multiplying by 3 →  $\underline{3v_A - 3v_C = 3v_{S1}}$   
and subtracting  $6v_C = 2v_{S2} - 3v_{S1}$

$$v_C = \frac{1}{3}v_{S2} - \frac{1}{2}v_{S1}$$

$$v_o = v_C = \frac{1}{3}v_{S2} - \frac{1}{2}v_{S1}$$