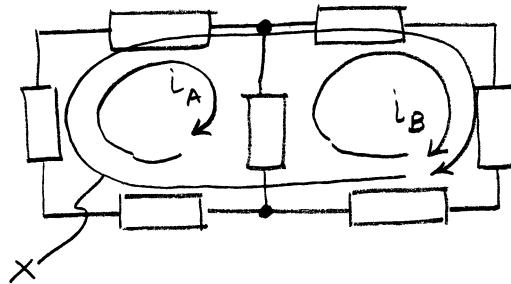


3-2 mesh Current

A loop is a closed path formed by passing through an ordered sequence of nodes without passing through any node more than once.

A mesh is a special type of loop that does not enclose any elements.




in this drawing i_A, i_B form meshes; but X is only a loop because it encloses an element

If the k -th two-terminal element is contained in meshes X and Y , then the element current can be expressed in terms of the two mesh currents as

$$i_k = i_x - i_y$$

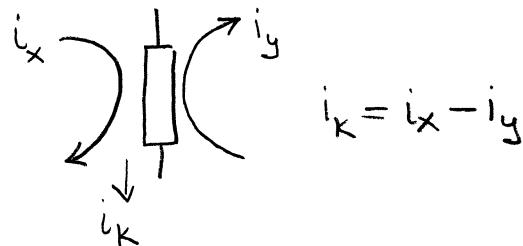where X is the mesh whose reference direction agrees with the reference direction of i_k




Mesh current analysis:

1. Identify a mesh current with every mesh and a voltage across every circuit element.
2. Write KVL connection equations in terms of the element voltages around every mesh.
3. Use KCL and the element i-v relationships (usually Ohm's Law) to express the element voltages in terms of the mesh currents.
4. Substitute the element constraints into the connection equations from 2 and arrange into standard form.

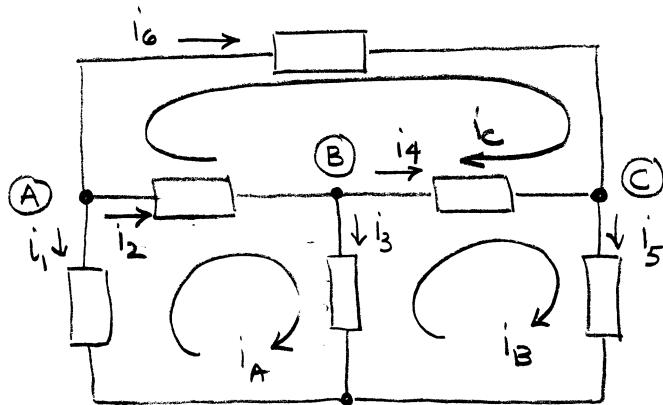Example 3-7


The mesh currents are $i_A = 10\text{ A}$, $i_B = 5\text{ A}$, and $i_c = -3\text{ A}$. Find the element currents i_1 through i_6 .



$$\text{By inspection} \quad \left. \begin{array}{l} i_6 = i_c = -3\text{ A} \\ i_5 = i_B = 5\text{ A} \\ i_1 = -i_A = -10\text{ A} \end{array} \right\} \text{outside elements have only one current}$$

$$\left. \begin{array}{l} i_2 = i_A - i_c = 10 - (-3) = 13\text{ A} \\ i_3 = i_A - i_B = 10 - (5) = 5\text{ A} \\ i_4 = i_B - i_c = 5 - (-3) = 8\text{ A} \end{array} \right\} \text{inside elements have two currents}$$

Figure 3-18

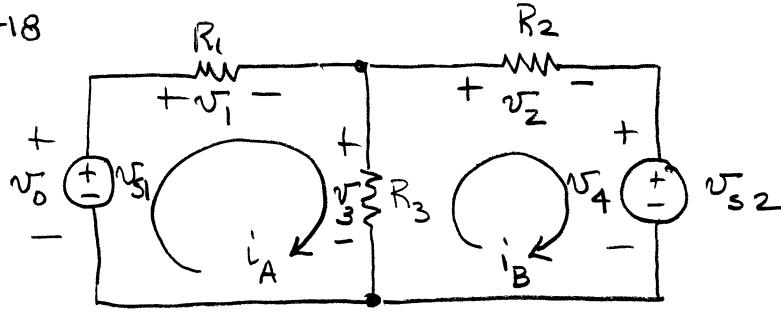

$$\text{mesh A: } \sum_{\text{C1}} V = -v_s 1 + v_1 + v_3 = 0$$

$$\text{mesh B: } \sum_{\text{C2}} V = -v_3 + v_2 + v_4 = 0$$

element equations:

$$v_1 = i_A R_1 \quad v_s 1 = v_{s1}$$

$$v_2 = i_B R_2 \quad v_s 2 = v_{s2}$$

$$v_3 = (i_A - i_B) R_3$$

$$\begin{aligned} \text{Substitute} \quad -v_{s1} + i_A R_1 + (i_A - i_B) R_3 &= 0 \\ -(i_A - i_B) R_3 + i_B R_2 + v_{s2} &= 0 \end{aligned}$$

Put into standard form

$$(R_1 + R_3) i_A + (-R_3) i_B = v_{s1}$$


$$(-R_3) i_A + (R_2 + R_3) i_B = -v_{s2}$$

Solve using Cramer's Rule


$$i_A = \frac{\Delta_A}{\Delta} = \frac{\begin{vmatrix} v_{s1} & -R_3 \\ -v_{s2} & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} = \frac{(R_2 + R_3) v_{s1} - R_3 v_{s2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_B = \frac{\Delta_B}{\Delta} = \frac{\begin{vmatrix} R_1 + R_3 & v_{s1} \\ -R_3 & -v_{s2} \end{vmatrix}}{\begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix}} = \frac{R_3 v_{s1} - (R_1 + R_3) v_{s2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

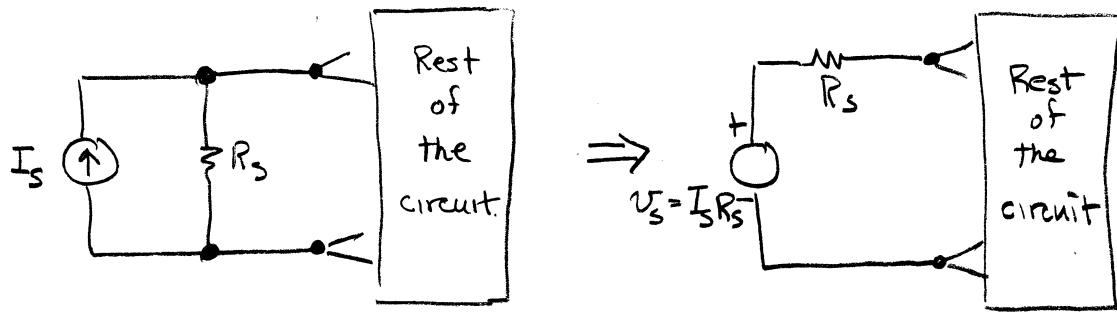
Three methods of dealing with current sources in mesh analysis.



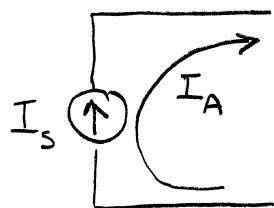- I. Whenever there is a parallel R with the current source transform to an equivalent current source.



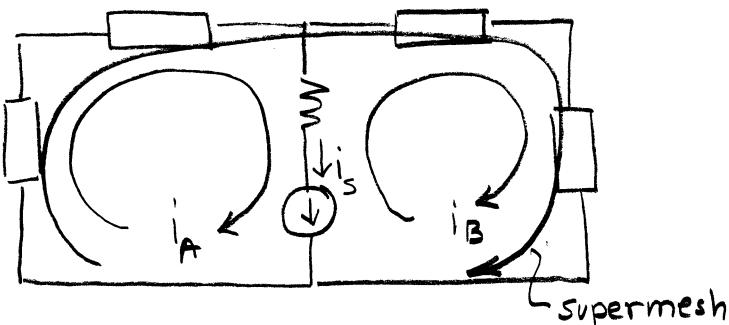- II. If a current source I_s is contained in only one mesh then that mesh current is determined by I_s .



- III. If a current source is contained in two meshes or is not connected in parallel with a resistance we can create a super mesh which excludes the current source and any series elements.


Write KVL for supermesh using i_A and i_B .

Write one additional equation


$$i_s = i_A - i_B$$

Solve.

Example: Find i_o by mesh analysis.

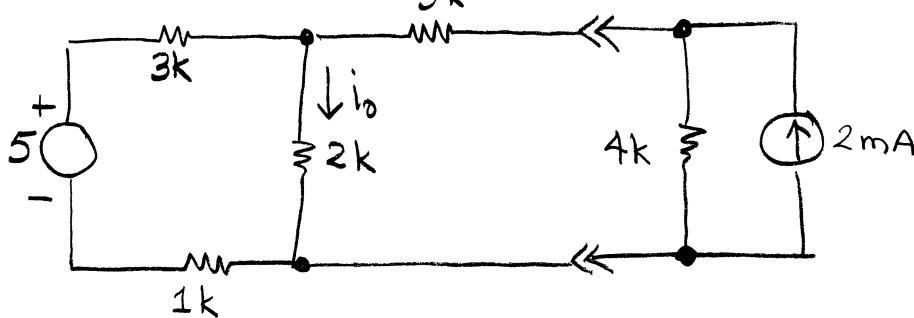

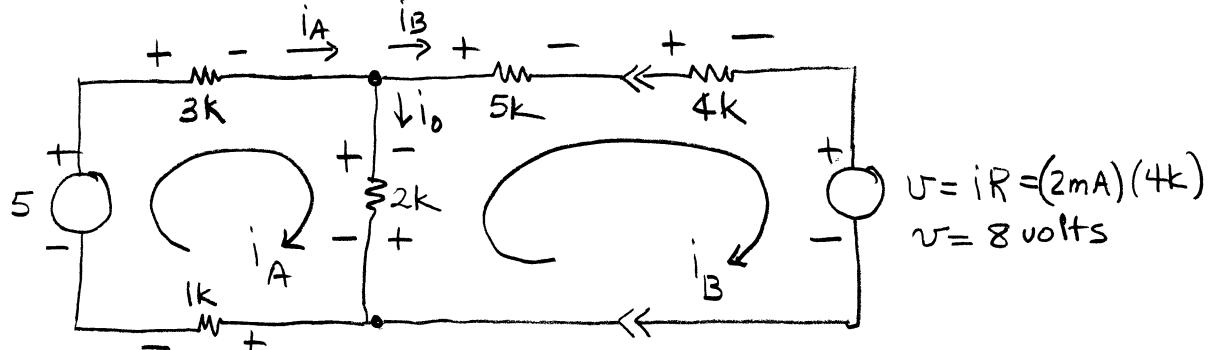Use a source transformation to get rid of the current source.



$$\text{KVL for mesh A: } -5 + 3000i_A + 2000i_A - 2000i_B + 1000i_A = 0$$

$$\text{KVL for mesh B: } +2000i_B - 2000i_A + 5000i_B + 4000i_B + 8 = 0$$

standard form

$$6000i_A - 2000i_B = 5$$

$$-2000i_A + 11000i_B = -8$$

$$\text{Solving gives } i_A = 0.6290 \text{ mA}$$

$$i_B = -0.6129 \text{ mA}$$

Now do KCL @ node to determine i_o


$$\sum_{\text{in}} i + i_A - i_o - i_B = 0$$

$$(0.6290) - i_o - (-0.6129) = 0$$

$$i_o = 0.6290 + 0.6129 = 1.2419 \text{ mA}$$

Example 3-9

use mesh-current equations to find v_o .

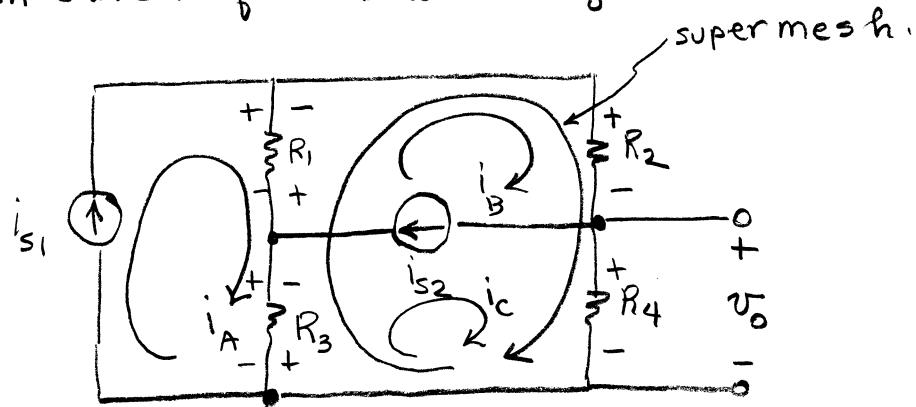

Since we have a current source i_{s1} which is isolated
the mesh current $i_A = i_{s1}$.

However, we have a current source i_{s2} which is contained
in two meshes. Write a super mesh around it.

For the supermesh write KVL

$$(+i_c - i_A)R_3 + (i_B - i_A)R_1 + i_B R_2 + i_c R_4 = 0$$

and use the constraint that $i_{s2} = i_B - i_c$

Then substitute and solve

$$i_c(R_3 + R_4) - i_A(R_1 + R_3) + i_B(R_1 + R_2) = 0$$

$$\text{rearranging } (R_1 + R_2)i_B + (R_3 + R_4)i_c = (R_1 + R_3)i_{s1}$$

$$i_c = i_B - i_{s2}$$

$$\text{Solving gives } (R_1 + R_2)i_B + (R_3 + R_4)i_B - (R_3 + R_4)i_{s2} = (R_1 + R_3)i_{s1}$$

$$i_c = \frac{(R_1 + R_3)i_{s1} + (R_3 + R_4)i_{s2}}{R_1 + R_2 + R_3 + R_4}$$

$$v_o = i_c R_4 = R_4 \frac{(R_1 + R_3)i_{s1} + (R_3 + R_4)i_{s2}}{R_1 + R_2 + R_3 + R_4}$$