

3-3 Linearity Properties

The title of our book includes "linear" circuits
What is a linear circuit?

One that contains only linear elements and independent sources.

For a linear circuit output is a linear function of the input.

homogeneity, output \propto input (also called proportionality)

$$f(kx) = k f(x)$$

\uparrow
increasing input output increases k times
 K times


Only applies when input is voltage or current.

* additivity *

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$

This is called superposition.

Example

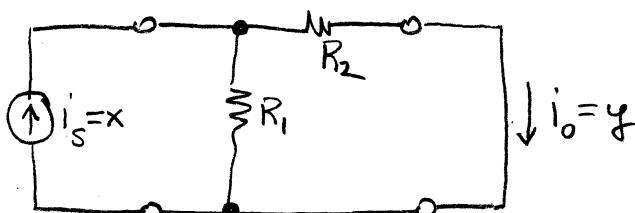

If the input current is $i_s = x$

If the output current i_o is y

This is a current divider so

$$i_o = \frac{R_1}{R_1 + R_2} i_s$$

can be written as $y = \frac{R_1}{R_1 + R_2} x$


This is k

the constant of proportionality

Also called gain

Example 3-10

Given the bridge circuit below

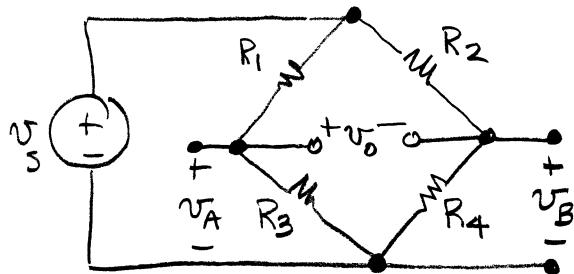

(a) Find the proportionality constant K in the input-output relationship $v_o = Kv_s$.

(b) Find the sign of K when $R_2R_3 > R_1R_4$, $R_2R_3 = R_1R_4$, and $R_2R_3 < R_1R_4$.

- (a) This circuit is two side by side voltage dividers.
Using the voltage division rule

$$v_A = \frac{R_3}{R_1+R_3} v_s$$

$$v_B = \frac{R_4}{R_2+R_4} v_s$$

$$v_o = v_A - v_B = \left(\frac{R_3}{R_1+R_3} - \frac{R_4}{R_2+R_4} \right) v_s = \frac{\cancel{R_2R_3 + R_3R_4} - R_1R_4 - \cancel{R_3R_4}}{(R_1+R_3)(R_2+R_4)} v_s$$

$$v_o = \underbrace{\frac{R_2R_3 - R_1R_4}{(R_1+R_3)(R_2+R_4)}}_{\text{proportionality constant } K} v_s$$

proportionality constant K

(b) $K > 0$ if $R_2R_3 > R_1R_4$

$K = 0$ if $R_2R_3 = R_1R_4$ ← this is called a balanced bridge

$K < 0$ if $R_2R_3 < R_1R_4$

Unit output method

Use proportionality property to find K.

Let output = 1 (amp or volt) and determine corresponding input.


$$K = \frac{\text{Output}}{\text{Input}} = \frac{1}{K}$$

Additivity

Output of a circuit with multiple inputs can be written as a linear combination of the inputs.

$$y = k_1 x_1 + k_2 x_2 + \dots + k_n x_n$$

Figure 3-31

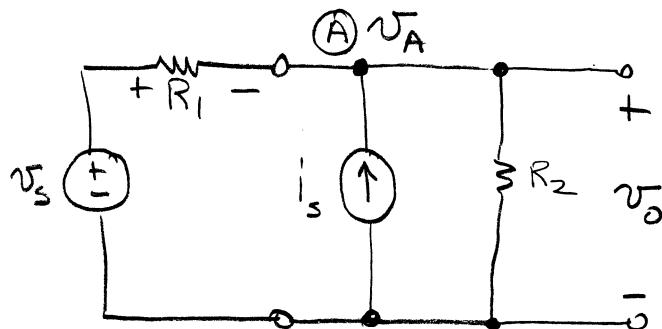


use KCL @ A $\sum i = 0$ $\frac{v_s - v_A}{R_1} + i_s - \frac{v_A}{R_2} = 0$


Rearranging $\left[\frac{1}{R_1} + \frac{1}{R_2} \right] v_A = \frac{v_s}{R_1} + i_s$

$$v_o = v_A = \left[\frac{R_2}{R_1 + R_2} \right] v_s + \left[\frac{R_1 R_2}{R_1 + R_2} \right] i_s$$

$$\therefore y = k_1 x_1 + k_2 x_2$$

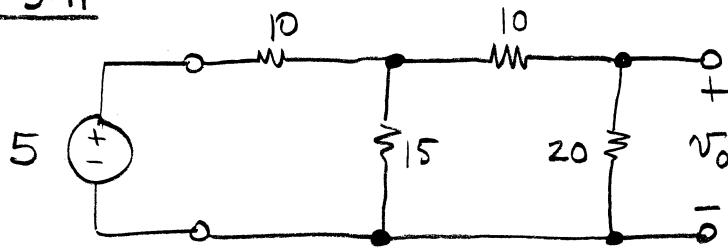Example 3-11

Use the unit output method to find v_o .

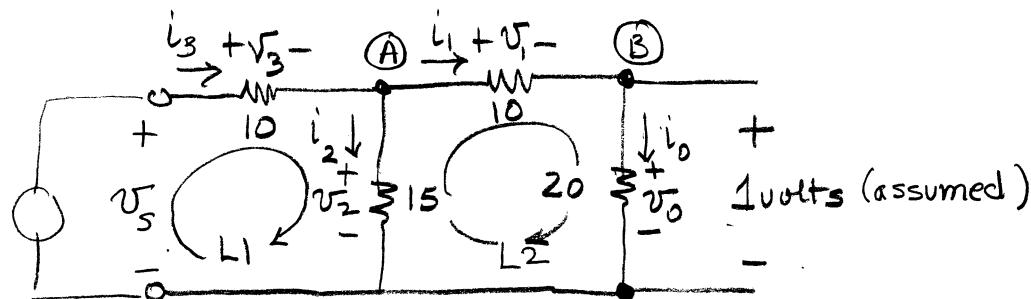

By inspection v_o is the voltage across the 20Ω resistor so

$$i_o = \frac{v}{R} = \frac{1}{20} = .05 \text{ A}$$

$$\text{KCL @ B} \quad \sum_{\text{in}} i = 0 \quad i_1 - i_o = 0 \Rightarrow i_1 = i_o = .05 \text{ A}$$

Use Ohm's Law to find v_i

$$v_i = i_1 R_1 = (.05)(10) = 0.5 \text{ volts.}$$

$$\text{KVL around } L_2 \quad \sum_{\text{in}} v = 0 \quad -v_2 + v_i + v_o = 0 \\ -v_2 + 0.5 + 1 = 0$$

$$v_2 = 1.5 \text{ V.}$$

$$\text{Ohm's Law} \quad i_2 = \frac{v_2}{R_2} = \frac{1.5}{15} = 0.1 \text{ A}$$

$$\text{KCL @ A} \quad \sum_{\text{in}} i = 0 \quad +i_3 - i_2 - i_o = 0 \\ i_3 - 0.1 - 0.05 = 0 \\ i_3 = 0.15 \text{ A.}$$

$$\text{Ohm's Law} \quad v_3 = i_3 R_3 = (0.15)(10) = 1.5 \text{ V.}$$

$$\text{KVL around } L_1 \quad -v_s + v_3 + v_2 = 0 \\ v_s = v_3 + v_2 = 1.5 + 1.5 = 3 \text{ V.}$$

$$\therefore K = \frac{v_o}{v_s} = \frac{1}{3} \text{ and output for } v_s = 5 \text{ is } v_o = Kv_s = \frac{1}{3}5 = \frac{5}{3}$$