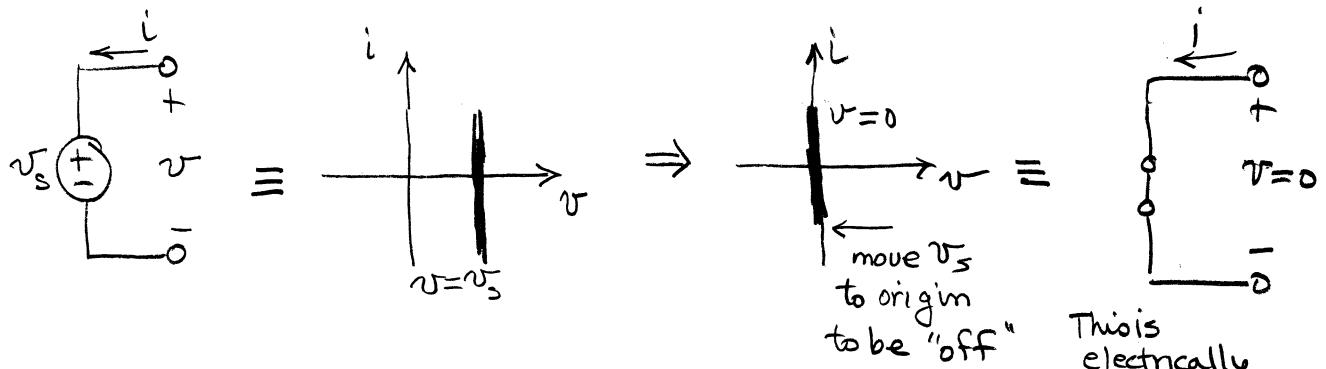



Superposition

Output can be found by finding the contribution to the output from each source.


- ① "Turn Off" all independent sources except one and find output from that one alone.
- ② Repeat ① for each independent source.
- ③ Algebraically sum all outputs from each source.



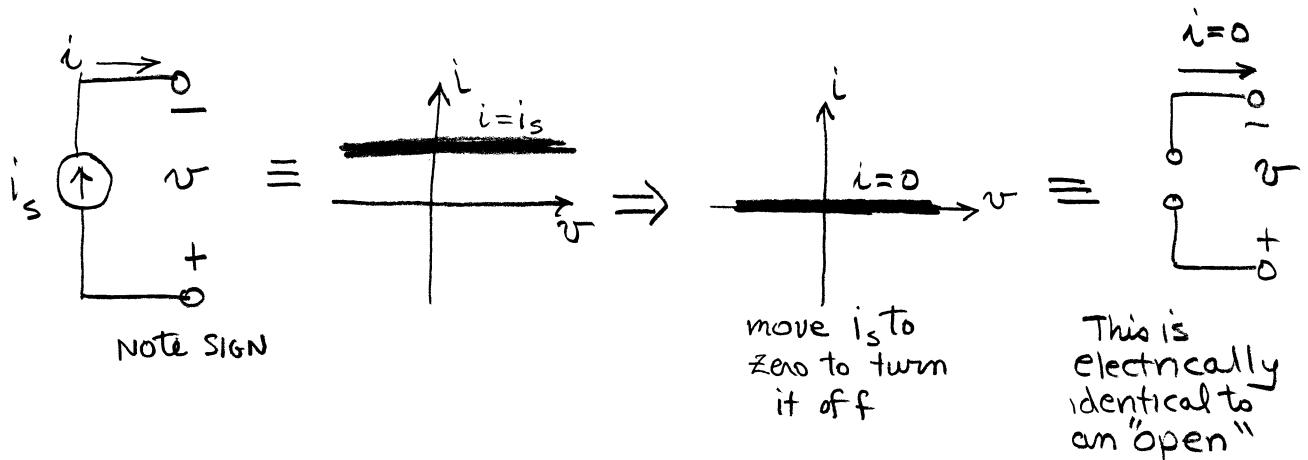
Turning "off" an independent voltage source means replacing it by a short.



Solve for v_o using superposition.

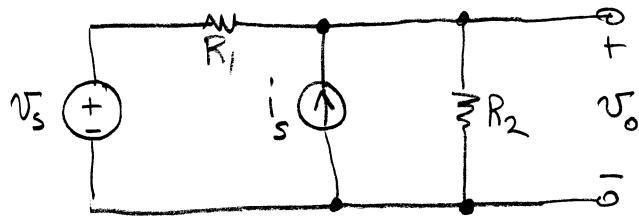

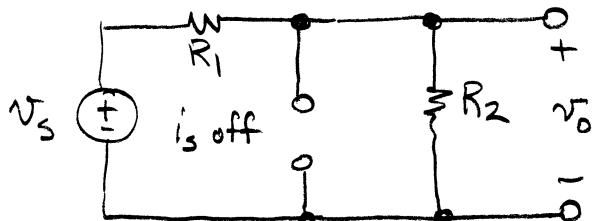
(a) "Turn off" i_s and find output due to V_s .




i_s becomes an "open" and the circuit is a voltage divider.

$$v_{o_v} = \frac{R_2}{R_1 + R_2} V_s$$

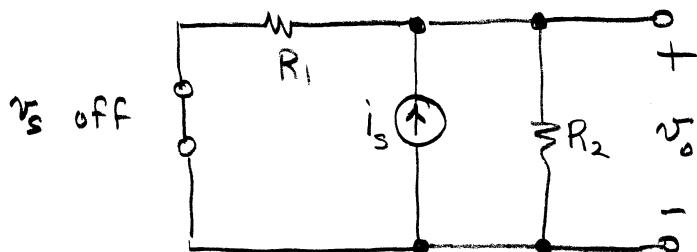(b) "Turn off" V_s and find output due to i_s .



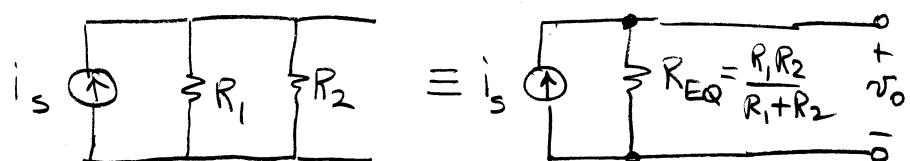This looks like two resistors in parallel.




$$v_{o_i} = i_s \frac{R_1 R_2}{R_1 + R_2}$$


$$\therefore v_o = v_{o_v} + v_{o_i} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_1 R_2}{R_1 + R_2} i_s$$

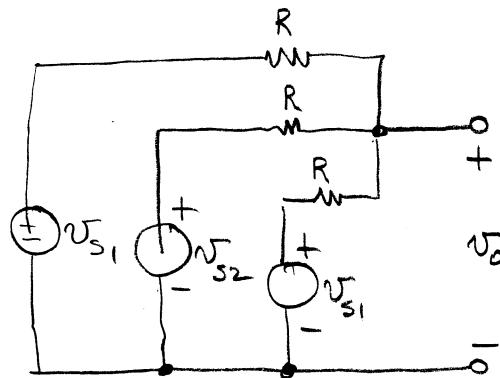Example 3-12.


Show that the output is a weighted sum of the inputs v_{s1} , v_{s2} , and v_{s3} .



Turn off v_{s2} and v_{s3} .

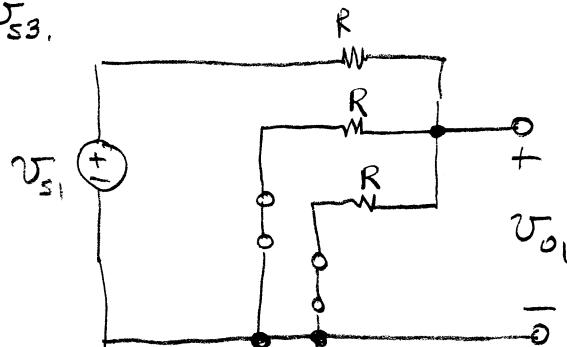

Redrawing

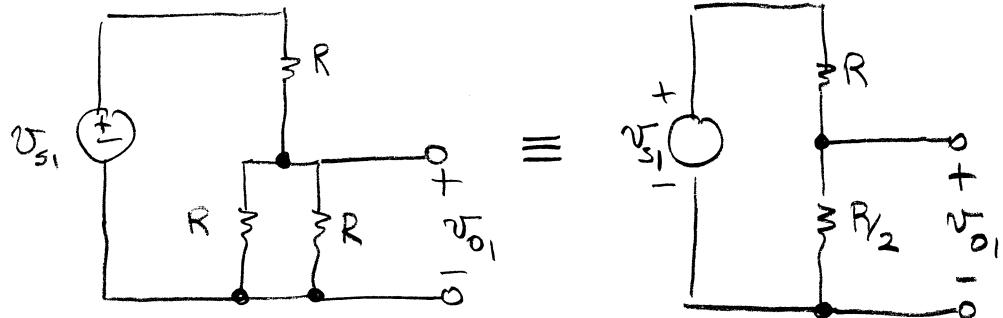

$$\therefore v_{o1} = \frac{R/2}{R + R/2} v_{s1} = \frac{R/2}{3R/2} v_{s1} = \frac{1}{3} v_{s1}$$

The other two source calculations are identical.

$$v_o = v_{o1} + v_{o2} + v_{o3} = \frac{1}{3} v_{s1} + \frac{1}{3} v_{s2} + \frac{1}{3} v_{s3}$$