
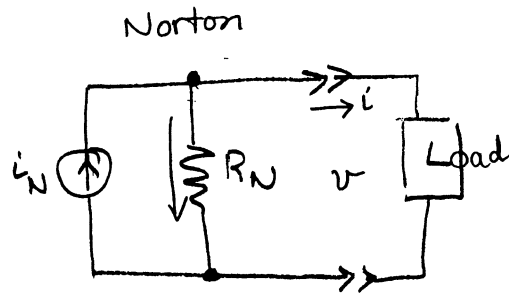

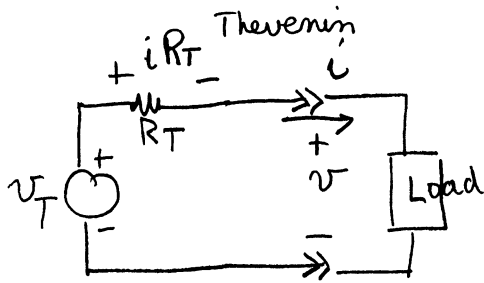
### 3-4 Thevenin & Norton Equivalent Circuits



These voltage and current source representations of the source are identical.

If each is open, i.e., remove Load

$$v_{oc} = v_T$$

$$v_{oc} = I_N R_N$$

If each is shorted, i.e., replace the load by a short

$$i_{sc} = \frac{v_T}{R_T}$$

$$i_{sc} = I_N$$

Everywhere in between they are equivalent. We can show this by comparing v-i equations,

by KVL  $\sum v = 0$

by KCL  $\sum i = 0$

$$-v_T + iR_T + v = 0$$

$$+I_N - \frac{v}{R_N} - i = 0$$

$$v = v_T - iR_T$$

rearranging

$$v = I_N R_N - iR_N$$

compare


if we set  $R_T = R_N$

and  $v_T = I_N R_N$

These expressions for Norton & Thevenin are identical.

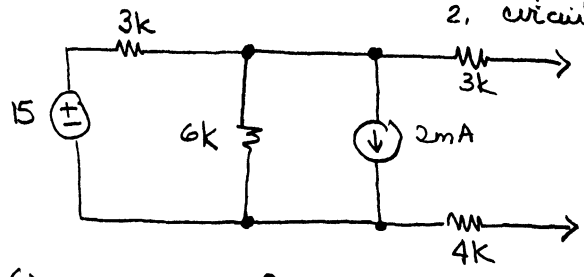
Example 3-13

Find Thevenin equivalent  
 1. superposition always works.  
 2. circuit reductions (ladder networks)




This is a ladder network.

(a) source transformation

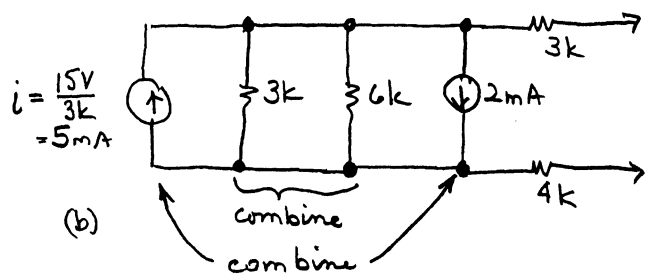


$$R_{in} = \frac{3 \cdot 6}{3+6} = \frac{18}{9} = 2k$$


(c) source transform

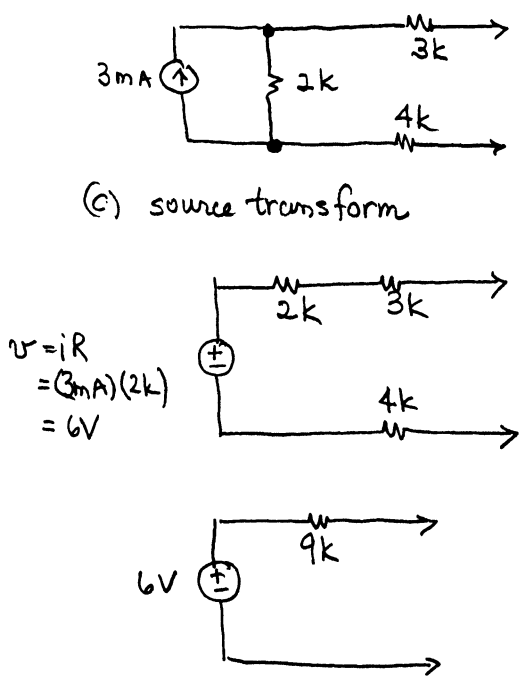


load 1

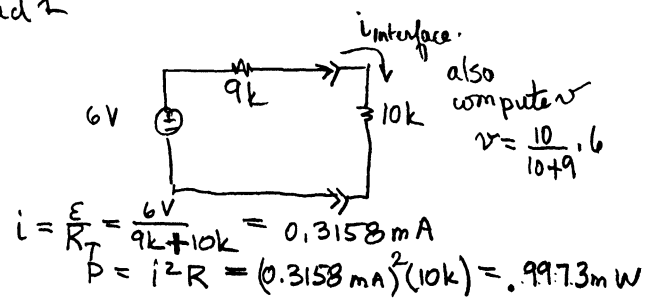

load 2

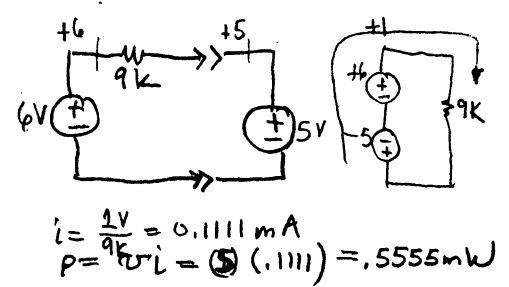

Example 3-14.

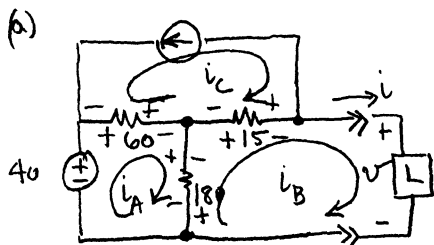

must use mesh equations  
to find Norton in this  
case

by inspection  $i_C = -2A$ ,  $i_B = i$

$$A: -40 + 60i_A - 60i_C + 180i_A - 180i_B = 0$$

$$B: +180i_B - 180i_A + 15i_B - 15i_C + v = 0$$

$$-40 + 240i_A + 120 - 180i = 0$$

$$195i - 180i_A + 30 + v = 0$$

$$240i_A - 180i = -80$$

$$-180i_A + 195i = -30 - v$$

using determinants

$$i = \frac{\begin{vmatrix} 240 & -80 \\ -180 & -30-v \end{vmatrix}}{\begin{vmatrix} 240 & -180 \\ -180 & 195 \end{vmatrix}} = \frac{-21600 - 240v}{14400}$$

$$i = -1.5 - \frac{v}{60}$$

compare this with equation of norton source.

apply KCL  $\sum i = 0$

$$+i_N - \frac{v}{R_N} - i = 0$$

$$i = +i_N - \frac{v}{R_N}$$

compare

$$\therefore i_N = -1.5 \text{ Amps}$$

$$R_N = 60 \Omega$$

if  $P_{load} = 5 \text{ watts}$  find  $i$

(b)  $v i = 5 \text{ watts}$   
find  $i$  for  $v = 5/i$

$$i = -1.5 - \frac{(5/i)}{60}$$


$$60i^2 = -90i - 5$$

$$12i^2 + 18i + 1 = 0$$


$$i = 7.05778 \text{ A}$$

$$\Rightarrow i = -1.442 \text{ A}$$



## Derivation of Thevenin's Theorem

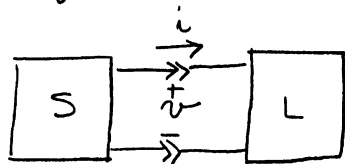

start with typical source/load

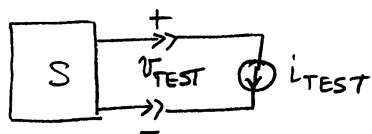

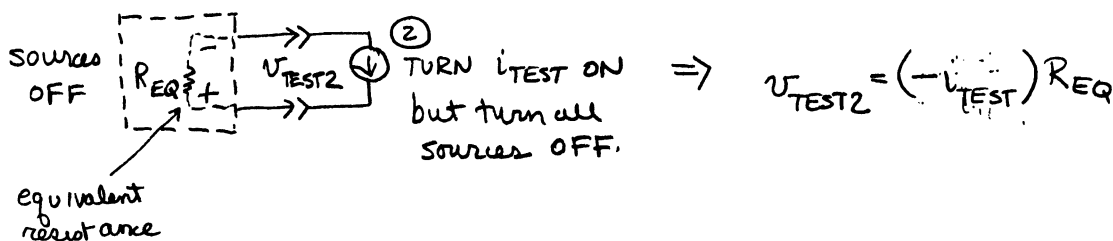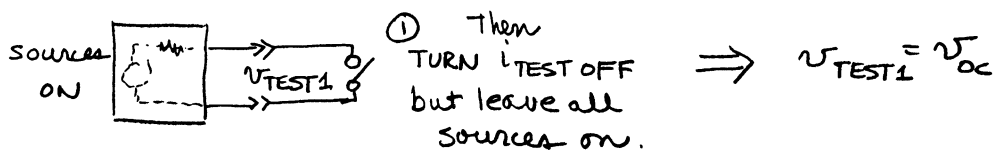apply a current source  $i_{TEST}$   
we know  $i_{TEST}$  and let  $v = v_{TEST}$



using superposition the sum of ① and ② must be  $v_{TEST}$

$$v_{TEST} = v_{TEST1} + v_{TEST2}$$

$$v_{TEST} = v_{OC} - i_{TEST} R_{EQ}$$

$$v = v_T - i R_T$$

looks exactly  
like KVL for Thevenin  
which we got on first page.

$$\text{Let } \Rightarrow v_{TEST} = v$$


$$v_{OC} = v_T$$

$$R_T = R_{EQ}$$

$$i_{TEST} = i$$




This gives us a great  
method to determine  $R_T$   
Simply turn off all sources  
and determine  $R_{EQ}$ .

Exercise 3-16(a)

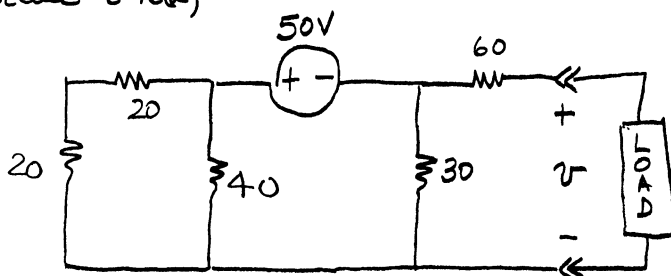

Now use what we just learned to determine Thevenin & Norton

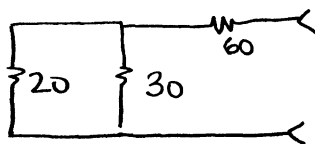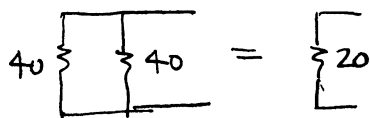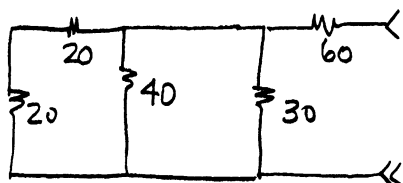
If we eliminate all sources we can find  $R_T$



$$R = \frac{20 \cdot 30}{20 + 30} = \frac{600}{50} = 12$$

$$R_T = 12 + 60 = 72 \Omega$$

We then find open circuit voltage

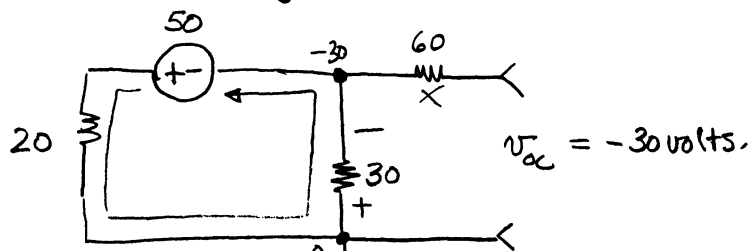

$$i = \frac{E}{R} = \frac{50}{50} = 1 \text{ A}$$

$$V = iR = (1 \text{ A})(30 \Omega) = 30 \text{ volts}$$

since they are related 
$$i_N = \frac{V_T}{R_T} = \frac{-30 \text{ V}}{72 \Omega} = -417 \text{ mA}$$